

Scilab Textbook Companion for  
Electrical Circuit Theory And Technology  
by J. O. Bird<sup>1</sup>

Created by  
Pankaj Goyal  
B.Tech  
Others  
IIT BOMBAY  
College Teacher  
Prabhu Ramchandran  
Cross-Checked by

October 4, 2013

<sup>1</sup>Funded by a grant from the National Mission on Education through ICT, <http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab codes written in it can be downloaded from the "Textbook Companion Project" section at the website <http://scilab.in>

# Book Description

**Title:** Electrical Circuit Theory And Technology

**Author:** J. O. Bird

**Publisher:** Routledge

**Edition:** 2

**Year:** 2003

**ISBN:** 0-7506-5784-7

Scilab numbering policy used in this document and the relation to the above book.

**Exa** Example (Solved example)

**Eqn** Equation (Particular equation of the above book)

**AP** Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

# Contents

|  |     |
|--|-----|
| List of Scilab Codes                                 | 6   |
| 1 Units associated with basic electrical quantities  | 21  |
| 2 An introduction to electric circuits               | 26  |
| 3 Resistance variation                               | 38  |
| 4 Chemical effects of electricity                    | 47  |
| 5 Series and parallel networks                       | 50  |
| 6 Capacitors and capacitance                         | 61  |
| 7 Magnetic circuits                                  | 73  |
| 8 Electromagnetism                                   | 85  |
| 9 Electromagnetic induction                          | 90  |
| 10 Electrical measuring instruments and measurements | 100 |
| 13 DC circuit theory                                 | 116 |
| 14 Alternating voltages and currents                 | 134 |
| 15 Single phase series ac circuits                   | 142 |
| 16 Single phase parallel ac circuits                 | 166 |

|   |     |
|---|-----|
| 17 DC transients  | 180 |
| 18 Operational amplifiers                                 | 197 |
| 19 Three phase systems                                    | 204 |
| 20 Transformers   | 220 |
| 21 DC machines  | 246 |
| 22 Three phase induction motors                           | 271 |
| 23 Revision of complex numbers                            | 284 |
| 24 Application of complex numbers to series ac circuits   | 291 |
| 25 Application of complex numbers to parallel ac networks | 305 |
| 26 Power in ac circuits                                   | 316 |
| 27 AC bridges   | 325 |
| 28 Series resonance and Q factor                          | 328 |
| 29 Parallel resonance and Q factor                        | 340 |
| 30 Introduction to network analysis                       | 347 |
| 31 Mesh current and nodal analysis                        | 353 |
| 32 The superposition theorem                              | 366 |
| 33 Thevenins and Nortons theorems                         | 375 |
| 34 Delta star and star delta transformations              | 397 |
| 35 Maximum power transfer theorems and impedance matching | 402 |
| 36 Complex Waveforms                                      | 413 |

|    |                                   |     |
|----|-----------------------------------|-----|
| 38 | Magnetic materials                | 428 |
| 39 | Dielectrics and dielectric loss   | 438 |
| 40 | Field theory                      | 441 |
| 41 | Attenuators                       | 461 |
| 42 | Filter networks                   | 474 |
| 43 | Magnetically coupled circuits     | 486 |
| 44 | Transmission lines                | 504 |
| 45 | Transients and Laplace transforms | 521 |

# List of Scilab Codes

|          |            |    |
|----------|------------|----|
| Exa 1.01 | Example 1  | 21 |
| Exa 1.02 | Example 2  | 21 |
| Exa 1.03 | Example 3  | 22 |
| Exa 1.04 | Example 4  | 22 |
| Exa 1.05 | Example 5  | 23 |
| Exa 1.06 | Example 6  | 24 |
| Exa 1.07 | Example 7  | 24 |
| Exa 1.08 | Example 8  | 25 |
| Exa 2.01 | Example 1  | 26 |
| Exa 2.02 | Example 2  | 26 |
| Exa 2.03 | Example 3  | 27 |
| Exa 2.04 | Example 4  | 27 |
| Exa 2.05 | Example 5  | 28 |
| Exa 2.06 | Example 6  | 28 |
| Exa 2.07 | Example 7  | 29 |
| Exa 2.08 | Example 8  | 30 |
| Exa 2.09 | Example 9  | 30 |
| Exa 2.10 | Example 10 | 31 |
| Exa 2.11 | Example 11 | 31 |
| Exa 2.12 | Example 12 | 32 |
| Exa 2.13 | Example 13 | 33 |
| Exa 2.14 | Example 14 | 33 |
| Exa 2.15 | Example 15 | 34 |
| Exa 2.16 | Example 16 | 34 |
| Exa 2.17 | Example 17 | 35 |
| Exa 2.18 | Example 18 | 36 |
| Exa 2.19 | Example 19 | 36 |
| Exa 3.01 | Example 1  | 38 |

|          |            |    |
|----------|------------|----|
| Exa 3.02 | Example 2  | 39 |
| Exa 3.03 | Example 3  | 39 |
| Exa 3.04 | Example 4  | 40 |
| Exa 3.05 | Example 5  | 40 |
| Exa 3.06 | Example 6  | 41 |
| Exa 3.07 | Example 7  | 42 |
| Exa 3.08 | Example 8  | 42 |
| Exa 3.09 | Example 9  | 43 |
| Exa 3.10 | Example 10 | 43 |
| Exa 3.11 | Example 11 | 44 |
| Exa 3.12 | Example 12 | 45 |
| Exa 3.13 | Example 13 | 45 |
| Exa 4.01 | Example 1  | 47 |
| Exa 4.02 | Example 2  | 48 |
| Exa 4.03 | Example 3  | 48 |
| Exa 4.04 | Example 4  | 49 |
| Exa 5.01 | Example 1  | 50 |
| Exa 5.02 | Example 2  | 51 |
| Exa 5.03 | Example 3  | 51 |
| Exa 5.04 | Example 4  | 52 |
| Exa 5.05 | Example 5  | 53 |
| Exa 5.06 | Example 6  | 54 |
| Exa 5.07 | Example 7  | 54 |
| Exa 5.08 | Example 8  | 55 |
| Exa 5.10 | Example 10 | 55 |
| Exa 5.11 | Example 11 | 56 |
| Exa 5.12 | Example 12 | 57 |
| Exa 5.13 | Example 13 | 58 |
| Exa 5.14 | Example 14 | 59 |
| Exa 5.15 | Example 15 | 59 |
| Exa 6.01 | Example 1  | 61 |
| Exa 6.02 | Example 2  | 62 |
| Exa 6.03 | Example 3  | 62 |
| Exa 6.04 | Example 4  | 63 |
| Exa 6.05 | Example 5  | 63 |
| Exa 6.06 | Example 6  | 64 |
| Exa 6.07 | Example 7  | 65 |
| Exa 6.08 | Example 8  | 65 |



|          |            |    |
|----------|------------|----|
| Exa 6.09 | Example 9  | 66 |
| Exa 6.10 | Example 10 | 67 |
| Exa 6.11 | Example 11 | 67 |
| Exa 6.12 | Example 12 | 68 |
| Exa 6.13 | Example 13 | 69 |
| Exa 6.14 | Example 14 | 70 |
| Exa 6.15 | Example 15 | 70 |
| Exa 6.16 | Example 16 | 71 |
| Exa 6.17 | Example 17 | 72 |
| Exa 7.01 | Example 1  | 73 |
| Exa 7.02 | Example 2  | 73 |
| Exa 7.03 | Example 3  | 74 |
| Exa 7.04 | Example 4  | 75 |
| Exa 7.05 | Example 5  | 75 |
| Exa 7.06 | Example 6  | 76 |
| Exa 7.07 | Example 7  | 77 |
| Exa 7.08 | Example 8  | 78 |
| Exa 7.09 | Example 9  | 78 |
| Exa 7.10 | Example 10 | 79 |
| Exa 7.11 | Example 11 | 80 |
| Exa 7.12 | Example 12 | 81 |
| Exa 7.13 | Example 13 | 82 |
| Exa 7.14 | Example 14 | 83 |
| Exa 8.02 | Example 2  | 85 |
| Exa 8.03 | Example 3  | 86 |
| Exa 8.04 | Example 4  | 86 |
| Exa 8.06 | Example 6  | 87 |
| Exa 8.07 | Example 7  | 88 |
| Exa 9.01 | Example 1  | 90 |
| Exa 9.02 | Example 2  | 91 |
| Exa 9.03 | Example 3  | 91 |
| Exa 9.04 | Example 4  | 92 |
| Exa 9.06 | Example 6  | 93 |
| Exa 9.07 | Example 7  | 93 |
| Exa 9.08 | Example 8  | 94 |
| Exa 9.09 | Example 9  | 95 |
| Exa 9.10 | Example 10 | 95 |
| Exa 9.11 | Example 11 | 96 |

|           |            |     |
|-----------|------------|-----|
| Exa 9.12  | Example 12 | 96  |
| Exa 9.13  | Example 13 | 97  |
| Exa 9.14  | Example 14 | 98  |
| Exa 9.15  | Example 15 | 98  |
| Exa 9.16  | Example 16 | 99  |
| Exa 10.01 | Example 1  | 100 |
| Exa 10.02 | Example 2  | 101 |
| Exa 10.03 | Example 3  | 101 |
| Exa 10.04 | Example 4  | 102 |
| Exa 10.05 | Example 5  | 103 |
| Exa 10.06 | Example 6  | 104 |
| Exa 10.08 | Example 8  | 105 |
| Exa 10.09 | Example 9  | 106 |
| Exa 10.10 | Example 10 | 106 |
| Exa 10.11 | Example 11 | 107 |
| Exa 10.12 | Example 12 | 108 |
| Exa 10.13 | Example 13 | 109 |
| Exa 10.14 | Example 14 | 110 |
| Exa 10.15 | Example 15 | 110 |
| Exa 10.16 | Example 16 | 111 |
| Exa 10.17 | Example 17 | 111 |
| Exa 10.18 | Example 18 | 112 |
| Exa 10.19 | Example 19 | 112 |
| Exa 10.20 | Example 20 | 113 |
| Exa 10.21 | Example 21 | 114 |
| Exa 13.01 | Example 1  | 116 |
| Exa 13.06 | Example 6  | 117 |
| Exa 13.07 | Example 7  | 119 |
| Exa 13.08 | Example 8  | 120 |
| Exa 13.09 | Example 9  | 120 |
| Exa 13.10 | Example 10 | 121 |
| Exa 13.11 | Example 11 | 122 |
| Exa 13.12 | Example 12 | 123 |
| Exa 13.13 | Example 13 | 124 |
| Exa 13.14 | Example 14 | 125 |
| Exa 13.15 | Example 15 | 126 |
| Exa 13.18 | Example 18 | 127 |
| Exa 13.19 | Example 19 | 128 |

|           |            |     |
|-----------|------------|-----|
| Exa 13.20 | Example 20 | 130 |
| Exa 13.21 | Example 21 | 131 |
| Exa 13.22 | Example 22 | 132 |
| Exa 14.01 | Example 1  | 134 |
| Exa 14.02 | Example 2  | 134 |
| Exa 14.03 | Example 3  | 135 |
| Exa 14.04 | Example 4  | 135 |
| Exa 14.06 | Example 6  | 137 |
| Exa 14.07 | Example 7  | 137 |
| Exa 14.08 | Example 8  | 138 |
| Exa 14.09 | Example 9  | 138 |
| Exa 14.10 | Example 10 | 139 |
| Exa 14.12 | Example 12 | 140 |
| Exa 15.01 | Example 1  | 142 |
| Exa 15.02 | Example 2  | 143 |
| Exa 15.03 | Example 3  | 143 |
| Exa 15.04 | Example 4  | 144 |
| Exa 15.05 | Example 5  | 144 |
| Exa 15.06 | Example 6  | 145 |
| Exa 15.07 | Example 7  | 146 |
| Exa 15.08 | Example 8  | 146 |
| Exa 15.09 | Example 9  | 147 |
| Exa 15.10 | Example 10 | 148 |
| Exa 15.11 | Example 11 | 149 |
| Exa 15.12 | Example 12 | 150 |
| Exa 15.13 | Example 13 | 151 |
| Exa 15.14 | Example 14 | 152 |
| Exa 15.15 | Example 15 | 153 |
| Exa 15.16 | Example 16 | 154 |
| Exa 15.17 | Example 17 | 155 |
| Exa 15.18 | Example 18 | 156 |
| Exa 15.19 | Example 19 | 157 |
| Exa 15.20 | Example 20 | 158 |
| Exa 15.21 | Example 21 | 159 |
| Exa 15.22 | Example 22 | 159 |
| Exa 15.23 | Example 23 | 160 |
| Exa 15.24 | Example 24 | 161 |
| Exa 15.25 | Example 25 | 161 |

|           |            |     |
|-----------|------------|-----|
| Exa 15.26 | Example 26 | 162 |
| Exa 15.27 | Example 27 | 163 |
| Exa 15.28 | Example 28 | 163 |
| Exa 15.29 | Example 29 | 164 |
| Exa 16.01 | Example 1  | 166 |
| Exa 16.02 | Example 2  | 167 |
| Exa 16.03 | Example 3  | 168 |
| Exa 16.04 | Example 4  | 169 |
| Exa 16.05 | Example 5  | 170 |
| Exa 16.06 | Example 6  | 171 |
| Exa 16.07 | Example 7  | 172 |
| Exa 16.08 | Example 8  | 173 |
| Exa 16.09 | Example 9  | 174 |
| Exa 16.10 | Example 10 | 175 |
| Exa 16.11 | Example 11 | 176 |
| Exa 16.12 | Example 12 | 177 |
| Exa 16.13 | Example 13 | 178 |
| Exa 17.01 | Example 1  | 180 |
| Exa 17.02 | Example 2  | 182 |
| Exa 17.03 | Example 3  | 184 |
| Exa 17.04 | Example 4  | 185 |
| Exa 17.05 | Example 5  | 186 |
| Exa 17.06 | Example 6  | 187 |
| Exa 17.07 | Example 7  | 188 |
| Exa 17.08 | Example 8  | 190 |
| Exa 17.09 | Example 9  | 191 |
| Exa 17.10 | Example 10 | 192 |
| Exa 17.11 | Example 11 | 194 |
| Exa 17.12 | Example 12 | 195 |
| Exa 18.01 | Example 1  | 197 |
| Exa 18.02 | Example 2  | 197 |
| Exa 18.03 | Example 3  | 198 |
| Exa 18.04 | Example 4  | 199 |
| Exa 18.05 | Example 5  | 199 |
| Exa 18.06 | Example 6  | 200 |
| Exa 18.07 | Example 7  | 201 |
| Exa 18.08 | Example 8  | 201 |
| Exa 18.10 | Example 10 | 202 |

|           |            |     |
|-----------|------------|-----|
| Exa 18.11 | Example 11 | 202 |
| Exa 19.01 | Example 1  | 204 |
| Exa 19.02 | Example 2  | 205 |
| Exa 19.04 | Example 4  | 205 |
| Exa 19.05 | Example 5  | 206 |
| Exa 19.06 | Example 6  | 207 |
| Exa 19.07 | Example 7  | 208 |
| Exa 19.08 | Example 8  | 209 |
| Exa 19.09 | Example 9  | 210 |
| Exa 19.10 | Example 10 | 211 |
| Exa 19.11 | Example 11 | 212 |
| Exa 19.13 | Example 13 | 213 |
| Exa 19.14 | Example 14 | 214 |
| Exa 19.15 | Example 15 | 215 |
| Exa 19.16 | Example 16 | 216 |
| Exa 19.17 | Example 17 | 217 |
| Exa 19.18 | Example 18 | 217 |
| Exa 20.01 | Example 1  | 220 |
| Exa 20.02 | Example 2  | 220 |
| Exa 20.03 | Example 3  | 221 |
| Exa 20.04 | Example 4  | 222 |
| Exa 20.05 | Example 5  | 222 |
| Exa 20.06 | Example 6  | 223 |
| Exa 20.07 | Example 7  | 224 |
| Exa 20.08 | Example 8  | 225 |
| Exa 20.09 | Example 9  | 226 |
| Exa 20.10 | Example 10 | 227 |
| Exa 20.11 | Example 11 | 228 |
| Exa 20.12 | Example 12 | 229 |
| Exa 20.13 | Example 13 | 230 |
| Exa 20.14 | Example 14 | 231 |
| Exa 20.15 | Example 15 | 232 |
| Exa 20.16 | Example 16 | 233 |
| Exa 20.17 | Example 17 | 234 |
| Exa 20.18 | Example 18 | 234 |
| Exa 20.19 | Example 19 | 236 |
| Exa 20.20 | Example 20 | 237 |
| Exa 20.21 | Example 21 | 238 |

|           |            |     |
|-----------|------------|-----|
| Exa 20.22 | Example 22 | 239 |
| Exa 20.23 | Example 23 | 239 |
| Exa 20.24 | Example 24 | 240 |
| Exa 20.25 | Example 25 | 241 |
| Exa 20.26 | Example 26 | 242 |
| Exa 20.27 | Example 27 | 243 |
| Exa 20.28 | Example 28 | 244 |
| Exa 21.01 | Example 1  | 246 |
| Exa 21.02 | Example 2  | 247 |
| Exa 21.03 | Example 3  | 247 |
| Exa 21.04 | Example 4  | 248 |
| Exa 21.06 | Example 6  | 248 |
| Exa 21.07 | Example 7  | 249 |
| Exa 21.08 | Example 8  | 250 |
| Exa 21.09 | Example 9  | 251 |
| Exa 21.10 | Example 10 | 252 |
| Exa 21.11 | Example 11 | 253 |
| Exa 21.12 | Example 12 | 253 |
| Exa 21.13 | Example 13 | 254 |
| Exa 21.14 | Example 14 | 255 |
| Exa 21.15 | Example 15 | 256 |
| Exa 21.16 | Example 16 | 256 |
| Exa 21.17 | Example 17 | 257 |
| Exa 21.18 | Example 18 | 258 |
| Exa 21.19 | Example 19 | 259 |
| Exa 21.20 | Example 20 | 260 |
| Exa 21.21 | Example 21 | 261 |
| Exa 21.22 | Example 22 | 262 |
| Exa 21.23 | Example 23 | 263 |
| Exa 21.24 | Example 24 | 264 |
| Exa 21.25 | Example 25 | 265 |
| Exa 21.26 | Example 26 | 266 |
| Exa 21.27 | Example 27 | 267 |
| Exa 21.28 | Example 28 | 267 |
| Exa 21.29 | Example 29 | 268 |
| Exa 21.30 | Example 30 | 269 |
| Exa 22.01 | Example 1  | 271 |
| Exa 22.02 | Example 2  | 272 |

|           |            |     |
|-----------|------------|-----|
| Exa 22.03 | Example 3  | 272 |
| Exa 22.04 | Example 4  | 273 |
| Exa 22.05 | Example 5  | 273 |
| Exa 22.06 | Example 6  | 274 |
| Exa 22.07 | Example 7  | 275 |
| Exa 22.08 | Example 8  | 276 |
| Exa 22.09 | Example 9  | 277 |
| Exa 22.10 | Example 10 | 278 |
| Exa 22.11 | Example 11 | 280 |
| Exa 22.12 | Example 12 | 281 |
| Exa 22.13 | Example 13 | 282 |
| Exa 23.01 | Example 1  | 284 |
| Exa 23.02 | Example 2  | 285 |
| Exa 23.03 | Example 3  | 285 |
| Exa 23.05 | Example 5  | 286 |
| Exa 23.06 | Example 6  | 287 |
| Exa 23.07 | Example 7  | 288 |
| Exa 23.08 | Example 8  | 288 |
| Exa 24.01 | Example 1  | 291 |
| Exa 24.02 | Example 2  | 292 |
| Exa 24.03 | Example 3  | 293 |
| Exa 24.04 | Example 4  | 294 |
| Exa 24.05 | Example 5  | 295 |
| Exa 24.06 | Example 6  | 297 |
| Exa 24.07 | Example 7  | 298 |
| Exa 24.08 | Example 8  | 299 |
| Exa 24.09 | Example 9  | 300 |
| Exa 24.10 | Example 10 | 301 |
| Exa 24.11 | Example 11 | 302 |
| Exa 24.12 | Example 12 | 303 |
| Exa 25.01 | Example 1  | 305 |
| Exa 25.02 | Example 2  | 306 |
| Exa 25.03 | Example 3  | 307 |
| Exa 25.04 | Example 4  | 308 |
| Exa 25.05 | Example 5  | 309 |
| Exa 25.06 | Example 6  | 310 |
| Exa 25.07 | Example 7  | 312 |
| Exa 25.08 | Example 8  | 314 |

|           |            |     |
|-----------|------------|-----|
| Exa 26.01 | Example 1  | 316 |
| Exa 26.02 | Example 2  | 317 |
| Exa 26.03 | Example 3  | 317 |
| Exa 26.04 | Example 4  | 319 |
| Exa 26.05 | Example 5  | 320 |
| Exa 26.06 | Example 6  | 321 |
| Exa 26.07 | Example 7  | 322 |
| Exa 27.02 | Example 2  | 325 |
| Exa 27.03 | Example 3  | 326 |
| Exa 28.01 | Example 1  | 328 |
| Exa 28.02 | Example 2  | 329 |
| Exa 28.03 | Example 3  | 329 |
| Exa 28.04 | Example 4  | 330 |
| Exa 28.05 | Example 5  | 332 |
| Exa 28.06 | Example 6  | 333 |
| Exa 28.07 | Example 7  | 333 |
| Exa 28.08 | Example 8  | 334 |
| Exa 28.09 | Example 9  | 335 |
| Exa 28.10 | Example 10 | 336 |
| Exa 28.11 | Example 11 | 337 |
| Exa 29.01 | Example 1  | 340 |
| Exa 29.02 | Example 2  | 341 |
| Exa 29.03 | Example 3  | 342 |
| Exa 29.04 | Example 4  | 343 |
| Exa 29.05 | Example 5  | 344 |
| Exa 29.06 | Example 6  | 345 |
| Exa 29.07 | Example 7  | 345 |
| Exa 30.01 | Example 1  | 347 |
| Exa 30.02 | Example 2  | 348 |
| Exa 30.03 | Example 3  | 350 |
| Exa 30.04 | Example 4  | 351 |
| Exa 31.01 | Example 1  | 353 |
| Exa 31.02 | Example 2  | 354 |
| Exa 31.03 | Example 3  | 356 |
| Exa 31.04 | Example 4  | 357 |
| Exa 31.05 | Example 5  | 358 |
| Exa 31.06 | Example 6  | 359 |
| Exa 31.07 | Example 7  | 360 |



|           |            |     |
|-----------|------------|-----|
| Exa 31.08 | Example 8  | 362 |
| Exa 31.09 | Example 9  | 363 |
| Exa 32.01 | Example 1  | 366 |
| Exa 32.02 | Example 2  | 367 |
| Exa 32.03 | Example 3  | 369 |
| Exa 32.04 | Example 4  | 370 |
| Exa 32.05 | Example 5  | 372 |
| Exa 33.01 | Example 1  | 375 |
| Exa 33.02 | Example 2  | 376 |
| Exa 33.03 | Example 3  | 378 |
| Exa 33.04 | Example 4  | 379 |
| Exa 33.05 | Example 5  | 380 |
| Exa 33.06 | Example 6  | 381 |
| Exa 33.07 | Example 7  | 383 |
| Exa 33.08 | Example 8  | 384 |
| Exa 33.09 | Example 9  | 386 |
| Exa 33.10 | Example 10 | 387 |
| Exa 33.11 | Example 11 | 388 |
| Exa 33.12 | Example 12 | 389 |
| Exa 33.13 | Example 13 | 390 |
| Exa 33.15 | Example 15 | 392 |
| Exa 33.16 | Example 16 | 393 |
| Exa 33.17 | Example 17 | 395 |
| Exa 34.02 | Example 2  | 397 |
| Exa 34.03 | Example 3  | 398 |
| Exa 34.05 | Example 5  | 400 |
| Exa 35.01 | Example 1  | 402 |
| Exa 35.02 | Example 2  | 403 |
| Exa 35.03 | Example 3  | 404 |
| Exa 35.04 | Example 4  | 405 |
| Exa 35.05 | Example 5  | 406 |
| Exa 35.06 | Example 6  | 407 |
| Exa 35.07 | Example 7  | 408 |
| Exa 35.08 | Example 8  | 409 |
| Exa 35.09 | Example 9  | 410 |
| Exa 35.10 | Example 10 | 411 |
| Exa 36.03 | Example 3  | 413 |
| Exa 36.04 | Example 4  | 413 |

|           |            |     |
|-----------|------------|-----|
| Exa 36.06 | Example 6  | 414 |
| Exa 36.07 | Example 7  | 415 |
| Exa 36.09 | Example 9  | 416 |
| Exa 36.10 | Example 10 | 418 |
| Exa 36.11 | Example 11 | 420 |
| Exa 36.12 | Example 12 | 422 |
| Exa 36.13 | Example 13 | 423 |
| Exa 36.14 | Example 14 | 425 |
| Exa 36.15 | Example 15 | 426 |
| Exa 38.01 | Example 1  | 428 |
| Exa 38.02 | Example 2  | 429 |
| Exa 38.03 | Example 3  | 429 |
| Exa 38.04 | Example 4  | 430 |
| Exa 38.05 | Example 5  | 431 |
| Exa 38.06 | Example 6  | 432 |
| Exa 38.07 | Example 7  | 433 |
| Exa 38.08 | Example 8  | 435 |
| Exa 38.10 | Example 10 | 436 |
| Exa 39.01 | Example 1  | 438 |
| Exa 39.02 | Example 2  | 439 |
| Exa 39.03 | Example 3  | 440 |
| Exa 40.01 | Example 1  | 441 |
| Exa 40.02 | Example 2  | 442 |
| Exa 40.03 | Example 3  | 442 |
| Exa 40.04 | Example 4  | 443 |
| Exa 40.05 | Example 5  | 444 |
| Exa 40.06 | Example 6  | 445 |
| Exa 40.07 | Example 7  | 446 |
| Exa 40.08 | Example 8  | 447 |
| Exa 40.09 | Example 9  | 448 |
| Exa 40.10 | Example 10 | 448 |
| Exa 40.11 | Example 11 | 449 |
| Exa 40.12 | Example 12 | 450 |
| Exa 40.13 | Example 13 | 451 |
| Exa 40.14 | Example 14 | 452 |
| Exa 40.15 | Example 15 | 453 |
| Exa 40.16 | Example 16 | 453 |
| Exa 40.17 | Example 17 | 454 |

|           |            |     |
|-----------|------------|-----|
| Exa 40.18 | Example 18 | 455 |
| Exa 40.19 | Example 19 | 456 |
| Exa 40.20 | Example 20 | 456 |
| Exa 40.21 | Example 21 | 457 |
| Exa 40.22 | Example 22 | 458 |
| Exa 40.23 | Example 23 | 458 |
| Exa 40.24 | Example 24 | 459 |
| Exa 41.01 | Example 1  | 461 |
| Exa 41.02 | Example 2  | 462 |
| Exa 41.03 | Example 3  | 462 |
| Exa 41.04 | Example 4  | 463 |
| Exa 41.05 | Example 5  | 464 |
| Exa 41.06 | Example 6  | 464 |
| Exa 41.07 | Example 7  | 465 |
| Exa 41.10 | Example 10 | 466 |
| Exa 41.11 | Example 11 | 467 |
| Exa 41.12 | Example 12 | 468 |
| Exa 41.13 | Example 13 | 469 |
| Exa 41.14 | Example 14 | 470 |
| Exa 41.15 | Example 15 | 471 |
| Exa 41.16 | Example 16 | 472 |
| Exa 42.01 | Example 1  | 474 |
| Exa 42.02 | Example 2  | 475 |
| Exa 42.03 | Example 3  | 475 |
| Exa 42.04 | Example 4  | 476 |
| Exa 42.05 | Example 5  | 477 |
| Exa 42.07 | Example 7  | 478 |
| Exa 42.08 | Example 8  | 479 |
| Exa 42.09 | Example 9  | 480 |
| Exa 42.10 | Example 10 | 480 |
| Exa 42.11 | Example 11 | 482 |
| Exa 42.12 | Example 12 | 483 |
| Exa 42.13 | Example 13 | 484 |
| Exa 42.14 | Example 14 | 485 |
| Exa 43.01 | Example 1  | 486 |
| Exa 43.02 | Example 2  | 487 |
| Exa 43.03 | Example 3  | 487 |
| Exa 43.04 | Example 4  | 488 |

|           |            |     |
|-----------|------------|-----|
| Exa 43.05 | Example 5  | 489 |
| Exa 43.06 | Example 6  | 490 |
| Exa 43.07 | Example 7  | 491 |
| Exa 43.08 | Example 8  | 492 |
| Exa 43.09 | Example 9  | 492 |
| Exa 43.10 | Example 10 | 493 |
| Exa 43.11 | Example 11 | 494 |
| Exa 43.12 | Example 12 | 496 |
| Exa 43.13 | Example 13 | 497 |
| Exa 43.14 | Example 14 | 498 |
| Exa 43.15 | Example 15 | 500 |
| Exa 43.16 | Example 16 | 501 |
| Exa 44.01 | Example 1  | 504 |
| Exa 44.02 | Example 2  | 505 |
| Exa 44.03 | Example 3  | 505 |
| Exa 44.04 | Example 4  | 506 |
| Exa 44.05 | Example 5  | 507 |
| Exa 44.06 | Example 6  | 508 |
| Exa 44.07 | Example 7  | 509 |
| Exa 44.08 | Example 8  | 510 |
| Exa 44.09 | Example 9  | 511 |
| Exa 44.10 | Example 10 | 512 |
| Exa 44.11 | Example 11 | 513 |
| Exa 44.12 | Example 12 | 514 |
| Exa 44.13 | Example 13 | 515 |
| Exa 44.14 | Example 14 | 516 |
| Exa 44.15 | Example 15 | 517 |
| Exa 44.16 | Example 16 | 518 |
| Exa 44.17 | Example 17 | 519 |
| Exa 44.18 | Example 18 | 520 |
| Exa 45.01 | Example 1  | 521 |
| Exa 45.02 | Example 2  | 522 |
| Exa 45.03 | Example 3  | 523 |
| Exa 45.04 | Example 4  | 524 |
| Exa 45.05 | Example 5  | 525 |
| Exa 45.06 | Example 6  | 526 |

# List of Figures

|                           |     |
|---------------------------|-----|
| 13.1 Example 20 . . . . . | 130 |
| 17.1 Example 1 . . . . .  | 181 |
| 17.2 Example 2 . . . . .  | 183 |
| 17.3 Example 7 . . . . .  | 189 |
| 17.4 Example 10 . . . . . | 193 |

# Chapter 1

## Units associated with basic electrical quantities

Scilab code Exa 1.01 Example 1

```
1 //Problem 1.01: If a current of 5 A flows for 2
   minutes, find the quantity of electricity
   transferred.
2
3 //initializing the variables:
4 I = 5; // in Ampere
5 t = 120; // in sec
6
7 //calculation:
8 Q = I*t
9
10 printf("\n\nResult\n\n")
11 printf("\nQ: %.0f coulomb(C)\n",Q)
```

---

Scilab code Exa 1.02 Example 2

```

1 //Problem 1.02: A mass of 5000 g is accelerated at 2
    m/s2 by a force. Determine the force needed.
2
3 //initializing the variables:
4 M = 5; // in Kg
5 a = 2; // in m/s2
6
7 //calculation:
8 F = M*a
9
10 printf("\n\nResult\n\n")
11 printf("\nForce: %.0f Newton(N)\n",F)

```

---

#### Scilab code Exa 1.03 Example 3

```

1 //Problem 1.03: Find the force acting vertically
    downwards on a mass of 200 g attached to a wire.
2
3 //initializing the variables:
4 M = 0.2; // in Kg
5 g = 9.81; // in m/s2
6
7 //calculation:
8 F = M*g
9
10 printf("\n\nResult\n\n")
11 printf("\nForce: %.3f Newton(N)\n",F)

```

---

#### Scilab code Exa 1.04 Example 4

```

1 //Problem 1.04: A portable machine requires a force
    of 200 N to move it. How much work is done if the

```

```

    machine is moved 20 m and what average power is
    utilized if the movement takes 25 s?
2
3 //initializing the variables:
4 F = 200; // in Newton
5 d = 20; // in m
6 t = 25; // in sec
7
8 //calculation:
9 W = F*d
10 P = W/t
11
12 printf("\n\nResult\n\n")
13 printf("\nPower: %.0f watt (W)\n",P)

```

---

#### Scilab code Exa 1.05 Example 5

```

1 //Problem 1.05: A mass of 1000 kg is raised through
    a height of 10m in 20s. What is (a) the work done
    and (b) the power developed?
2
3 //initializing the variables:
4 M = 1000; // in Kg
5 h = 10; // in m
6 t = 20; // in sec
7 g = 9.81 // in m/s2
8
9 //calculation:
10 W = M*g*h
11 P = W/t
12
13 printf("\n\nResult\n\n")
14 printf("\nWork Done: %.0f Joule (J)\n",W)
15 printf("\nPower: %.0f watt (W)\n",P)

```

---



### Scilab code Exa 1.06 Example 6

```
1 //Problem 1.06: Find the conductance of a conductor
   of resistance (a) 10 ohm , (b) 5 kohm and (c) 100
   ohm.
2
3 //initializing the variables:
4 R1 = 10; // in ohm
5 R2 = 5000; // in ohm
6 R3 = 0.1; // in ohm
7 //calculation:
8 G1 = 1/R1
9 G2 = 1/R2
10 G3 = 1/R3
11
12 printf("\n\nResult\n\n")
13 printf("\nconductance(G1): %.1 f seimen(S)\n",G1)
14 printf("\nconductance(G2): %.4 f seimen(S)\n",G2)
15 printf("\nconductance(G3): %.0 f seimen(S)\n",G3)
```

---

### Scilab code Exa 1.07 Example 7

```
1 //Problem 1.07: A source e.m.f. of 5 V supplies a
   current of 3 A for 10 minutes. How much energy is
   provided in this time?
2
3 //initializing the variables:
4 V = 5; // in Volts
5 I = 3; // in Ampere
6 t = 600; // in sec
7 //calculation:
8 P = V*I
```

```
9 E = P*t
10
11 printf("\n\nResult\n\n")
12 printf("\nEnergy(E): %.0f Joule(J)\n",E)
```

---

### Scilab code Exa 1.08 Example 8

```
1 //Problem 1.08: An electric heater consumes 1.8 MJ
   when connected to a 250 V supply for 30 minutes.
   Find the power rating of the heater and the
   current taken from the supply.
2
3 //initializing the variables:
4 E = 18E5; // in Joule
5 V = 250; // in Volts
6 t = 1800; // in sec
7
8 //calculation:
9 P = E/t
10 I = P/V
11
12 printf("\n\nResult\n\n")
13 printf("\nPower(P): %.0f Watt(W)",P)
14 printf("\nCurrent(I): %.0f Ampere(A)\n",I)
```

---

## Chapter 2

# An introduction to electric circuits

Scilab code Exa 2.01 Example 1

```
1 //Problem 2.01: What current must flow if 0.24
   coulombs is to be transferred in 15 ms?
2
3 //initializing the variables:
4 Q = 0.24; // in Coulomb
5 t = 0.015; // in sec
6
7 //calculation:
8 I = Q/t
9
10 printf("\n\nResult\n\n")
11 printf("\nCurrent (I): %.0f Ampere(A)\n", I)
```

---

Scilab code Exa 2.02 Example 2

```
1 //Problem 2.02: If a current of 10 A flows for four
```

```

    minutes, find the quantity of electricity
    transferred.
2
3 //initializing the variables:
4 I = 10; // in Ampere
5 t = 240; // in sec
6
7 //calculation:
8 Q = I*t
9
10 printf("\n\nResult\n\n")
11 printf("\nCharge(Q): %.0f Coulomb(C)\n",Q)

```

---

### Scilab code Exa 2.03 Example 3

```

1 //Problem 2.03: The current flowing through a
    resistor is 0.8 A when a p.d. of 20 V is applied.
    Determine the value of the resistance.
2
3 //initializing the variables:
4 I = 0.8; // in Ampere
5 V = 20; // in Volts
6
7 //calculation:
8 R = V/I
9
10 printf("\n\nResult\n\n")
11 printf("\nResistance(R): %.0f Ohms\n",R)

```

---

### Scilab code Exa 2.04 Example 4

```

1 //Problem 2.04: Determine the p.d. which must be
    applied to a 2 kohm resistor in order that a
    current of 10 mA may flow.
2
3 //initializing the variables:
4 I = 0.010; // in Ampere
5 R = 2000; // in ohms
6
7 //calculation:
8 V = I*R
9
10 printf("\n\nResult\n\n")
11 printf("\np.d.(V): %.0f Volts(V)\n",V)

```

---

#### Scilab code Exa 2.05 Example 5

```

1 //Problem 2.05: A coil has a current of 50 mA
    flowing through it when the applied voltage is 12
    V. What is the resistance of the coil?
2
3 //initializing the variables:
4 I = 0.050; // in Ampere
5 V = 12; // in Volts
6
7 //calculation:
8 R = V/I
9
10 printf("\n\nResult\n\n")
11 printf("\nResistance(R): %.0f Ohms\n",R)

```

---

#### Scilab code Exa 2.06 Example 6

```

1 //Problem 2.06: A 100 V battery is connected across
  a resistor and causes a current of 5 mA to flow.
  Determine the resistance of the resistor. If the
  voltage is now reduced to 25 V, what will be the
  new value of the current flowing?
2
3 //initializing the variables:
4 I = 0.005; // in Ampere
5 V1 = 100; // in Volts
6 V2 = 25; // in Volts
7
8 //calculation:
9 //resistance
10 R = V1/I
11 //Current when voltage is reduced to 25 V,
12 I = V2/R
13
14 printf("\n\nResult\n\n")
15 printf("\nResistance(R): %.0f Ohms",R)
16 printf("\n Current when voltage is reduced to 25 V
  is %.2E A",I)

```

---

#### Scilab code Exa 2.07 Example 7

```

1 //Problem 2.07: What is the resistance of a coil
  which draws a current of (a) 50 mA and (b) 200
  A from a 120 V supply?
2
3 //initializing the variables:
4 I1 = 0.050; // in Ampere
5 I2 = 200E-6; // in Ampere
6 V = 120; // in Volts
7
8 //calculation:
9 R1 = V/I1

```

```

10 R2 = V/I2
11
12 printf("\n\nResult\n\n")
13 printf("\nResistance (R1): %.0 f Ohms",R1)
14 printf("\nResistance (R2): %.0 f Ohms\n",R2)

```

---

### Scilab code Exa 2.08 Example 8

```

1 //Problem 2.08: A 100 W electric light bulb is
   connected to a 250 V supply. Determine (a) the
   current flowing in the bulb, and (b) the
   resistance of the bulb.
2
3 //initializing the variables:
4 P = 100; // in Watt
5 V = 250; // in Volts
6
7 //calculation:
8 I = P/V
9 R = V/I
10
11 printf("\n\nResult\n\n")
12 printf("\nCurrent (I): %.1 f Ampere(A)",I)
13 printf("\nResistance (R): %.0 f Ohms\n",R)

```

---

### Scilab code Exa 2.09 Example 9

```

1 //Problem 2.09: Calculate the power dissipated when
   a current of 4 mA flows through a resistance of 5
   k
2
3 //initializing the variables:
4 I = 0.004; // in ampere

```

```

5 R = 5000; // in ohms
6
7 //calculation:
8 P = I*I*R
9
10 printf("\n\nResult\n\n")
11 printf("\nPower(P): %.2f Watt(W)\n",P)

```

---

### Scilab code Exa 2.10 Example 10

```

1 //Problem 2.10: An electric kettle has a resistance
   of 30. What current will flow when it is
   connected to a 240 V supply? Find also the power
   rating of the kettle.
2
3 //initializing the variables:
4 V = 240; // in Volts
5 R = 30; // in ohms
6
7 //calculation:
8 I = V/R
9 P = V*I
10
11 printf("\n\nResult\n\n")
12 printf("\nCurrent(I): %.0f Ampere(A)",I)
13 printf("\nPower(P): %.0f Watt(W)\n",P)

```

---

### Scilab code Exa 2.11 Example 11

```

1 //Problem 2.11: A current of 5 A flows in the
   winding of an electric motor, the resistance of
   the winding being 100. Determine (a) the p.d.

```



across the winding, and (b) the power dissipated by the coil.

```
2
3 //initializing the variables:
4 I = 5; // in ampere
5 R = 100; // in ohms
6
7 //calculation:
8 V = I*R
9 P = I*R*I
10
11 printf("\n\nResult\n\n")
12 printf("\np.d(V): %.0f Volts(V)",V)
13 printf("\nPower(P): %.0f Watt(W)\n",P)
```

---

#### Scilab code Exa 2.12 Example 12

```
1 //Problem 2.12: The current/voltage relationship for
   two resistors A and B is as shown in Figure 2.5.
   Determine the value of the resistance of each
   resistor.
2
3 //initializing the variables:
4 I1 = 0.020; // in ampere
5 V1 = 20; // in Volts
6 I2 = 0.005; // in ampere
7 V2 = 16; // in Volts
8
9 //calculation:
10 R1 = V1/I1
11 R2 = V2/I2
12
13 printf("\n\nResult\n\n")
14 printf("\nResistance(R1): %.0f Ohms",R1)
15 printf("\nResistance(R2): %.0f Ohms\n",R2)
```

---

**Scilab code Exa 2.13** Example 13

```
1 //Problem 2.13: The hot resistance of a 240 V
   filament lamp is 960. Find the current taken by
   the lamp and its power rating.
2
3 //initializing the variables:
4 V = 240; // in Volts
5 R = 960; // in ohms
6
7 //calculation:
8 I = V/R
9 P = I*V
10
11 printf("\n\nResult\n\n")
12 printf("\nCurrent (I): %.2 f Ampere(A)",I)
13 printf("\nPower (P): %.0 f Watt(W)\n",P)
```

---

**Scilab code Exa 2.14** Example 14

```
1 //Problem 2.14: A 12 V battery is connected across a
   load having a resistance of 40ohms. Determine
   the current flowing in the load, the power
   consumed and the energy dissipated in 2 minutes.
2
3 //initializing the variables:
4 V = 12; // in Volts
5 R = 40; // in ohms
6 t = 120; // in sec
7
8 //calculation:
```

```

9 I = V/R
10 P = I*V
11 E = P*t
12
13 printf("\n\nResult\n\n")
14 printf("\nCurrent(I): %.1 f Ampere(A)",I)
15 printf("\nPower(P): %.1 f Watt(W)",P)
16 printf("\nEnergy(E): %.0 f Joule(J)\n",E)

```

---

### Scilab code Exa 2.15 Example 15

```

1 //Problem 2.15: A source of e.m.f. of 15 V supplies
   a current of 2 A for six minutes. How much energy
   is provided in this time?
2
3 //initializing the variables:
4 V = 15; // in Volts
5 I = 2; // in ampere
6 t = 360; // in sec
7
8 //calculation:
9 E = V*I*t
10
11 printf("\n\nResult\n\n")
12 printf("\nEnergy(E): %.0 f Joule(J)\n",E)

```

---

### Scilab code Exa 2.16 Example 16

```

1 //Problem 2.16: Electrical equipment in an office
   takes a current of 13 A from a 240 V supply.
   Estimate the cost per week of electricity if the
   equipment is used for 30 hours each week and 1
   kWh of energy costs 7p?

```

```

2
3 //initializing the variables:
4 V = 240; // in Volts
5 I = 13; // in ampere
6 t = 30; // in hours
7 p = 7; // in paise per kWh
8
9 //calculation:
10 P = V*I
11 E = P*t/1000 // in kWh
12 C = E*p
13
14 printf("\n\nResult\n\n")
15 printf("\nCost per week: %.1f Paise(p)\n",C)

```

---

### Scilab code Exa 2.17 Example 17

```

1 //Problem 2.17: An electric heater consumes 3.6 MJ
  when connected to a 250 V supply for 40 minutes.
  Find the power rating of the heater and the
  current taken from the supply.
2
3 //initializing the variables:
4 V = 250; // in Volts
5 E = 3.6E6; // energy in J
6 t = 2400; // in sec
7
8 //calculation:
9 P = E/t
10 I = P/V
11
12 printf("\n\nResult\n\n")
13 printf("\nPower(P): %.0f Watt(W)",P)
14 printf("\nCurrent(I): %.0f Ampere(A)\n",I)

```

---

**Scilab code Exa 2.18** Example 18

```
1 //Problem 2.18: Determine the power dissipated by
   the element of an electric fire of resistance 20
   ohms when a current of 10 A flows through it. If
   the fire is on for 6 hours determine the energy
   used and the cost if 1 unit of electricity costs
   7p.
2
3 //initializing the variables:
4 R = 20; // in ohms
5 I = 10; // in ampere
6 t = 6; // in hours
7 p = 7; // in paise per kWh
8
9 //calculation:
10 P = I*I*R
11 E = P*t/1000 // in kWh
12 C = E*p
13
14 printf("\n\nResult\n\n")
15 printf("\nPower(P): %.0f Watt(W)",P)
16 printf("\nCost per week: %.0f Paise(p)\n",C)
```

---

**Scilab code Exa 2.19** Example 19

```
1 //Problem 2.19: A business uses two 3 kW fires for
   an average of 20 hours each per week, and six 150
   W lights for 30 hours each per week. If the cost
   of electricity is 7p per unit, determine the
   weekly cost of electricity to the business.
2
```

```
3 //initializing the variables:
4 P1 = 3; // in kW
5 P2 = 150; // in Watt
6 n1 = 2; // no. of P1 Equips
7 n2 = 6; // no. of P2 Equips
8 t1 = 20; // in hours each per week
9 t2 = 30; // in hours each per week
10 p = 7; // in paise per kWh
11
12 //calculation:
13 E1 = P1*t1*n1 // in kWh by two P1 eqips
14 E2 = P2*t2*n2/1000 // in kWh by six P2 eqips
15 Et = E1 + E2
16 C = Et * 7
17 printf("\n\nResult\n\n")
18 printf("\nCost per week: %.0f Paise(p)\n",C)
```

---

# Chapter 3

## Resistance variation

Scilab code Exa 3.01 Example 1

```
1 //Problem 3.01: The resistance of a 5 m length of
  wire is 600 ohms. Determine (a) the resistance of
  an 8 m length of the same wire, and (b) the
  length of the same wire when the resistance is
  420 ohms.
2
3 //initializing the variables:
4 R = 600; // in ohms
5 L = 5; // in meter
6 L1 = 8; // in meter
7 R2 = 420; // in ohms
8
9 //calculation:
10 R1 = R*L1/L
11 L2 = R2*L/R
12
13 printf("\n\nResult\n\n")
14 printf("\n(a) Resistance %.0f Ohms",R1)
15 printf("\n(b) Length: %.1f meters(m)\n",L2)
```

---

### Scilab code Exa 3.02 Example 2

```
1 //Problem 3.02: A piece of wire of cross-sectional
   area 2 mm2 has a resistance of 300 ohms. Find (a)
   the resistance of a wire of the same length and
   material if the cross-sectional area is 5 mm2, (b
   ) the cross-sectional area of a wire of the same
   length and material of resistance 750 ohms.
2
3 //initializing the variables:
4 R = 300; // in ohms
5 A = 2; // in mm2
6 A1 = 5; // in mm2
7 R2 = 750; // in ohms
8
9 //calculation:
10 R1 = R*A/A1
11 A2 = R*A/R2
12
13 printf("\n\nResult\n\n")
14 printf("\n(a) Resistance %.0f Ohms",R1)
15 printf("\n(b)C.S.A: %.1f mm2\n",A2)
```

---

### Scilab code Exa 3.03 Example 3

```
1 //Problem 3.03: A wire of length 8 m and cross-
   sectional area 3 mm2 has a resistance of 0.16
   ohms. If the wire is drawn out until its
   crossectional area is 1 mm2, determine the
   resistance of the wire.
2
3 //initializing the variables:
```



```

4 R = 0.16; // in ohms
5 A = 3; // in mm2
6 L = 8; // in m
7 A1 = 1; // in mm2
8
9 //calculation:
10 L1 = L*3
11 R1 = R*A*L1/(A1*L)
12
13 printf("\n\nResult\n\n")
14 printf("\nResistance %.2 f Ohms\n",R1)

```

---

#### Scilab code Exa 3.04 Example 4

```

1 //Problem 3.04: Calculate the resistance of a 2 km
   length of aluminium overhead power cable if the
   cross-sectional area of the cable is 100 mm2.
   Take the resistivity of aluminium to be 0.03E-6
   ohm m.
2
3 //initializing the variables:
4 A = 100E-6; // in m2
5 L = 2000; // in m
6 p = 0.03E-6; // in ohm m
7
8 //calculation:
9 R = p*L/A
10
11 printf("\n\nResult\n\n")
12 printf("\nResistance %.1 f Ohms\n",R)

```

---

#### Scilab code Exa 3.05 Example 5

```

1 //Problem 3.05: Calculate the cross-sectional area,
   in mm2, of a piece of copper wire, 40 m in length
   and having a resistance of 0.25 ohms. Take the
   resistivity of copper as 0.02E-6ohm m.
2
3 //initializing the variables:
4 R = 0.25; // in ohms
5 L = 40; // in m
6 p = 0.02E-6; // in ohm m
7
8 //calculation:
9 A = p*L*1E6/R
10
11 printf("\n\nResult\n\n")
12 printf("\nC.S.A %.1 f Ohms\n",A)

```

---

### Scilab code Exa 3.06 Example 6

```

1 //Problem 3.06: The resistance of 1.5 km of wire of
   cross-sectional area 0.17 mm2 is 150 ohms.
   Determine the resistivity of the wire.
2
3 //initializing the variables:
4 R = 150; // in ohms
5 L = 1500; // in m
6 A = 0.17E-6; // in m2
7
8 //calculation:
9 p = R*A/L
10
11 printf("\n\nResult\n\n")
12 printf("\nresistivity %.3E Ohm m\n",p)

```

---

### Scilab code Exa 3.07 Example 7

```
1 //Problem 3.07: Determine the resistance of 1200 m
   of copper cable having a diameter of 12 mm if the
   resistivity of copper is 1.7E-8 ohm m.
2
3 //initializing the variables:
4 d = 0.012; // in m
5 L = 1200; // in m
6 p = 1.7E-8; // in ohm m
7 pi = 3.14;
8
9 //calculation:
10 A = pi*d*d/4
11 R = p*L/A
12
13 printf("\n\nResult\n\n")
14 printf("\nresistance %.3f Ohm\n",R)
```

---

### Scilab code Exa 3.08 Example 8

```
1 //Problem 3.08: A coil of copper wire has a
   resistance of 100 ohms when its temperature is 0
   C. Determine its resistance at 70 C if the
   temperature coefficient of resistance of copper
   at 0 C is 0.0043/ C
2
3 //initializing the variables:
4 R0 = 100; // in ohms
5 T0 = 0; // in C
6 T1 = 70; // in C
7 a0 = 0.0043; // in per C
8 pi = 3.14;
9
10 //calculation:
```

```

11 R70 = R0*[1 + (a0*T1)]
12
13 printf("\n\nResult\n\n")
14 printf("\nresistance %.1 f Ohm\n",R70)

```

---

### Scilab code Exa 3.09 Example 9

```

1 //Problem 3.09: An aluminium cable has a resistance
  of 27 ohms at a temperature of 35 C . Determine
  its resistance at 0 C . Take the temperature
  coefficient of resistance at 0 C to be 0.0038/
  C
2
3 //initializing the variables:
4 R1 = 27; // in ohms
5 T0 = 0; // in C
6 T1 = 35; // in C
7 a0 = 0.0038; // in per C
8 pi = 3.14;
9
10 //calculation:
11 R0 = R1/[1 + (a0*T1)]
12
13 printf("\n\nResult\n\n")
14 printf("\nresistance %.2 f Ohm\n",R0)

```

---

### Scilab code Exa 3.10 Example 10

```

1 //Problem 3.10: A carbon resistor has a resistance
  of 1 kohms at 0 C . Determine its resistance at
  80 C . Assume that the temperature coefficient of
  resistance for carbon at 0 C is 0.0005/ C
2

```

```

3 //initializing the variables:
4 R0 = 1000; // in ohms
5 T0 = 0; // in C
6 T1 = 80; // in C
7 a0 = -0.0005; // in per C
8 pi = 3.14;
9
10 //calculation:
11 R80 = R0*[1 + (a0*T1)]
12
13 printf("\n\nResult\n\n")
14 printf("\nresistance %.0f Ohm\n",R80)

```

---

### Scilab code Exa 3.11 Example 11

```

1 //Problem 3.11: A coil of copper wire has a
   resistance of 10 ohms at 20 C . If the
   temperature coefficient of resistance of copper
   at 20 C is 0.004/ C determine the resistance of
   the coil when the temperature rises to 100 C .
2
3 //initializing the variables:
4 R20 = 10; // in ohms
5 T0 = 20; // in C
6 T1 = 100; // in C
7 a20 = 0.004; // in per C
8 pi = 3.14;
9
10 //calculation:
11 R100 = R20*[1 + (a20)*(T1 - T0)]
12
13 printf("\n\nResult\n\n")
14 printf("\nresistance %.1f Ohm\n",R100)

```

---

**Scilab code Exa 3.12** Example 12

```
1 //Problem 3.12: The resistance of a coil of
  aluminium wire at 18 C is 200 ohms. The
  temperature of the wire is increased and the
  resistance rises to 240 ohms. If the temperature
  coefficient of resistance of aluminium is 0.0039/
  C at 18 C determine the temperature to which
  the coil has risen.
2
3 //initializing the variables:
4 R18 = 200; // in ohms
5 R1 = 240; // in ohms
6 T0 = 18; // in C
7 a18 = 0.0039; // in per C
8 pi = 3.14;
9
10 //calculation:
11 T1 = (((R1/R18)-1)/a18) + T0
12
13 printf("\n\nResult\n\n")
14 printf("\nTemperature %.2f C\n",T1)
```

---

**Scilab code Exa 3.13** Example 13

```
1 //Problem 3.13: Some copper wire has a resistance of
  200 ohms at 20 C . A current is passed through
  the wire and the temperature rises to 90 C .
  Determine the resistance of the wire at 90 C ,
  correct to the nearest ohm, assuming that the
  temperature coefficient of resistance is 0.004/
  C at 0 C .
```

```
2
3 //initializing the variables:
4 R20 = 200; // in ohms
5 T0 = 20; // in C
6 T1 = 90; // in C
7 a0 = 0.004; // in per C
8 pi = 3.14;
9
10 //calculation:
11 R90 = R20*[1 + (a0*T1)]/[1 + (a0*T0)]
12
13 printf("\n\nResult\n\n")
14 printf("\nResistance %.0f ohms\n",R90)
```

---

# Chapter 4

## Chemical effects of electricity

Scilab code Exa 4.01 Example 1

```
1 //Problem 4.01: Eight cells , each with an internal
   resistance of 0.2 ohms and an e.m.f. of 2.2 V are
   connected (a) in series , (b) in parallel.
   Determine the e.m.f. and the internal resistance
   of the batteries so formed.
2
3 //initializing the variables:
4 R = 0.2; // in ohms
5 n = 8; // no. of cells
6 e = 2.2; // in volts
7
8 //calculation:
9 es = n*e
10 ep = e
11 Rs = n*R
12 Rp = R/n
13
14 printf("\n\nResult\n\n")
15 printf("\n(a) Resistance %.1f ohms",Rs)
16 printf("\n(a) e.m. f %.1f Volts(V)",es)
17 printf("\n(b) Resistance %.3f ohms",Rp)
```



```
18 printf("\n(b) e.m.f %.1f Volts(V)", ep)
```

---

#### Scilab code Exa 4.02 Example 2

```
1 //Problem 4.02: A cell has an internal resistance of
    0.02 ohms and an e.m.f. of 2.0 V. Calculate its
    terminal p.d. if it delivers (a) 5 A, (b) 50 A
2
3 //initializing the variables:
4 r = 0.02; // in ohms
5 e = 2; // in volts
6 I1 = 5; // in Amperes
7 I2 = 50; // in Amperes
8
9 //calculation:
10 pd1 = e - (I1*r)
11 pd2 = e - (I2*r)
12
13 printf("\n\nResult\n\n")
14 printf("\n(a)p.d %.1f Volts(V)", pd1)
15 printf("\n(b)p.d %.1f Volts(V)\n", pd2)
```

---

#### Scilab code Exa 4.03 Example 3

```
1 //Problem 4.03: The p.d. at the terminals of a
    battery is 25 V when no load is connected and 24
    V when a load taking 10 A is connected. Determine
    the internal resistance of the battery.
2
3 //initializing the variables:
4 e1 = 25; // in volts
5 e2 = 24; // in volts
6 I2 = 10; // in Amperes
```

```

7
8 //calculation:
9 r = (e1 - e2)/I2
10
11 printf("\n\nResult\n\n")
12 printf("\n Resistance %.1 f Ohms\n",r)

```

---

#### Scilab code Exa 4.04 Example 4

```

1 //Problem 4.04: Ten 1.5 V cells , each having an
  internal resistance of 0.2 ohms, are connected in
  series to a load of 58 ohms . Determine(a) the
  current flowing in the circuit and (b) the p.d.
  at the battery terminals.
2
3 //initializing the variables:
4 r = 0.2; // in ohms
5 n = 10; // no. of cells
6 e = 1.5; // in volts
7 R = 58; // in ohms
8
9 //calculation:
10 es = n*e
11 rs = n*r
12 I = es/(rs + R)
13 pd = es - (I*rs)
14
15 printf("\n\nResult\n\n")
16 printf("\n (a) Current %.2 f Amperes(A)",I)
17 printf("\n (b)p.d %.1 f Volts(V)\n",pd)

```

---

# Chapter 5

## Series and parallel networks

Scilab code Exa 5.01 Example 1

```
1 //Problem 5.01: For the circuit shown in Figure 5.2,
   determine (a) the battery voltage V, (b) the
   total resistance of the circuit , and (c) the
   values of resistance of resistors R1, R2 and R3,
   given that the p.d. s across R1, R2 and R3 are
   5 V, 2 V and 6 V respectively.
2
3 //initializing the variables:
4 V1 = 5; // in volts
5 V2 = 2; // in volts
6 V3 = 6; // in volts
7 I = 4; // in Amperes
8
9 //calculation:
10 Vt = V1 + V2 + V3
11 Rt = Vt/I
12 R1 = V1/I
13 R2 = V2/I
14 R3 = V3/I
15
16 printf("\n\nResult\n\n")
```

```
17 printf("\n (a) Total Voltage %.0f Volts(V)",Vt)
18 printf("\n (b) Total Resistance %.2f Ohms",Rt)
19 printf("\n (c) Resistance(R1) %.2f Ohms",R1)
20 printf("\n (c) Resistance(R2) %.1f Ohms",R2)
21 printf("\n (c) Resistance(R3) %.1f Ohms",R3)
```

---

### Scilab code Exa 5.02 Example 2

```
1 //Problem 5.02: For the circuit shown in Figure 5.3,
   determine the p.d. across resistor R3. If the
   total resistance of the circuit is 100 ohms,
   determine the current flowing through resistor R1
   . Find also the value of resistor R2
2
3 //initializing the variables:
4 V1 = 10; // in volts
5 V2 = 4; // in volts
6 Vt = 25; // in volts
7 Rt = 100; // in ohms
8
9 //calculation:
10 V3 = Vt - V1 - V2
11 I = Vt/Rt
12 R2 = V2/I
13
14 printf("\n\nResult\n\n")
15 printf("\n (a) Voltage(V3) %.0f Volts(V)",V3)
16 printf("\n (b) current %.2f Amperes(A)",I)
17 printf("\n (c) Resistance(R2) %.0f Ohms",R2)
```

---

### Scilab code Exa 5.03 Example 3

```

1 //Problem 5.03: A 12 V battery is connected in a
  circuit having three series-connected resistors
  having resistances of 4 ohms, 9 ohms and 11 ohms.
  Determine the current flowing through, and the p
  .d. across the 9 ohms resistor. Find also the
  power dissipated in the 11 ohms resistor.
2
3 //initializing the variables:
4 Vt = 12; // in volts
5 R1 = 4; // in ohms
6 R2 = 9; // in ohms
7 R3 = 11; // in ohms
8
9 //calculation:
10 Rt = R1 + R2 + R3
11 I = Vt/Rt
12 V9 = I*R2
13 P11 = I*I*R3
14
15 printf("\n\nResult\n\n")
16 printf("\n (a) current %.1 f Amperes(A)",I)
17 printf("\n (b) Voltage(V2) %.1 f Volts(V)",V9)
18 printf("\n (c) Power %.2 f Watt(W)",P11)

```

---

#### Scilab code Exa 5.04 Example 4

```

1 //Problem 5.04:Determine the value of voltage V
  shown in Figure 5.6.
2
3 //initializing the variables:
4 Vt = 50; // in volts
5 R1 = 4; // in ohms
6 R2 = 6; // in ohms
7
8 //calculation:

```

```

9 Rt = R1 + R2
10 I = Vt/Rt
11 V2 = I*R2
12
13 printf("\n\nResult\n\n")
14 printf("\n Voltage (V) %.0f Volts(V)\n",V2)

```

---

### Scilab code Exa 5.05 Example 5

```

1 //Problem 5.05:Two resistors are connected in series
  across a 24 V supply and a current of 3 A flows
  in the circuit. If one of the resistors has a
  resistance of 2 ohms determine (a) the value of
  the other resistor , and (b) the p.d. across the 2
  resistor. If the circuit is connected for 50
  hours , how much energy is used?
2
3 //initializing the variables:
4 Vt = 24; // in volts
5 R1 = 2; // in ohms
6 I = 3; // in Amperes
7 t = 50; // in hrs
8
9 //calculation:
10 V1 = I*R1
11 R2 = [Vt-(I*R1)]/I
12 E = Vt*I*t
13
14 printf("\n\nResult\n\n")
15 printf("\n (a) Voltage (V1) %.0f Volts (V)",V1)
16 printf("\n (b) Resistance (R2) %.0f Ohms",R2)
17 printf("\n (a) Energy (E) %.2E Wh",E)

```

---

### Scilab code Exa 5.06 Example 6

```
1 //Problem 5.06:For the circuit shown in Figure 5.10,  
    determine (a) the reading on the ammeter, and (b  
    ) the value of resistor R2  
2  
3 //initializing the variables:  
4 R1 = 5; // in ohms  
5 R3 = 20; // in ohms  
6 I1 = 8; // in Amperes  
7 It = 11; // in Amperes  
8  
9 //calculation:  
10 Vt = I1*R1  
11 I3 = Vt/R3  
12 R2 = Vt/[It - I1 - I3]  
13  
14 printf("\n\nResult\n\n")  
15 printf("\n (a)Ammeter Reading %.0 f Amperes(A)",I3)  
16 printf("\n (b)Resistance(R2) %.0 f Ohms\n",R2)
```

---

### Scilab code Exa 5.07 Example 7

```
1 //Problem 5.07: Two resistors , of resistance 3 ohms  
    and 6 ohms, are connected in parallel across a  
    battery having a voltage of 12 V. Determine (a)  
    the total circuit resistance and (b) the current  
    flowing in the 3 ohms resistor.  
2  
3 //initializing the variables:  
4 R1 = 3; // in ohms  
5 R2 = 6; // in ohms  
6 Vt = 12; // in volts  
7  
8 //calculation:
```

```

9 Rt = R1*R2/[R1 + R2]
10 I1 = [Vt/R1]
11
12 printf("\n\nResult\n\n")
13 printf("\n (a) Total Resistance %.0f Ohms", Rt)
14 printf("\n (b) Current(I1) %.0f Amperes(A)\n", I1)

```

---

#### Scilab code Exa 5.08 Example 8

```

1 //Problem 5.08: For the circuit shown in Figure
   5.12, find (a) the value of the supply voltage V
   and (b) the value of current I.
2
3 //initializing the variables:
4 R1 = 10; // in ohms
5 R2 = 20; // in ohms
6 R3 = 60; // in ohms
7 I2 = 3; // in Amperes
8
9 //calculation:
10 Vt = I2*R2
11 I1 = Vt/R1
12 I3 = Vt/R3
13 I = I1 +I2 + I3
14
15 printf("\n\nResult\n\n")
16 printf("\n (a) Voltage(V) %.0f Volts(V)", Vt)
17 printf("\n (b) Total Current(I) %.0f Amperes(A)", I)

```

---

#### Scilab code Exa 5.10 Example 10

```

1 //Problem 5.10: Find the equivalent resistance for
   the circuit shown in Figure 5.17.

```



```

2
3 //initializing the variables:
4 R1 = 1; // in ohms
5 R2 = 2.2; // in ohms
6 R3 = 3; // in ohms
7 R4 = 6; // in ohms
8 R5 = 18; // in ohms
9 R6 = 4; // in ohms
10
11
12 //calculation:
13 R0 = 1/[(1/3) + (1/6) + (1/18)]
14 Rt = R1 + R2 + R0 + R6
15
16 printf("\n\nResult\n\n")
17 printf("\n Equivalent Resistance %.0f Ohms\n",Rt)

```

---

#### Scilab code Exa 5.11 Example 11

```

1 //Problem 5.11: For the series-parallel arrangement
   shown in Figure 5.19, find (a) the supply current
   , (b) the current flowing through each resistor
   and (c) the p.d. across each resistor.
2
3 //initializing the variables:
4 R1 = 2.5; // in ohms
5 R2 = 6; // in ohms
6 R3 = 2; // in ohms
7 R4 = 4; // in ohms
8 Vt = 200; // in volts
9
10 //calculation:
11 R0 = 1/[(1/R2) + (1/R3)]
12 Rt = R1 + R0 + R4
13 It = Vt/Rt

```

```

14 I1 = It
15 I4 = It
16 I2 = R3*It/(R3+R2)
17 I3 = It - I2
18 V1 = I1*R1
19 V2 = I2*R2
20 V3 = I3*R3
21 V4 = I4*R4
22
23 printf("\n\nResult\n\n")
24 printf("\n (a) Total Current Supply %.0f Amperes(A)",
    It)
25 printf("\n (b) Current through resistors (R1, R2, R3,
    R4)%.0f, %.2f, %.2f, %.0f Amperes(A)
    respectively", I1, I2, I3, I4)
26 printf("\n (c) voltage across resistors (R1, R2, R3,
    R4)%.1f, %.1f, %.1f, %.0f Volts(V) respectively",
    V1, V2, V3, V4)

```

---

### Scilab code Exa 5.12 Example 12

```

1 //Problem 5.12: For the circuit shown in Figure 5.21
    calculate (a) the value of resistor Rx such that
    the total power dissipated in the circuit is 2.5
    kW, and (b) the current flowing in each of the
    four resistors.
2
3 //initializing the variables:
4 R1 = 15; // in ohms
5 R2 = 10; // in ohms
6 R3 = 38; // in ohms
7 Vt = 250; // in volts
8 P = 2500; // in Watt
9
10 //calculation:

```

```

11 It = P/Vt
12 I2 = R1*It/(R1+R2)
13 I1 = It - I2
14 Re1 = 1/[(1/R1) + (1/R2)]
15 Rt = Vt/It
16 Re2 = Rt - Re1
17 Rx = 1/[(1/Re2) - (1/R3)]
18 I4 = R3*It/(R3+Rx)
19 I3 = It - I4
20
21 printf("\n\nResult\n\n")
22 printf("\n (a) Resistance (Rx) %.0f Ohms",Rx)
23 printf("\n (b) Current through resistors (R1, R2, R3,
      R4): %.0f, %.0f, %.0f, %.0f Amperes(A)
      respectively",I1, I2, I3, I4)

```

---

### Scilab code Exa 5.13 Example 13

```

1 //Problem 5.13: For the arrangement shown in Figure
  5.22, find the current Ix
2
3 //initializing the variables:
4 R1 = 8; // in ohms
5 R2 = 2; // in ohms
6 R3 = 1.4; // in ohms
7 R4 = 9; // in ohms
8 R5 = 2; // in ohms
9 Vt = 17; // in volts
10
11 //calculation:
12 R01 = R1*R2/(R1 + R2)
13 R02 = R01 + R3
14 R03 = R4*R02/(R4 +R02)
15 Rt = R5 + R03
16 It = Vt/Rt

```

```

17 I1 = R4*It/(R4 + R02)
18 Ix = R2*I1/(R1 + R2)
19
20 printf("\n\nResult\n\n")
21 printf("\n Current (Ix) %.1 f Amperes (A)\n", Ix)

```

---

#### Scilab code Exa 5.14 Example 14

```

1 //Problem 5.14: If three identical lamps are
   connected in parallel and the combined resistance
   is 150 ohms, find the resistance of one lamp.
2
3 //initializing the variables:
4 Rt = 150; // in ohms
5 n = 3; // no. of identical lamp
6
7 //calculation:
8 R = Rt*3 // (1/Rt)=(1/R)+(1/R)+(1/R)
9
10 printf("\n\nResult\n\n")
11 printf("\n Resistance %.0 f Ohms\n", R)

```

---

#### Scilab code Exa 5.15 Example 15

```

1 //Problem 5.15: Three identical lamps A, B and C are
   connected in series across a 150 V supply. State
   (a) the voltage across each lamp, and (b) the
   effect of lamp C failing.
2
3 //initializing the variables:
4 //series connection
5 n = 3; // no. of identical lamp
6 Vt = 150; // in volts

```

```
7
8 //calculation:
9 V = Vt/3 // Since each lamp is identical , then V
    volts across each.
10
11 printf("\n\nResult\n\n")
12 printf("\n Voltage across each resistor = %.0f Volts
    (V)",V)
```

---

# Chapter 6

## Capacitors and capacitance

Scilab code Exa 6.01 Example 1

```
1 //Problem 6.01:(a) Determine the p.d. across a 4 F
   capacitor when charged with 5 mC. (b) Find the
   charge on a 50 pF capacitor when the voltage
   applied to it is 2 kV.
2
3 //initializing the variables:
4 C1 = 4E-6; // in Farad
5 C2 = 50E-12; // in Farad
6 Q1 = 5E-3; // in Coulomb
7 V2 = 2000; // in volts
8
9 //calculation:
10 V1 = Q1/C1
11 Q2 = C2*V2
12
13 printf("\n\nResult\n\n")
14 printf("\n (a)P.d %.0f Volts(V)",V1)
15 printf("\n (b)Charge(Q) %.2E Coulomb(C)",Q2)
```

---

### Scilab code Exa 6.02 Example 2

```
1 //Problem 6.02: A direct current of 4 A flows into a
   previously uncharged 20 F capacitor for 3 ms.
   Determine the pd between the plates.
2
3 //initializing the variables:
4 I = 4; // in amperes
5 C = 20E-6; // in Farad
6 t = 3E-3; // in sec
7
8 //calculation:
9 Q = I*t
10 V = Q/C
11
12 printf("\n\nResult\n\n")
13 printf("\n (a)P.d %.0f Volts(V)\n",V)
```

---

### Scilab code Exa 6.03 Example 3

```
1 //Problem 6.03:A 5 F capacitor is charged so that
   the pd between its plates is 800 V. Calculate how
   long the capacitor can provide an average
   discharge current of 2 mA.
2
3 //initializing the variables:
4 I = 2E-3; // in amperes
5 C = 5E-6; // in Farad
6 V = 800; // in volts
7
8 //calculation:
9 Q = C*V
10 t = Q/I
11
12 printf("\n\nResult\n\n")
```

```
13 printf("\n capacitor can provide an average
    discharge current of 2mA for %.0f Sec\n",t)
```

---

#### Scilab code Exa 6.04 Example 4

```
1 //Problem 6.04: Two parallel rectangular plates
    measuring 20 cm by 40 cm carry an electric charge
    of 0.2 C. Calculate the electric flux density.
    If the plates are spaced 5 mm apart and the
    voltage between them is 0.25 kV determine the
    electric field strength.
2
3 //initializing the variables:
4 Q = 0.2E-6; // in Coulomb
5 A = 800E-4; // in m2
6 d = 0.005; // in m
7 V = 250; // in Volts
8
9 //calculation:
10 D = Q/A
11 E = V/d
12
13 printf("\n\nResult\n\n")
14 printf("\n (a) Electric flux density D %.2E C/m2",D)
15 printf("\n (b) Electric field strength E %.2E V/m\n",
    E)
```

---

#### Scilab code Exa 6.05 Example 5

```
1 //Problem 6.05: The flux density between two plates
    separated by mica of relative permittivity 5 is 2
    C/m2. Find the voltage gradient between the
    plates.
```



```

2
3 //initializing the variables:
4 D = 2E-6; // in C/m2
5 e0 = 8.85E-12; // in F/m
6 er = 5;
7
8 //calculation:
9 E = D/(e0*er)
10
11 printf("\n\nResult\n\n")
12 printf("\n Electric field strength E %.2E V/m\n",E)

```

---

#### Scilab code Exa 6.06 Example 6

```

1 //Problem 6.06: Two parallel plates having a pd of
   200 V between them are spaced 0.8 mm apart. What
   is the electric field strength? Find also the
   flux density when the dielectric between the
   plates is (a) air, and (b) polythene of relative
   permittivity 2.3
2
3 //initializing the variables:
4 d = 0.8E-3; // in m
5 e0 = 8.85E-12; // in F/m
6 era = 1; // for air
7 erp = 2.3; // for polythene
8 V =200; // in Volts
9
10 //calculation:
11 E = V/d
12 //for air
13 Da = E*e0*era
14 //for polythene
15 Dp = E*e0*erp
16 printf("\n\nResult\n\n")

```

```

17 printf("\n (a) Electric flux density for air %.2E C/
    m2", Da)
18 printf("\n (b) Electric flux density for polythene %
    .2E C/m2\n", Dp)

```

---

### Scilab code Exa 6.07 Example 7

```

1 //Problem 6.07: (a) A ceramic capacitor has an
    effective plate area of 4 cm2 separated by 0.1 mm
    of ceramic of relative permittivity 100.
    Calculate the capacitance of the capacitor in
    picofarads. (b) If the capacitor in part (a) is
    given a charge of 1.2 C what will be the pd
    between the plates?
2
3 //initializing the variables:
4 A = 4E-4; // in m2
5 d = 0.1E-3; // in m
6 e0 = 8.85E-12; // in F/m
7 er = 100;
8 Q = 1.2E-6; // in coulomb
9
10 //calculation:
11 C = e0*er*A/d
12 V = Q/C
13
14 printf("\n\nResult\n\n")
15 printf("\n (a) Capacitance %.2E F", C)
16 printf("\n (b) P.d.= %.0f Volts(V)\n", V)

```

---

### Scilab code Exa 6.08 Example 8

```

1 //Problem 6.08: A waxed paper capacitor has two
  parallel plates , each of effective area 800 cm2.
  If the capacitance of the capacitor is 4425 pF
  determine the effective thickness of the paper if
  its relative permittivity is 2.5
2
3 //initializing the variables:
4 A = 800E-4; // in m2
5 C = 4425E-12; // in Farads
6 e0 = 8.85E-12; // in F/m
7 er = 2.5;
8
9 //calculation:
10 d = e0*er*A/C
11
12 printf("\n\nResult\n\n")
13 printf("\n Thickness  %.2E m\n" ,d)

```

---

#### Scilab code Exa 6.09 Example 9

```

1 //Problem 6.09: A parallel plate capacitor has
  nineteen interleaved plates each 75 mm by 75 mm
  separated by mica sheets 0.2 mm thick. Assuming
  the relative permittivity of the mica is 5,
  calculate the capacitance of the capacitor.
2
3 //initializing the variables:
4 n = 19; // no. of plates
5 L = 75E-3; // in m
6 B = 75E-3; // in m
7 d = 0.2E-3; // in m
8 e0 = 8.85E-12; // in F/m
9 er = 5;
10
11 //calculation:

```

```

12 A = L*B
13 C = e0*er*A*(n-1)/d
14
15 printf("\n\nResult\n\n")
16 printf("\n Capacitance %.2E F\n",C)

```

---

### Scilab code Exa 6.10 Example 10

```

1 //Problem 6.10: Calculate the equivalent capacitance
   of two capacitors of 6 F and 4 F connected (
   a) in parallel and (b) in series
2
3 //initializing the variables:
4 C1 = 6E-6; // in Farads
5 C2 = 4E-6; // in Farads
6
7 //calculation:
8 // in Parallel
9 Cp = C1 +C2
10 // in Series
11 Cs = 1/[(1/C1) + (1/C2)]
12
13 printf("\n\nResult\n\n")
14 printf("\n (a) Capacitance in parallel %.2E F",Cp)
15 printf("\n (b) Capacitance in Series %.2E F\n",Cs)

```

---

### Scilab code Exa 6.11 Example 11

```

1 //Problem 6.11: What capacitance must be connected
   in series with a 30 F capacitor for the
   equivalent capacitance to be 12 F?
2
3 //initializing the variables:

```

```

4 C1 = 30E-6; // in Farads
5 Cs = 12E-6; // in Farads
6
7 //calculation:
8 // in Series
9 C2 = 1/[(1/Cs) - (1/C1)]
10
11 printf("\n\nResult\n\n")
12 printf("\n (a) Capacitance in series %.2E F\n",C2)

```

---

### Scilab code Exa 6.12 Example 12

```

1 //Problem 6.12: Capacitances of 1 F , 3 F , 5 F
   and 6 F are connected in parallel to a direct
   voltage supply of 100 V. Determine (a) the
   equivalent circuit capacitance , (b) the total
   charge and (c) the charge on each capacitor.
2
3 //initializing the variables:
4 C1 = 1E-6; // in Farads
5 C2 = 3E-6; // in Farads
6 C3 = 5E-6; // in Farads
7 C4 = 6E-6; // in Farads
8 Vt = 100; // in Volts
9
10 //calculation:
11 // in Parallel
12 Cp = C1 + C2 + C3 + C4
13 Qt = Vt*Cp
14 Q1 = C1*Vt
15 Q2 = C2*Vt
16 Q3 = C3*Vt
17 Q4 = C4*Vt
18
19 printf("\n\nResult\n\n")

```

```

20 printf("\n (a)Equivalent Capacitance in Parallel %.2
    E F", Cp)
21 printf("\n (b)Total charge %.2E C", Qt)
22 printf("\n (c)Charge on each capacitors (C1, C2, C3,
    C4) %.2E C, %.2E C, %.2E C, %.2E C respectively"
    , Q1, Q2, Q3, Q4)

```

---

### Scilab code Exa 6.13 Example 13

```

1 //Problem 6.13: Capacitances of 3 F , 6 F and 12
    F are connected in series across a 350 V supply
    . Calculate (a) the equivalent circuit
    capacitance , (b) the charge on each capacitor and
    (c) the pd across each capacitor .
2
3 //initializing the variables :
4 C1 = 3E-6; // in Farads
5 C2 = 6E-6; // in Farads
6 C3 = 12E-6; // in Farads
7 Vt = 350; // in Volts
8
9 //calculation :
10 // in series
11 Cs = 1/[(1/C1) + (1/C2) + (1/C3)]
12 Qt = Vt*Cs
13 V1 = Qt/C1
14 V2 = Qt/C2
15 V3 = Qt/C3
16
17 printf("\n\nResult\n\n")
18 printf("\n (a)Equivalent Capacitance in Series %.2E
    F", Cs)
19 printf("\n (b)Charge on each capacitors (C1, C2, C3)
    %.2E C", Qt)
20 printf("\n (b)P.d Across each capacitors (C1, C2, C3

```

```
) %.0f V, %.0f V, %.0f V respectively",V1, V2, V3
)
```

---

#### Scilab code Exa 6.14 Example 14

```
1 //Problem 6.14: A capacitor is to be constructed so
  that its capacitance is 0.2 F and to take a p.d
  . of 1.25 kV across its terminals. The dielectric
  is to be mica which, after allowing a safety
  factor of 2, has a dielectric strength of 50 MV/m
  . Find (a) the thickness of the mica needed, and
  (b) the area of a plate assuming a two-plate
  construction. (Assume  $\epsilon_r$  for mica to be 6)
2
3 //initializing the variables:
4 C = 0.2E-6; // in Farads
5 V = 1250; // in Volts
6 E = 50E6; // in V/m
7 e0 = 8.85E-12; // in F/m
8 er = 6;
9
10 //calculation:
11 d = V/E
12 A = C*d/e0/er
13
14 printf("\n\nResult\n\n")
15 printf("\n (a) Thickness %.2E m",d)
16 printf("\n (b) Area of plate is %.2E m2 \n",A)
```

---

#### Scilab code Exa 6.15 Example 15

```

1 //Problem 6.15: (a) Determine the energy stored in a
   3 F capacitor when charged to 400 V. (b) Find
   also the average power developed if this energy
   is dissipated in a time of 10 s
2
3 //initializing the variables:
4 C = 3E-6; // in Farads
5 V = 400; // in Volts
6 t = 10E-6; // in secs
7
8 //calculation:
9 W = C*V*V/2
10 P = W/t
11
12 printf("\n\nResult\n\n")
13 printf("\n (a)Energy stored %.2f J",W)
14 printf("\n (b)Power developed %.2E W ",P)

```

---

#### Scilab code Exa 6.16 Example 16

```

1 //Problem 6.16: A 12 F capacitor is required to
   store 4 J of energy. Find the pd to which the
   capacitor must be charged.
2
3 //initializing the variables:
4 C = 12E-6; // in Farads
5 W = 4; // in Joules
6
7 //calculation:
8 V = (2*W/C)^0.5
9
10 printf("\n\nResult\n\n")
11 printf("\n P.d %.1f V\n",V)

```

---



Scilab code Exa 6.17 Example 17

```
1 //Problem 6.17: A capacitor is charged with 10 mC.  
   If the energystored is 1.2 J find (a) the voltage  
   and (b) the capacitance.  
2  
3 //initializing the variables:  
4 W = 1.2; // in Joules  
5 Q = 10E-3; // in Coulomb  
6  
7 //calculation:  
8 V = 2*W/Q  
9 C = Q/V  
10  
11 printf("\n\nResult\n\n")  
12 printf("\n (a)P.d %.0f V",V)  
13 printf("\n (b)Capacitance %.2E F\n",C)
```

---

# Chapter 7

## Magnetic circuits

Scilab code Exa 7.01 Example 1

```
1 //Problem 7.01: A magnetic pole face has a
   rectangular section having dimensions 200 mm by
   100 mm. If the total flux emerging from the pole
   is 150 Wb , calculate the flux density.
2
3 //initializing the variables:
4 Phi = 150E-6; // in Wb
5 l = 200E-3; // in m
6 b = 100E-3; // in m
7
8 //calculation:
9 A = l*b
10 B = Phi/A
11
12 printf("\n\nResult\n\n")
13 printf("\n Flux density %.2E T\n",B)
```

---

Scilab code Exa 7.02 Example 2

```

1 //Problem 7.02: The maximum working flux density of
  a lifting electromagnet is 1.8 T and the
  effective area of a pole face is circular in
  cross-section. If the total magnetic flux
  produced is 353 mWb, determine the radius of the
  pole face.
2
3 //initializing the variables:
4 Phi = 353E-3; // in Wb
5 B = 1.8; // in tesla
6 Pi = 3.14;
7
8 //calculation:
9 A = Phi/B
10 r = (A/Pi)^0.5
11
12 printf("\n\nResult\n\n")
13 printf("\n radius of the pole face is %.2E m\n",r)

```

---

### Scilab code Exa 7.03 Example 3

```

1 //Problem 7.03: A magnetizing force of 8000 A/m is
  applied to a circular magnetic circuit of mean
  diameter 30 cm by passing a current through a
  coil wound on the circuit. If the coil is
  uniformly wound around the circuit and has 750
  turns, find the current in the coil.
2
3 //initializing the variables:
4 H = 8000; // in A/m
5 d = 0.30; // in m
6 N = 750; // no. of turns
7 Pi = 3.14;
8
9 //calculation:

```

```

10 l = Pi*d
11 I = H*l/N
12
13 printf("\n\nResult\n\n")
14 printf("\n current I = %.2f Ampere(A)\n",I)

```

---

#### Scilab code Exa 7.04 Example 4

```

1 //Problem 7.04: A flux density of 1.2 T is produced
  in a piece of cast steel by a magnetizing force
  of 1250 A/m. Find the relative permeability of
  the steel under these conditions.
2
3 //initializing the variables:
4 B = 1.2; // in Tesla
5 H = 1250; // in A/m
6 Pi = 3.14;
7 u0 = 4*Pi*1E-7;
8
9 //calculation:
10 ur = B/(u0*H)
11
12 printf("\n\nResult\n\n")
13 printf("\n relative permeability of the steel = %.0f
  \n",ur)

```

---

#### Scilab code Exa 7.05 Example 5

```

1 //Problem 7.05: Determine the magnetic field
  strength and the mmf required to produce a flux
  density of 0.25 T in an air gap of length 12 mm.
2
3 //initializing the variables:

```

```

4 B = 0.25; // in Tesla
5 u0 = 4*%pi*1E-7;
6 l = 12E-3; // in m
7
8 //calculation:
9 H = B/u0
10 mmf = H*l
11
12 printf("\n\nResult\n\n")
13 printf("\n (a)Magnetic field strength H = %.0f A/m",
      H)
14 printf("\n (b)mmf = %.0f A\n",mmf)

```

---

#### Scilab code Exa 7.06 Example 6

```

1 //Problem 7.06: A coil of 300 turns is wound
      uniformly on a ring of non-magnetic material. The
      ring has a mean circumference of 40 cm and a
      uniform cross sectional area of 4 cm2. If the
      current in the coil is 5 A, calculate (a) the
      magnetic field strength, (b) the flux density and
      (c) the total magnetic flux in the ring.
2
3 //initializing the variables:
4 N = 300; // no. of turns
5 l = 0.40; // in m
6 A = 4E-4; // in m2
7 I = 5; // in Amperes
8 u0 = 4*%pi*1E-7;
9 ur = 1
10 //calculation:
11 H = N*I/l
12 B = u0*ur*H
13 Phi = B*A
14

```

```

15 printf("\n\nResult\n\n")
16 printf("\n (a)Magnetic field strength H = %.0f A/m
    \",H)
17 printf("\n (b)Flux Density = %.2E T",B)
18 printf("\n (c)total magnetic flux = %.2E Wb",Phi)

```

---

### Scilab code Exa 7.07 Example 7

```

1 //Problem 7.07: An iron ring of mean diameter 10 cm
  is uniformly wound with 2000 turns of wire. When
  a current of 0.25 A is passed through the coil a
  flux density of 0.4 T is set up in the iron. Find
  (a) the magnetizing force and (b) the relative
  permeability of the iron under these conditions.
2
3 //initializing the variables:
4 N = 2000; // no. of turns
5 d = 0.10; // in m
6 B = 0.4; // in Tesla
7 I = 0.25; // in Amperes
8 u0 = 4*%pi*1E-7;
9
10 //calculation:
11 l = %pi*d
12 H = N*I/l
13 ur = B/(u0*H)
14
15 printf("\n\nResult\n\n")
16 printf("\n (a)Magnetic field strength H = %.0f A/m",
    H)
17 printf("\n (b)relative permeability of the iron = %
    .0f ",ur)

```

---

### Scilab code Exa 7.08 Example 8

```
1 //Problem 7.08: A uniform ring of cast iron has a
   cross-sectional area of 10 cm2 and a mean
   circumference of 20 cm. Determine the mmf
   necessary to produce a flux of 0.3 mWb in the
   ring.
2
3 //initializing the variables:
4 A = 10E-4; // in m2
5 l = 0.20; // in m
6 Phi = 0.3E-3; // in Wb
7 u0 = 4*%pi*1E-7;
8
9 //calculation:
10 B = Phi/A
11 // from the magnetisation curve, corresponding the
   value of B
12 H = 1000
13 mmf = H*l
14 printf("\n\nResult\n\n")
15 printf("\n (a)mmf = %.0f A\n",mmf)
```

---

### Scilab code Exa 7.09 Example 9

```
1 //Problem 7.09: Determine the reluctance of a piece
   of mumetal of length 150 mm and cross-sectional
   area 1800 mm2 when the relative permeability is
   4000. Find also the absolute permeability of the
   mumetal.
2
3 //initializing the variables:
4 A = 18E-4; // in m2
5 l = 0.15; // in m
6 u0 = 4*%pi*1E-7;
```

```

7 ur = 4000;
8
9 // calculation :
10 S = 1/(u0*ur*A)
11 u = u0*ur
12
13 printf("\n\nResult\n\n")
14 printf("\n (a) Reluctance S = %.0f /H",S)
15 printf("\n (b) Absolute permeability ,      = %.2E H/m\n
      ",u)

```

---

#### Scilab code Exa 7.10 Example 10

```

1 //Problem 7.10: A mild steel ring has a radius of 50
  mm and a crosssectional area of 400 mm2. A
  current of 0.5 A flows in a coil wound uniformly
  around the ring and the flux produced is 0.1 mWb.
  If the relative permeability at this value of
  current is 200 find (a) the reluctance of the
  mild steel and (b) the number of turns on the
  coil.
2
3 //initializing the variables:
4 A = 4E-4; // in m2
5 r = 0.05; // in m
6 I = 0.5; // in Amperes
7 Phi = 0.1E-3; // in Wb
8 u0 = 4*%pi*1E-7;
9 ur = 200;
10
11 // calculation :
12 l = 2*%pi*r
13 S = 1/(u0*ur*A)
14 N = S*Phi/I
15

```



```

16 printf("\n\nResult\n\n")
17 printf("\n (a) Reluctance S = %.2E /H",S)
18 printf("\n (b) number of turns on the coil = %.0f ",N
    )

```

---

### Scilab code Exa 7.11 Example 11

```

1 //Problem 7.11: A closed magnetic circuit of cast
  steel contains a 6 cm long path of cross-
  sectional area 1 cm2 and a 2 cm path of cross-
  sectional area 0.5 cm2. A coil of 200 turns is
  wound around the 6 cm length of the circuit and a
  current of 0.4 A flows. Determine the flux
  density in the 2 cm path, if the relative
  permeability of the cast steel is 750.
2
3 //initializing the variables:
4 A1 = 1E-4; // in m2
5 A2 = 0.5E-4; // in m2
6 l1 = 0.06; // in m
7 l2 = 0.02; // in m
8 N1 = 200; // no. of turns about 6 cm coil
9 I = 0.4; // in Amperes
10 u0 = 4*%pi*1E-7;
11 ur = 750;
12
13 //calculation:
14 //Reluctance
15 S1 = l1/(u0*ur*A1) // for 6 cm
16 S2 = l2/(u0*ur*A2) // for 2 cm
17 St = S1 + S2
18 Phi = N1*I/St
19 B2 = Phi/A2
20
21 printf("\n\nResult\n\n")

```

```
22 printf("\n flux density in the 2 cm path = %.2f T\n"
    ,B2)
```

---

### Scilab code Exa 7.12 Example 12

```
1 //Problem 7.12: A silicon iron ring of cross-
    sectional area 5 cm2 has a radial air gap of 2 mm
    cut into it. If the mean length of the silicon
    iron path is 40 cm, calculate the magnetomotive
    force to produce a flux of 0.7 mWb.
2
3 //initializing the variables:
4 A = 5E-4; // in m2
5 l = 0.4; // in m
6 r = 2E-3; // in m
7 u0 = 4*%pi*1E-7;
8 Phi = 0.7E-3; // in Wb
9
10 //calculation:
11 //For the silicon iron:
12 B = Phi/A
13 //From the B H curve for silicon iron,
    corresponding to value of B
14 Hs = 1650
15 mmfs = Hs*l
16 //For the air gap:
17 Ha = B/u0
18 mmfa = Ha*r
19 mmft = mmfs + mmfa
20
21 printf("\n\nResult\n\n")
22 printf("\n Total mmf to produce a flux of 0.7 mWb =
    %.0f A\n",mmft)
```

---

**Scilab code Exa 7.13** Example 13

```
1 //Problem 7.13: Figure 7.4 shows a ring formed with
   two different materials cast steel and mild
   steel. The dimensions are:
2 //          mean length          cross-
   sectional area
3 // Mild steel          400 mm
   500 mm2
4 // Cast steel          300 mm
   312.5 mm2
5 //Find the total mmf required to cause a flux of 500
   Wb in the magnetic circuit. Determine also the
   total circuit reluctance.
6
7 //initializing the variables:
8 A1 = 5E-4; // in m2
9 A2 = 3.125E-4; // in m2
10 l1 = 0.4; // in m
11 l2 = 0.3; // in m
12 u0 = 4*%pi*1E-7;
13 Phi = 0.5E-3; // in Wb
14
15 //calculation:
16 //For the mild steel:
17 B1 = Phi/A1
18 //From the B H curve for Mild steel, corresponding
   to value of B
19 Hm = 1400
20 mmfm = Hm*l1
21 //For the cast steel:
22 B2 = Phi/A2
23 //From the B H curve for cast steel steel,
   corresponding to value of B
```

```

24 Hc = 4800
25 mmfc = Hc*l2
26 mmft = mmfm + mmfc
27 //Reluctance
28 S = mmft/Phi
29
30 printf("\n\nResult\n\n")
31 printf("\n Total mmf to produce a flux of 0.5 mWb =
    %.0f A",mmft)
32 printf("\n Total circuit reluctance = %.2E /H",S)

```

---

#### Scilab code Exa 7.14 Example 14

```

1 //Problem 7.14: A section through a magnetic circuit
    of uniform cross-sectional area 2 cm2 is shown
    in Figure 7.5. The cast steel core has a mean
    length of 25 cm. The air gap is 1 mm wide and the
    coil has 5000 turns. The B H curve for cast
    steel is shown on page 78. Determine the current
    in the coil to produce a flux density of 0.80 T
    in the air gap, assuming that all the flux passes
    through both parts of the magnetic circuit.
2
3 //initializing the variables:
4 A = 2E-4; // in m2
5 l1 = 0.25; // in m
6 l2 = 0.001; // in m
7 u0 = 4*%pi*1E-7;
8 N = 5000; // no. of turns
9 B = 0.8; // in tesla
10 ua = 1; // for air
11
12 //calculation:
13 //for the core
14 //From the B H curve for Mild steel , corresponding

```

```
        to value of B = 0.8
15 H = 750
16 ur = B/(u0*H)
17 S1 = l1/(u0*ur*A)
18 //For the air gap:
19 S2 = l2/(u0*ua*A)
20 St = S1 + S2
21 //flux
22 Phi = B*A
23 //current
24 I = St*Phi/N
25
26 printf("\n\nResult\n\n")
27 printf("\n current = %.3f A",I)
```

---

# Chapter 8

## Electromagnetism

Scilab code Exa 8.02 Example 2

```
1 //Problem 8.02: A conductor carries a current of 20
  A and is at rightangles to a magnetic field
  having a flux density of 0.9 T. If the length of
  the conductor in the field is 30 cm, calculate
  the force acting on the conductor. Determine also
  the value of the force if the conductor is
  inclined at an angle of 30 to the direction of
  the field.
2
3 //initializing the variables:
4 B = 0.9; // in tesla
5 I = 20; // in Amperes
6 l = 0.30; // in m
7 alpha = 30; // in degree
8 u0 = 4*%pi*1E-7;
9
10 //calculation:
11 F1 = B*I*l
12 F2 = B*I*l*sin(alpha*%pi/180)
13
14 printf("\n\nResult\n\n")
```

```
15 printf("\n (a)Force when the conductor is at right
    angles to the field = %.1f N",F1)
16 printf("\n (b)Force when the conductor is at 30
    angle to the field = %.1f N",F2)
```

---

### Scilab code Exa 8.03 Example 3

```
1 //Problem 8.03: Determine the current required in a
    400 mm length of conductor of an electric motor,
    when the conductor is situated at right-angles to
    a magnetic field of flux density 1.2 T, if a
    force of 1.92 N is to be exerted on the conductor
    .
2
3 //initializing the variables:
4 F = 1.92; // in newton
5 B = 1.2; // in tesla
6 l = 0.40; // in m
7 u0 = 4*%pi*1E-7;
8
9 //calculation:
10 I = F/(B*l)
11
12 printf("\n\nResult\n\n")
13 printf("\n (a) Current I = %.0f Amperes(A)",I)
```

---

### Scilab code Exa 8.04 Example 4

```
1 //Problem 8.04: A conductor 350 mm long carries a
    current of 10 A and is at right-angles to a
    magnetic field lying between two circular pole
    faces each of radius 60 mm. If the total flux
```

```

    between the pole faces is 0.5 mWb, calculate the
    magnitude of the force exerted on the conductor.
2
3 //initializing the variables:
4 r = 0.06; // in m
5 I = 10; // in Amperes
6 l = 0.35; // in m
7 Phi = 0.5E-3; // in Wb
8 u0 = 4*%pi*1E-7;
9
10 //calculation:
11 A = %pi*r*r
12 B = Phi/A
13 F = B*I*l
14
15 printf("\n\nResult\n\n")
16 printf("\n (a) Force F = %.3f N\n",F)

```

---

### Scilab code Exa 8.06 Example 6

```

1 //Problem 8.06: A coil is wound on a rectangular
  former of width 24 mm and length 30 mm. The
  former is pivoted about an axis passing through
  the middle of the two shorter sides and is placed
  in a uniform magnetic field of flux density 0.8
  T, the axis being perpendicular to the field. If
  the coil carries a current of 50 mA, determine
  the force on each coil side (a) for a single-turn
  coil, (b) for a coil wound with 300 turns.
2
3 //initializing the variables:
4 N1 = 1; // for a single-turn coil
5 N2 = 300; // no. of turns
6 b = 0.024; // in m
7 B = 0.8; // in Tesla

```



```

8 I = 0.05; // in Amperes
9 l = 0.030; // in m
10 u0 = 4*%pi*1E-7;
11
12 //calculation:
13 //For a single-turn coil,
14 F1 = N1*B*I*l
15 //for a coil wound with 300 turns.
16 F2 = N2*B*I*l
17
18 printf("\n\nResult\n\n")
19 printf("\n (a) For a single-turn coil, force on each
    coil side = %.4f N",F1)
20 printf("\n (b) For a 300-turn coil, force on each
    coil side = %.2f N",F2)

```

---

#### Scilab code Exa 8.07 Example 7

```

1 //Problem 8.07: An electron in a television tube has
    a charge of 1.6 1019 coulombs and travels at
    3 107 m/s perpendicular to a field of flux
    density 18.5 T. Determine the force exerted on
    the electron in the field.
2
3 //initializing the variables:
4 Q = 1.6E-19; // in Coulomb
5 v = 3E7; // in m/s
6 B = 18.5E-6; // in Tesla
7 u0 = 4*%pi*1E-7;
8
9 //calculation:
10 F = Q*v*B
11
12 printf("\n\nResult\n\n")
13 printf("\n Force exerted on the electron in the

```

field . = %.2E N" ,F)

---

# Chapter 9

## Electromagnetic induction

Scilab code Exa 9.01 Example 1

```
1 //Problem 9.01: A conductor 300 mm long moves at a
  uniform speed of 4 m/s at right-angles to a
  uniform magnetic field of flux density 1.25 T.
  Determine the current flowing in the conductor
  when (a) its ends are open-circuited , (b) its
  ends are connected to a load of 20 ohm resistance
  .
2
3 //initializing the variables:
4 l = 0.3; // in m
5 v = 4; // in m/s
6 B = 1.25; // in Tesla
7 R = 20; // in ohms
8 u0 = 4*%pi*1E-7;
9
10 //calculation:
11 E = B*l*v
12 I2 = E/R
13
14 printf("\n\nResult\n\n")
15 printf("\n (a) If the ends of the conductor are open
```

```
    circuited no current will flow even though %.1f V
    has been induced",E)
16 printf("\n (b)From Ohm s law , I = %.3f Ampere",I2)
```

---

### Scilab code Exa 9.02 Example 2

```
1 //Problem 9.02: At what velocity must a conductor 75
    mm long cut a magnetic field of flux density 0.6
    T if an e.m.f. of 9 V is to be induced in it?
    Assume the conductor, the field and the direction
    of motion are mutually perpendicular.
2
3 //initializing the variables:
4 l = 0.075; // in m
5 E = 9; // in Volts
6 B = 0.6; // in Tesla
7 R = 20; // in ohms
8 u0 = 4*%pi*1E-7;
9
10 //calculation:
11 v = E/(B*l)
12
13 printf("\n\nResult\n\n")
14 printf("\n velocity v = %.0f m/s\n",v)
```

---

### Scilab code Exa 9.03 Example 3

```
1 //Problem 9.03: A conductor moves with a velocity of
    15 m/s at an angle of (a) 90°, (b) 60° and (c)
    30° to a magnetic field produced between two
    square-faced poles of side length 2 cm. If the
    flux leaving a pole face is 5 Wb, find the
    magnitude of the induced e.m.f. in each case.
```

```

2
3 //initializing the variables:
4 l = 0.02; // in m
5 b = 0.02; // in m
6 v = 15; // in m/s
7 R = 20; // in ohms
8 Phi = 5E-6; // in Wb
9 u0 = 4*pi*1E-7;
10 a1 = 90; // in degrees
11 a2 = 60; // in degrees
12 a3 = 30; // in degrees
13
14 //calculation:
15 A = l*b
16 B = Phi/A
17 E90 = B*l*v*sin(a1*pi/180)
18 E60 = B*l*v*sin(a2*pi/180)
19 E30 = B*l*v*sin(a3*pi/180)
20
21 printf("\n\nResult\n\n")
22 printf("\n Induced e.m.f. at angles 90 , 60 , 30
      are %.2E V, %.2E V, %.3E V respectively\n",E90,
      E60 ,E30)

```

---

#### Scilab code Exa 9.04 Example 4

```

1 //Problem 9.04: The wing span of a metal aeroplane
  is 36 m. If the aeroplane is flying at 400 km/h,
  determine the e.m.f. induced between its wing
  tips. Assume the vertical component of the
  earth s magnetic field is 40 T
2
3 //initializing the variables:
4 s = 36; // in m
5 v = 400; // in km/h

```

```

6 u0 = 4*%pi*1E-7;
7 B = 40E-6; // in Tesla
8
9 //calculation:
10 v0 = v*5/18
11 E = B*s*v0
12
13 printf("\n\nResult\n\n")
14 printf("\n Induced e.m.f. = %.2 f V\n",E)

```

---

#### Scilab code Exa 9.06 Example 6

```

1 //Problem 9.06: Determine the e.m.f. induced in a
   coil of 200 turns when there is a change of flux
   of 25 mWb linking with it in 50 ms
2
3 //initializing the variables:
4 N = 200; // no. of turns
5 dt = 0.050; // change of time in sec
6 u0 = 4*%pi*1E-7;
7 dPhi = 0.025; // change of flux in Wb
8
9 //calculation:
10 E = -1*N*dPhi/dt
11
12 printf("\n\nResult\n\n")
13 printf("\n Induced e.m.f. = %.0 f V\n",E)

```

---

#### Scilab code Exa 9.07 Example 7

```

1 //Problem 9.07: A flux of 400 Wb passing through a
   150-turn coil is reversed in 40 ms. Find the
   average e.m.f. induced.

```

```

2
3 //initializing the variables:
4 N = 150; // no. of turns
5 dt = 0.040; // change of time in sec
6 u0 = 4*%pi*1E-7;
7 dPhi = 800E-6; // change of flux in Wb
8
9 //calculation:
10 //Since the flux reverses, the flux changes from
    C400 Wb to 400 Wb, a total change of flux of
    800 Wb
11 E = -1*N*dPhi/dt
12
13 printf("\n\nResult\n\n")
14 printf("\n Induced e.m.f. = %.0f V\n",E)

```

---

#### Scilab code Exa 9.08 Example 8

```

1 //Problem 9.08: Calculate the e.m.f. induced in a
    coil of inductance 12 H by a current changing at
    the rate of 4 A/s
2
3 //initializing the variables:
4 L = 12; // in Henry
5 u0 = 4*%pi*1E-7;
6 dIdt = 4; // change of current with change in time
    in A/s
7
8 //calculation:
9 E = -1*L*dIdt
10
11 printf("\n\nResult\n\n")
12 printf("\n Induced e.m.f. = %.0f V\n",E)

```

---

**Scilab code Exa 9.09** Example 9

```
1 //Problem 9.09: An e.m.f. of 1.5 kV is induced in a
   coil when a current of 4 A reduced to 0 A in a 8
   ms. find the inductance of the coil.
2
3 //initializing the variables:
4 E = 1500; // in Volts
5 dt = 0.008; // Change of time in sec
6 dI = 4; // change of current in A/s
7
8 //calculation:
9 L = abs(E)*dt/dI
10
11 printf("\n\n Result \n\n")
12 printf("\n Inductance L = %.0f H\n",L)
```

---

**Scilab code Exa 9.10** Example 10

```
1 //Problem 9.10: An 8 H inductor has a current of 3 A
   flowing through it. How much energy is stored in
   the magnetic field of the inductor?
2
3 //initializing the variables:
4 L = 8; // in Henry
5 I = 3; // in Amperes
6
7 //calculation:
8 W = L*I*I/2
9
10 printf("\n\n Result \n\n")
11 printf("\n Energy stored , W = %.0f J\n",W)
```



---

**Scilab code Exa 9.11** Example 11

```
1 //Problem 9.11: Calculate the coil inductance when a
   current of 4 A in a coil of 800 turns produces a
   flux of 5 mWb linking with the coil.
2
3 //initializing the variables:
4 I = 4; // in Amperes
5 N = 800; //turns
6 Phi = 0.005; // in Wb
7
8 //calculation:
9 L = N*Phi/I
10
11 printf("\n\n Result \n\n")
12 printf("\n Inductance L = %.0f H\n",L)
```

---

**Scilab code Exa 9.12** Example 12

```
1 //Problem 9.12: A flux of 25 mWb links with a 1500
   turn coil when a current of 3 A passes through
   the coil. Calculate (a) the inductance of the
   coil, (b) the energy stored in the magnetic field
   , and (c) the average e.m.f. induced if the
   current falls to zero in 150 ms.
2
3 //initializing the variables:
4 I1 = 3; // in Amperes
5 I2 = 0; // in Amperes
6 dt = 0.150; // in secs
7 N = 1500; //turns
```

```

8 Phi = 0.025; // in Wb
9
10 //calculation:
11 L = N*Phi/I1
12 W = L*I1*I1/2
13 dI = I1 - I2
14 E = -1*L*dI/dt
15
16 printf("\n\n Result \n\n")
17 printf("\n (a) Inductance L = %.1f H",L)
18 printf("\n (b) energy stored W = %.2f J",W)
19 printf("\n (c) e.m.f. induced = %.0f V",E)

```

---

### Scilab code Exa 9.13 Example 13

```

1 //Problem 9.13: A 750 turn coil of inductance 3 H
   carries a current of 2 A. Calculate the flux
   linking the coil and the e.m.f. induced in the
   coil when the current collapses to zero in 20 ms
2
3 //initializing the variables:
4 I1 = 2; // in Amperes
5 I2 = 0; // in Amperes
6 dt = 0.020; // in secs
7 N = 750; //turns
8 L = 3; // in Henry
9
10 //calculation:
11 Phi = L*I1/N
12 dI = I1 - I2
13 E = -1*L*dI/dt
14
15 printf("\n\n Result \n\n")
16 printf("\n (a) Flux = %.3f Wb",Phi)
17 printf("\n (b) e.m.f. induced = %.0f V",E)

```

---

**Scilab code Exa 9.14** Example 14

```
1 //Problem 9.14: Calculate the mutual inductance
   between two coils when a current changing at 200
   A/s in one coil induces an e.m.f. of 1.5 V in the
   other.
2
3 //initializing the variables:
4 dI1dt = 200; // change of current with change in
   time in A/s
5 N = 2; // no. of coils
6 E2 = 1.5; // in Volts
7
8 //calculation:
9 M = abs(E2)/dI1dt
10
11 printf("\n\n Result \n\n")
12 printf("\n mutual inductance , M = %.4 f H\n", M)
```

---

**Scilab code Exa 9.15** Example 15

```
1 //Problem 9.15: The mutual inductance between two
   coils is 18 mH. Calculate the steady rate of
   change of current in one coil to induce an e.m.f.
   of 0.72 V in the other.
2
3 //initializing the variables:
4 M = 0.018; // in Henry
5 N = 2; // no. of coils
6 E2 = 0.72; // in Volts
7
```

```

8 //calculation :
9 dI1dt = abs(E2)/M
10
11 printf("\n\n Result \n\n")
12 printf("\n rate of change of current dI1/dt = %.0f A
    /s\n", dI1dt)

```

---

### Scilab code Exa 9.16 Example 16

```

1 //Problem 9.16: Two coils have a mutual inductance
    of 0.2 H. If the current in one coil is changed
    from 10 A to 4 A in 10 ms, calculate (a) the
    average induced e.m.f. in the second coil , (b)
    the change of flux linked with the second coil if
    it is wound with 500 turns.
2
3 //initializing the variables :
4 M = 0.2; // in Henry
5 I1 = 10; // in Amperes
6 I2 = 4; // in Amperes
7 dt = 0.010; // in secs
8 N = 500; // turns
9
10 //calculation :
11 dI1dt = (I1 -I2)/dt
12 E2 = -1*dI1dt*M
13 dPhi = abs(E2)*dt/N
14
15 printf("\n\n Result \n\n")
16 printf("\n (a)Induced e.m.f. E2 = %.0f V", E2)
17 printf("\n (b)change of flux = %.4f Wb", dPhi)

```

---

# Chapter 10

## Electrical measuring instruments and measurements

Scilab code Exa 10.01 Example 1

```
1 //Problem 10.01: A moving-coil instrument gives a f.
   s.d. when the current is 40 mA and its resistance
   is 25 ohms. Calculate the value of the shunt to
   be connected in parallel with the meter to enable
   it to be used as an ammeter for measuring
   currents up to 50 A.
2
3 //initializing the variables:
4 Ia = 0.040; // in Amperes
5 I = 50; // in Amperes
6 ra = 25; // in ohms
7
8
9 //calculation:
10 Is = I - Ia
11 V = Ia*ra
12 Rs = V/Is
13
14 printf("\n\n Result \n\n")
```

```
15 printf("\n value of the shunt to be connected in
    parallel = %.3E ohms",Rs)
```

---

### Scilab code Exa 10.02 Example 2

```
1 //Problem 10.02: A moving-coil instrument having a
    resistance of 10 ohms, gives a f.s.d. when the
    current is 8 mA. Calculate the value of the
    multiplier to be connected in series with the
    instrument so that it can be used as a voltmeter
    for measuring p.d.s. up to 100 V.
2
3 //initializing the variables:
4 V = 100; // in volts
5 I = 0.008; // in Amperes
6 ra = 10; // in ohms
7
8
9 //calculation:
10 Rm = (V/I) - ra
11
12 printf("\n\n Result \n\n")
13 printf("\n value of the multiplier to be connected
    in series = %.3Eohms\n", Rm)
```

---

### Scilab code Exa 10.03 Example 3

```
1 //Problem 10.03: Calculate the power dissipated by
    the voltmeter and by resistor R in Figure 10.9
    when (a) R = 250 ohms (b) R = 2 Mohms. Assume
    that the voltmeter sensitivity (sometimes called
    figure of merit) is 10 kohms/V.
2
```

```

3 //initializing the variables:
4 fsd = 200; // in volts
5 R1 = 250; // in ohms
6 R2 = 2E6; // in ohms
7 sensitivity = 10000; // in ohms/V
8
9 //calculation:
10 Rv = sensitivity*fsd
11 Iv = V/Rv
12 Pv = V*Iv
13 I1 = V/R1
14 P1 = V*I1
15 I2 = V/R2
16 P2 = V*I2
17
18 printf("\n\n Result \n\n")
19 printf("\n (a)the power dissipated by the voltmeter
    = %.2E W", Pv)
20 printf("\n (b)the power dissipated by resistor 250
    ohm = %.0f W", P1)
21 printf("\n (c)the power dissipated by resistor 2
    Mohm = %.2E W", P2)

```

---

#### Scilab code Exa 10.04 Example 4

```

1 //Problem 10.04: An ammeter has a f.s.d. of 100 mA
    and a resistance of 50 ohms. The ammeter is used
    to measure the current in a load of resistance
    500 ohms when the supply voltage is 10 V.
    Calculate (a) the ammeter reading expected (
    neglecting its resistance), (b) the actual
    current in the circuit, (c) the power dissipaed
    in the ammeter, and (d) the power dissipated in
    the load.

```

2

```

3 //initializing the variables:
4 V = 10; // in volts
5 fsd = 0.1; // in Amperes
6 ra = 50; // in ohms
7 R = 500; // in ohms
8
9 //calculation:
10 Ie = V/R
11 Ia = V/(R + ra)
12 Pa = Ia*Ia*ra
13 PR = Ia*Ia*R
14
15 printf("\n\n Result \n\n")
16 printf("\n (a)expected ammeter reading = %.2E A\n",
    Ie)
17 printf("\n (b)Actual ammeter reading = %.2E A",Ia)
18 printf("\n (c)Power dissipated in the ammeter = %.2E
    W", Pa)
19 printf("\n (d)Power dissipated in the load resistor
    = %.2E W",PR)

```

---

#### Scilab code Exa 10.05 Example 5

```

1 //Problem 10.05: A voltmeter having a f.s.d. of 100
    V and a sensitivity of 1.6 kohms/V is used to
    measure voltage V1 in the circuit of Figure
    10.11. Determine (a) the value of voltage V1 with
    the voltmeter not connected, and (b) the voltage
    indicated by the voltmeter when connected
    between A and B.
2
3 //initializing the variables:
4 fsd = 100; // in volts
5 R1 = 40E3; // in ohms
6 R2 = 60E3; // in ohms

```



```

7 sensitivity = 1600; // in ohms/V
8
9 //calculation:
10 V1 = (R1/(R1 + R2))*fsd
11 Rv = fsd*sensitivity
12 Rep = R1*Rv/(R1 + Rv)
13 V1n = (Rep/(Rep + R2))*fsd
14
15 printf("\n\n Result \n\n")
16 printf("\n (a)the value of voltage V1 with the
    vltmeter6 not connected = %.0f V", V1)
17 printf("\n (b)the voltage indicated by the vltmeter
    when connected between A and B = %.2f V",V1n)

```

---

#### Scilab code Exa 10.06 Example 6

```

1 //Problem 10.06: (a) A current of 20 A flows through
    a load having a resistance of 2 ohms. Determine
    the power dissipated in the load. (b) A wattmeter
    , whose current coil has a resistance of 0.01 ohm
    is connected as shown in Figure 10.13. Determine
    the wattmeter reading.
2
3 //initializing the variables:
4 I = 20; // in amperes
5 R = 2; // in ohms
6 Rw = 0.01; // in ohms
7
8 //calculation:
9 PR = I*I*R
10 Rt = R + Rw
11 Pw = I*I*Rt
12
13 printf("\n\n Result \n\n")
14 printf("\n (a)the power dissipated in the load = %.0

```

```
    f W", PR)
15 printf("\n (b) the wattmeter reading. = %.0f W\n", Pw)
```

---

### Scilab code Exa 10.08 Example 8

```
1 //Problem 10.08: (For the c.r.o. square voltage
   waveform shown in Figure 10.15 determine (a) the
   periodic time, (b) the frequency and (c) the peak
   -to-peak voltage. The time/cm (or timebase
   control) switch is on 100 s/cm and the volts
   /cm (or signal amplitude control) switch is on
   20 V/cm.
2 //(In Figures 10.15 to 10.18 assume that the squares
   shown are 1 cm by 1 cm)
3
4 //initializing the variables:
5 tc = 100E-6; // in s/cm
6 Vc = 20; // in V/cm
7 w = 5.2; // in cm ( width of one complete cycle )
8 h = 3.6; // in cm ( peak-to-peak height of the
   display )
9
10 //calculation:
11 T = w*tc
12 f = 1/T
13 ptpv = h*Vc
14
15 printf("\n\n Result \n\n")
16 printf("\n (a) the periodic time, T = %.2E sec", T)
17 printf("\n (b) Frequency, f = %.0f Hz", f)
18 printf("\n (c) the peak-to-peak voltage = %.0f V",
   ptpv)
```

---

### Scilab code Exa 10.09 Example 9

```
1 //Problem 10.09: (For the c.r.o. display of a pulse
   waveform shown in Figure 10.16 the time/cm
   switch is on 50 ms/cm and the volts/cm
   switch is on 0.2 V/cm. Determine (a) the periodic
   time, (b) the frequency, (c) the magnitude of
   the pulse voltage.
2 //(In Figures 10.15 to 10.18 assume that the squares
   shown are 1 cm by 1 cm)
3
4 //initializing the variables:
5 tc = 50E-3; // in s/cm
6 Vc = 0.2; // in V/cm
7 w = 3.5; // in cm ( width of one complete cycle )
8 h = 3.4; // in cm ( peak-to-peak height of the
   display )
9
10 //calculation:
11 T = w*tc
12 f = 1/T
13 ptpv = h*Vc
14
15 printf("\n\n Result \n\n")
16 printf("\n (a)the periodic time, T = %.2E sec ",T)
17 printf("\n (b)Frequency, f = %.2f Hz",f)
18 printf("\n (c)the peak-to-peak voltage = %.2f V",
   ptpv)
```

---

### Scilab code Exa 10.10 Example 10

```
1 //Problem 10.10: A sinusoidal voltage trace
   displayed by a c.r.o. is shown in Figure 10.17.
   If the time/cm switch is on 500 s/cm and
   the volts/cm switch is on 5 V/cm, find, for
```

```

    the waveform, (a) the frequency, (b) the peak-to-
    -peak voltage, (c) the amplitude, (d) the r.m.s.
    value.
2 // (In Figures 10.15 to 10.18 assume that the squares
    shown are 1 cm by 1 cm)
3
4 // initializing the variables:
5 tc = 500E-6; // in s/cm
6 Vc = 5; // in V/cm
7 w = 4; // in cm ( width of one complete cycle )
8 h = 5; // in cm ( peak-to-peak height of the display
    )
9
10 // calculation:
11 T = w*tc
12 f = 1/T
13 ptpv = h*Vc
14 Amp = ptpv/2
15 Vrms = Amp/(2^0.5)
16
17 printf("\n\n Result \n\n")
18 printf("\n (a) Frequency, f = %.0f Hz", f)
19 printf("\n (b) the peak-to-peak voltage = %.0f V",
    ptpv)
20 printf("\n (c) Amplitude = %.1f V", Amp)
21 printf("\n (d) r.m.s voltage = %.2f V", Vrms)

```

---

### Scilab code Exa 10.11 Example 11

```

1 // Problem 10.11: For the double-beam oscilloscope
    displays shown in Figure 10.18 determine (a)
    their frequency, (b) their r.m.s. values, (c)
    their phase difference. The time/cm switch
    is on 100 s/cm and the volts/cm switch on
    2 V/cm.

```

```

2 //(In Figures 10.15 to 10.18 assume that the squares
   shown are 1 cm by 1 cm)
3
4 //initializing the variables:
5 tc = 100E-6; // in s/cm
6 Vc = 2; // in V/cm
7 w = 5; // in cm ( width of one complete cycle for
   both waveform )
8 h1 = 2; // in cm ( peak-to-peak height of the
   display )
9 h2 = 2.5; // in cm ( peak-to-peak height of the
   display )
10
11 //calculation:
12 T = w*tc
13 f = 1/T
14 ptpv1 = h1*Vc
15 Vrms1 = ptpv1/(2^0.5)
16 ptpv2 = h2*Vc
17 Vrms2 = ptpv2/(2^0.5)
18 phi = 0.5*360/w
19
20 printf("\n\n Result \n\n")
21 printf("\n (a)Frequency, f = %.0f Hz",f)
22 printf("\n (b1)r.m.s voltage of 1st waveform = %.2f
   V",Vrms1)
23 printf("\n (b2)r.m.s voltage of 2nd waveform = %.2f
   V",Vrms2)
24 printf("\n (c)Phase difference = %.0f ",phi)

```

---

### Scilab code Exa 10.12 Example 12

```

1 //Problem 10.12: The ratio of two powers is (a) 3 (b
   ) 20 (c) 400 (d) 1/20. Determine the decibel
   power ratio in each case.

```

```

2
3 //initializing the variables:
4 rP1 = 3; // ratio of two powers
5 rP2 = 20; // ratio of two powers
6 rP3 = 400; // ratio of two powers
7 rP4 = 1/20; // ratio of two powers
8
9 //calculation:
10 X1 = 10*log10(3)
11 X2 = 10*log10(20)
12 X3 = 10*log10(400)
13 X4 = 10*log10(1/20)
14
15 printf("\n\n Result \n\n")
16 printf("\n (a) decibel power ratio for power ratio 3
    = %.2f dB ",X1)
17 printf("\n (b) decibel power ratio for power ratio 20
    = %.1f dB ",X2)
18 printf("\n (c) decibel power ratio for power ratio
    400 = %.1f dB ",X3)
19 printf("\n (d) decibel power ratio for power ratio
    1/20 = %.1f dB ",X4)

```

---

### Scilab code Exa 10.13 Example 13

```

1 //Problem 10.13: The current input to a system is 5
    mA and the current output is 20 mA. Find the
    decibel current ratio assuming the input and load
    resistances of the system are equal.
2
3 //initializing the variables:
4 I2 = 0.020; // in ampere
5 I1 = 0.005; // in ampere
6
7 //calculation:

```

```

8 X = 20*log10(I2/I1)
9
10 printf("\n\n Result \n\n")
11 printf("\n decibel current ratio = %.0f dB\n",X)

```

---

#### Scilab code Exa 10.14 Example 14

```

1 //Problem 10.14: 6% of the power supplied to a cable
   appears at the output terminals. Determine the
   power loss in decibels.
2
3 //initializing the variables:
4 rP = 0.06; // power ratios rP = P2/P1
5
6 //calculation:
7 X = 10*log10(rP)
8
9 printf("\n\n Result \n\n")
10 printf("\n decibel Power ratios = %.2f dB\n",X)

```

---

#### Scilab code Exa 10.15 Example 15

```

1 //Problem 10.15: An amplifier has a gain of 14 dB.
   Its input power is 8 mW. Find its output power.
2
3 //initializing the variables:
4 X = 14; // decibal power ratio in dB
5 P1 = 0.008; // in Watt
6
7 //calculation:
8 rP = 10^(X/10)
9 P2 = rP*P1
10

```

```
11 printf("\n\n Result \n\n")
12 printf("\n output power P2 = %.3f W\n",P2)
```

---

#### Scilab code Exa 10.16 Example 16

```
1 //Problem 10.16: The output voltage from an
    amplifier is 4 V. If the voltage gain is 27 dB,
    calculate the value of the input voltage assuming
    that the amplifier input resistance and load
    resistance are equal.
2
3 //initializing the variables:
4 X = 27; // Voltage gain in decibels
5 V2 = 4; // output voltage in Volts
6
7 //calculation:
8 V1 = V2/(10^(27/20))
9
10 printf("\n\n Result \n\n")
11 printf("\n input Voltage V1 = %.3f V\n",V1)
```

---

#### Scilab code Exa 10.17 Example 17

```
1 //Problem 10.17: In a Wheatstone bridge ABCD, a
    galvanometer is connected between A and C, and a
    battery between B and D. A resistor of unknown
    value is connected between A and B. When the
    bridge is balanced, the resistance between B and
    C is 100 ohms, that between C and D is 10 ohms
    and that between D and A is 400 ohms. calculate
    the value of the unknown resistance.
2
3 //initializing the variables:
```



```

4 R2 = 100; // in ohms
5 R3 = 400; // in ohms
6 R4 = 10; // in ohms
7
8 //calculation:
9 R1 = R2*R3/R4
10
11 printf("\n\n Result \n\n")
12 printf("\n unknown resistance , R1 = %.0f Ohms\n",R1)

```

---

#### Scilab code Exa 10.18 Example 18

```

1 //Problem 10.18: In a d.c. potentiometer , balance is
   obtained at a length of 400 mm when using a
   standard cell of 1.0186 volts. Determine the e.m.
   f. of a dry cell if balance is obtained with a
   length of 650 mm
2
3 //initializing the variables:
4 E1 = 1.0186; // in Volts
5 l1 = 0.400; // in m
6 l2 = 0.650; // in m
7
8 //calculation:
9 E2 = (l2/l1)*E1
10
11 printf("\n\n Result \n\n")
12 printf("\n the e.m.f. of a dry cell = %.3f Volts\n",
   E2)

```

---

#### Scilab code Exa 10.19 Example 19

```

1 //Problem 10.19: The current flowing through a
   resistor of 5 kohm(+−)0.4% is measured as 2.5 mA
   with an accuracy of measurement of (+−)0.5%.
   Determine the nominal value of the voltage across
   the resistor and its accuracy.
2
3 //initializing the variables:
4 I = 0.0025; // in Amperes
5 R = 5000; // in ohms
6 e1 = 0.4; // in %
7 e2 = 0.5; // in %
8
9 //calculation:
10 V = I*R
11 em = e1 + e2
12 Ve = em*V/100
13
14 printf("\n\n Result \n\n")
15 printf("\n voltage V = %.1fV(+−)%.2fV\n",V,Ve)

```

---

### Scilab code Exa 10.20 Example 20

```

1 //Problem 10.20: The current I flowing in a resistor
   R is measured by a 0 10 A ammeter which gives
   an indication of 6.25 A. The voltage V across the
   resistor is measured by a 0 50 V voltmeter ,
   which gives an indication of 36.5 V. Determine
   the resistance of the resistor , and its accuracy
   of measurement if both instruments have a limit
   of error of 2% of f.s.d. Neglect any loading
   effects of the instruments.
2
3 //initializing the variables:
4 I = 6.25; // in Amperes
5 Im = 10; // max in Amperes

```

```

6 V = 36.5; // in volts
7 Vm = 50; // max in volts
8 e = 2; // in %
9
10 //calculation:
11 R = V/I
12 Ve = e*Vm/100
13 Ve1 = Ve*100/V // in %
14 Ie = e*Im/100
15 Ie1 = Ie*100/I // in %
16 em = Ve1 + Ie1
17 Re = em*R/100
18
19 printf("\n\n Result \n\n")
20 printf("\n Resistance R = %.2f ohms(+-%).2f ohms\n",
    R,Re)

```

---

### Scilab code Exa 10.21 Example 21

```

1 //Problem 10.21: The arms of a Wheatstone bridge
  ABCD have the following resistances: AB: R1 =
  1000 ohms (+-) 1.0% ; BC: R2 = 100 ohm (+-) 0.5%;
  CD: unknown resistance Rx; DA: R3 = 432.5 ohms
  (+-)0.2%. Determine the value of the unknown
  resistance and its accuracy of measurement.
2
3 //initializing the variables:
4 R1 = 1000; // in ohms
5 R2 = 100; // in ohms
6 R3 = 432.5; // in ohms
7 e1 = 1; // in %
8 e2 = 0.5; // in %
9 e3 = 0.2; // in %
10
11 //calculation:

```

```
12 Rx = R2*R3/R1
13 em = e1 + e2 + e3
14 Re = em*Rx/100
15
16 printf("\n\n Result \n\n")
17 printf("\n Resistance R = %.2 f ohms(+-%.2 f ohms\n",
    Rx,Re)
```

---

# Chapter 13

## DC circuit theory

Scilab code Exa 13.01 Example 1

```
1 //Problem 13.01: (a) Find the unknown currents
   marked in Figure 13.3(a). (b) Determine the value
   of e.m.f. E in Figure 13.3(b).
2
3 //initializing the variables:
4 Iab = 50; // in ampere
5 Ibc = 20; // in ampere
6 Iec = 15; // in ampere
7 Idf = 120; // in ampere
8 Ifg = 40; // in ampere
9 Iab = 50; // in ampere
10 I = 2; // in ampere
11 V1 = 4; // in volts
12 V2 = 3; // in volts
13 V3 = 6; // in volts
14 R1 = 1; // in ohms
15 R2 = 2; // in ohms
16 R3 = 2.5; // in ohms
17 R4 = 1.5; // in ohms
18
19 //calculation:
```

```

20 I1 = Iab - Ibc
21 I2 = Ibc + Iec
22 I3 = I1 - Idf
23 I4 = Iec - I3
24 I5 = Idf - Ifg
25 // Applying Kirchhoff s voltage law and moving
    clockwise around the loop of Figure 13.3(b)
    starting at point A:
26 E = I*R2 + I*R3 + I*R4 + I*R1 - V2 - V3 + V1
27
28 printf("\n\n Result \n\n")
29 printf("\n (a) unknown currents I1 , I2 , I3 , I4 , I5
    are %.0fA , %.0fA , %.0fA , %.0fA , %.0fA respectively
    ",I1, I2, I3, I4, I5)
30 printf("\n (b) value of e.m.f. E = %.0f Volts",E)

```

---

#### Scilab code Exa 13.06 Example 6

```

1 //Problem 13.06: For the circuit shown in Figure
    13.16, find , using the superposition theorem , (a)
    the current flowing in and the pd across the 18
    ohm resistor , (b) the current in the 8 V battery
    and (c) the current in the 3 V battery.
2
3 //initializing the variables:
4 E1 = 8; // in volts
5 E2 = 3; // in volts
6 R1 = 3; // in ohms
7 R2 = 2; // in ohms
8 R3 = 18; // in ohms
9
10 //calculation:
11 //Removing source E2 gives the circuit of Figure
    13.17(a).
12 //The current directions are labelled as shown in

```

```

    Figure 13.17(a), I1 flowing from the positive
    terminal of E1.
13 //From Figure 13.17(b), I1
14 r1 = 1/(1/R2 + 1/R3)
15 I1 = E1/(R1 + r1)
16 //From Figure 13.17(a), I2
17 I2 = (R3/(R3 + R2))*I1
18 I3 = (R2/(R3 + R2))*I1
19 //Removing source E1 gives the circuit of Figure
    13.18(a)
20 //The current directions are labelled as shown in
    Figures 13.18(a) and 13.18(b), I4 flowing from
    the positive terminal of E2
21 //From Figure 13.18(c), I4
22 r2 = 1/(1/R3 + 1/R1)
23 I4 = E2/(r2 + R2)
24 //From Figure 13.18(b), I5
25 I5 = (R3/(R1 + R3))*I4
26 I6 = (R1/(R1 + R3))*I4
27 //Resultant current in the R3 resistor
28 I18 = I3 - I6
29 //P.d. across the R3
30 V3 = I18*R3
31 //Resultant current in the E1
32 Ie1 = I1 + I5
33 //Resultant current in the E2
34 Ie2 = I2 + I4
35
36 printf("\n\n Result \n\n")
37 printf("\n Resultant current in the 18 ohm resistor
    is %.3f A",I18)
38 printf("\n P.d. across the 18 ohm resistor is %.3f V
    ",V3)
39 printf("\n Resultant current in the E1 is %.3f A",
    Ie1)
40 printf("\n Resultant current in the E2 is %.3f A",
    Ie2)

```

---

### Scilab code Exa 13.07 Example 7

```
1 //Problem 13.07: Use Th evenin s theorem to find
   the current flowing in the 10 ohm resistor for
   the circuit shown in Figure 13.28(a).
2
3 //initializing the variables:
4 V = 10; // in volts
5 R1 = 2; // in ohms
6 R2 = 8; // in ohms
7 R3 = 5; // in ohms
8 R = 10; // in ohms
9
10 //calculation:
11 //The 10 ohm resistance branch is short-circuited as
   shown in Figure 13.28(b).
12 //Current I1
13 I1 = V/(R1 + R2)
14 //p.d. across AB, E
15 E = R2*I1
16 //the resistance looking -in at a break made
   between A and B is given by
17 r = R3 + (R1*R2)/(R2 + R1)
18 //The equivalent Th evenin s circuit is shown in
   Figure 13.28(d), the current in the 10 ohm
   resistance is given by:
19 I = E/(r + R)
20
21 printf("\n\n Result \n\n")
22 printf("\n the current in the 10 ohm resistance is
   given by %.3f A",I)
```

---



### Scilab code Exa 13.08 Example 8

```
1 //Problem 13.08: For the network shown in Figure
   13.29(a) determine the current in the 0.8 ohm
   resistor using Th evenin s theorem.
2
3 //initializing the variables:
4 V = 12; // in volts
5 R1 = 5; // in ohms
6 R2 = 1; // in ohms
7 R3 = 4; // in ohms
8 R = 0.8; // in ohms
9
10 //calculation:
11 //The 0.8 ohm resistance branch is short-circuited
   as shown in Figure 13.29(b).
12 //Current I1
13 I1 = V/(R1 + R2 + R3)
14 //p.d. across AB, E
15 E = R3*I1
16 //the resistance looking-in at a break made
   between A and B is given by
17 r = R3*(R1 + R2)/(R2 + R1 + R3)
18 //The equivalent Th evenin s circuit is shown in
   Figure 13.29(d), the current in the 0.8 ohm
   resistance is given by:
19 I = E/(r + R)
20
21 printf("\n\n Result \n\n")
22 printf("\n the current in the 0.8 ohm resistance is
   given by %.1f A",I)
```

---

### Scilab code Exa 13.09 Example 9

```
1 //Problem 13.09: Use Th evenin s theorem to
```

determine the current  $I$  flowing in the 4 ohm resistor shown in Figure 13.30(a). Find also the power dissipated in the 4 ohm resistor.

```
2
3 //initializing the variables:
4 E1 = 4; // in volts
5 E2 = 2; // in volts
6 R1 = 2; // in ohms
7 R2 = 1; // in ohms
8 R3 = 4; // in ohms
9
10 //calculation:
11 //The 4 ohm resistance branch is short-circuited as
    shown in Figure 13.30(b).
12 //Current I1
13 I1 = (E1 - E2)/(R1 + R2)
14 //p.d. across AB, E
15 E = E1 - I1*R1
16 //the resistance looking -in at a break made
    between A and B is given by
17 r = R2*R1/(R2 + R1)
18 //The equivalent Th evenin s circuit is shown in
    Figure 13.30(d), the current in the 4ohm
    resistance is given by:
19 I = E/(r + R3)
20 //Power dissipated in R3
21 P3 = R3*I^2
22
23 printf("\n\n Result \n\n")
24 printf("\n the current in the 4 ohm resistance is
    given by %.3f A",I)
25 printf("\n power disipated in 4 ohm resistor is
    given by %.3f W",P3)
```

---

Scilab code Exa 13.10 Example 10

```

1 //Problem 13.10: Use Thevenin's theorem to
   determine the current flowing in the 3 ohm
   resistance of the network shown in Figure 13.31(a
   ). The voltage source has negligible internal
   resistance.
2
3 //initializing the variables:
4 V = 24; // in volts
5 R1 = 20; // in ohms
6 R2 = 5; // in ohms
7 R3 = 10; // in ohms
8 R4 = 5/3; // in ohms
9 R5 = 3; // in ohms
10
11 //calculation:
12 //The 3 ohm resistance branch is short-circuited as
   shown in Figure 13.31(b).
13 //P.d. across R3
14 V3 = (R3/(R3 + R2))*V
15 //p.d. across AB, E
16 E = V3
17 //the resistance looking-in at a break made
   between A and B is given by
18 r = R4 + R2*R3/(R2 + R3)
19 //The equivalent Thevenin's circuit is shown in
   Figure 13.31(e), the current in the 3 ohm
   resistance is given by:
20 I = E/(r + R5)
21
22 printf("\n\n Result \n\n")
23 printf("\n the current in the 3 ohm resistance is
   given by %.0f A",I)

```

---

Scilab code Exa 13.11 Example 11

```

1 //Problem 13.11: A Wheatstone Bridge network is
  shown in Figure 13.32(a). Calculate the current
  flowing in the 32 ohm resistor , and its direction
  , using Th evenin s theorem. Assume the source
  of e.m.f. to have negligible resistance.
2
3 //initializing the variables:
4 E = 54; // in volts
5 R1 = 2; // in ohms
6 R2 = 14; // in ohms
7 R3 = 3; // in ohms
8 R4 = 11; // in ohms
9 R5 = 32; // in ohms
10
11 //calculation:
12 //The 32ohm resistance branch is short-circuited as
  shown in Figure 13.32(b).
13 //The p.d. between A and C,
14 Vac = (R1/(R1 + R4))*E
15 //The p.d. between B and C,
16 Vbc = (R2/(R2 + R3))*E
17 //Hence the p.d. between A and B
18 Vab = Vbc - Vac
19 //the resistance looking -in at a break made
  between A and B is given by
20 r = R1*R4/(R1 + R4) + R2*R3/(R2 + R3)
21 //The equivalent Th evenin s circuit is shown in
  Figure 13.32(f), the current in the 32 ohm
  resistance is given by:
22 I = E/(r + R5)
23
24 printf("\n\n Result \n\n")
25 printf("\n the current in the 32 ohm resistance is
  given by %.0f A",I)

```

---

### Scilab code Exa 13.12 Example 12

```
1 //Problem 13.12: Use Norton s theorem to determine
   the current flowing in the 10 ohm resistance for
   the circuit shown in Figure 13.34(a).
2
3 //initializing the variables:
4 V = 10; // in volts
5 R1 = 2; // in ohms
6 R2 = 8; // in ohms
7 R3 = 5; // in ohms
8 R4 = 10; // in ohms
9
10 //calculation:
11 //The 10ohm resistance branch is short-circuited as
   shown in Figure 13.34(b).
12 //Figure 13.34(c) is equivalent to Figure 13.34(b).
   Hence
13 Isc = V/R1
14 //the resistance looking-in at a break made
   between A and B is given by
15 r = R1*R2/(R1 + R2)
16 //From the Norton equivalent network shown in Figure
   13.34(d) the current in the 10 ohm resistance is
   given by:
17 I = (r/(r + R3 + R4))*Isc
18
19 printf("\n\n Result \n\n")
20 printf("\n the current in the 10 ohm resistance is
   given by %.3f A",I)
```

---

### Scilab code Exa 13.13 Example 13

```
1 //Problem 13.13: Use Norton s theorem to determine
   the current I flowing in the 4 ohm resistance
```

```

        shown in Figure 13.35(a).
2
3 //initializing the variables:
4 V1 = 4; // in volts
5 V2 = 2; // in volts
6 R1 = 2; // in ohms
7 R2 = 1; // in ohms
8 R3 = 4; // in ohms
9
10 //calculation:
11 //The 4ohm resistance branch is short-circuited as
    shown in Figure 13.35(b).
12 //Figure 13.35(b)
13 Isc = V1/R1 + V2/R2
14 //the resistance looking-in at a break made
    between A and B is given by
15 r = R1*R2/(R1 + R2)
16 //From the Norton equivalent network shown in Figure
    13.35(c) the current in the 4ohm resistance is
    given by:
17 I = (r/(r + R3))*Isc
18
19 printf("\n\n Result \n\n")
20 printf("\n the current in the 4ohm resistance is
    given by %.3f A",I)

```

---

#### Scilab code Exa 13.14 Example 14

```

1 //Problem 13.14: Use Norton s theorem to determine
    the current flowing in the 3 ohm resistance of
    the network shown in Figure 13.36(a). The voltage
    source has negligible internal resistance.
2
3 //initializing the variables:
4 V = 24; // in volts

```

```

5 R1 = 20; // in ohms
6 R2 = 5; // in ohms
7 R3 = 10; // in ohms
8 R4 = 5/3; // in ohms
9 R5 = 3; // in ohms
10
11 //calculation:
12 //The 3ohm resistance branch is short-circuited as
    shown in Figure 13.36(b).
13 //Figure 13.36(c) is equivalent to Figure 13.36(b).
14 Isc = V/R2
15 //the resistance looking-in at a break made
    between A and B is given by
16 r = R3*R2/(R3 + R2)
17 //From the Norton equivalent network shown in Figure
    13.36(f) the current in the 3ohm resistance is
    given by:
18 I = (r/(r + R4 + R5))*Isc
19
20 printf("\n\n Result \n\n")
21 printf("\n the current in the 3ohm resistance is
    given by %.0f A",I)

```

---

### Scilab code Exa 13.15 Example 15

```

1 //Problem 13.15: Determine the current flowing in
    the 2ohm resistance in the network shown in
    Figure 13.37(a).
2
3 //initializing the variables:
4 I = 15; // in amperes
5 R1 = 6; // in ohms
6 R2 = 4; // in ohms
7 R3 = 8; // in ohms
8 R4 = 2; // in ohms

```

```

9 R5 = 7; // in ohms
10
11 //calculation:
12 //The 2ohm resistance branch is short-circuited as
    shown in Figure 13.37(b).
13 //Figure 13.37(c) is equivalent to Figure 13.37(b).
14 Isc = (R1/(R1 + R2))*I
15 //the resistance looking-in at a break made
    between A and B is given by
16 r = ((R1 + R2)*(R3 + R5)/(R1 + R2 + R3 + R5))
17 //From the Norton equivalent network shown in Figure
    13.37(e) the current in the 2ohm resistance is
    given by:
18 I = (r/(r + R4))*Isc
19
20 printf("\n\n Result \n\n")
21 printf("\n the current in the 2ohm resistance is
    given by %.2f A",I)

```

---

### Scilab code Exa 13.18 Example 18

```

1 //Problem 13.18: (a) Convert the circuit to the left
    of terminals AB in Figure 13.45(a) to an
    equivalent Th evenin circuit by initially
    converting to a Norton equivalent circuit. (b)
    Determine the current flowing in the 1.8 ohm
    resistor.
2
3 //initializing the variables:
4 E1 = 12; // in volts
5 E2 = 24; // in volts
6 R1 = 3; // in ohms
7 R2 = 2; // in ohms
8 R3 = 1.8; // in ohms
9

```



```

10 //calculation :
11 //For the branch containing the V1 source ,
    converting to a Norton equivalent network gives
12 Isc1 = E1/R1
13 r1 = R1
14 //For the branch containing the V2 source ,
    converting to a Norton equivalent network gives
15 Isc2 = E2/R2
16 r2 = R2
17 //Thus the network of Figure 13.46(a) converts to
    Figure 13.46(b).
18 //total short-circuit current
19 Isct = Isc1 + Isc2
20 //the resistance is
21 z = r1*r2/(r1 + r2)
22 //Both of the Norton equivalent networks shown in
    Figure 13.46(c) may be converted to Th evenin
    equivalent circuits. The open-circuit voltage
    across CD is
23 Vcd = Isct*z
24 //the current I flowing in a 1.8 ohm resistance
    connected between A and B is given by:
25 I = Vcd/(z + R3)
26
27 printf("\n\n Result \n\n")
28 printf("\n the current I flowing in a 1.8 ohm
    resistance connected between A and B is given by
    %.2f A",I)

```

---

### Scilab code Exa 13.19 Example 19

```

1 //Problem 13.19: Determine by successive conversions
    between Th evenin and Norton equivalent
    networks a Th evenin equivalent circuit for
    terminals AB of Figure 13.46(a). Hence determine

```

```

    the current flowing in the 200 ohm resistance.
2
3 //initializing the variables:
4 V1 = 10; // in volts
5 V2 = 6; // in volts
6 R1 = 2000; // in ohms
7 R2 = 3000; // in ohms
8 R3 = 600; // in ohms
9 R4 = 200; // in ohms
10 i = 0.001; // in amperes
11
12 //calculation:
13 //For the branch containing the V1 source ,
    converting to a Norton equivalent network gives
14 Isc1 = V1/R1
15 r1 = R1
16 //For the branch containing the V2 source ,
    converting to a Norton equivalent network gives
17 Isc2 = V2/R2
18 r2 = R2
19 //Thus the network of Figure 13.46(a) converts to
    Figure 13.46(b).
20 //total short-circuit current
21 Isct = Isc1 + Isc2
22 //the resistance is
23 z = r1*r2/(r1 + r2)
24 //Both of the Norton equivalent networks shown in
    Figure 13.46(c) may be converted to Th evenin
    equivalent circuits. The open-circuit voltage
    across CD is
25 Vcd = Isct*z
26 //The open-circuit voltage across EF is
27 Vef = i*R3
28 //the resistance looking -in at EF is
29 r3 = R3
30 //Thus Figure 13.46(c) converts to Figure 13.46(d).
    Combining the two Th evenin circuits gives
31 E = Vcd - Vef

```

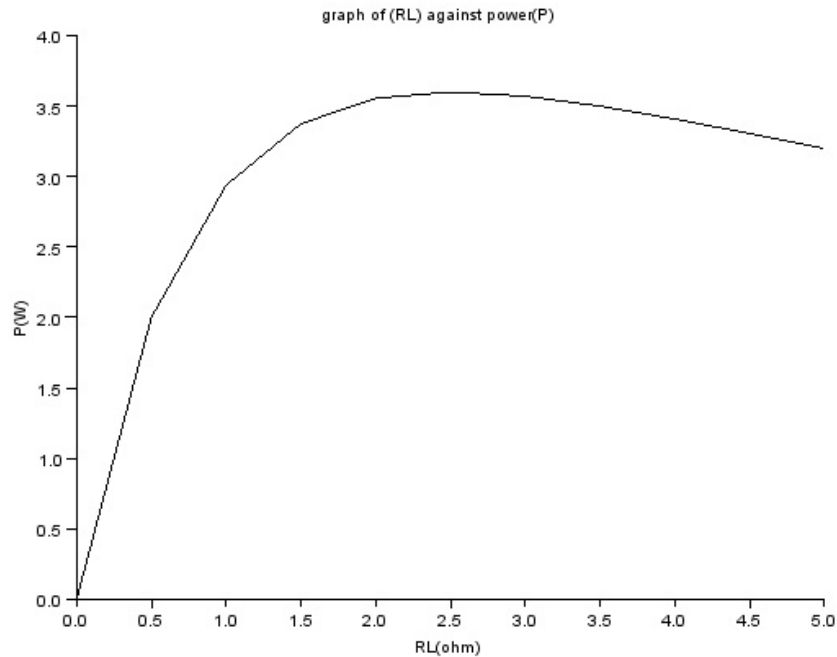


Figure 13.1: Example 20

```

32 r = z + r3
33 //the current I flowing in a 200 ohm resistance
   connected between A and B is given by:
34 I = E/(r + R4)
35
36 printf("\n\n Result \n\n")
37 printf("\n the current I flowing in a 200ohm
   resistance connected between A and B is given by:
   is %.2E A",I)

```

---

Scilab code Exa 13.20 Example 20

```

1 //Problem 13.20: The circuit diagram of Figure 13.48
   shows dry cells of source e.m.f. 6 V, and
   internal resistance 2.5 ohm. If the load
   resistance RL is varied from 0 to 5 ohm in 0.5
   ohm steps, calculate the power dissipated by the
   load in each case. Plot a graph of RL (
   horizontally) against power (vertically) and
   determine the maximum power dissipated.
2
3 //initializing the variables:
4 V = 6; // in volts
5 r = 2.5; // in ohms
6
7 //calculation:
8 RL=(0:0.5:5)';
9 function [y]=f(RL)
10     y = RL*(V/(r + RL))^2;
11 endfunction
12 fplot2d(RL, f)
13 xtitle("graph of (RL) against power(P)", "RL(ohm)",
        "P(W)")

```

---

### Scilab code Exa 13.21 Example 21

```

1 //Problem 13.21: A d.c. source has an open-circuit
   voltage of 30 V and an internal resistance of 1.5
   ohm. State the value of load resistance that
   gives maximum power dissipation and determine the
   value of this power.
2
3 //initializing the variables:
4 V = 30; // in volts
5 r = 1.5; // in ohms
6
7 //calculation:

```

```

8 //current  $I = E/(r + RL)$ 
9 //For maximum power,  $RL = r$ 
10  $RL = r$ 
11  $I = V/(r + RL)$ 
12 //Power, P, dissipated in load RL, P
13  $P = RL*I^2$ 
14
15 printf("\n\n Result \n\n")
16 printf("\n (a) the value of the load resistor RL is
    %.1f ohm",RL)
17 printf("\n (b) maximum power dissipation = %.0f W",P
    )

```

---

#### Scilab code Exa 13.22 Example 22

```

1 //Problem 13.22: Find the value of the load resistor
    RL shown in Figure 13.51(a) that gives maximum
    power dissipation and determine the value of this
    power.
2
3 //initializing the variables:
4  $V = 15$ ; // in volts
5  $R1 = 3$ ; // in ohms
6  $R2 = 12$ ; // in ohms
7
8 //calculation:
9 //Resistance RL is removed from the circuit as shown
    in Figure 13.51(b).
10 //The p.d. across AB is the same as the p.d. across
    the 12 ohm resistor.
11  $E = (R2/(R1 + R2))*V$ 
12 //Removing the source of e.m.f. gives the circuit of
    Figure 13.51(c),
13 //from which resistance, r
14  $r = R1*R2/(R1 + R2)$ 

```

```

15 //The equivalent Th evenin s circuit supplying
    terminals AB is shown in Figure 13.51(d), from
    which, current  $I = E/(r + RL)$ 
16 //For maximum power,  $RL = r$ 
17  $RL = r$ 
18  $I = E/(r + RL)$ 
19 //Power, P, dissipated in load RL, P
20  $P = RL * I^2$ 
21
22 printf("\n\n Result \n\n")
23 printf("\n (a) the value of the load resistor RL is
    %.1f ohm",RL)
24 printf("\n (b) maximum power dissipation = %.0f W",P
    )

```

---

# Chapter 14

## Alternating voltages and currents

Scilab code Exa 14.01 Example 1

```
1 //Problem 14.01: Determine the periodic time for
   frequencies of (a) 50 Hz and (b) 20 kHz
2
3 //initializing the variables:
4 f1 = 50; // in Hz
5 f2 = 20000; // in Hz
6
7 //calculation:
8 T1 = 1/f1
9 T2 = 1/f2
10
11 printf("\n\n Result \n\n")
12 printf("\n (a) Periodic time T = %.2f secs",T1)
13 printf("\n (b) Periodic time T = %.2E secs\n",T2)
```

---

Scilab code Exa 14.02 Example 2

```

1 //Problem 14.02: Determine the frequencies for
   periodic times of (a) 4 ms, (b) 4 s
2
3 //initializing the variables:
4 T1 = 0.004; // in secs
5 T2 = 4E-6; // in secs
6
7 //calculation:
8 f1 = 1/T1
9 f2 = 1/T2
10
11 printf("\n\n Result \n\n")
12 printf("\n (a) Frequency f = %.0f Hz",f1)
13 printf("\n (b) Frequency f = %.2E secs",f2)

```

---

#### Scilab code Exa 14.03 Example 3

```

1 //Problem 14.03: An alternating current completes 5
   cycles in 8 ms. What is its frequency?
2
3 //initializing the variables:
4 T = (8E-3)/5; // in secs
5
6 //calculation:
7 f = 1/T
8
9 printf("\n\n Result \n\n")
10 printf("\n Frequency f = %.0f Hz\n",f)

```

---

#### Scilab code Exa 14.04 Example 4



```

1 //Problem 14.04: For the periodic waveforms shown in
   Figure 14.5 determine for each: (i) frequency (
   ii) average value over half a cycle (iii) rms
   value (iv) form factor and (v) peak factor
2
3 //initializing the variables:
4 Ta = 0.02; // Time for 1 complete cycle in secs
5 Vamax = 200; // in volts
6 Va1 = 25; // in volts
7 Va2 = 75; // in volts
8 Va3 = 125; // in volts
9 Va4 = 175; // in volts
10 Tb = 0.016; // Time for 1 complete cycle in secs
11 Ibmax = 10; // in Amperes
12
13 //calculation:
14 //for Triangular waveform (Figure 14.5(a))
15 fa = 1/Ta
16 Aaw = Ta*Vamax/4
17 Vaavg = Aaw*2/Ta
18 Varms = (((Va1^2) + (Va2^2) + (Va3^2) + (Va4^2))/4)
   ^0.5 //Note that the greater the number of
   intervals chosen, the greater the accuracy of the
   result
19 Ffa = Varms/Vaavg
20 Pfa = Vamax/Varms
21
22 //for Rectangular waveform (Figure 14.5(b))
23 fb = 1/Tb
24 Abw = Tb*Ibmax/2
25 Ibavg = Abw*2/Tb
26 Ibrms = 10
27 Ffb = Ibrms/Ibavg
28 Pfb = Ibmax/Ibrms
29
30 printf("\n\n Result \n\n")
31 printf("\n (a1)Frequency f = %.0f Hz",fa)
32 printf("\n (a2)average value over half a cycle = %.0

```

```

    f V",Vaavg)
33 printf("\n (a3)rms value = %.1 f V",Varms)
34 printf("\n (a4)Form factor = %.2 f",Ffa)
35 printf("\n (a5)Peak factor = %.2 f",Pfa)
36 printf("\n (b1)Frequency f = %.1 f Hz",fb)
37 printf("\n (b2)average value over half a cycle = %.0
    f A",Ibavg)
38 printf("\n (b3)rms value = %.0 f A",Ibrms)
39 printf("\n (b4)Form factor = %.0 f",Ffb)
40 printf("\n (b5)Peak factor = %.0 f",Pfb)

```

---

#### Scilab code Exa 14.06 Example 6

```

1 //Problem 14.06: Calculate the rms value of a
    sinusoidal current of maximum value 20 A
2
3 //initializing the variables:
4 Imax = 20; // in Amperes
5
6 //calculation:
7 //for a sine wave
8 Irms = Imax/(20.5)
9
10 printf("\n\n Result \n\n")
11 printf("\n Rms value = %.2 f A\n",Irms)

```

---

#### Scilab code Exa 14.07 Example 7

```

1 //Problem 14.07: Determine the peak and mean values
    for a 240 V mains supply.
2
3 //initializing the variables:
4 Vrms = 240; // in Volts

```

```

5
6 //calculation:
7 //for a sine wave
8 Vmax = Vrms*(2^0.5)
9 Vmean = 0.637*Vmax
10
11 printf("\n\n Result \n\n")
12 printf("\n peak value = %.1f V",Vmax)
13 printf("\n mean value = %.1f V",Vmean)

```

---

#### Scilab code Exa 14.08 Example 8

```

1 //Problem 14.08: A supply voltage has a mean value
  of 150 V. Determine its maximum value and its rms
  value
2
3 //initializing the variables:
4 Vmean = 150; // in Volts
5
6 //calculation:
7 //for a sine wave
8 Vmax = Vmean/0.637
9 Vrms = 0.707*Vmax
10
11 printf("\n\n Result \n\n")
12 printf("\n peak value = %.1f V",Vmax)
13 printf("\n rms value = %.1f V",Vrms)

```

---

#### Scilab code Exa 14.09 Example 9

```

1 //Problem 14.09: An alternating voltage is given by
  v = 282.8 sin 314t volts. Find (a) the rms

```

```

    voltage, (b) the frequency and (c) the
    instantaneous value of voltage when t = 4 ms
2
3 //initializing the variables:
4 Vmax = 282.8; // in Volts
5 w = 314; // in rad/sec
6 t = 0.004; // in sec
7
8 //calculation:
9 //for a sine wave
10 Vrms = 0.707*Vmax
11 f = w/(2*pi)
12 v = Vmax*sin(w*t)
13
14 printf("\n\n Result \n\n")
15 printf("\n (a)rms value = %.0f V",Vrms)
16 printf("\n (b)frequency f = %.0f Hz",f)
17 printf("\n (c)instantaneous value of voltage at 4 ms
    = %.1f V",v)

```

---

#### Scilab code Exa 14.10 Example 10

```

1 //Problem 14.10: An alternating voltage is given by
    v = 75sin(200*pi*t -0.25) volts. Find (a) the
    amplitude, (b) the peak-to-peak value, (c) the
    rms value, (d) the periodic time, (e) the
    frequency, and (f) the phase angle (in degrees
    and minutes) relative to 75 sin 200t
2
3 //initializing the variables:
4 Vmax = 75; // in Volts
5 w = 200*pi; // in rad/sec
6 t = 0.004; // in sec
7 phi = 0.25; // in radians
8

```

```

 9 //calculation :
10 //for a sine wave
11 Vptp = 2*Vmax
12 Vrms = 0.707*Vmax
13 f = w/(2*%pi)
14 T = 1/f
15 v = Vmax*sin(w*t)
16 phid = phi*180/%pi
17
18 printf("\n\n Result \n\n")
19 printf("\n (a) Amplitude , or peak value = %.0f V" ,
    Vmax)
20 printf("\n (b) Peak-to-peak value = %.0f V" ,Vptp)
21 printf("\n (c)rms value = %.0f V" ,Vrms)
22 printf("\n (d) periodic time , T = %.2f sec" ,T)
23 printf("\n (e) frequency f = %.0f Hz" ,f)
24 printf("\n (f) phase angle = %.2f " ,phid)

```

---

#### Scilab code Exa 14.12 Example 12

```

1 //Problem 14.12: The current in an a.c. circuit at
  any time t seconds is given by:  $i = 120 \sin(100\pi t + 0.36)$  amperes. Find: (a) the peak value, the
  periodic time, the frequency and phase angle
  relative to  $120 \sin 100\pi t$  (b) the value of the
  current when  $t = 0$  (c) the value of the current
  when  $t = 8$  ms (d) the time when the current first
  reaches 60 A, and (e) the time when the current
  is first a maximum
2
3 //initializing the variables :
4 Imax = 120; // in Amperes
5 w = 100*%pi; // in rad/sec
6 phi = 0.36; // in rad
7 t1 = 0; // in secs

```

```

8 t2 = 0.008; // in secs
9 i = 60; // in amperes
10
11 //calculation:
12 //for a sine wave
13 f = w/(2*%pi)
14 T = 1/f
15 phid = phi*180/%pi
16 i0 = Imax*sin((w*t1) + phi)
17 i8 = Imax*sin((w*t2)+phi)
18 ti = (asin(i/Imax) - phi)/w
19 tm1 = (asin(Imax/Imax) - phi)/w
20
21 printf("\n\n Result \n\n")
22 printf("\n (a)Peak value = %.0f A, Periodic time T =
      %.2f sec , Frequency , f = %.0f Hz Phase angle = %
      .1f ", Imax, T, f, phid)
23 printf("\n (b) When t = 0, i = %.1f A",i0)
24 printf("\n (c)When t = 8 ms = %.1f A", i8)
25 printf("\n (d)When i is 60 A, then time t = %.2E s",
      ti)
26 printf("\n (e)When the current is a maximum, time, t
      = %.2E s",tm1)

```

---

# Chapter 15

## Single phase series ac circuits

Scilab code Exa 15.01 Example 1

```
1 //Problem 15.01: (a) Calculate the reactance of a
   coil of inductance 0.32 H when it is connected to
   a 50 Hz supply. (b) A coil has a reactance of
   124 ohm in a circuit with a supply of frequency 5
   kHz. Determine the inductance of the coil.
2
3 //initializing the variables:
4 L = 0.32; // in Henry
5 f1 = 50; // in Hz
6 f2 = 5000; // in Hz
7 Z = 124; // in ohms
8
9 //calculation:
10 XL = 2*%pi*f1*L
11 L = Z/(2*%pi*f2)
12
13 printf("\n\n Result \n\n")
14 printf("\n (a)Inductive reactance , XL = %.1f ohms ",
   XL)
15 printf("\n (b)Inductance L = %.2E H",L)
```

---

### Scilab code Exa 15.02 Example 2

```
1 //Problem 15.02: A coil has an inductance of 40 mH
   and negligible resistance. Calculate its
   inductive reactance and the resulting current if
   connected to (a) a 240 V, 50 Hz supply, and (b) a
   100 V, 1 kHz supply.
2
3 //initializing the variables:
4 L = 0.040; // in Henry
5 V1 = 240; // in volts
6 V2 = 100; // in volts
7 f1 = 50; // in Hz
8 f2 = 1000; // in Hz
9
10 //calculation:
11 XL1 = 2*%pi*f1*L
12 I1 = V1/XL1
13 XL2 = 2*%pi*f2*L
14 I2 = V2/XL2
15
16 printf("\n\n Result \n\n")
17 printf("\n (a) Inductive reactance, XL = %.2 f ohms
   and current I = %.2 f A", XL1, I1)
18 printf("\n (b) Inductive reactance, XL = %.1 f ohms
   and current I = %.3 f A", XL2, I2)
```

---

### Scilab code Exa 15.03 Example 3

```
1 //Problem 15.03: Determine the capacitive reactance
   of a capacitor of 10 F when connected to a
   circuit of frequency (a) 50 Hz (b) 20 kHz
```



```

2
3 //initializing the variables:
4 C = 10E-6; // in Farads
5 f1 = 50; // in Hz
6 f2 = 20000; // in Hz
7
8 //calculation:
9 Xc1 = 1/(2*%pi*f1*C)
10 Xc2 = 1/(2*%pi*f2*C)
11
12 printf("\n\n Result \n\n")
13 printf("\n (a) Capacitive reactance , Xc = %.1f ohms "
    , Xc1)
14 printf("\n (b) Capacitive reactance , Xc = %.3f ohms "
    , Xc2)

```

---

#### Scilab code Exa 15.04 Example 4

```

1 //Problem 15.04: A capacitor has a reactance of 40
    ohms when operated on a 50 Hz supply. Determine
    the value of its capacitance.
2
3 //initializing the variables:
4 Z = 40; // in ohms
5 f = 50; // in Hz
6
7 //calculation:
8 C = 1/(2*%pi*f*Z)
9
10 printf("\n\n Result \n\n")
11 printf("\n Capacitance ,C = %.2E F ", C)

```

---

#### Scilab code Exa 15.05 Example 5

```

1 //Problem 15.05: Calculate the current taken by a 23
   F capacitor when connected to a 240 V, 50 Hz
   supply.
2
3 //initializing the variables:
4 C = 23E-6; // in Farads
5 f = 50; // in Hz
6 V = 240; // in volts
7
8 //calculation:
9 Xc = 1/(2*%pi*f1*C)
10 I = V/Xc
11
12 printf("\n\n Result \n\n")
13 printf("\n current I = %.2 f A ",I)

```

---

#### Scilab code Exa 15.06 Example 6

```

1 //Problem 15.06: In a series R L circuit the p.d.
   across the resistance R is 12 V and the p.d.
   across the inductance L is 5 V. Find the supply
   voltage and the phase angle between current and
   voltage.
2
3 //initializing the variables:
4 Vr = 12; // in volts
5 Vl = 5; // in volts
6
7 //calculation:
8 V = (Vr^2 + Vl^2)^0.5
9 phi = atan(Vl/Vr)
10 phid = phi*180/%pi
11
12 printf("\n\n Result \n\n")
13 printf("\n supply voltage V = %.0 f V, phase angle

```

between current and voltage is %.2 f ",V, phid)

---

### Scilab code Exa 15.07 Example 7

```
1 //Problem 15.07: A coil has a resistance of 4 ohms
  and an inductance of 9.55 mH. Calculate (a) the
  reactance , (b) the impedance, and (c) the current
  taken from a 240 V, 50 Hz supply. Determine also
  the phase angle between the supply voltage and
  current.
2
3 //initializing the variables:
4 V = 240; // in volts
5 R = 4; // in ohms
6 L = 0.00955; // in Henry
7 f = 50; // in Hz
8
9 //calculation:
10 XL = 2*%pi*f*L
11 Z = (R^2 + XL^2)^0.5
12 I = V/Z
13 phid = atan(XL/R)*180/%pi
14
15 printf("\n\n Result \n\n")
16 printf("\n (a)Inductive reactance , XL = %.0 f ohms",
  XL)
17 printf("\n (b)Impedance , Z = %.0 f ohms",Z)
18 printf("\n (c)Current , I = %.0 f A",I)
19 printf("\n (d)phase angle between the supply voltage
  and current is %.2 f ",phid)
```

---

### Scilab code Exa 15.08 Example 8

```

1 //Problem 15.08: A coil takes a current of 2 A from
  a 12 V d.c. supply. When connected to a 240 V, 50
  Hz supply the current is 20 A. Calculate the
  resistance, impedance, inductive reactance and
  inductance of the coil.
2
3 //initializing the variables:
4 Vdc = 12; // in volts
5 Vac = 240; // in volts
6 Iac = 20; // in Amperes
7 Idc = 2; // in Amperes
8 f = 50; // in Hz
9
10 //calculation:
11 R = Vdc/Idc
12 Z = Vac/Iac
13 XL = (Z^2 - R^2)^0.5
14 L = XL/(2*pi*f)
15
16 printf("\n\n Result \n\n")
17 printf("\n (a) Resistance, R = %.0f ohms",R)
18 printf("\n (b) Impedance, Z = %.0f ohms",Z)
19 printf("\n (c) Inductive reactance, XL = %.2f ohms",
  XL)
20 printf("\n (d) Inductance, L = %.4f H",L)

```

---

#### Scilab code Exa 15.09 Example 9

```

1 //Problem 15.09: A coil of inductance 318.3 mH and
  negligible resistance is connected in series with
  a 200 ohms resistor to a 240 V, 50 Hz supply.
  Calculate (a) the inductive reactance of the coil
  , (b) the impedance of the circuit, (c) the
  current in the circuit, (d) the p.d. across each
  component, and (e) the circuit phase angle

```

```

2
3 //initializing the variables:
4 R = 200; // in ohms
5 L = 0.3183; // in henry
6 Vac = 240; // in volts
7 f = 50; // in Hz
8
9 //calculation:
10 XL = 2*%pi*f*L
11 Z = (R^2 + XL^2)^0.5
12 I = V/Z
13 VL = I*XL
14 VR = I*R
15 phid = atan(XL/R)*180/%pi
16
17 printf("\n\n Result \n\n")
18 printf("\n (a) Inductive reactance , XL = %.0 f ohms",
        XL)
19 printf("\n (b) Impedance , Z = %.1 f ohms" ,Z)
20 printf("\n (c) current , I = %.3 f A" ,I)
21 printf("\n (d) p.d. across Inductor , VL = %.1 f V and
        p.d. across resistance , VR = %.1 f V" ,VL, VR)
22 printf("\n (e) circuit phase angle is %.2 f ",phid)

```

---

### Scilab code Exa 15.10 Example 10

```

1 //Problem 15.10: A coil consists of a resistance of
  100 ohms and an inductance of 200 mH. If an
  alternating voltage , v, given by  $v = 200 \sin 500t$ 
  volts is applied across the coil , calculate (a)
  the circuit impedance , (b) the current flowing , (
  c) the p.d. across the resistance , (d) the p.d.
  across the inductance and (e) the phase angle
  between voltage and current.
2

```

```

3 //initializing the variables:
4 R = 100; // in ohms
5 L = 0.2; // in henry
6 Vmax = 200; // in volts
7 w = 500; // in rad/sec
8
9 //calculation:
10 Vrms = 0.707*Vmax
11 f = w/(2*%pi)
12 XL = 2*%pi*f*L
13 Z = (R^2 + XL^2)^0.5
14 I = Vrms/Z
15 VL = I*XL
16 VR = I*R
17 phid = atan(XL/R)*180/%pi
18
19 printf("\n\n Result \n\n")
20 printf("\n (a) Impedance , Z = %.1f ohms",Z)
21 printf("\n (b) current , I = %.0f A",I)
22 printf("\n (c) p.d. across resistance , VR = %.0f V",
    VR)
23 printf("\n (d) p.d. across Inductor , VL = %.0f V",VL)
24 printf("\n (e) circuit phase angle is %.0f ",phid)

```

---

### Scilab code Exa 15.11 Example 11

```

1 //Problem 15.11: A pure inductance of 1.273 mH is
    connected in series with a pure resistance of 30
    ohms. If the frequency of the sinusoidal supply
    is 5 kHz and the p.d. across the 30 ohm resistor
    is 6 V, determine the value of the supply voltage
    and the voltage across the 1.273 mH inductance.
    Draw the phasor diagram.
2
3 //initializing the variables:

```

```

4 R = 30; // in ohms
5 L = 1.2273E-3; // in henry
6 f = 5000; // in Hz
7 VR = 6; // in volts
8
9 //calculation:
10 I =VR/R
11 XL = 2*%pi*f*L
12 Z = (R^2 + XL^2)^0.5
13 V = I*Z
14 VL = I*XL
15
16 printf("\n\n Result \n\n")
17 printf("\n (a)supply voltage = %.0f Volts",V)
18 printf("\n (b)p.d. across Inductor , VL = %.0f V",VL)

```

---

#### Scilab code Exa 15.12 Example 12

```

1 //Problem 15.12: A coil of inductance 159.2 mH and
   resistance 20 ohms is connected in series with a
   60 ohms resistor to a 240 V, 50 Hz supply.
   Determine (a) the impedance of the circuit , (b)
   the current in the circuit , (c) the circuit phase
   angle , (d) the p.d. across the 60 ohms resistor
   and (e) the p.d. across the coil. (f) Draw the
   circuit phasor diagram showing all voltages.
2
3 //initializing the variables:
4 R = 60; // in ohms
5 Rc = 20; // in ohms
6 L = 159.2E-3; // in henry
7 f = 50; // in Hz
8 V = 240; // in volts
9
10 //calculation:

```

```

11 XL = 2*%pi*f*L
12 Rt = R + Rc
13 Z = (Rt^2 + XL^2)^0.5
14 I = V/Z
15 phid = atan(XL/Rt)*180/%pi
16 VR = I*R
17 Zc = (Rc^2 + XL^2)^0.5
18 Vc = I*Zc
19 VL = I*XL
20 VRc = I*Rc
21
22 printf("\n\n Result \n\n")
23 printf("\n (a) Impedance , Z = %.2 f ohms" ,Z)
24 printf("\n (b) current , I = %.3 f A" ,I)
25 printf("\n (c) circuit phase angle is %.0 f " ,phid)
26 printf("\n (d) p.d. across resistance , VR = %.1 f V" ,
    VR)
27 printf("\n (e) p.d. across coil , Vc = %.0 f V" ,Vc)
28 printf("\n (f1) p.d. across Inductor , VL = %.1 f V" ,VL
    )
29 printf("\n (f2) p.d. across coil resistance , VRc = %
    .2 f V" ,VRc)

```

---

### Scilab code Exa 15.13 Example 13

```

1 //Problem 15.13: A resistor of 25 ohms is connected
  in series with a capacitor of 45 F . Calculate (
  a) the impedance, and (b) the current taken from
  a 240 V, 50 Hz supply. Find also the phase angle
  between the supply voltage and the current.
2
3 //initializing the variables:
4 R = 25; // in ohms
5 C = 45E-6; // in Farads
6 f = 50; // in Hz

```



```

7 V = 240; // in volts
8
9 //calculation:
10 Xc = 1/(2*%pi*f*C)
11 Z = (R^2 + Xc^2)^0.5
12 I = V/Z
13 phid = atan(Xc/R)*180/%pi
14
15 printf("\n\n Result \n\n")
16 printf("\n (a) Impedance , Z = %.2f ohms",Z)
17 printf("\n (b) current , I = %.2f A",I)
18 printf("\n (c) phase angle between the supply voltage
    and current is %.2f ",phid)

```

---

#### Scilab code Exa 15.14 Example 14

```

1 //Problem 15.14: A capacitor C is connected in
    series with a 40 ohm resistor across a supply of
    frequency 60 Hz. A current of 3 A flows and the
    circuit impedance is 50 ohms. Calculate: (a) the
    value of capacitance , C, (b) the supply voltage ,
    (c) the phase angle between the supply voltage
    and current , (d) the p.d. across the resistor ,
    and (e) the p.d. across the capacitor. Draw the
    phasor diagram.
2
3 //initializing the variables:
4 R = 40; // in ohms
5 f = 60; // in Hz
6 I = 3; //in amperes
7 Z = 50; // in ohms
8
9 //calculation:
10 Xc = (Z^2 - R^2)^0.5
11 C = 1/(2*%pi*f*Xc)

```

```

12 V = I*Z
13 phid = atan(Xc/R)*180/%pi
14 VR = I*R
15 Vc = I*Xc
16
17 printf("\n\n Result \n\n")
18 printf("\n (a) capacitance , C = %.2E F",C)
19 printf("\n (b) Voltage , V = %.0f Volts",V)
20 printf("\n (c) phase angle between the supply voltage
    and current is %.2 f ",phid)
21 printf("\n (d) p.d. across resistance , VR = %.0f V",
    VR)
22 printf("\n (e) p.d. across Capacitor , Vc = %.0f V",Vc
    )

```

---

### Scilab code Exa 15.15 Example 15

```

1 //Problem 15.15: A coil of resistance 5 ohms and
    inductance 120 mH in series with a 100 F
    capacitor , is connected to a 300 V, 50 Hz supply.
    Calculate (a) the current flowing , (b) the phase
    difference between the supply voltage and
    current , (c) the voltage across the coil and (d)
    the voltage across the capacitor.
2
3 //initializing the variables :
4 R = 5; // in ohms
5 C = 100E-6; // in Farads
6 L = 0.12; // in Henry
7 f = 50; // in Hz
8 V = 300; // in volts
9
10 //calculation :
11 XL = 2*%pi*f*L
12 Xc = 1/(2*%pi*f*C)

```

```

13 X = XL - Xc
14 //Since XL is greater than Xc, the circuit is
    inductive.
15 Z = (R^2 + (XL-Xc)^2)^0.5
16 I = V/Z
17 phid = atan((XL-Xc)/R)*180/%pi
18 Zcl = (R^2 + XL^2)^0.5
19 Vcl = I*Zcl
20 phidc = atan(XL/R)*180/%pi
21 Vc = I*Xc
22
23 printf("\n\n Result \n\n")
24 printf("\n (a) Current, I = %.2 f A", I)
25 printf("\n (b) phase angle between the supply voltage
    and current is %.2 f ", phid)
26 printf("\n (c) Voltage across the coil , Vcoil = %.0 f
    Volts", Vcl)
27 printf("\n (d) p.d. across Capacitor , Vc = %.0 f V", Vc
    )

```

---

### Scilab code Exa 15.16 Example 16

```

1 //Problem 15.16: The following three impedances are
    connected in series across a 40 V, 20 kHz supply:
    (i) a resistance of 8 ohms, (ii) a coil of
    inductance 130 H and 5 ohms resistance , and (
    iii) a 10 ohms resistor in series with a 0.25
    F capacitor. Calculate (a) the circuit current ,
    (b) the circuit phase angle and (c) the voltage
    drop across each impedance.
2
3 //initializing the variables:
4 R1 = 8; // in ohms
5 C = 0.25E-6; // in Farads
6 L = 130E-6; // in Henry

```

```

7 Rc = 5; // in ohms
8 R2 = 10; // in ohms
9 f = 20000; // in Hz
10 V = 40; // in volts
11
12 //calculation:
13 XL = 2*%pi*f*L
14 Xc = 1/(2*%pi*f*C)
15 X = Xc - XL
16 R = R1 + R2 + Rc
17 //Since Xc is greater than XL, the circuit is
    capacitive.
18 Z = (R^2 + (Xc-XL)^2)^0.5
19 I = V/Z
20 phid = atan((Xc-XL)/R)*180/%pi
21 V1 = I*R1
22 V2 = I*((Rc^2 + XL^2)^0.5)
23 V3 = I*((R2^2 + Xc^2)^0.5)
24
25 printf("\n\n Result \n\n")
26 printf("\n (a) Current , I = %.3 f A",I)
27 printf("\n (b) circuit phase angle is %.2 f ",phid)
28 printf("\n (c1) Voltage across the Resistance of 8
    ohms = %.2 f Volts",V1)
29 printf("\n (c2) Voltage across the coil , Vcoil = %.2 f
    Volts",V2)
30 printf("\n (c3)p.d. across Capacitor resistance
    circuit = %.2 f Volts",V3)

```

---

#### Scilab code Exa 15.17 Example 17

```

1 //Problem 15.17: Determine the p.d. s V1 and V2
    for the circuit shown in Figure 15.17 if the
    frequency of the supply is 5 kHz. Draw the phasor
    diagram and hence determine the supply voltage V

```

```

        and the circuit phase angle.
2
3 //initializing the variables:
4 R1 = 4; // in ohms
5 C = 1.273E-6; // in Farads
6 L = 286E-6; // in Henry
7 R2 = 8; // in ohms
8 f = 5000; // in Hz
9 I = 5; // in amperes
10
11 //calculation:
12 XL = 2*%pi*f*L
13 phid1 = atan(XL/R)*180/%pi
14 V1 = I*((R1^2 + XL^2)^0.5)
15 Xc = 1/(2*%pi*f*C)
16 V2 = I*((R2^2 + Xc^2)^0.5)
17 phid2 = atan(Xc/R)*180/%pi
18 Z = ((R1+R2)^2 + (Xc-XL)^2)^0.5
19 V = I*Z
20 phid = atan((Xc-XL)/(R1+R2))*180/%pi
21
22 printf("\n\n Result \n\n")
23 printf("\n Voltage V1 = %.2f V and V2 = %.1f V",V1,
        V2)
24 printf("\n Voltage supply , V = %.0f V",V)
25 printf("\n circuit phase angle is %.2f ",phid)

```

---

### Scilab code Exa 15.18 Example 18

```

1 //Problem 15.18: A coil having a resistance of 10
  ohms and an inductance of 125 mH is connected in
  series with a 60 F capacitor across a 120 V
  supply. At what frequency does resonance occur?
  Find the current flowing at the resonant
  frequency.

```

```

2
3 //initializing the variables:
4 R = 10; // in ohms
5 C = 60E-6; // in Farads
6 L = 125E-3; // in Henry
7 V = 120; // in Volts
8
9 //calculation:
10 fr = 1/(2*%pi*(L*C)^0.5)
11 //At resonance , XL = Xc and impedance Z = R
12 I = V/R
13
14 printf("\n\n Result \n\n")
15 printf("\n (a)Resonance frequency ,Fr = %.2 f Hz",fr)
16 printf("\n (b)Current , I = %.0 f",I)

```

---

#### Scilab code Exa 15.19 Example 19

```

1 //Problem 15.19: The current at resonance in a
   series L C R circuit is 100 A . If the
   applied voltage is 2 mV at a frequency of 200 kHz
   , and the circuit inductance is 50 H , find (a)
   the circuit resistance , and (b) the circuit
   capacitance .
2
3 //initializing the variables:
4 L = 0.05E-3; // in Henry
5 fr = 200000; // in Hz
6 V = 0.002; // in Volts
7 I = 0.1E-3; // in amperes
8
9 //calculation:
10 // L-C-R
11 //At resonance , XL = Xc and impedance Z = R
12 R = V/I

```

```

13 C = 1/(L*(2*%pi*fr)^2)
14
15 printf("\n\n Result \n\n")
16 printf("\n (a) Resistance , R = %.0 f ohms",R)
17 printf("\n (b) Capacitance , C = %.2E F",C)

```

---

### Scilab code Exa 15.20 Example 20

```

1 //Problem 15.20: A coil of inductance 80 mH and
  negligible resistance is connected in series with
  a capacitance of 0.25 F and a resistor of
  resistance 12.5 ohms across a 100 V, variable
  frequency supply. Determine (a) the resonant
  frequency , and (b) the current at resonance. How
  many times greater than the supply voltage is the
  voltage across the reactances at resonance?
2
3 //initializing the variables:
4 L = 80E-3; // in Henry
5 C = 0.25E-6; // in Farads
6 R = 12.5; // in ohms
7 V = 100; // in Volts
8
9 //calculation:
10 fr = 1/(2*%pi*((L*C)^0.5))
11 //At resonance , XL = Xc and impedance Z = R
12 I = V/R
13 VL = I*(2*%pi*fr*L)
14 Vc = I/(2*%pi*fr*C)
15 Vm = VL/V
16
17 printf("\n\n Result \n\n")
18 printf("\n (a)the resonant frequency = %.1 f Hz",fr)
19 printf("\n (b) Current , I = %.0 f A",I)
20 printf("\n (b) Voltage magnification at resonance = %"

```

.3 f V",Vm)

---

**Scilab code Exa 15.21** Example 21

```
1 //Problem 15.21: A series circuit comprises a coil
  of resistance 2 ohms and inductance 60 mH, and a
  30 F capacitor. Determine the Qfactor of the
  circuit at resonance.
2
3 //initializing the variables:
4 L = 60E-3; // in Henry
5 C = 30E-6; // in Farads
6 R = 2; // in ohms
7
8 //calculation:
9 Q = ((L/C)^0.5)/R
10
11 printf("\n\n Result \n\n")
12 printf("\n At resonance , Q-factor = %.2f",Q)
```

---

**Scilab code Exa 15.22** Example 22

```
1 //Problem 15.22: A coil of negligible resistance and
  inductance 100 mH is connected in series with a
  capacitance of 2 F and a resistance of 10
  across a 50 V, variable frequency supply.
  Determine (a) the resonant frequency, (b) the
  current at resonance, (c) the voltages across the
  coil and the capacitor at resonance, and (d) the
  Q-factor of the circuit.
2
3 //initializing the variables:
4 L = 100E-3; // in Henry
```



```

5 C = 2E-6; // in Farads
6 R = 10; // in ohms
7 V = 50; // in Volts
8
9 //calculation:
10 fr = 1/(2*pi*((L*C)^0.5))
11 //At resonance, XL = Xc and impedance Z = R
12 I = V/R
13 VL = I*(2*pi*fr*L)
14 Vc = I/(2*pi*fr*C)
15 Q = VL/V
16
17 printf("\n\n Result \n\n")
18 printf("\n (a)the resonant frequency = %.1f Hz",fr)
19 printf("\n (b)Current, I = %.0f A",I)
20 printf("\n (c)Voltage across coil at resonance is %
    .0fV and Voltage across capacitance at resonance
    is %.0fV",VL, Vc)
21 printf("\n (d)At resonance, Q-factor = %.2f",Q)

```

---

### Scilab code Exa 15.23 Example 23

```

1 //Problem 15.23: A filter in the form of a series
  L R C circuit is designed to operate at a
  resonant frequency of 5 kHz. Included within the
  filter is a 20 mH inductance and 10 ohm
  resistance. Determine the bandwidth of the filter
  .
2
3 //initializing the variables:
4 L = 20E-3; // in Henry
5 R = 10; // in ohms
6 fr = 5000; // in Hz
7
8 //calculation:

```

```

9 Qr = (2*%pi*fr)*L/R
10 bw = fr/Qr
11
12 printf("\n\n Result \n\n")
13 printf("\n Bandwidth, (f2-f1) = %.1 f Hz",bw)

```

---

#### Scilab code Exa 15.24 Example 24

```

1 //Problem 15.24: An instantaneous current , i = 250
   sin w
2 t mA flows through a pure resistance of 5 kohm. Find
   the power dissipated in the resistor.
3
4 //initializing the variables:
5 R = 5000; // in ohms
6 Imax = 0.250; // in Amperes
7
8 //calculation:
9 Irms = 0.707*Imax
10 P = Irms*Irms*R
11
12 printf("\n\n Result \n\n")
13 printf("\n Power, P = %.1 f Watts",P)

```

---

#### Scilab code Exa 15.25 Example 25

```

1 //Problem 15.25: A series circuit of resistance 60
   ohm and inductance 75 mH is connected to a 110 V,
   60 Hz supply. Calculate the power dissipated.
2
3 //initializing the variables:
4 R = 60; // in ohms

```

```

5 L = 75E-3; // in Henry
6 V = 110; // in Volts
7 f = 60; // in Hz
8
9 //calculation:
10 XL = 2*%pi*f*L
11 Z = (R^2 + XL^2)^0.5
12 I = V/Z
13 P = I*I*R
14
15 printf("\n\n Result \n\n")
16 printf("\n Power, P = %.0f Watts",P)

```

---

#### Scilab code Exa 15.26 Example 26

```

1 //Problem 15.26: A pure inductance is connected to a
   150 V, 50 Hz supply, and the apparent power of
   the circuit is 300 VA. Find the value of the
   inductance.
2
3 //initializing the variables:
4 VI = 300; // in VA
5 V = 150; // in Volts
6 f = 50; // in Hz
7
8 //calculation:
9 I = VI/V
10 XL = V/I
11 L = XL/(2*%pi*f)
12
13 printf("\n\n Result \n\n")
14 printf("\n Inductance = %.3f H",L)

```

---

**Scilab code Exa 15.27** Example 27

```
1 //Problem 15.27: A transformer has a rated output of
    200 kVA at a power factor of 0.8. Determine the
    rated power output and the corresponding reactive
    power.
2
3 //initializing the variables:
4 VI = 200000; // in VA
5 pf = 0.8; // power factor
6
7 //calculation:
8 P = VI*pf
9 Q = VI*sin(acos(pf))
10
11 printf("\n\n Result \n\n")
12 printf("\n rated power output is %.0fW and the
    corresponding reactive power is %.0f var",P,Q)
```

---

**Scilab code Exa 15.28** Example 28

```
1 //Problem 15.28: The power taken by an inductive
    circuit when connected to a 120 V, 50 Hz supply
    is 400 W and the current is 8 A. Calculate (a)
    the resistance, (b) the impedance, (c) the
    reactance, (d) the power factor, and (e) the
    phase angle between voltage and current.
2
3 //initializing the variables:
4 V = 120; // in Volts
5 f = 50; // in Hz
6 P = 400; // in Watt
7 I = 8; // in Amperes
8
9 //calculation:
```

```

10 R = P/(I*I)
11 Z = V/I
12 XL = (Z^2 - R^2)^0.5
13 pf = P/(V*I)
14 phi = acos(pf)*180/%pi
15
16 printf("\n\n Result \n\n")
17 printf("\n (a) resistance = %.2 f ohm ",R)
18 printf("\n (b) Impedance Z = %.0 f Ohm ",Z)
19 printf("\n (c) reactance = %.2 f ohm ",XL)
20 printf("\n (d) Power factor = %.4 f",pf)
21 printf("\n (e) phase angle = %.2 f ",phi)

```

---

#### Scilab code Exa 15.29 Example 29

```

1 //Problem 15.29: A circuit consisting of a resistor
  in series with a capacitor takes 100 watts at a
  power factor of 0.5 from a 100 V, 60 Hz supply.
  Find (a) the current flowing, (b) the phase angle
  , (c) the resistance, (d) the impedance, and (e)
  the capacitance.
2
3 //initializing the variables:
4 V = 100; // in Volts
5 f = 60; // in Hz
6 P = 100; // in Watt
7 pf = 0.5; // power factor
8
9 //calculation:
10 I = P/(pf*V)
11 phi = acos(pf)*180/%pi
12 R = P/(I*I)
13 Z = V/I
14 Xc = (Z^2 - R^2)^0.5
15 C = 1/(2*%pi*f*Xc)

```

```
16
17 printf("\n\n Result \n\n")
18 printf("\n (a) Current I = %.0f A ",I)
19 printf("\n (b) phase angle = %.0f ",phi)
20 printf("\n (c) resistance = %.0f ohm ",R)
21 printf("\n (d) Impedance Z = %.0f Ohm ",Z)
22 printf("\n (e) capacitance = %.2E F ",C)
```

---

# Chapter 16

## Single phase parallel ac circuits

Scilab code Exa 16.01 Example 1

```
1 //Problem 16.01: A 20 ohm resistor is connected in
  parallel with an inductance of 2.387 mH across a
  60 V, 1 kHz supply. Calculate (a) the current in
  each branch, (b) the supply current, (c) the
  circuit phase angle, (d) the circuit impedance,
  and (e) the power consumed.
2
3 //initializing the variables:
4 R = 20; // in Ohms
5 L = 2.387E-3; // in Henry
6 V = 60; // in Volts
7 f = 1000; // in Hz
8
9 //calculation:
10 IR = V/R
11 XL = 2*%pi*f*L
12 IL = V/XL
13 I = (IR^2 + IL^2)^0.5
14 phi = atan(IL/IR)
15 phid = phi*180/%pi
16 Z = V/I
```

```

17 P = V*I*cos(phi)
18
19 printf("\n\n Result \n\n")
20 printf("\n (a) Current through resistor is %.0f A
    and current through Inductor is %.0f A",IR, IL)
21 printf("\n (b) current , I = %.0f A ",I)
22 printf("\n (c) phase angle = %.2 f ",phid)
23 printf("\n (d) Impedance Z = %.0f Ohm ",Z)
24 printf("\n (e) Power consumed = %.0f Watt ",P)

```

---

### Scilab code Exa 16.02 Example 2

```

1 //Problem 16.02: A 30 F capacitor is connected in
  parallel with an 80 ohms resistor across a 240 V,
  50 Hz supply. Calculate (a) the current in each
  branch, (b) the supply current, (c) the circuit
  phase angle, (d) the circuit impedance, (e) the
  power dissipated, and (f) the apparent power.
2
3 //initializing the variables:
4 R = 80; // in Ohms
5 C = 30E-6; // in Farads
6 V = 240; // in Volts
7 f = 50; // in Hz
8
9 //calculation:
10 IR = V/R
11 Xc = 1/(2*%pi*f*C)
12 Ic = V/Xc
13 I = (IR^2 + Ic^2)^0.5
14 phi = atan(Ic/IR)
15 phid = phi*180/%pi
16 Z = V/I
17 P = V*I*cos(phi)
18 S = V*I

```



```

19
20 printf("\n\n Result \n\n")
21 printf("\n (a) Current through resistor is %.0f A
    and current through capacitor is %.3f A",IR, Ic)
22 printf("\n (b) current , I = %.3f A ",I)
23 printf("\n (c) phase angle = %.2 f ",phid)
24 printf("\n (d) Impedance Z = %.2 f Ohm ",Z)
25 printf("\n (e) Power consumed = %.0f Watt ",P)
26 printf("\n (f) apparent Power = %.1 f VA ",S)

```

---

### Scilab code Exa 16.03 Example 3

```

1 //Problem 16.03: A capacitor C is connected in
    parallel with a resistor R across a 120 V, 200 Hz
    supply. The supply current is 2 A at a power
    factor of 0.6 leading. Determine the values of C
    and R.
2
3 //initializing the variables:
4 pf = 0.6; // power factor
5 V = 120; // in Volts
6 f = 200; // in Hz
7 I = 2; // in Amperes
8
9 //calculation:
10 phi = acos(pf)
11 phid = phi*180/%pi
12 IR = I*cos(phi)
13 Ic = I*sin(phi)
14 R = V/IR
15 C = Ic/(2*%pi*f*V)
16
17 printf("\n\n Result \n\n")
18 printf("\n (a) Resistance R = %.0f Ohm ",R)
19 printf("\n (b) Capacitance ,C = %.2E F ",C)

```

---

**Scilab code Exa 16.04** Example 4

```
1 //Problem 16.04: A pure inductance of 120 mH is
   connected in parallel with a 25 F capacitor and
   the network is connected to a 100 V, 50 Hz
   supply. Determine (a) the branch currents, (b)
   the supply current and its phase angle, (c) the
   circuit impedance, and (d) the power consumed.
2
3 //initializing the variables:
4 C = 25E-6; // in Farads
5 L = 120E-3; // in Henry
6 V = 100; // in Volts
7 f = 50; // in Hz
8
9 //calculation:
10 XL = 2*%pi*f*L
11 IL = V/XL
12 Xc = 1/(2*%pi*f*C)
13 Ic = V/Xc
14 //IL and Ic are anti-phase. Hence supply current,
15 I = IL - Ic
16 //the current lags the supply voltage V by 90
17 phi = %pi/2
18 phid = phi*180/%pi
19 Z = V/I
20 P = V*I*cos(phi)
21
22 printf("\n\n Result \n\n")
23 printf("\n (a) Current through Inductor is %.3f A
   and current through capacitor is %.3f A",IL, Ic)
24 printf("\n (b) current, I = %.3f A ",I)
25 printf("\n (c) phase angle = %.0 f ",phid)
26 printf("\n (d) Impedance Z = %.2f Ohm ",Z)
```

```
27 printf("\n (e)Power consumed = %.0f Watt ",P)
```

---

### Scilab code Exa 16.05 Example 5

```
1 //Problem 16.05: Repeat Problem 16.04 for the
   condition when the frequency is changed to 150 Hz
2
3 //initializing the variables:
4 C = 25E-6; // in Farads
5 L = 120E-3; // in Henry
6 V = 100; // in Volts
7 f = 150; // in Hz
8
9 //calculation:
10 XL = 2*%pi*f*L
11 IL = V/XL
12 Xc = 1/(2*%pi*f*C)
13 Ic = V/Xc
14 //IL and Ic are anti-phase. Hence supply current,
15 I = Ic - IL
16 //the current leads the supply voltage V by 90
17 phi = %pi/2
18 phid = phi*180/%pi
19 Z = V/I
20 P = V*I*cos(phi)
21
22 printf("\n\n Result \n\n")
23 printf("\n (a)Current through Inductor is %.3f A
   and current through capacitor is %.3f A",IL, Ic)
24 printf("\n (b)current, I = %.3f A ",I)
25 printf("\n (c)phase angle = %.0f ",phid)
26 printf("\n (d)Impedance Z = %.2f Ohm ",Z)
27 printf("\n (e)Power consumed = %.0f Watt ",P)
```

---

### Scilab code Exa 16.06 Example 6

```
1 //Problem 16.06: A coil of inductance 159.2 mH and
   resistance 40 ohm is connected in parallel with a
   30 F capacitor across a 240 V, 50 Hz supply.
   Calculate (a) the current in the coil and its
   phase angle, (b) the current in the capacitor and
   its phase angle, (c) the supply current and its
   phase angle, (d) the circuit impedance, (e) the
   power consumed, (f) the apparent power, and (g)
   the reactive power. Draw the phasor diagram.
2
3 //initializing the variables:
4 C = 30E-6; // in Farads
5 R = 40; // in Ohms
6 L = 159.2E-3; // in Henry
7 V = 240; // in Volts
8 f = 50; // in Hz
9
10 //calculation:
11 XL = 2*%pi*f*L
12 Z1 = (R^2 + XL^2)^0.5
13 ILR = V/Z1
14 phi1 = atan(XL/R)
15 phi1d = phi1*180/%pi
16 Xc = 1/(2*%pi*f*C)
17 Ic = V/Xc
18 phi2 = %pi/2
19 phi2d = phi2*180/%pi
20 Ih = ILR*cos(phi1) + Ic*cos(phi2)
21 Iv = -1*ILR*sin(phi1) + Ic*sin(phi2)
22 I = (Ih^2 + Iv^2)^0.5
23 phi = atan(abs(Iv)/Ih)
24 Z = V/I
```

```

25 P = V*I*cos(phi)
26 phid = phi*180/%pi
27 S = V*I
28 Q = V*I*sin(phi)
29
30 printf("\n\n Result \n\n")
31 printf("\n (a)Current through coil is %.3f A and
        lagged by phase angle is %.2 f ",ILR,phi1d)
32 printf("\n (b)Current through capacitor is %.3f A
        and lead by phase angle is %.0 f ",Ic,phi2d)
33 printf("\n (c)supply Current is %.3f A and lagged by
        phase angle is %.2 f ",I,phid)
34 printf("\n (d)Impedance Z = %.2f Ohm ",Z)
35 printf("\n (e)Power consumed = %.0f Watt ",P)
36 printf("\n (f)apparent Power = %.1f VA ",S)
37 printf("\n (g)reactive Power = %.1f var ",Q)

```

---

### Scilab code Exa 16.07 Example 7

```

1 //Problem 16.07: A coil of inductance 0.12 H and
  resistance 3 kohm is connected in parallel with a
  0.02 F capacitor and is supplied at 40 V at a
  frequency of 5 kHz. Determine (a) the current in
  the coil, and (b) the current in the capacitor. (
  c) Draw to scale the phasor diagram and measure
  the supply current and its phase angle; check the
  answer by calculation. Determine (d) the circuit
  impedance and (e) the power consumed.
2
3 //initializing the variables:
4 C = 0.02E-6; // in Farads
5 R = 3000; // in Ohms
6 L = 120E-3; // in Henry
7 V = 40; // in Volts
8 f = 5000; // in Hz

```

```

9
10 //calculation:
11 XL = 2*%pi*f*L
12 Z1 = (R^2 + XL^2)^0.5
13 ILR = V/Z1
14 phi1 = atan(XL/R)
15 phi1d = phi1*180/%pi
16 Xc = 1/(2*%pi*f*C)
17 Ic = V/Xc
18 phi2 = %pi/2
19 phi2d = phi2*180/%pi
20 Ih = ILR*cos(phi1) + Ic*cos(phi2)
21 Iv = -1*ILR*sin(phi1) + Ic*sin(phi2)
22 I = (Ih^2 + Iv^2)^0.5
23 phi = atan((Iv)/Ih)
24 phid = phi*180/%pi
25 Z = V/I
26 P = V*I*cos(phi)
27
28 printf("\n\n Result \n\n")
29 printf("\n (a)Current through coil is %.5f A and
        lagged by phase angle is %.2 f ",ILR,phi1d)
30 printf("\n (b)Current through capacitor is %.5f A
        and lead by phase angle is %.0 f ",Ic,phi2d)
31 printf("\n (c)supply Current is %.5f A and lagged by
        phase angle is %.2 f ",I,phid)
32 printf("\n (d)Impedance Z = %.2 f Ohm ",Z)
33 printf("\n (e)Power consumed = %.4 f Watt ",P)

```

---

### Scilab code Exa 16.08 Example 8

- 1 //Problem 16.08: A pure inductance of 150 mH is connected in parallel with a 40 F capacitor across a 50 V, variable frequency supply. Determine (a) the resonant frequency of the

```

    circuit and (b) the current circulating in the
    capacitor and inductance at resonance.
2
3 //initializing the variables:
4 C = 40E-6; // in Farads
5 R = 0; // in Ohms
6 L = 150E-3; // in Henry
7 V = 50; // in Volts
8
9 //calculation:
10 fr = ((1/(L*C) - R*R/(L*L))^0.5)/(2*pi)
11 Xc = 1/(2*pi*fr*C)
12 Icirc = V/Xc
13
14 printf("\n\n Result \n\n")
15 printf("\n (a) Parallel resonant frequency , fr = %.2f
    Hz ",fr)
16 printf("\n (b) Current circulating in L and C at
    resonance = %.3f A ",Icirc)

```

---

### Scilab code Exa 16.09 Example 9

```

1 //Problem 16.09: A coil of inductance 0.20 H and
    resistance 60 ohm is connected in parallel with a
    20 F capacitor across a 20 V, variable
    frequency supply. Calculate (a) the resonant
    frequency, (b) the dynamic resistance, (c) the
    current at resonance and (d) the circuit Q-factor
    at resonance.
2
3 //initializing the variables:
4 C = 20E-6; // in Farads
5 R = 60; // in Ohms
6 L = 200E-3; // in Henry
7 V = 20; // in Volts

```

```

8
9 //calculation:
10 fr = ((1/(L*C) - R*R/(L*L))^0.5)/(2*pi)
11 Rd = L/(R*C)
12 Ir = V/Rd
13 Q = 2*pi*fr*L/R
14
15 printf("\n\n Result \n\n")
16 printf("\n (a) Parallel resonant frequency , fr = %.2 f
      Hz ",fr)
17 printf("\n (b) the dynamic resistance ,RD = %.1 f ohm "
      ,Rd)
18 printf("\n (c) Current at resonance = %.2 f A ",Ir)
19 printf("\n (d) Q-factor = %.2 f",Q)

```

---

#### Scilab code Exa 16.10 Example 10

```

1 //Problem 16.10: A coil of inductance 100 mH and
      resistance 800 ohm is connected in parallel with
      a variable capacitor across a 12 V, 5 kHz supply.
      Determine for the condition when the supply
      current is a minimum: (a) the capacitance of the
      capacitor , (b) the dynamic resistance , (c) the
      supply current , and (d) the Q-factor.
2
3 //initializing the variables:
4 fr = 5000; // in ohm
5 R = 800; // in Ohms
6 L = 100E-3; // in Henry
7 V = 12; // in Volts
8
9 //calculation:
10 C = 1/(L*{(2*pi*fr)^2 + R*R/(L*L)})
11 Rd = L/(R*C)
12 Ir = V/Rd

```



```

13 Q = 2*%pi*fr*L/R
14
15 printf("\n\n Result \n\n")
16 printf("\n (a) capacitance , C = %.3E F ",C)
17 printf("\n (b) the dynamic resistance ,RD = %.0f ohm "
    ,Rd)
18 printf("\n (c) Current at resonance = %.3E A ",Ir)
19 printf("\n (d) Q-factor = %.2f ",Q)

```

---

### Scilab code Exa 16.11 Example 11

```

1 //Problem 16.11: A single-phase motor takes 50 A at
    a power factor of 0.6 lagging from a 240 V, 50 Hz
    supply. Determine (a) the current taken by a
    capacitor connected in parallel with the motor to
    correct the power factor to unity, and (b) the
    value of the supply current after power factor
    correction.
2
3 //initializing the variables:
4 f = 50; // in ohm
5 V = 240; // in Volts
6 pf = 0.6// power factor
7 Im = 50; // in amperes
8
9 //calculation:
10 phi = acos(pf)
11 phid = phi*180/%pi
12 Ic = Im*sin(phi)
13 I = Im*cos(phi)
14
15 printf("\n\n Result \n\n")
16 printf("\n (a) the capacitor current Ic must be %.0f
    A for the power factor to be unity. ",Ic)
17 printf("\n (b) Supply current I = %.0f A ",I)

```

---

**Scilab code Exa 16.12** Example 12

```
1 //Problem 16.12: A motor has an output of 4.8 kW, an
   efficiency of 80% and a power factor of 0.625
   lagging when operated from a 240 V, 50 Hz supply.
   It is required to improve the power factor to
   0.95 lagging by connecting a capacitor in
   parallel with the motor. Determine (a) the
   current taken by the motor, (b) the supply
   current after power factor correction, (c) the
   current taken by the capacitor, (d) the
   capacitance of the capacitor, and (e) the kvar
   rating of the capacitor.
2
3 //initializing the variables:
4 Pout = 4800; // in Watt
5 eff = 0.8; // efficiency
6 f = 50; // in ohm
7 V = 240; // in Volts
8 pf1 = 0.625 // power factor
9 pf2 = 0.95 // power factor
10
11 //calculation:
12 Pin = Pout/eff
13 Im = Pin/(V*pf1)
14 phi1 = acos(pf1)
15 phi1d = phi1*180/%pi
16 //When a capacitor C is connected in parallel with
   the motor a current Ic flows which leads V by 90
   .
17 phi2 = acos(pf2)
18 phi2d = phi2*180/%pi
19 Imh = Im*cos(phi1)
20 //Ih = I*cos(phi2)
```

```

21 Ih = Imh
22 I = Ih/cos(phi2)
23 Imv = Im*sin(phi1)
24 Iv = I*sin(phi2)
25 Ic = Imv - Iv
26 C = Ic/(2*pi*f*V)
27 kvar = V*Ic/1000
28
29 printf("\n\n Result \n\n")
30 printf("\n (a) current taken by the motor , Im = %.0f
    A",Im)
31 printf("\n (b) supply current after p.f. correction ,
    I = %.2f A ",I)
32 printf("\n (c) magnitude of the capacitor current Ic
    = %.0f A",Ic)
33 printf("\n (d) capacitance , C = %.0f F ",(C/1E-6))
34 printf("\n (d) kvar rating of the capacitor = %.2f
    kvar ",kvar)

```

---

### Scilab code Exa 16.13 Example 13

```

1 //Problem 16.13: A 250 V, 50 Hz single-phase supply
  feeds the following loads (i) incandescent lamps
  taking a current of 10 A at unity power factor , (
  ii) fluorescent lamps taking 8 A at a power
  factor of 0.7 lagging , (iii) a 3 kVA motor
  operating at full load and at a power factor of
  0.8 lagging and (iv) a static capacitor.
  Determine, for the lamps and motor, (a) the total
  current, (b) the overall power factor and (c)
  the total power. (d) Find the value of the static
  capacitor to improve the overall power factor to
  0.975 lagging.
2
3 //initializing the variables:

```

```

4 S = 3000; // in VA
5 f = 50; // in ohm
6 V = 250; // in Volts
7 Ii1 = 10; // in Amperes
8 If1 = 8; // in Amperes
9 pfil = 1 // power factor
10 pffl = 0.7 // power factor
11 pfm = 0.8 // power factor
12 pf0 = 0.975 // power factor
13
14 //calculation:
15 phiil = acos(pfil)
16 phiild = phiil*180/%pi
17 phifl = acos(pffl)
18 phifld = phifl*180/%pi
19 phim = acos(pfm)
20 phimd = phim*180/%pi
21 phi0 = acos(pf0)
22 phi0d = phi0*180/%pi
23 Im = S/V
24 Ih = Ii1*cos(phiil) + If1*cos(phifl) + Im*cos(phim)
25 Iv = Ii1*sin(phiil) - If1*sin(phifl) - Im*sin(phim)
26 Il = (Ih^2 + Iv^2)^0.5
27 phi = atan(abs(Iv)/Ih)
28 phid = phi*180/%pi
29 pf = cos(phi)
30 P = V*Il*pf
31 I = Il*cos(phi)/cos(phi0)
32 Ic = Il*sin(phi) - I*sin(phi0)
33 C = Ic/(2*%pi*f*V)
34
35 printf("\n\n Result \n\n")
36 printf("\n (a) total current , Il = %.2 f A", Il)
37 printf("\n (b) Power factor = %.3 f", pf)
38 printf("\n (c) Total power , P = %.3 f Watt", P)
39 printf("\n (d) capacitance , C = %.2E F ", C)

```

---

# Chapter 17

## DC transients

Scilab code Exa 17.01 Example 1

```
1 //Problem 17.01: A 15 F uncharged capacitor is
   connected in series with a 47 kohm resistor
   across a 120 V, d.c. supply. Use the tangential
   graphical method to draw the capacitor voltage/
   time characteristic of the circuit. From the
   characteristic , determine the capacitor voltage
   at a time equal to one time constant after being
   connected to the supply , and also two seconds
   after being connected to the supply. Also , find
   the time for the capacitor voltage to reach one
   half of its steady state value.
2
3 //initializing the variables:
4 C = 15E-6; // in Farads
5 R = 47000; // in ohms
6 V = 120; // in Volts
7
8 //calculation:
9 tou = R*C
```

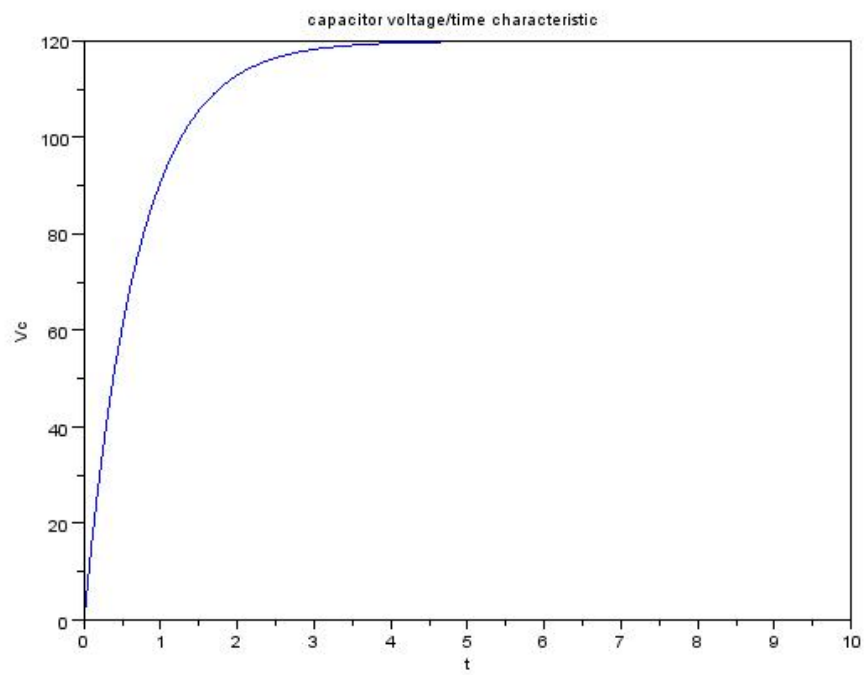


Figure 17.1: Example 1

```

10 t1 = tou
11 Vctou = V*(1-%e^(-1*t1/tou))
12 Vct = V/2
13 t = 0:0.1:10
14 Vc = V*(1-%e^(-1*t/tou));
15 plot(t,Vc)
16 xtitle("capacitor voltage/time characteristic", "t",
        "Vc")
17 t = -1*tou*log(1 - Vct/V)
18
19 printf("\ = \n\n Result \n\n")
20 printf("\n (a)the capacitor voltage at a time equal
        to one time constant = %.2f V",Vctou)
21 printf("\n (b)the time for the capacitor voltage to
        reach one half of its steady state value = %.1f
        sec",t)

```

---

### Scilab code Exa 17.02 Example 2

```

1 //Problem 17.02: A 4 F capacitor is charged to 24
  V and then discharged through a 220 kohms
  resistor. Use the initial slope and three
  point method to draw: (a) the capacitor
  voltage/time characteristic , (b) the resistor
  voltage/time characteristic and (c) the current/
  time characteristic , for the transients which
  occur. From the characteristics determine the
  value of capacitor voltage , resistor voltage and
  current one and a half seconds after discharge
  has started.
2
3 //initializing the variables:
4 C = 4E-6; // in Farads

```

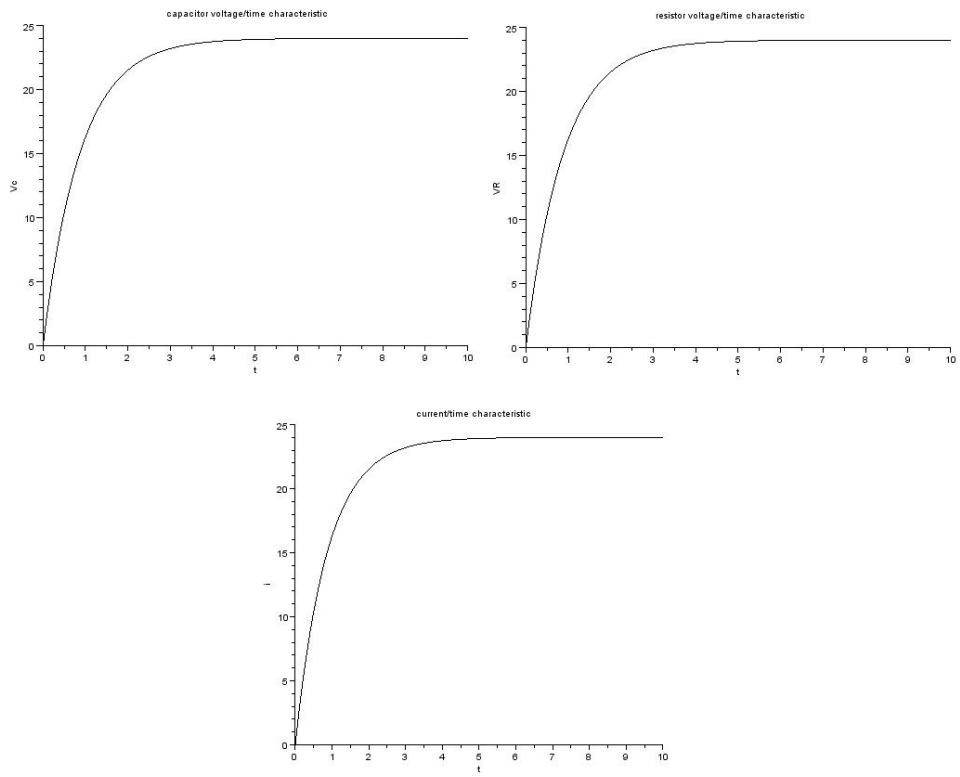


Figure 17.2: Example 2



```

5 R = 220000; // in ohms
6 V = 24; // in Volts
7 t1 = 1.5; // in secs
8
9 //calculation:
10 tou = R*C
11 t = 0:0.1:10
12 Vc = V*(1-%e^(-1*t/tou));
13 plot2d(t,Vc)
14 xtitle("capacitor voltage/time characteristic", "t",
        "Vc")
15 xset('window',1)
16 VR = V*(1-%e^(-1*t/tou));
17 plot2d(t,VR)
18 xtitle("resistor voltage/time characteristic", "t",
        "VR")
19 xset('window',2)
20 I = V/R
21 i = I*%e^(-1*t/tou)
22 plot2d(t,i)
23 xtitle("current/time characteristic", "t", "i")
24 Vct1 = V*%e^(-1*t1/tou)
25 VRt1 = V*%e^(-1*t1/tou)
26 it1 = I*%e^(-1*t1/tou)
27
28 printf("\n = \n\n Result \n\n")
29 printf("\n the value of capacitor voltage is %.2f V,
        resistor voltage is %.2f V, current is %.1E A at
        one and a half seconds after discharge has
        started.",Vct1, VRt1,it1)

```

---

### Scilab code Exa 17.03 Example 3

```

1 //Problem 17.03: A 20 F capacitor is connected in
  series with a 50 kohm resistor and the circuit is

```

connected to a 20 V, d.c. supply. Determine (a) the initial value of the current flowing, (b) the time constant of the circuit, (c) the value of the current one second after connection, (d) the value of the capacitor voltage two seconds after connection, and (e) the time after connection when the resistor voltage is 15 V

```

2
3 //initializing the variables:
4 C = 20E-6; // in Farads
5 R = 50000; // in ohms
6 V = 20; // in Volts
7 t1 = 1; // in secs
8 t2 = 2; // in secs
9 VRt = 15; // in Volts
10
11 //calculation:
12 tou = R*C
13 I = V/R
14 Vct1 = V*(1-%e^(-1*t2/tou))
15 t3 = -1*tou*log(VRt/V)
16 it1 = I*%e^(-1*t1/tou)
17
18 printf("\ = \n\n Result \n\n")
19 printf("\n (a) initial value of the current flowing
    is %.4f A",I)
20 printf("\n (b)time constant of the circuit %.0f Sec"
    ,tou)
21 printf("\n (c)the value of the current one second
    after connection , %.3f mA",(it1/1E-3))
22 printf("\n (d)the value of the capacitor voltage two
    seconds after connection %.1f V",Vct1)
23 printf("\n (e)the time after connection when the
    resistor voltage is 15 V is %.3f sec",t3)

```

---

#### Scilab code Exa 17.04 Example 4

```
1 //Problem 17.04: A circuit consists of a resistor
   connected in series with a 0.5 F capacitor and
   has a time constant of 12 ms. Determine (a) the
   value of the resistor , and (b) the capacitor
   voltage 7 ms after connecting the circuit to a 10
   V supply
2
3 //initializing the variables:
4 C = 0.5E-6; // in Farads
5 V = 10; // in Volts
6 tau = 0.012; // in secs
7 t1 = 0.007; // in secs
8
9 //calculation:
10 R = tau/C
11 Vc = V*(1-%e^(-1*t1/tau))
12
13 printf("\ = \n\n Result \n\n")
14 printf("\n (a) value of the resistor is %.0f ohm",R)
15 printf("\n (b) capacitor voltage is %.2f V",Vc)
```

---

#### Scilab code Exa 17.05 Example 5

```
1 //Problem 17.05: A capacitor is charged to 100 V and
   then discharged through a 50 kohm resistor. If
   the time constant of the circuit is 0.8 s,
   determine: (a) the value of the capacitor, (b)
   the time for the capacitor voltage to fall to 20
   V, (c) the current flowing when the capacitor has
   been discharging for 0.5 s, and (d) the voltage
   drop across the resistor when the capacitor has
   been discharging for one second.
2
```

```

3 //initializing the variables:
4 R = 50000; // in ohms
5 V = 100; // in Volts
6 Vc1 = 20; // in Volts
7 tou = 0.8; // in secs
8 t1 = 0.5; // in secs
9 t2 = 1; // in secs
10
11 //calculation:
12 C = tou/R
13 t = -1*tou*log(Vc1/V)
14 I = V/R
15 it1 = I*%e^(-1*t1/tou)
16 Vc = V*%e^(-1*t2/tou)
17
18 printf("\ = \n\n Result \n\n")
19 printf("\n (a)the value of the capacitor is %.2E F",
    C)
20 printf("\n (b)the time for the capacitor voltage to
    fall to 20 V is %.2f sec",t)
21 printf("\n (c)the current flowing when the capacitor
    has been discharging for 0.5 s is %.5f A",it1)
22 printf("\n (d)the voltage drop across the resistor
    when the capacitor has been discharging for one
    second is %.1f V",Vc)

```

---

#### Scilab code Exa 17.06 Example 6

```

1 //Problem 17.06: A 0.1 F capacitor is charged to
    200 V before being connected across a 4 kohm
    resistor. Determine (a) the initial discharge
    current, (b) the time constant of the circuit,
    and (c) the minimum time required for the voltage
    across the capacitor to fall to less than 2 V
2

```

```

3 //initializing the variables:
4 C = 0.1E-6; // in Farads
5 R = 4000; // in ohms
6 V = 200; // in Volts
7 Vc1 = 2; // in Volts
8
9 //calculation:
10 tou = R*C
11 I = V/R
12 t = -1*tou*log(Vc1/V)
13
14 printf("\ = \n\n Result \n\n")
15 printf("\n (a) initial discharge current is %.2f A",
    I)
16 printf("\n (b)Time constant tou is %.4f sec",tou)
17 printf("\n (c)minimum time required for the voltage
    across the capacitor to fall to less than 2 V is
    %.3f sec",t)

```

---

#### Scilab code Exa 17.07 Example 7

```

1 //Problem 17.07: A relay has an inductance of 100 mH
    and a resistance of 20 ohm. It is connected to a
    60 V, d.c. supply. Use the initial slope and
    three point method to draw the current/time
    characteristic and hence determine the value of
    current flowing at a time equal to two time
    constants and the time for the current to grow to
    1.5 A.
2
3 //initializing the variables:
4 L = 0.1; // in Henry
5 R = 20; // in ohms

```

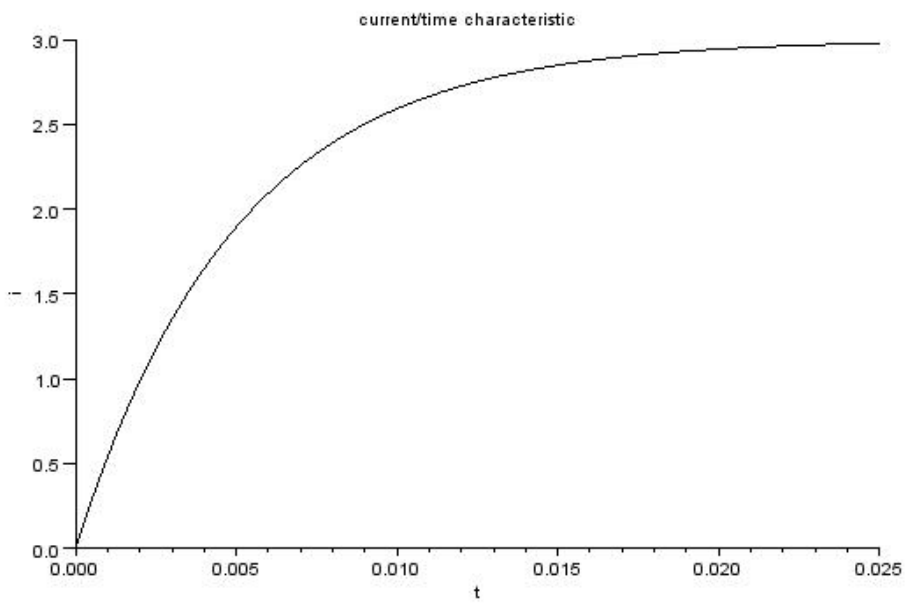


Figure 17.3: Example 7

```

6 V = 60; // in Volts
7 i2 = 1.5; // in Amperes
8
9 //calculation:
10 tou = L/R
11 t1 = 2*tou
12 t = 0:0.0001:0.025
13 I = V/R
14 i = I*(1 - %e^(-1*t/tou))
15 plot2d(t,i)
16 xtitle("current/time characteristic", "t", "i")
17 i1 = I*(1 - %e^(-1*t1/tou))
18 t2 = -1*tou*log(1 - i2/I)
19
20 printf("\ = \n\n Result \n\n")
21 printf("\n (a) the value of current flowing at a
    time equal to two time constants is %.3f A",i1)
22 printf("\n (b)the time for the current to grow to
    1.5 A is %.7f sec",t2)

```

---

### Scilab code Exa 17.08 Example 8

```

1 //Problem 17.08: A coil of inductance 0.04 H and
    resistance 10 ohm is connected to a 120 V, d.c.
    supply. Determine (a) the final value of current,
    (b) the time constant of the circuit, (c) the
    value of current after a time equal to the time
    constant from the instant the supply voltage is
    connected, (d) the expected time for the current
    to rise to within 1% of its final value.
2
3 //initializing the variables:
4 L = 0.04; // in Henry
5 R = 10; // in ohms
6 V = 120; // in Volts

```

```

7 i2 = 0.01*I; // in amperes
8
9 //calculation:
10 tou = L/R
11 t1 = tou
12 I = V/R
13 i1 = I*(1 - %e^(-1*t1/tou))
14 i2 = 0.01*I
15 t2 = -1*tou*log(i2/I)
16
17 printf("\n = \n\n Result \n\n")
18 printf("\n (a) the final value of current is %.0f A"
, I)
19 printf("\n (b)time constant of the circuit is %.3f
sec", tou)
20 printf("\n (c) value of current after a time equal
to the time constant is %.2f A", i1)
21 printf("\n (d)the expected time for the current to
rise to within 0.01 times of its final value is %
.2f sec", t2)

```

---

#### Scilab code Exa 17.09 Example 9

```

1 //Problem 17.09: The winding of an electromagnet has
an inductance of 3 H and a resistance of 15 ohm.
When it is connected to a 120 V, d.c. supply,
calculate: (a) the steady state value of current
flowing in the winding, (b) the time constant of
the circuit, (c) the value of the induced e.m.f.
after 0.1 s, (d) the time for the current to rise
to 85% of its final value, and (e) the value of
the current after 0.3 s.
2
3 //initializing the variables:
4 L = 3; // in Henry

```



```

5 R = 15; // in ohms
6 V = 120; // in Volts
7 t1 = 0.1; // in secs
8 t3 = 0.3; // in secs
9
10 //calculation:
11 tau = L/R
12 I = V/R
13 i2 = 0.85*I
14 VL = V*%e^(-1*t1/tau)
15 t2 = -1*tau*log(1 - (i2/I))
16 i3 = I*(1 - %e^(-1*t3/tau))
17
18 printf("\n = \n\n Result \n\n")
19 printf("\n (a) steady state value of current is %.0f
    A",I)
20 printf("\n (b)time constant of the circuit is %.3f
    sec",tau)
21 printf("\n (c)value of the induced e.m.f. after 0.1
    s is %.2f V",VL)
22 printf("\n (d) time for the current to rise to 0.85
    times of its final values is %.3f sec",t2)
23 printf("\n (e)value of the current after 0.3 s is %
    .3f A",i3)

```

---

### Scilab code Exa 17.10 Example 10

```

1 //Problem 17.10: The field winding of a 110 V, d.c.
  motor has a resistance of 15 ohms and a time
  constant of 2 s. Determine the inductance and use
  the tangential method to draw the current/time
  characteristic when the supply is removed and
  replaced by a shorting link. From the

```

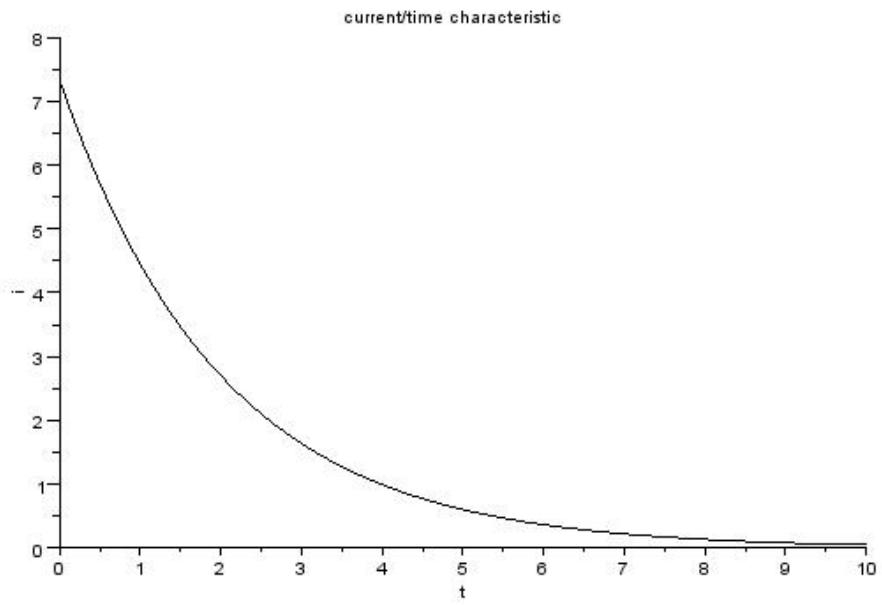


Figure 17.4: Example 10

```

        characteristic determine (a) the current flowing
        in the winding 3 s after being shorted-out and (b
        ) the time for the current to decay to 5 A.
2
3 //initializing the variables:
4 R = 15; // in ohms
5 V = 110; // in Volts
6 tau = 2; // in secs
7 t1 = 3; // in secs
8 i2 =5; // in amperes
9
10 //calculation:
11 L = tau*R
12 t = 0:0.1:10
13 I = V/R
14 i = I*(%e^(-1*t/tau))
15 plot2d(t,i)
16 xtitle("current/time characteristic", "t", "i")
17 i1 = I*(%e^(-1*t1/tau))
18 t2 = -1*tau*log((i2/I))
19
20 printf("\ = \n\n Result \n\n")
21 printf("\n inductance is %.0f H",L)
22 printf("\n (a)the current flowing in the winding 3 s
        after being shorted-out is %.2f A",i1)
23 printf("\n (b)the time for the current to decay to 5
        A is %.3f sec",t2)

```

---

### Scilab code Exa 17.11 Example 11

```

1 //Problem 17.11 A coil having an inductance of 6 H
    and a resistance of R is connected in series
    with a resistor of 10 to a 120 V, d.c. supply.
    The time constant of the circuit is 300 ms. When
    steady-state conditions have been reached, the

```

supply is replaced instantaneously by a short-circuit. Determine: (a) the resistance of the coil, (b) the current flowing in the circuit one second after the shorting link has been placed in the circuit, and (c) the time taken for the current to fall to 10% of its initial value.

```

2
3 //initializing the variables:
4 L = 6; // in Henry
5 r = 10; // in ohms
6 V = 120; // in Volts
7 tou = 0.3; // in secs
8 t1 = 1; // in secs
9
10 //calculation:
11 R = (L/tou) - r
12 Rt = R + r
13 I = V/Rt
14 i2 = 0.1*I
15 i1 = I*(%e^(-1*t1/tou))
16 t2 = -1*tou*log((i2/I))
17
18 printf("\ = \n\n Result \n\n")
19 printf("\n (a) resistance of the coil is %.0f ohm",R
    )
20 printf("\n (b) current flowing in the circuit one
    second after the shorting link has been placed is
    %.3f A",i1)
21 printf("\n (c)the time for the current to decay to
    0.1 times of initial value is %.3f sec",t2)

```

---

### Scilab code Exa 17.12 Example 12

```

1 //Problem 17.12: An inductor has a negligible
    resistance and an inductance of 200 mH and is

```

connected in series with a 1 kohm resistor to a 24 V, d.c. supply. Determine the time constant of the circuit and the steady-state value of the current flowing in the circuit. Find (a) the current flowing in the circuit at a time equal to one time constant, (b) the voltage drop across the inductor at a time equal to two time constants and (c) the voltage drop across the resistor after a time equal to three time constants.

```

2
3 //initializing the variables:
4 L = 0.2; // in Henry
5 R = 1000; // in ohms
6 V = 24; // in Volts
7
8 //calculation:
9 tou = L/R
10 t1 = 1*tou // in secs
11 t2 = 2*tou // in secs
12 t3 = 3*tou // in secs
13 I = V/R
14 i1 = I*(1 - %e^(-1*t1/tou))
15 VL = V*(%e^(-1*t2/tou))
16 VR = V*(1 - %e^(-1*t3/tou))
17
18 printf("\ = \n\n Result \n\n")
19 printf("\n time constant of the circuit is %.4f sec ,
    and the steady-state value of the current is %
    .3f A",tou, I)
20 printf("\n (a) urrent flowing in the circuit at a
    time equal to one time constant is %.5f A",i1)
21 printf("\n (b) voltage drop across the inductor at a
    time equal to two time constants is %.3f V",VL)
22 printf("\n (c)the voltage drop across the resistor
    after a time equal to three time constants is %.2
    f V",VR)

```

---

# Chapter 18

## Operational amplifiers

Scilab code Exa 18.01 Example 1

```
1 //Problem 18.01: A differential amplifier has an
   open-loop voltage gain of 120. The input signals
   are 2.45 V and 2.35 V. Calculate the output
   voltage of the amplifier
2
3 //initializing the variables:
4 Vi2 = 2.45; // in Volts
5 Vi1 = 2.35; // in Volts
6 A0 = 120; // open-loop voltage gain
7
8 //calculation:
9 Vo = A0*(Vi2 - Vi1)
10
11 printf("\n\n Result \n\n")
12 printf("\n the output voltage is %.0f V",Vo)
```

---

Scilab code Exa 18.02 Example 2

```

1 //Problem 18.02: Determine the common-mode gain of
   an op amp that has a differential voltage gain of
   150E3 and a CMRR of 90 dB.
2
3 //initializing the variables:
4 Vg = 150E3; // differential voltage gain
5 CMRR = 90; // in dB
6
7 //calculation:
8 CMG = Vg/(10^(CMRR/20))
9
10 printf("\n\n Result \n\n")
11 printf("\n common-mode gain is %.2f",CMG)

```

---

### Scilab code Exa 18.03 Example 3

```

1 //Problem 18.03: A differential amplifier has an
   open-loop voltage gain of 120 and a common input
   signal of 3.0 V to both terminals. An output
   signal of 24 mV results. Calculate the common-
   mode gain and the CMRR.
2
3 //initializing the variables:
4 Vg = 120; // differential voltage gain
5 Vi = 3; // in Volts
6 Vo = 0.024; // in Volts
7
8 //calculation:
9 CMG = Vo/Vi
10 CMRR = 20*log10(Vg/CMG)
11
12 printf("\n\n Result \n\n")
13 printf("\n common-mode gain is %.3f and CMRR is %.2f
   dB",CMG, CMRR)

```

---

#### Scilab code Exa 18.04 Example 4

```
1 //Problem 18.04: In the inverting amplifier of
   Figure 18.5,  $R_i = 1$  kohm and  $R_f = 2$  kohm.
   Determine the output voltage when the input
   voltage is: (a)+0.4 V (b) -1.2 V
2
3 //initializing the variables:
4 Rf = 2000; // in ohms
5 Ri = 1000; // in ohms
6 Vi1 = 0.4; // in Volts
7 Vi2 = -1.2; // in Volts
8
9 //calculation:
10 Vo1 = -1*Rf*Vi1/Ri
11 Vo2 = -1*Rf*Vi2/Ri
12
13 printf("\n\n Result \n\n")
14 printf("\n output voltage when the input voltage is
   0.4V is %.1f V and when the input voltage is -1.2
   V is %.1f V",Vo1, Vo2)
```

---

#### Scilab code Exa 18.05 Example 5

```
1 //Problem 18.05: The op amp shown in Figure 18.6 has
   an input bias current of 100 nA at 20 C .
   Calculate (a) the voltage gain , and (b) the
   output offset voltage due to the input bias
   current. (c) How can the effect of input bias
   current be minimised?
2
3 //initializing the variables:
```



```

4 Ii = 100E-9; // in Amperes
5 T = 20; // in C
6 Rf = 1E6; // in ohms
7 Ri = 10000; // in ohms
8
9 //calculation:
10 A = -1*Rf/Ri
11 Vos = Ii*Ri*Rf/(Ri+Rf)
12
13 printf("\n\n Result \n\n")
14 printf("\n (a)the voltage gain is %.0f",A)
15 printf("\n (b)output offset voltage is %.5f V",Vos)

```

---

#### Scilab code Exa 18.06 Example 6

```

1 //Problem 18.06: Design an inverting amplifier to
   have a voltage gain of 40 dB, a closed-loop
   bandwidth of 5 kHz and an input resistance of 10
   kohm.
2
3 //initializing the variables:
4 Vg = 40; // in dB
5 bf = 5000; // in Hz
6 Ri = 10000; // in ohms
7
8 //calculation:
9 A = 10^(Vg/20)
10 Rf = A*Ri
11 f = A*bf
12
13 printf("\n\n Result \n\n")
14 printf("\n the voltage gain is %.0f, Rf = %.0f ohm
   and frequency = %.0f Hz",A, Rf, f)

```

---

### Scilab code Exa 18.07 Example 7

```
1 //Problem 18.07: For the op amp shown in Figure
   18.8, R1 = 4.7 kohm and R2 = 10 kohm. If the
   input voltage is - 0.4 V, determine (a) the
   voltage gain (b) the output voltage
2
3 //initializing the variables:
4 Vi = -0.4; // in Volts
5 R1 = 4700; // in ohms
6 R2 = 10000; // in ohms
7
8 //calculation:
9 A = 1 + (R2/R1)
10 Vo = A*Vi
11
12 printf("\n\n Result \n\n")
13 printf("\n(a) the voltage gain is %.2f",A)
14 printf("\n(b) output voltage is %.2f V",Vo)
```

---

### Scilab code Exa 18.08 Example 8

```
1 //Problem 18.08: For the summing op amp shown in
   Figure 18.11, determine the output voltage, Vo
2
3 //initializing the variables:
4 V1 = 0.5; // in Volts
5 V2 = 0.8; // in Volts
6 V3 = 1.2; // in Volts
7 R1 = 10000; // in ohms
8 R2 = 20000; // in ohms
9 R3 = 30000; // in ohms
```

```

10 Rf = 50000; // in ohms
11
12 //calculation:
13 Vo = -1*Rf*(V1/R1 + V2/R2 + V3/R3)
14
15 printf("\n\n Result \n\n")
16 printf("\n output voltage is %.1f V",Vo)

```

---

### Scilab code Exa 18.10 Example 10

```

1 //Problem 18.10: A steady voltage of  $-0.75V$  is
  applied to an op amp integrator having component
  values of  $R = 200$  kohm and  $C = 2.5$  F. Assuming
  that the initial capacitor charge is zero,
  determine the value of the output voltage 100 ms
  after application of the input.
2
3 //initializing the variables:
4 Vs = -0.75; // in Volts
5 R = 200000; // in ohms
6 C = 2.5E-6; // in Farads
7 t = 0.1; // in secs
8
9 //calculation:
10 Vo = (-1/(C*R))*integrate(' -0.75 ', 't', 0, 0.1)
11
12 printf("\n\n Result \n\n")
13 printf("\n output voltage is %.2f V",Vo)

```

---

### Scilab code Exa 18.11 Example 11

```

1 //Problem 18.11: In the differential amplifier shown
   in Figure 18.16, R1 = 10 kohm, R2 = 10 kohm, R3
   = 100 kohm and Rf = 100 kohm. Determine the
   output voltage Vo if:
2 //(a) V1 = 5 mV and V2 = 0
3 //(b) V1 = 0 and V2 = 5mV
4 //(c) V1 = 50 mV and V2 = 25mV
5 //(d) V1 = 25 mV and V2 = 50mV
6
7 //initializing the variables:
8 V1a = 0.005; // in Volts
9 V2a = 0; // in Volts
10 V1b = 0; // in Volts
11 V2b = 0.005; // in Volts
12 V1c = 0.05; // in Volts
13 V2c = 0.025; // in Volts
14 V1d = 0.025; // in Volts
15 V2d = 0.05; // in Volts
16 R1 = 10000; // in ohms
17 R2 = 10000; // in ohms
18 R3 = 100000; // in ohms
19 Rf = 100000; // in ohms
20
21 //calculation:
22 Vo1 = -1*Rf*V1a/R1
23 Vo2 = (R3/(R2+R3))*(1 + (Rf/R1))*V2b
24 Vo3 = -1*Rf*(V1c-V2c)/R1
25 Vo4 = (R3/(R2+R3))*(1 + (Rf/R1))*(V2d-V1d)
26
27 printf("\n\n Result \n\n")
28 printf("\n (a)output voltage is %.3f V",Vo1)
29 printf("\n (b)output voltage is %.3f V",Vo2)
30 printf("\n (c)output voltage is %.3f V",Vo3)
31 printf("\n (d)output voltage is %.3f V",Vo4)

```

---

# Chapter 19

## Three phase systems

Scilab code Exa 19.01 Example 1

```
1 //Problem 19.01: Three loads , each of resistance 30
  ohm
2 , are connected in star to a 415 V, 3-phase supply.
  Determine (a) the system phase voltage, (b) the
  phase current and (c) the line current.
3
4 //initializing the variables:
5 V1 = 415; // in Volts
6 Rp = 30; // in ohms
7
8 //calculation:
9 Vp = V1/(3^0.5)
10 Ip = Vp/Rp
11 Il = Ip
12
13 printf("\n\n Result \n\n")
14 printf("\n (a)the system phase voltage is %.1f V",Vp
  )
15 printf("\n (b)phase current is %.0f A",Ip)
16 printf("\n (c)line current is %.0f A",Il)
```

---

### Scilab code Exa 19.02 Example 2

```
1 //Problem 19.02: A star-connected load consists of
   three identical coils each of resistance 30
2 ohm and inductance 127.3 mH. If the line current is
   5.08 A, calculate the line voltage if the supply
   frequency is 50 Hz.
3
4 //initializing the variables:
5 R = 30; // in ohms
6 L = 0.1273; // in Henry
7 Ip = 5.08; // in Amperes
8 f = 50; // in Hz
9
10 //calculation:
11 XL = 2*%pi*f*L
12 Zp = (R*R + XL*XL)^0.5
13 Il = Ip
14 Vp = Ip*Zp
15 Vl = Vp*(3^0.5)
16
17 printf("\n\n Result \n\n")
18 printf("\n (a)line voltage is %.0f V",Vl)
```

---

### Scilab code Exa 19.04 Example 4

```
1 //Problem 19.04: A 415 V, 3-phase, 4 wire, star-
   connected system supplies three resistive loads
   as shown in Figure 19.7. Determine (a) the
   current in each line and (b) the current in the
   neutral conductor.
2
```

```

3 //initializing the variables:
4 V = 415; // in Volts
5 PR = 24000; // in Watt
6 Py = 18000; // in Watt
7 Pb = 12000; // in Watt
8 VR = 240; // in Volts
9 Vy = 240; // in Volts
10 Vb = 240; // in Volts
11
12 //calculation:
13 //For a star-connected system VL = Vp*(3^0.5)
14 Vp = Vl/(3^0.5)
15 phir = 90*%pi/180
16 phiy = 330*%pi/180
17 phib = 210*%pi/180
18 // I = P/V for a resistive load
19 IR = PR/VR
20 Iy = Py/Vy
21 Ib = Pb/Vb
22 Inh = IR*cos(phir) + Ib*cos(phib) + Iy*cos(phiy)
23 Inv = IR*sin(phir) + Ib*sin(phib) + Iy*sin(phiy)
24 In = (Inh^2 + Inv^2)^0.5
25
26 printf("\n\n Result \n\n")
27 printf("\n (a) cuurnt in R line is %.0f A, cuurnt in
    Y line is %.0f A and cuurnt in B line is %.0f A",
    IR, Iy, Ib)
28 printf("\n (b) cuurnt in neutral line is %.1f A", In)

```

---

#### Scilab code Exa 19.05 Example 5

```

1 //Problem 19.05: Three identical coils each of
    resistance 30 ohm
2 and inductance 127.3 mH are connected in delta to a
    440 V, 50 Hz, 3-phase supply. Determine (a) the

```

```

        phase current, and (b) the line current.
3
4 //initializing the variables:
5 R = 30; // in ohms
6 L = 0.1273; // in Henry
7 VL = 440; // in Volts
8 f = 50; // in Hz
9
10 //calculation:
11 XL = 2*%pi*f*L
12 Zp = (R*R + XL*XL)^0.5
13 Vp = VL
14 //Phase current
15 Ip = Vp/Zp
16 //For a delta connection ,
17 IL = Ip*(3^0.5)
18
19 printf("\n\n Result \n\n")
20 printf("\n (a)the phase current %.1f A",Ip)
21 printf("\n (b)line current %.2f A",IL)

```

---

#### Scilab code Exa 19.06 Example 6

```

1 //Problem 19.06: Three identical capacitors are
   connected in delta to a 415 V, 50 Hz, 3-phase
   supply. If the line current is 15 A, determine
   the capacitance of each of the capacitors.
2
3 //initializing the variables:
4 IL = 15; // in Amperes
5 VL = 415; // in Volts
6 f = 50; // in Hz
7
8 //calculation:
9 //For a delta connection

```



```

10 Ip = IL/(3^0.5)    //phase current
11 Vp = VL
12 //Capacitive reactance per phase
13 Xc = Vp/Ip
14 C = 1/(2*%pi*f*Xc)
15
16 printf("\n\n Result \n\n")
17 printf("\n capacitance is %.3E F",C)

```

---

#### Scilab code Exa 19.07 Example 7

```

1 //Problem 19.07: Three coils each having resistance
  3
2 ohm and inductive reactance 4 ohm
3 are connected (i) in star and (ii) in delta to a
  415 V, 3-phase supply. Calculate for each
  connection (a) the line and phase voltages and (
  b) the phase and line currents.
4
5 //initializing the variables:
6 R = 3; // in ohms
7 XL = 4; // in ohms
8 VL = 415; // in Volts
9
10 //calculation:
11 //For a star connection:
12 //IL = Ip
13 //VL = Vp*(3^0.5)
14 VLs = VL
15 Vps = VLs/(3^0.5)
16 //Impedance per phase,
17 Zp = (R*R + XL*XL)^0.5
18 Ips = Vps/Zp
19 ILs = Ips
20 //For a delta connection:

```

```

21 //VL = Vp
22 //IL = Ip*(3^0.5)
23 VLd = VL
24 Vpd = VLd
25 Ipd = Vpd/Zp
26 ILd = Ipd*(3^0.5)
27
28 printf("\n\n Result \n\n")
29 printf("\n (a)the line voltage for star connection
    is %.0f V and the phase voltage for star
    connection is %.0f V and the line voltage for
    delta connection is %.0f V and the phase voltage
    for delta connection is %.0f V", VLs, Vps, VLd, Vpd)
30 printf("\n (b)the line current for star connection
    is %.0f A and the phase current for star
    connection is %.0f A and the line current for
    delta connection is %.0f A and the phase current
    for delta connection is %.0f A", ILs, Ips, ILd, Ipd)

```

---

### Scilab code Exa 19.08 Example 8

```

1 //Problem 19.08: Three 12
2 ohms resistors are connected in star to a 415 V, 3-
    phase supply. Determine the total power
    dissipated by the resistors.
3
4 //initializing the variables:
5 Rp = 12; // in ohms
6 VL = 415; // in Volts
7
8 //calculation:
9 //Power dissipated , P = VL*IL*(3^0.5)*cos(phi) or
    P = 3*Ip*Ip*Rp)
10 Vp = VL/(3^0.5) // since the resistors are star-
    connected

```

```

11 //Phase current , Ip
12 Zp = Rp
13 Ip = Vp/Zp
14 //For a star connection
15 IL = Ip
16 // For a purely resistive load, the power factor cos
    (phi) = 1
17 pf = 1
18 P = VL*IL*(3^0.5)*pf
19
20 printf("\n\n Result \n\n")
21 printf("\n (a)total power dissipated by the
    resistors is %.0f W",P)

```

---

#### Scilab code Exa 19.09 Example 9

```

1 //Problem 19.09: The input power to a 3-phase a.c.
    motor is measured as 5 kW. If the voltage and
    current to the motor are 400 V and 8.6 A
    respectively , determine the power factor of the
    system.
2
3 //initializing the variables:
4 P = 5000; // in Watts
5 IL = 8.6; // in amperes
6 VL = 400; // in Volts
7
8 //calculation:
9 //Power dissipated , P = VL*IL*(3^0.5)*cos(phi) or
    P = 3*Ip*Ip*Rp)
10 pf = P/(VL*IL*(3^0.5))
11
12 printf("\n\n Result \n\n")
13 printf("\n power factor is %.3f",pf)

```

---

Scilab code Exa 19.10 Example 10

```
1 //Problem 19.10: Three identical coils , each of
   resistance 10 ohm
2 and inductance 42 mH are connected (a) in star and
   (b) in delta to a 415 V, 50 Hz, 3-phase supply.
   Determine the total power dissipated in each
   case.
3
4 //initializing the variables:
5 R = 10; // in ohms
6 L = 0.042; // in Henry
7 VL = 415; // in Volts
8 f = 50; // in Hz
9
10 //calculation:
11 //For a star connection:
12 //IL = Ip
13 //VL = Vp*(3^0.5)
14 XL = 2*%pi*f*L
15 Zp = (R*R + XL*XL)^0.5
16 VLs = VL
17 Vps = VLs/(3^0.5)
18 //Impedance per phase ,
19 Ips = Vps/Zp
20 ILs = Ips
21 //Power dissipated , P = VL*IL*(3^0.5)*cos(phi) or
   P = 3*Ip*Ip*Rp)
22 pfs = R/Zp
23 Ps = VLs*ILs*(3^0.5)*pfs
24
25 //For a delta connection:
26 //VL = Vp
27 //IL = Ip*(3^0.5)
```

```

28 VLd = VL
29 Vpd = VLd
30 Ipd = Vpd/Zp
31 ILd = Ipd*(3^0.5)
32 //Power dissipated , P = VL*IL*(3^0.5)*cos(phi) or
    P = 3*Ip*Ip*Rp)
33 pfd = R/Zp
34 Pd = VLd*ILd*(3^0.5)*pfd
35
36 printf("\n\n Result \n\n")
37 printf("\n total power dissipated in star is %.1E W
    and in delta is %.2E W",Ps, Pd)

```

---

#### Scilab code Exa 19.11 Example 11

```

1 //Problem 19.11: A 415 V, 3-phase a.c. motor has a
    power output of 12.75 kW and operates at a power
    factor of 0.77 lagging and with an efficiency of
    85%. If the motor is delta-connected, determine (
    a) the power input, (b) the line current and (c)
    the phase current.
2
3 //initializing the variables:
4 Po = 12750; // in Watts
5 pf = 0.77; // power factor
6 eff = 0.85;
7 VL = 415; // in Volts
8
9 //calculation:
10 //eff = power_out/power_in
11 Pi = Po/eff
12 //Power P = VL*IL*(3^0.5)*cos(phi) or P = 3*Ip*Ip*
    Rp)
13 IL = Pi/(VL*(3^0.5)*pf) // line current
14

```

```

15 //For a delta connection:
16 //IL = Ip*(3^0.5)
17 Ip = IL/(3^0.5)
18
19 printf("\n\n Result \n\n")
20 printf("\n (a)power input is %.2E W",Pi)
21 printf("\n (b)line current is %.2f A",IL)
22 printf("\n (c)phase current is %.2f A",Ip)

```

---

### Scilab code Exa 19.13 Example 13

```

1 //Problem 19.13: A 400 V, 3-phase star connected
   alternator supplies a delta-connected load, each
   phase of which has a resistance of 30 ohm
2 and inductive reactance 40
3 ohm. Calculate (a) the current supplied by the
   alternator and (b) the output power and the kVA
   of the alternator, neglecting losses in the line
   between the alternator and load.
4
5 //initializing the variables:
6 R = 30; // in ohms
7 XL = 40; // in ohms
8 VL = 400; // in Volts
9
10 //calculation:
11 Zp = (R*R + XL*XL)^0.5
12 //a delta-connected load
13 Vp = VL
14 //Phase current
15 Ip = Vp/Zp
16 IL = Ip*(3^0.5)
17 //Alternator output power is equal to the power
   dissipated by the load.
18 //Power P = VL*IL*(3^0.5)*cos(phi) or P = 3*Ip*Ip*

```

```

    Rp)
19 pf = R/Zp
20 P = VL*IL*(3^0.5)*pf
21 //Alternator output kVA,
22 S = VL*IL*(3^0.5)
23
24 printf("\n\n Result \n\n")
25 printf("\n (a)the current supplied by the alternator
    is %.2f A",IL)
26 printf("\n (b)output power is %.2E W and kVA of the
    alternator is %.2E kVA",P, S)

```

---

#### Scilab code Exa 19.14 Example 14

```

1 //Problem 19.14: Each phase of a delta-connected
  load comprises a resistance of 30 ohm
2 and an 80 F capacitor in series. The load is
  connected to a 400 V, 50 Hz, 3-phase supply.
  Calculate (a) the phase current, (b) the line
  current, (c) the total power dissipated and (d)
  the kVA rating of the load. Draw the complete
  phasor diagram for the load.
3
4 //initializing the variables:
5 R = 30; // in ohms
6 C = 80E-6; // in Farads
7 f = 50; // in Hz
8 VL = 400; // in Volts
9
10 //calculation:
11 //Capacitive reactance
12 Xc = 1/(2*pi*f*C)
13 Zp = (R*R + Xc*Xc)^0.5
14 pf = R/Zp
15 //a delta-connected load

```

```

16 Vp = VL
17 //Phase current
18 Ip = Vp/Zp
19 IL = Ip*(3^0.5)
20 //Power P = VL*IL*(3^0.5)*cos(phi) or P = 3*Ip*Ip*
    Rp)
21 P = VL*IL*(3^0.5)*pf
22 //Alternator output kVA,
23 S = VL*IL*(3^0.5)
24
25 printf("\n\n Result \n\n")
26 printf("\n (a)the phase current is %.3f A",Ip)
27 printf("\n (b)the line current is %.2f A",IL)
28 printf("\n (c) power is %.2E W and \n(d)kVA of the
    alternator is %.2E kVA",P, S)

```

---

#### Scilab code Exa 19.15 Example 15

```

1 //Problem 19.15: Two wattmeters are connected to
    measure the input power to a balanced 3-phase
    load by the two-wattmeter method. If the
    instrument readings are 8 kW and 4 kW, determine
    (a) the total power input and (b) the load power
    factor.
2
3 //initializing the variables:
4 Pi1 = 8000; // in Watts
5 Pi2 = 4000; // in Watts
6
7 //calculation:
8 //Total input power
9 Pi = Pi1 + Pi2
10 phi = atan((Pi1 - Pi2)*(3^0.5)/(Pi1 + Pi2))
11 //Power factor
12 pf = cos(phi)

```



```
13
14 printf("\n\n Result \n\n")
15 printf("\n (a)power input is %.1E W",Pi)
16 printf("\n (b)power factor is %.3f",pf)
```

---

### Scilab code Exa 19.16 Example 16

```
1 //Problem 19.16: Two wattmeters connected to a 3-
   phase motor indicate the total power input to be
   12 kW. The power factor is 0.6. Determine the
   readings of each wattmeter.
2
3 //initializing the variables:
4 Pi = 12000; // in Watts
5 pf = 0.6; // power factor
6
7 //calculation:
8 //If the two wattmeters indicate Pi1 and Pi2
   respectively
9 // Pit = Pi1 + Pi2
10 Pit = Pi
11 // Pid = Pi1 - Pi2
12 //power factor = 0.6 = cos(phi)
13 phi = acos(pf)
14 Pid = Pit*tan(phi)/(3^0.5)
15 //Hence wattmeter 1 reads
16 Pi1 = (Pid + Pit)/2
17 //wattmeter 2 reads
18 Pi2 = Pit - Pi1
19
20 printf("\n\n Result \n\n")
21 printf("\n reading in each wattameter are %.2E W and
   %.2E W",Pi1,Pi2)
```

---

### Scilab code Exa 19.17 Example 17

```
1 //Problem 19.17: Two wattmeters indicate 10 kW and 3
   kW respectively when connected to measure the
   input power to a 3-phase balanced load, the
   reverse switch being operated on the meter
   indicating the 3 kW reading. Determine (a) the
   input power and (b) the load power factor.
2
3 //initializing the variables:
4 Pi1 = 10000; // in Watts
5 Pi2 = -3000; // in Watts
6
7 //calculation:
8 //Total input power
9 Pi = Pi1 + Pi2
10 phi = atan((Pi1 - Pi2)*(3^0.5)/(Pi1 + Pi2))
11 //Power factor
12 pf = cos(phi)
13
14 printf("\n\n Result \n\n")
15 printf("\n (a)power input is %.2E W",Pi)
16 printf("\n (b)power factor is %.3f",pf)
```

---

### Scilab code Exa 19.18 Example 18

```
1 //Problem 19.18: Three similar coils , each having a
   resistance of 8 ohm and an inductive reactance
   of 8 ohm are connected (a) in star and (b) in
   delta , across a 415 V, 3-phase supply. Calculate
   for each connection the readings on each of two
```

```

    wattmeters connected to measure the power by the
    two-wattmeter method.
2
3 //initializing the variables:
4 R = 8; // in ohms
5 XL = 8; // in ohms
6 VL = 415; // in Volts
7
8 //calculation:
9 //For a star connection:
10 //IL = Ip
11 //VL = Vp*(3^0.5)
12 VLs = VL
13 Vps = VLs/(3^0.5)
14 //Impedance per phase,
15 Zp = (R*R + XL*XL)^0.5
16 Ips = Vps/Zp
17 ILs = Ips
18 //Power dissipated , P = VL*IL*(3^0.5)*cos(phi) or
    P = 3*Ip*Ip*Rp)
19 pf = R/Zp
20 Ps = VLs*ILs*(3^0.5)*pf
21 //If wattmeter readings are P1 and P2 then P1 + P2 =
    Pst
22 Pst = Ps
23 // Pid = Pi1 - Pi2
24 phi = acos(pf)
25 Psd = Pst*tan(phi)/(3^0.5)
26 //Hence wattmeter 1 reads
27 Ps1 = (Psd + Pst)/2
28 //wattmeter 2 reads
29 Ps2 = Pst - Ps1
30
31 //For a delta connection:
32 //VL = Vp
33 //IL = Ip*(3^0.5)
34 VLd = VL
35 Vpd = VLd

```

```

36 Ipd = Vpd/Zp
37 ILd = Ipd*(3^0.5)
38 //Power dissipated , P = VL*IL*(3^0.5)*cos(phi) or
    P = 3*Ip*Ip*Rp)
39 Pd = VLd*ILd*(3^0.5)*pf
40 //If wattmeter readings are P1 and P2 then P1 + P2 =
    Pdt
41 Pdt = Pd
42 // Pid = Pi1 - Pi2
43 Pdd = Pdt*tan(phi)/(3^0.5)
44 //Hence wattmeter 1 reads
45 Pd1 = (Pdd + Pdt)/2
46 //wattmeter 2 reads
47 Pd2 = Pdt - Pd1
48
49 printf("\n\n Result \n\n")
50 printf("\n (a)When the coils are star-connected the
    wattmeter readings are %.3E W and %.3E W",Ps1,Ps2
    )
51 printf("\n (b)When the coils are delta-connected the
    wattmeter readings are are %.3E W and %.3E W",
    Pd1,Pd2)

```

---

# Chapter 20

## Transformers

Scilab code Exa 20.01 Example 1

```
1 //Problem 20.01: A transformer has 500 primary turns
   and 3000 secondary turns. If the primary voltage
   is 240 V, determine the secondary voltage,
   assuming an ideal transformer.
2
3 //initializing the variables:
4 N1 = 500; // primary turns
5 N2 = 3000; // secondary turns
6 V1 = 240; // in Volts
7
8 //calculation:
9 //For an ideal transformer, voltage ratio = turns
   ratio
10 V2 = V1*N2/N1
11
12 printf("\n\n Result \n\n")
13 printf("\n secondary voltage %.2E V",V2)
```

---

Scilab code Exa 20.02 Example 2

```

1 //Problem 20.02: An ideal transformer with a turns
  ratio of 2:7 is fed from a 240 V supply.
  Determine its output voltage.
2
3 //initializing the variables:
4 tr = 2/7; // turns ratio
5 V1 = 240; // in Volts
6
7 //calculation:
8 //A turns ratio of 2:7 means that the transformer
  has 2 turns on the primary for every 7 turns on
  the secondary
9 V2 = V1/tr
10
11 printf("\n\n Result \n\n")
12 printf("\n output voltage %.0f V",V2)

```

---

### Scilab code Exa 20.03 Example 3

```

1 //Problem 20.03: An ideal transformer has a turns
  ratio of 8:1 and the primary current is 3 A when
  it is supplied at 240 V. Calculate the secondary
  voltage and current.
2
3 //initializing the variables:
4 tr = 8/1; // turns ratio
5 I1 = 3; // in Amperes
6 V1 = 240; // in Volts
7
8 //calculation:
9 //A turns ratio of 8:1 means that the transformer
  has 28 turns on the primary for every 1turns on
  the secondary
10 V2 = V1/tr
11 //secondary current

```

```

12 I2 = I1*tr
13
14 printf("\n\n Result \n\n")
15 printf("\n secondary voltage is %.0f V and secondary
    current is %.0f A",V2, I2)

```

---

#### Scilab code Exa 20.04 Example 4

```

1 //Problem 20.04: An ideal transformer , connected to
  a 240 V mains , supplies a 12 V, 150 W lamp.
  Calculate the transformer turns ratio and the
  current taken from the supply .
2
3 //initializing the variables:
4 V1 = 240; // in Volts
5 V2 = 12; // in Volts
6 P = 150; // in Watts
7
8 //calculation:
9 I2 = P/V2
10 //A turns ratio = Vp/Vs
11 tr = V1/V2 // turn ratio
12 // V1/V2 = I2/I1
13 //current taken from the supply
14 I1 = I2*V2/V1
15
16 printf("\n\n Result \n\n")
17 printf("\n turn ratio is %.0f and current taken from
    the supply is %.3f A",tr, I1)

```

---

#### Scilab code Exa 20.05 Example 5

```

1 //Problem 20.05: A 5 kVA single-phase transformer
  has a turns ratio of 10:1 and is fed from a 2.5
  kV supply. Neglecting losses , determine (a) the
  full-load secondary current , (b) the minimum load
  resistance which can be connected across the
  secondary winding to give full load kVA, (c) the
  primary current at full load kVA.
2
3 //initializing the variables:
4 S = 5000; // in VA
5 tr = 10; // turn ratio
6 V1 = 2500; // in Volts
7
8 //calculation:
9 //A turns ratio of 8:1 means that the transformer
  has 28 turns on the primary for every 1turns on
  the secondary
10 V2 = V1/tr
11 //transformer rating in volt-amperes = Vs*Is
12 I2 = S/V2
13 //Minimum value of load resistance
14 RL = V2/I2
15 // tr = I2/I1
16 I1 = I2/tr
17
18 printf("\n\n Result \n\n")
19 printf("\n (a)full-load secondary current is %.0f A"
  ,I2)
20 printf("\n (b)minimum load resistance is %.1f ohm",
  RL)
21 printf("\n (c) primary current is %.0f A",I1)

```

---

#### Scilab code Exa 20.06 Example 6

```

1 //Problem 20.06: A 2400 V/400 V single-phase

```



transformer takes a no load current of 0.5 A and the core loss is 400 W. Determine the values of the magnetizing and core loss components of the no load current. Draw to scale the no-load phasor diagram for the transformer.

```

2
3 //initializing the variables:
4 V1 = 2400; // in Volts
5 V2 = 400; // in Volts
6 I0 = 0.5; // in Amperes
7 Pc = 400; // in Watts
8
9 //calculation:
10 //Core loss (i.e. iron loss)  $P = V1*I0*\cos(\phi_0)$ 
11 pf = Pc/(V1*I0)
12 phi0 = acos(pf)
13 //Magnetizing component
14 Im = I0*sin(phi0)
15 //Core loss component
16 Ic = I0*cos(phi0)
17
18 printf("\n\n Result \n\n")
19 printf("\n (a)magnetizing component is %.3f A and
    Core loss component is %.3f A",Im, Ic)

```

---

#### Scilab code Exa 20.07 Example 7

```

1 //Problem 20.07: A transformer takes a current of
    0.8 A when its primary is connected to a 240 volt
    , 50 Hz supply , the secondary being on open
    circuit. If the power absorbed is 72 watts ,
    determine (a) the iron loss current , (b) the
    power factor on no-load , and (c) the magnetizing
    current.
2

```

```

3 //initializing the variables:
4 V = 240; // in Volts
5 I0 = 0.8; // in Amperes
6 P = 72; // in Watts
7 f = 50; // in Hz
8
9 //calculation:
10 //Power absorbed = total core loss , P = V*I0*cos(
    phi0)
11 //Ic = I0*cos(phi0)
12 Ic = P/V
13 pf = Ic/I0
14 //From the right-angled triangle in Figure 20.2(b)
    and using
15 //Pythagoras theorem,
16 Im = (I0*I0 - Ic*Ic)^0.5
17
18 printf("\n\n Result \n\n")
19 printf("\n (a) Core loss component is %.2f A", Ic)
20 printf("\n (b) power factor is %.3f", pf)
21 printf("\n (c) magnetizing component is %.2f A", Im)

```

---

#### Scilab code Exa 20.08 Example 8

```

1 //Problem 20.08: A 100 kVA, 4000 V/200 V, 50 Hz
    single-phase transformer has 100 secondary turns.
    Determine (a) the primary and secondary current,
    (b) the number of primary turns, and (c) the
    maximum value of the flux.
2
3 //initializing the variables:
4 S = 100000; // in VA
5 V1 = 4000; // in Volts
6 V2 = 200; // in Volts
7 N2 = 100; // sec turns

```

```

8 f = 50; // in Hz
9
10 // calculation :
11 //Transformer rating = V1*I1 = V2*I2
12 //primary current
13 I1 = S/V1
14 //secondary current
15 I2 = S/V2
16 //primary turns
17 N1 = N2*V1/V2
18 //maximum flux
19 //assuming E2 = V2
20 Phim = V2/(4.44*f*N2)
21
22 printf("\n\n Result \n\n")
23 printf("\n (a)primary current is %.0f A and
        secondary current is %.0f A", I1, I2)
24 printf("\n (b)number of primary turns is %.0f", N1)
25 printf("\n (c)maximum value of the flux is %.2E Wb",
        Phim)

```

---

#### Scilab code Exa 20.09 Example 9

```

1 //Problem 20.09: A single-phase, 50 Hz transformer
  has 25 primary turns and 300 secondary turns. The
  cross-sectional area of the core is 300 cm2.
  When the primary winding is connected to a 250 V
  supply, determine (a) the maximum value of the
  flux density in the core, and (b) the voltage
  induced in the secondary winding.
2
3 //initializing the variables:
4 V1 = 250; // in Volts
5 A = 0.03; // in m2
6 N2 = 300; // sec turns

```

```

7 N1 = 25; // prim turns
8 f = 50; // in Hz
9
10 //calculation:
11 //e.m.f. E1 = 4.44*f*Phim*N1
12 //maximum flux density ,
13 Phim = V1/(4.44*f*N1)
14 //Phim = Bm*A, where Bm = maximum core flux density
    and A = cross-sectional area of the core
15 //maximum core flux density
16 Bm = Phim/A
17 //voltage induced in the secondary winding ,
18 V2 = V1*N2/N1
19
20 printf("\n\n Result \n\n")
21 printf("\n (a)maximum core flux density %.2f T", Bm)
22 printf("\n (b)voltage induced in the secondary
    winding is %.0f V", V2)

```

---

### Scilab code Exa 20.10 Example 10

```

1 //Problem 20.10: A single-phase 500 V/100 V, 50 Hz
    transformer has a maximum core flux density of
    1.5 T and an effective core crosssectional area
    of 50 cm2. Determine the number of primary and
    secondary turns.
2
3 //initializing the variables:
4 V1 = 500; // in Volts
5 V2 = 100; // in Volts
6 Bm = 1.5; // in Tesla
7 A = 0.005; // in m2
8 f = 50; // in Hz
9
10 //calculation:

```

```

11 //Phim = Bm*A, where Bm = maximum core flux density
    and A = cross-sectional area of the core
12 //maximum core flux density
13 Phim = Bm*A
14 //e.m.f. E1 = 4.44*f*Phim*N1
15 //primary turns ,
16 N1 = V1/(4.44*f*Phim)
17 //secondary turns ,
18 N2 = V2*N1/V1
19
20 printf("\n\n Result \n\n")
21 printf("\n no. of primary and secondary turns are %
    .0f turns , and %.0f turns respectively" , N1 , N2)

```

---

#### Scilab code Exa 20.11 Example 11

```

1 //Problem 20.11: A 4500 V/225 V, 50 Hz single-phase
    transformer is to have an approximate e.m.f. per
    turn of 15 V and operate with a maximum flux of
    1.4 T. Calculate (a) the number of primary and
    secondary turns and (b) the cross-sectional area
    of the core.
2
3 //initializing the variables:
4 emfpt = 15; // in Volts
5 V1 = 4500; // in Volts
6 V2 = 225; // in Volts
7 Bm = 1.4; // in Tesla
8 f = 50; // in Hz
9
10 //calculation:
11 //E.m.f. per turn, V1/N1 = V2/N2 = emfpt
12 //primary turns ,
13 N1 = V1/emfpt
14 //secondary turns ,

```

```

15 N2 = V2/emfpt
16 //e.m.f. E1 = 4.44*f*Phim*N1
17 //maximum flux density ,
18 Phim = V1/(4.44*f*N1)
19 //Phim = Bm*A, where Bm = maximum core flux density
    and A = cross-sectional area of the core
20 //cross-sectional area
21 A = Phim/Bm
22
23 printf("\n\n Result \n\n")
24 printf("\n (a)no. of primary and secondary turns are
    %.0f turns, and %.0f turns respectively", N1, N2
    )
25 printf("\n (b)cross-sectional area is %.2E m2", A)

```

---

### Scilab code Exa 20.12 Example 12

```

1 //Problem 20.12: A single-phase transformer has 2000
    turns on the primary and 800 turns on the
    secondary. Its no-load current is 5 A at a power
    factor of 0.20 lagging. Assuming the volt drop in
    the windings is negligible, determine the
    primary current and power factor when the
    secondary current is 100 A at a power factor of
    0.85 lagging.
2
3 //initializing the variables:
4 N1 = 2000; // prim turns
5 N2 = 800; // sec turns
6 I0 = 5; // in Amperes
7 pf0 = 0.20; // power factor
8 I2 = 100; // in Amperes
9 pf2 = 0.85; // power factor
10
11 //calculation:

```

```

12 //Let I01 be the component of the primary current
    which provides the restoring mmf. Then  $I_{01}N_1 = I_2N_2$ 
13 I01 = I2*N2/N1
14 //If the power factor of the secondary is 0.85
15 phi2 = acos(pf2)
16 //If the power factor on no-load is 0.20,
17 phi0 = acos(pf0)
18 I1h = I0*cos(phi0) + I01*cos(phi2)
19 I1v = I0*sin(phi0) + I01*sin(phi2)
20 //Hence the magnitude of I1
21 I1 = (I1h*I1h + I1v*I1v)^0.5
22 pf1 = cos(atan(I1v/I1h))
23
24 printf("\n\n Result \n\n")
25 printf("\n Primary currnt is %.2f A, and Power
    factor is %.2f", I1, pf1)

```

---

### Scilab code Exa 20.13 Example 13

```

1 //Problem 20.13: A transformer has 600 primary turns
    and 150 secondary turns. The primary and
    secondary resistances are 0.25 ohm and 0.01 ohm
    respectively and the corresponding leakage
    reactances are 1.0 ohm and 0.04 ohm respectively
    . Determine (a) the equivalent resistance
    referred to the primary winding, (b) the
    equivalent reactance referred to the primary
    winding, (c) the equivalent impedance referred to
    the primary winding, and (d) the phase angle of
    the impedance.
2
3 //initializing the variables:
4 N1 = 600; // prim turns
5 N2 = 150; // sec turns

```

```

6 R1 = 0.25; // in ohms
7 R2 = 0.01; // in ohms
8 X1 = 1.0; // in ohms
9 X2 = 0.04; // in ohms
10
11 //calculation:
12 tr = N1/N2 // turn ratio
13 vr = tr // voltage ratio = turn raio , vr = V1/V2
14 //equivalent resistance Re
15 Re = R1 + R2*(vr^2)
16 //equivalent reactance , Xe
17 Xe = X1 + X2*(vr^2)
18 //equivalent impedance , Ze
19 Ze = (Re*Re + Xe*Xe)^0.5
20 //cos(phi) = Re/Ze
21 pfe = Re/Ze
22 phi = acos(pfe)
23 phied = phi*180/pi // in (deg)
24
25 printf("\n\n Result \n\n")
26 printf("\n (a)the equivalent resistance referred to
    the primary winding is %.2f ohm", Re)
27 printf("\n (b)the equivalent reactance referred to
    the primary winding is %.2f ohm", Xe)
28 printf("\n (c)the equivalent impedance referred to
    the primary winding is %.2f ohm", Ze)
29 printf("\n (d)phase angle is %.2 f ", phied)

```

---

#### Scilab code Exa 20.14 Example 14

```

1 //Problem 20.14: A 5 kVA, 200 V/400 V, single-phase
    transformer has a secondary terminal voltage of
    387.6 volts when loaded. Determine the regulation
    of the transformer.
2

```



```

3 //initializing the variables:
4 V1 = 200; // in Volts
5 V2 = 400; // in Volts
6 V2L = 387.6; // in Volts
7 S = 5000; // in VA
8
9 //calculation:
10 //regulation =(No-load secondary voltage - terminal
    voltage on load)*100/no-load secondary voltage
    in %
11 reg = (V2 - V2L)*100/V2
12
13 printf("\n\n Result \n\n")
14 printf("\n the regulation of the transformer is %.1f
    percent ", reg)

```

---

**Scilab code Exa 20.15** Example 15

```

1 //Problem 20.15: The open circuit voltage of a
    transformer is 240 V. A tap changing device is
    set to operate when the percentage regulation
    drops below 2.5%. Determine the load voltage at
    which the mechanism operates.
2
3 //initializing the variables:
4 VnL = 240; // in Volts
5 reg = 2.5; // in percent
6
7 //calculation:
8 //regulation =(No-load secondary voltage - terminal
    voltage on load)*100/no-load secondary voltage
    in %
9 VL = VnL - reg*VnL/100
10
11 printf("\n\n Result \n\n")

```

```
12 printf("\n the load voltage at which the mechanism
operates is %.0f V ", VL)
```

---

### Scilab code Exa 20.16 Example 16

```
1 //Problem 20.16: A 200 kVA rated transformer has a
full-load copper loss of 1.5 kW and an iron loss
of 1 kW. Determine the transformer efficiency at
full load and 0.85 power factor.
2
3 //initializing the variables:
4 S = 200000; // in VA
5 Pc = 1500; // in Watt
6 Pi = 1000; // in Watt
7 pf = 0.85; // power factor
8
9 //calculation:
10 //Efficiency = output power/input power = (input
power losses)/input power
11 //Efficiency = 1 - losses/input power
12 //Full-load output power = V*I*pf
13 Po = S*pf
14 //Total losses
15 Pl = Pc + Pi
16 //Input power = output power + losses
17 PI = Po + Pl
18 //efficiency
19 eff = 1-(Pl/PI)
20
21 printf("\n\n Result \n\n")
22 printf("\n the transformer efficiency at full load
is %.4f", eff)
```

---

### Scilab code Exa 20.17 Example 17

```
1 //Problem 20.17: Determine the efficiency of the
   transformer in Problem 20.16 at half full-load
   and 0.85 power factor.
2
3 //initializing the variables:
4 S = 200000; // in VA
5 Pc = 1500; // in Watt
6 Pi = 1000; // in Watt
7 pf = 0.85; // power factor
8
9 //calculation:
10 //Efficiency = output power/input power = (input
   power losses)/input power
11 //Efficiency = 1 - losses/input power
12 //Half full-load power output = V*I*pf/2
13 Po = S*pf/2
14 //Copper loss (or I*I*R loss) is proportional to
   current squared
15 //Hence the copper loss at half full-load is
16 Pch = Pc/(2*2)
17 //Iron loss = 1000 W (constant)
18 //Total losses
19 Pl = Pch + Pi
20 //Input power at half full-load = output power at
   half full-load + losses
21 PI = Po + Pl
22 //efficiency
23 eff = (1-(Pl/PI))*100
24
25 printf("\n\n Result \n\n")
26 printf("\n the transformer efficiency at half full
   load is %.2f percent", eff)
```

---

### Scilab code Exa 20.18 Example 18

```
1 //Problem 20.18: A 400 kVA transformer has a primary
   winding resistance of 0.5 ohm and a secondary
   winding resistance of 0.001 ohm . The iron loss
   is 2.5 kW and the primary and secondary voltages
   are 5 kV and 320 V respectively . If the power
   factor of the load is 0.85, determine the
   efficiency of the transformer (a) on full load ,
   and (b) on half load.
2
3 //initializing the variables:
4 S = 400000; // in VA
5 R1 = 0.5; // in Ohm
6 R2 = 0.001; // in Ohm
7 V1 = 5000; // in Volts
8 V2 = 320; // in Volts
9 Pi = 2500; // in Watt
10 pf = 0.85; // power factor
11
12 //calculation:
13 //Rating = 400 kVA = V1*I1 = V2*I2
14 //Hence primary current
15 I1 = S/V1
16 //secondary current
17 I2 = S/V2
18 //Total copper loss = I1*I1*R1 + I2*I2*R2,
19 Pcf = I1*I1*R1 + I2*I2*R2
20 //On full load , total loss = copper loss + iron loss
21 Plf = Pcf + Pi
22 // full-load power output = V2*I2*pf
23 Pof = S*pf
24 //Input power at full-load = output power at full-
   load + losses
25 PIf = Pof + Plf
26 //Efficiency = output power/input power = (input
   power losses)/input power
27 //Efficiency = 1 - losses/input power
```

```

28 efff = (1-(Plf/PIf))*100
29
30 //Half full-load power output = V*I*pf/2
31 Poh = S*pf/2
32 //Copper loss (or I*I*R loss) is proportional to
    current squared
33 //Hence the copper loss at half full-load is
34 Pch = Pcf/(2*2)
35 //Iron loss = 2500 W (constant)
36 //Total losses
37 Plh = Pch + Pi
38 //Input power at half full-load = output power at
    half full-load + losses
39 PIh = Poh + Plh
40 //efficiency
41 effh = (1-(Plh/PIh))*100
42
43 printf("\n\n Result \n\n")
44 printf("\n (a)the transformer efficiency at full
    load is %.2f percent", efff)
45 printf("\n (b)the transformer efficiency at half
    full load is %.2f percent", effh)

```

---

### Scilab code Exa 20.19 Example 19

```

1 //Problem 20.19: A 500 kVA transformer has a full
    load copper loss of 4 kW and an iron loss of 2.5
    kW. Determine (a) the output kVA at which the
    efficiency of the transformer is a maximum, and (
    b) the maximum efficiency, assuming the power
    factor of the load is 0.75.
2
3 //initializing the variables:
4 S = 500000; // in VA
5 Pcf = 4000; // in Watt

```

```

6 Pi = 2500; // in Watt
7 pf = 0.75; // power factor
8
9 //calculation:
10 //Let x be the fraction of full load kVA at which
    the efficiency is a maximum.
11 //The corresponding total copper loss = (4 kW)*(x^2)
12 //At maximum efficiency , copper loss = iron loss
    Hence
13 x = (Pi/Pcf)^0.5
14 //Hence the output kVA at maximum efficiency
15 So = x*S
16 //Total loss at maximum efficiency
17 Pl = 2*Pi
18 //Output power
19 Po = So*pf
20 //Input power = output power + losses
21 PI = Po + Pl
22 //Efficiency = output power/input power = (input
    power losses)/input power
23 //Efficiency = 1 - losses/input power
24 //Maximum efficiency
25 effm = (1 - Pl/PI)*100
26
27 printf("\n\n Result \n\n")
28 printf("\n the output kVA at maximum efficiency is %
    .2E VA", So)
29 printf("\n max. efficiency is %.2f percent", effm)

```

---

#### Scilab code Exa 20.20 Example 20

```

1 //Problem 20.20: A transformer having a turns ratio
    of 4:1 supplies a load of resistance 100 ohm.
    Determine the equivalent input resistance of the
    transformer.

```

```

2
3 //initializing the variables:
4 tr = 4; // turn ratio
5 RL = 100; // in Ohms
6
7 //calculation:
8 //the equivalent input resistance ,
9 Ri = RL*(tr^2)
10
11 printf("\n\n Result \n\n")
12 printf("\n the equivalent input resistance is %.0f
    ohm", Ri)

```

---

**Scilab code Exa 20.21** Example 21

```

1 //Problem 20.21: The output stage of an amplifier
    has an output resistance of 112 ohm. Calculate
    the optimum turns ratio of a transformer which
    would match a load resistance of 7 ohm to the
    output resistance of the amplifier.
2
3 //initializing the variables:
4 R1 = 112; // in Ohms
5 RL = 7; // in Ohms
6
7 //calculation:
8 //The equivalent input resistance , R1 of the
    transformer needs to be 112 ohm for maximum power
    transfer.
9 //R1 = RL*(tr^2)
10 // tr = N1/N2 turn ratio
11 tr = (R1/RL)^0.5
12
13 printf("\n\n Result \n\n")
14 printf("\n the optimum turns ratio is %.0f ", tr)

```

---

**Scilab code Exa 20.22** Example 22

```
1 //Problem 20.22: Determine the optimum value of load
    resistance for maximum power transfer if the
    load is connected to an amplifier of output
    resistance 150 ohm through a transformer with a
    turns ratio of 5:1..
2
3 //initializing the variables:
4 tr = 5; // turn ratio
5 R1 = 150; // in Ohms
6
7 //calculation:
8 //The equivalent input resistance , R1 of the
    transformer needs to be 150 ohm for maximum power
    transfer.
9 //R1 = RL*(tr^2)
10 RL = R1/(tr^2)
11
12 printf("\n\n Result \n\n")
13 printf("\n the optimum value of load resistance is %
    .0f ohm", RL)
```

---

**Scilab code Exa 20.23** Example 23

```
1 //Problem 20.23: A single-phase , 220 V/1760 V ideal
    transformer is supplied from a 220 V source
    through a cable of resistance 2 ohm. If the load
    across the secondary winding is 1.28 kohm
    determine (a) the primary current flowing and (b)
    the power dissipated in the load resistor.
```



```

2
3 //initializing the variables:
4 V1 = 220; // in Volts
5 V2 = 1760; // in Volts
6 V = 220; // in Volts
7 RL = 1280; // in Ohms
8 R = 2; // in Ohms
9
10 //calculation:
11 //Turns ratio, tr = N1/N2 = V1/V2
12 tr = V1/V2
13 //Equivalent input resistance of the transformer,
14 //R1 = RL*(tr^2)
15 R1 = RL*(tr^2)
16 //Total input resistance
17 Rin = R + R1
18 // Primary current
19 I1 = V1/Rin
20 //For an ideal transformer V1/V2 = I2/I1,
21 I2 = I1*tr
22 //Power dissipated in load resistor RL
23 P = I2*I2*RL
24
25 printf("\n\n Result \n\n")
26 printf("\n (a) primary current flowing is %.0f A",
        I1)
27 printf("\n (b) power dissipated in the load
        resistor is %.0f W", P)

```

---

**Scilab code Exa 20.24** Example 24

```

1 //Problem 20.24: An a.c. source of 24 V and internal
  resistance 15 kohm is matched to a load by a
  25:1 ideal transformer. Determine (a) the value
  of the load resistance and (b) the power

```

```

    dissipated in the load.
2
3 //initializing the variables:
4 tr = 25; // teurn ratio
5 V = 24; // in Volts
6 R1 = 15000; // in Ohms
7 Rin = 15000; // in ohms
8
9 //calculation:
10 //Turns ratio , tr = N1/N2 = V1/V2
11 //For maximum power transfer R1 needs to be equal to
    15 kohm
12 RL = R1/(tr^2)
13 //The total input resistance when the source is
    connected to the matching transformer is
14 Rt = Rin + R1
15 //Primary current ,
16 I1 = V/Rt
17 //N1/N2 = I2/I1
18 I2 = I1*tr
19 //Power dissipated in load resistor RL
20 P = I2*I2*RL
21
22 printf("\n\n Result \n\n")
23 printf("\n (a) the load resistance is %.0f ohm", RL)
24 printf("\n (b) power dissipated in the load
    resistor is %.2E W", P)

```

---

### Scilab code Exa 20.25 Example 25

```

1 //Problem 20.25: A single-phase auto transformer has
    a voltage ratio 320 V:250 V and supplies a load
    of 20 kVA at 250 V. Assuming an ideal transformer
    , determine the current in each section of the
    winding.

```

```

2
3 //initializing the variables:
4 V1 = 320; // in Volts
5 V2 = 250; // in Volts
6 S = 20000; // in VA
7
8 //calculation:
9 //Rating = 20 kVA = V1*I1 = V2*I2
10 //Hence primary current , I1
11 I1 = S/V1
12 //secondary current , I2
13 I2 = S/V2
14 //Hence current in common part of the winding
15 I = I2 - I1
16
17 printf("\n\n Result \n\n")
18 printf("\n current in common part of the winding is
19      %.1f A", I)
20 printf("\n primary current and secondary current are
21      %.1f A and %.0f A respectively",I1, I2)

```

---

**Scilab code Exa 20.26** Example 26

```

1 //Problem 20.26: Determine the saving in the volume
2   of copper used in an auto transformer compared
3   with a double-wound transformer for (a) a 200 V
4   :150 V transformer , and (b) a 500 V:100 V
5   transformer .
6
7 //initializing the variables:
8 V1a = 200; // in Volts
9 V2a = 150; // in Volts
10 V1b = 500; // in Volts
11 V2b = 100; // in Volts
12

```

```

 9 //calculation :
10 //For a 200 V:150 V transformer , xa
11 xa = V2a/V1a
12 //volume of copper in auto transformer
13 vca = (1 - xa)*100 // of copper in a double-wound
    transformer
14 //the saving is
15 vsa = 100 - vca
16 //For a 500 V:100 V transformer , xb
17 xb = V2b/V1b
18 //volume of copper in auto transformer
19 vcb = (1 - xb)*100 // of copper in a double-wound
    transformer
20 //the saving is
21 vsb = 100 - vcb
22
23 printf("\n\n Result \n\n")
24 printf("\n (a)For a 200 V:150 V transformer , the
    saving is %.0f percent", vsa)
25 printf("\n (b)For a 500 V:100 V transformer , the
    saving is %.0f percent", vsb)

```

---

### Scilab code Exa 20.27 Example 27

```

1 //Problem 20.27: A three-phase transformer has 500
    primary turns and 50 secondary turns. If the
    supply voltage is 2.4 kV find the secondary line
    voltage on no-load when the windings are
    connected a) star-delta , (b) delta-star.
2
3 //initializing the variables :
4 N1 = 500; // prim turns
5 N2 = 50; // sec turns
6 VL = 2400; // in Volts
7

```

```

8 //calculation :
9 //For a star-connection , VL = Vp*(3^0.5)
10 VL1s = VL
11 //Primary phase voltage
12 Vp1s = VL1s/(3^0.5)
13 //For a delta-connection , VL = Vp
14 //N1/N2 = V1/V2, from which ,
15 //secondary phase voltage , Vp2s
16 Vp2s = Vp1s*N2/N1
17 VL2d = Vp2s
18
19 //For a delta-connection , VL = Vp
20 VL1d = VL
21 //primary phase voltage Vp1d
22 Vp1d = VL1d
23 //Secondary phase voltage , Vp2d
24 Vp2d = Vp1d*N2/N1
25 //For a star-connection , VL = Vp*(3^0.5)
26 VL2s = Vp2d*(3^0.5)
27
28 printf("\n\n Result \n\n")
29 printf("\n the secondary line voltage for star and
    delta connection are %.0f V and %.1f V
    respectively", VL2s, VL2d)

```

---

### Scilab code Exa 20.28 Example 28

```

1 //Problem 20.28: A current transformer has a single
    turn on the primary winding and a secondary
    winding of 60 turns. The secondary winding is
    connected to an ammeter with a resistance of 0.15
    ohm. The resistance of the secondary winding is
    0.25 ohm. If the current in the primary winding
    is 300 A, determine (a) the reading on the
    ammeter, (b) the potential difference across the

```

```

    ammeter and (c) the total load (in VA) on the
    secondary.
2
3 //initializing the variables:
4 N1 = 1; // prim turns
5 N2 = 60; // sec turns
6 I1 = 300; // in amperes
7 Ra = 0.15; // in ohms
8 R2 = 0.25; // in ohms
9
10 //calculation:
11 //Reading on the ammeter,
12 I2 = I1*(N1/N2)
13 //P.d. across the ammeter = I2*RA, where RA is the
    ammeter resistance
14 pd = I2*Ra
15 //Total resistance of secondary circuit
16 Rt = Ra + R2
17 //Induced e.m.f. in secondary
18 V2 = I2*Rt
19 //Total load on secondary
20 S = V2*I2
21
22 printf("\n\n Result \n\n")
23 printf("\n (a)the reading on the ammeter is %.0f A "
    ,I2)
24 printf("\n (b)potential difference across the
    ammeter is %.2f V ",pd)
25 printf("\n (c)total load (in VA) on the secondary is
    %.0f VA ",S)

```

---

# Chapter 21

## DC machines

Scilab code Exa 21.01 Example 1

```
1 //Problem 21.01: An 8-pole , wave-connected armature
   has 600 conductors and is driven at 625 rev/min.
   If the flux per pole is 20 mWb, determine the
   generated e.m.f.
2
3 //initializing the variables:
4 Z = 600; // no. of conductors
5 c = 2; // for a wave winding
6 p = 4; // no. of pairs
7 n = 625/60; // in rev/sec
8 Phi = 20E-3; // in Wb
9
10 //calculation:
11 //Generated e.m.f.,  $E = 2*p*Phi*n*Z/c$ 
12 E = 2*p*Phi*n*Z/c
13
14 printf("\n\n Result \n\n")
15 printf("\n the generated e.m.f is %.0f V ",E)
```

---

### Scilab code Exa 21.02 Example 2

```
1 //Problem 21.02: A 4-pole generator has a lap-wound
   armature with 50 slots with 16 conductors per
   slot. The useful flux per pole is 30 mWb.
   Determine the speed at which the machine must be
   driven to generate an e.m.f. of 240 V.
2
3 //initializing the variables:
4 Z = 50*16; // no. of conductors
5 p = 1; // let no. of pairs
6 c = 2*p; // for a lap winding
7 Phi = 30E-3; // in Wb
8 E = 240; // in Volts
9
10 //calculation:
11 //Generated e.m.f.,  $E = 2*p*Phi*n*Z/c$ 
12 //Rearranging gives, speed
13  $n = E*c/(2*p*Phi*Z)$ 
14
15 printf("\n\n Result \n\n")
16 printf("\n the speed at which the machine must be
   driven is %.0f rev/sec ",n)
```

---

### Scilab code Exa 21.03 Example 3

```
1 //Problem 21.03: An 8-pole, lap-wound armature has
   1200 conductors and a flux per pole of 0.03 Wb.
   Determine the e.m.f. generated when running at
   500 rev/min.
2
3 //initializing the variables:
4 Z = 1200; // no. of conductors
5 p = 1; // let, no. of pairs
6 c = 2*p; // for a lap winding
```



```

7 Phi = 30E-3; // in Wb
8 n = 500/60; // in rev/sec
9
10 //calculation:
11 //Generated e.m.f.,  $E = 2*p*Phi*n*Z/c$ 
12 E = 2*p*Phi*n*Z/c
13
14 printf("\n\n Result \n\n")
15 printf("\n Generated e.m.f. is %.0f V ",E)

```

---

#### Scilab code Exa 21.04 Example 4

```

1 //Problem 21.04: Determine the generated e.m.f. in
   problem 21.03 if the armature is wave-wound.
2
3 //initializing the variables:
4 Z = 1200; // no. of conductors
5 p = 4; // let, no. of pairs
6 c = 2; // for a wave winding
7 Phi = 30E-3; // in Wb
8 n = 500/60; // in rev/sec
9
10 //calculation:
11 //Generated e.m.f.,  $E = 2*p*Phi*n*Z/c$ 
12 E = 2*p*Phi*n*Z/c
13
14 printf("\n\n Result \n\n")
15 printf("\n Generated e.m.f. is %.0f V ",E)

```

---

#### Scilab code Exa 21.06 Example 6

```

1 //Problem 21.06: A d.c. generator running at 30 rev/
  s generates an e.m.f. of 200 V. Determine the
  percentage increase in the flux per pole required
  to generate 250 V at 20 rev/s.
2
3 //initializing the variables:
4 n1 = 30; // in rev/sec
5 E1 = 200; // in Volts
6 n2 = 20; // in rev/sec
7 E2 = 250; // in Volts
8
9 //calculation:
10 //generated e.m.f., E proportional to phi*w and
  since w = 2*pi*n, then
11 // E proportional to phi*n
12 // E1/E2 = Phi1*n1/(Phi2*n2)
13 // let Phi2/Phi1 = Phi
14 Phi = E2*n1/(E1*n2)
15 Phi_inc = (Phi - 1)*100 ///in percent
16
17 printf("\n\n Result \n\n")
18 printf("\n percentage increase in the flux per pole
  is %.1f percent ",Phi_inc)

```

---

#### Scilab code Exa 21.07 Example 7

```

1 //Problem 21.07: Determine the terminal voltage of a
  generator which develops an e.m.f. of 200 V and
  has an armature current of 30 A on load. Assume
  the armature resistance is 0.30 ohm.
2
3 //initializing the variables:
4 Ra = 0.30; // in ohms
5 Ia = 30; // in Amperes
6 E = 200; // in Volts

```

```

7
8 //calculation:
9 //terminal voltage ,
10 //V = E - Ia*Ra
11 V = E - Ia*Ra
12
13 printf("\n\n Result \n\n")
14 printf("\n terminal voltage of a generator is %.0f V
      ",V)

```

---

#### Scilab code Exa 21.08 Example 8

```

1 //Problem 21.08: A generator is connected to a 60
   ohm load and a current of 8 A flows. If the
   armature resistance is 1 ohm determine (a) the
   terminal voltage , and (b) the generated e.m.f.
2
3 //initializing the variables:
4 RL = 60; // in ohms
5 Ia = 8; // in Amperes
6 Ra = 1; // in ohms
7
8 //calculation:
9 //terminal voltage ,
10 //V = Ia*RL
11 V = Ia*RL
12 //Generated e.m.f., E
13 E = V + Ia*Ra
14
15 printf("\n\n Result \n\n")
16 printf("\n (a) terminal voltage is %.0f V ",V)
17 printf("\n (b) generated e.m.f. is %.0f V ",E)

```

---

### Scilab code Exa 21.09 Example 9

```
1 //Problem 21.09: A separately-excited generator
   develops a no-load e.m.f. of 150 V at an armature
   speed of 20 rev/s and a flux per pole of 0.10 Wb
   . Determine the generated e.m.f. when (a) the
   speed increases to 25 rev/s and the pole flux
   remains unchanged, (b) the speed remains at 20
   rev/s and the pole flux is decreased to 0.08 Wb,
   and (c) the speed increases to 24 rev/s and the
   pole flux is decreased to 0.07 Wb.
2
3 //initializing the variables:
4 E1 = 150; // in Volts
5 n1 = 20; // in rev/sec
6 Phi1 = 0.10; // in Wb
7 n2 = 25; // in rev/sec
8 Phi2 = 0.10; // in Wb
9 n3 = 20; // in rev/sec
10 Phi3 = 0.08; // in Wb
11 n4 = 24; // in rev/sec
12 Phi4 = 0.07; // in Wb
13
14 //calculation:
15 //generated e.m.f., E proportional to phi*w and
   since  $w = 2\pi n$ , then
16 // E proportional to phi*n
17 //  $E1/E2 = Phi1*n1/(Phi2*n2)$ 
18 E2 = E1*Phi2*n2/(Phi1*n1)
19 E3 = E1*Phi3*n3/(Phi1*n1)
20 E4 = E1*Phi4*n4/(Phi1*n1)
21
22 printf("\n\n Result \n\n")
23 printf("\n (a)the generated e.m.f is %.1f V ",E2)
24 printf("\n (b)generated e.m.f. is %.0f V ",E3)
25 printf("\n (c)generated e.m.f. is %.0f V ",E4)
```

---

Scilab code Exa 21.10 Example 10

```
1 //Problem 21.10: A shunt generator supplies a 20 kW
   load at 200 V through cables of resistance , R =
   100 mohm. If the field winding resistance , Rf=50
   50ohm and the armature resistance , Ra = 40 mohm,
   determine (a) the terminal voltage , and (b) the
   e.m.f. generated in the armature.
2
3 //initializing the variables:
4 Ps = 20000; // in Watts
5 Vs = 200; // in Volts
6 Rs = 0.1; // in ohms
7 Rf = 50; // in ohms
8 Ra = 0.04; // in ohms
9
10 //calculation:
11 //Load current , I
12 Is = Ps/Vs
13 //Volt drop in the cables to the load
14 Vd = Is*Rs
15 //Hence terminal voltage ,
16 V = Vs + Vd
17 //Field current , If
18 If = V/Rf
19 //Armature current
20 Ia = If + Is
21 //Generated e.m.f. E
22 E = V + Ia*Ra
23
24 printf("\n\n Result \n\n")
25 printf("\n (a) terminal voltage is %.0f V ",V)
26 printf("\n (b) generated e.m.f. is %.2f V ",E)
```

---

**Scilab code Exa 21.11** Example 11

```
1 //Problem 21.11: A short-shunt compound generator
   supplies 80 A at 200 V. If the field resistance ,
   Rf = 40 ohm, the series resistance , Rse = 0.02
   ohms and the armature resistance , Ra = 0.04 ohm,
   determin the e.m.f. generated.
2
3 //initializing the variables:
4 Is = 80; // in amperes
5 Vs = 200; // in Volts
6 Rf = 40; // in ohms
7 Rse = 0.02; // in ohms
8 Ra = 0.04; // in ohms
9
10 //calculation:
11 //Volt drop in series winding
12 Vse = Is*Rse
13 //P.d. across the field winding = p.d. across
   armature
14 V1 = Vs + Vse
15 //Field current , If
16 If = V1/Rf
17 //Armature current
18 Ia = If + Is
19 //Generated e.m.f. E
20 E = V1 + Ia*Ra
21
22 printf("\n\n Result \n\n")
23 printf("\n generated e.m.f. is %.0f V ",E)
```

---

**Scilab code Exa 21.12** Example 12

```

1 //Problem 21.12: A 10 kW shunt generator having an
   armature circuit resistance of 0.75 ohm and a
   field resistance of 125 ohms , generates a
   terminal voltage of 250 V at full load. Determine
   the efficiency of the generator at full load ,
   assuming the iron , friction and windage losses
   amount to 600 W.
2
3 //initializing the variables:
4 Ps = 10000; // in Watt
5 Pl = 600; // in Watt
6 Ra = 0.75; // in ohms
7 Rf = 125; // in ohms
8 V = 250; // in Volts
9
10 //calculation:
11 //Output power Ps = V*I
12 //from which, load current I
13 I = Ps/V
14 //Field current , If
15 If = V/Rf
16 //Armature current
17 Ia = If + I
18 //Efficiency ,
19 eff = Ps*100/((V*I) + (Ia*Ia*Ra) + (If*V) + (Pl)) //
   in Percent
20
21 printf("\n\n Result \n\n")
22 printf("\n Efficiency is %.2f percent ",eff)

```

---

### Scilab code Exa 21.13 Example 13

```

1 //Problem 21.13: A d.c. motor operates from a 240 V
   supply. The armature resistance is 0.2 ohm.
   Determine the back e.m.f. when the armature

```

```

        current is 50 A.
2
3 //initializing the variables:
4 Ra = 0.2; // in ohms
5 V = 240; // in Volts
6 Ia = 50; // in Amperes
7
8 //calculation:
9 //For a motor,  $V = E + I_a * R_a$ 
10  $E = V - I_a * R_a$ 
11
12 printf("\n\n Result \n\n")
13 printf("\n back e.m.f. is %.0f V ",E)

```

---

#### Scilab code Exa 21.14 Example 14

```

1 //Problem 21.14: The armature of a d.c. machine has
  a resistance of 0.25 ohm and is connected to a
  300 V supply. Calculate the e.m.f. generated when
  it is running: (a) as a generator giving 100 A,
  and (b) as a motor taking 80 A.
2
3 //initializing the variables:
4 Ra = 0.25; // in ohms
5 V = 300; // in Volts
6 Ig = 100; // in Amperes
7 Im = 80; // in Amperes
8
9 //calculation:
10 //As a generator, generated e.m.f.,
11 //  $E = V + I_a * R_a$ 
12  $E_g = V + I_g * R_a$ 
13 //For a motor, generated e.m.f. (or back e.m.f.),
14 //  $E = V - I_a * R_a$ 
15  $E = V - I_m * R_a$ 

```



```

16
17 printf("\n\n Result \n\n")
18 printf("\n (a)As a generator , generated e.m.f. is %
    .0f V ",Eg)
19 printf("\n (b)back e.m.f. is %.0f V ",E)

```

---

### Scilab code Exa 21.15 Example 15

```

1 //Problem 21.15: An 8-pole d.c. motor has a wave-
    wound armature with 900 conductors. The useful
    flux per pole is 25 mWb. Determine the torque
    exerted when a current of 30 A flows in each
    armature conductor.
2
3 //initializing the variables:
4 p = 4;
5 c = 2; // for a wave winding
6 Phi = 25E-3; // Wb
7 Z = 900;
8 Ia = 30; // in Amperes
9
10 //calculation:
11 //torque  $T = p*Phi*Z*Ia/(pi*$ 
12 c)
13  $T = p*Phi*Z*Ia/(1*pi*c)$ 
14
15 printf("\n\n Result \n\n")
16 printf("\n the torque exerted is %.1f Nm ",T)

```

---

### Scilab code Exa 21.16 Example 16

```

1 //Problem 21.16: Determine the torque developed by a
   350 V d.c. motor having an armature resistance
   of 0.5 ohm and running at 15 rev/s. The armature
   current is 60 A.
2
3 //initializing the variables:
4 V = 350; // in Volts
5 Ra = 0.5; // in ohms
6 n = 15; // in rev/sec
7 Ia = 60; // in Amperes
8
9 //calculation:
10 //Back e.m.f.  $E = V - I_a R_a$ 
11 E = V - Ia*Ra
12 //torque  $T = E I_a / (2 *
13 n * \pi)$ 
14 T = E*Ia/(2*n*pi)
15
16 printf("\n\n Result \n\n")
17 printf("\n the torque exerted is %.1f Nm ",T)

```

---

#### Scilab code Exa 21.17 Example 17

```

1 //Problem 21.17: A six-pole lap-wound motor is
   connected to a 250 V d.c. supply. The armature
   has 500 conductors and a resistance of 1 ohm. The
   flux per pole is 20 mWb. Calculate (a) the speed
   and (b) the torque developed when the armature
   current is 40 A
2
3 //initializing the variables:
4 p = 1; // let
5 c = 2*p; // for a lap winding
6 Phi = 20E-3; // Wb

```

```

7 Z = 500;
8 V = 250; // in Volts
9 Ra = 1; // in ohms
10 Ia = 40; // in Amperes
11
12 // calculation:
13 //Back e.m.f.  $E = V - I_a * R_a$ 
14 E = V - Ia*Ra
15 //E.m.f.  $E = 2 * p * \Phi * n * Z / c$ 
16 // rearrange ,
17  $n = E * c / (2 * p * \Phi * Z)$ 
18 //torque  $T = E * I_a / (2 *$ 
19  $n * \pi)$ 
20  $T = E * I_a / (2 * n * \pi)$ 
21
22 printf("\n\n Result \n\n")
23 printf("\n (a) speed n is %.0f rev/sec ",n)
24 printf("\n (b) the torque exerted is %.2f Nm ",T)

```

---

### Scilab code Exa 21.18 Example 18

```

1 //Problem 21.18: The shaft torque of a diesel motor
   driving a 100 V d.c. shunt-wound generator is 25
   Nm. The armature current of the generator is 16 A
   at this value of torque. If the shunt field
   regulator is adjusted so that the flux is reduced
   by 15%, the torque increases to 35 Nm. Determine
   the armature current at this new value of torque
   .
2
3 //initializing the variables:
4 T1 = 25; // in Nm
5 T2 = 35; // in Nm
6 Ia1 = 16; // in Amperes

```

```

7 V = 100; // in Volts
8 x = 0.15;
9
10 //calculation:
11 //the shaft torque T of a generator is proportional
    to (phi*Ia), where Phi is the flux and Ia is the
    armature current. Thus,  $T = k*Phi*Ia$ , where k is
    a constant.
12 //The torque at flux phi1 and armature current Ia1
    is  $T1 = k*Phi1*Ia1$ .
13 //similarly  $T2 = k*Phi2*Ia2$ 
14 Phi2 = (1 - x)*Phi1
15 Ia2 = T2*Ia1*Phi1/(Phi2*T1)
16
17 printf("\n\n Result \n\n")
18 printf("\n armature current at the new value of
    torque is %.2f A ",Ia2)

```

---

### Scilab code Exa 21.19 Example 19

```

1 //Problem 21.19: A 100 V d.c. generator supplies a
    current of 15 A when running at 1500 rev/min. If
    the torque on the shaft driving the generator is
    12 Nm, determine (a) the efficiency of the
    generator and (b) the power loss in the generator
    .
2
3 //initializing the variables:
4 T = 12; // in Nm
5 I = 15; // in Amperes
6 V = 100; // in Volts
7 n = 1500/60; // in rev/sec
8
9 //calculation:
10 //the efficiency of a generator = (output power/

```

```

    input power)*100 %
11 //The output power is the electrical output, i.e. VI
    watts. The input power to a generator is the
    mechanical power in the shaft driving the
    generator, i.e. T*w or T(2*pi*n) watts, where T
    is the torque in Nm and n is speed of rotation in
    rev/s. Hence, for a generator
12 //efficiency = V*I*100/(T*2*pi*
13 n) %
14 eff = V*I*100/(T*2*pi*n) // in Percent
15 //The input power = output power + losses
16 // hence, T*2*pi*n = V*I + losses
17 P1 = T*2*pi*n - V*I
18
19 printf("\n\n Result \n\n")
20 printf("\n (a) efficiency is %.2f percent ",eff)
21 printf("\n (b) power loss is %.0f W ",P1)

```

---

### Scilab code Exa 21.20 Example 20

```

1 //Problem 21.20: A 240 V shunt motor takes a total
    current of 30 A. If the field winding resistance
    Rf = 150 ohm and the armature resistance Ra = 0.4
    ohm. determine (a) the current in the armature,
    and (b) the back e.m.f.
2
3 //initializing the variables:
4 Rf = 150; // in Ohms
5 Ra = 0.4; // in Ohms
6 I = 30; // in Amperes
7 V = 240; // in Volts
8
9 //calculation:
10 //Field current If

```

```

11 If = V/Rf
12 //Supply current I = Ia + If
13 //Hence armature current , Ia
14 Ia = I - If
15 //Back e.m.f. E = V - Ia*Ra
16 E = V - (Ia*Ra)
17
18 printf("\n\n Result \n\n")
19 printf("\n (a) current in the armature is %.1f A ",
    Ia)
20 printf("\n (b) Back e.m.f. E is %.2f V ",E)

```

---

**Scilab code Exa 21.21** Example 21

```

1 //Problem 21.21: A 200 V, d.c. shunt-wound motor has
    an armature resistance of 0.4 ohm and at a
    certain load has an armature current of 30 A and
    runs at 1350 rev/min. If the load on the shaft of
    the motor is increased so that the armature
    current increases to 45 A, determine the speed of
    the motor, assuming the flux remains constant.
2
3 //initializing the variables:
4 Ia1 = 30; // in Amperes
5 Ia2 = 45; // in Amperes
6 Ra = 0.4; // in ohm
7 n1 = 1350/60; // in Rev/sec
8 V = 200; // in Volts
9
10 //calculation:
11 //The relationship E proportional to (Phi*n) applies
    to both generators and motors. For a motor,
12 //E = V - (Ia*Ra)
13 E1 = V - (Ia1*Ra)
14 E2 = V - (Ia2*Ra)

```

```

15 //The relationship ,  $E_1/E_2 = \Phi_1*n_1/\Phi_2*n_2$ ,
    applies to both generators and motors. Since the
    flux is constant ,  $\Phi_1 = \Phi_2$ 
16  $\Phi_2 = \Phi_1$ 
17  $n_2 = E_2*\Phi_1*n_1/(\Phi_2*E_1)$ 
18
19 printf("\n\n Result \n\n")
20 printf("\n the speed of the motor is %.2f rev/sec ",
    n2)

```

---

### Scilab code Exa 21.22 Example 22

```

1 //Problem 21.22: A 220 V, d.c. shunt-wound motor
    runs at 800 rev/min and the armature current is
    30 A. The armature circuit resistance is 0.4 ohm.
    Determine (a) the maximum value of armature
    current if the flux is suddenly reduced by 10%
    and (b) the steady state value of the armature
    current at the new value of flux , assuming the
    shaft torque of the motor remains constant.
2
3 //initializing the variables:
4 Ia1 = 30; // in Amperes
5 Ra = 0.4; // in ohm
6 n = 800/60; // in Rev/sec
7 V = 220; // in Volts
8 x= 0.1;
9
10 //calculation:
11 //For a d.c. shunt-wound motor,  $E = V - (I_a*R_a)$ ,
    Hence initial generated e.m.f.,
12  $E_1 = V - (I_{a1}*R_a)$ 
13 //The generated e.m.f. is also such that E
    proportional to  $(\Phi*n)$  so at the instant the
    flux is reduced , the speed has not had time to

```

```

        change, and
14 E = E1*(1-x)
15 //Hence, the voltage drop due to the armature
    resistance is
16 Vd = V - E
17 //The instantaneous value of the current is
18 Ia = Vd/Ra
19 //T proportional to (Phi*Ia), since the torque is
    constant,
20 //Phi1*Ia1 = Phi2*Ia2, The flux  $\phi$  is reduced by 10%
    , hence
21 Phi2 = (1-x)*Phi1
22 Ia2 = Phi1*Ia1/Phi2
23
24 printf("\n\n Result \n\n")
25 printf("\n (a)instantaneous value of the current %.0
    f A ",Ia)
26 printf("\n (b)steady state value of armature current
    , %.2f A ",Ia2)

```

---

### Scilab code Exa 21.23 Example 23

```

1 //Problem 21.23: A series motor has an armature
    resistance of 0.2 ohm and a series field
    resistance of 0.3 ohm. It is connected to a 240 V
    supply and at a particular load runs at 24 rev/s
    when drawing 15 A from the supply. (a) Determine
    the generated e.m.f. at this load. (b) Calculate
    the speed of the motor when the load is changed
    such that the current is increased to 30 A.
    Assume that this causes a doubling of the flux.
2
3 //initializing the variables:
4 Ia1 = 15; // in Amperes
5 Ia2 = 30; // in Amperes

```



```

6 Rf = 0.3; // in ohms
7 Ra = 0.2; // in ohm
8 n1 = 24; // in Rev/sec
9 V = 240; // in Volts
10 x= 2;
11
12 //calculation:
13 //generated e.m.f., E, at initial load, is given by
14 E1 = V - Ia1*(Ra + Rf)
15 //When the current is increased to 30 A, the
    generated e.m.f. is given by:
16 E2 = V - Ia2*(Ra + Rf)
17 //E proportional to (Phi*n)
18 //E1/E2 = Phi1*n1/Phi2*n2
19 Phi2 = x*Phi1
20 n2 = E2*Phi1*n1/(Phi2*E1)
21
22 printf("\n\n Result \n\n")
23 printf("\n (a)generated e.m.f., E is %.1f V ",E1)
24 printf("\n (b)speed of motor, n2, %.2f A ",n2)

```

---

#### Scilab code Exa 21.24 Example 24

```

1 //Problem 21.24: A 320 V shunt motor takes a total
    current of 80 A and runs at 1000 rev/min. If the
    iron, friction and windage losses amount to 1.5
    kW, the shunt field resistance is 40 ohm and the
    armature resistance is 0.2 ohm, determine the
    overall efficiency of the motor.
2
3 //initializing the variables:
4 I = 80; // in Amperes
5 C = 1500; // in Watt
6 Rf = 40; // in ohms
7 Ra = 0.2; // in ohm

```

```

8 n = 1000/60; // in Rev/sec
9 V = 320; // in Volts
10
11 //calculation:
12 //Field current, If
13 If = V/Rf
14 //Armature current Ia
15 Ia = I - If
16 //Efficiency =((V*I - Ia*Ia*Ra - If*V - C)/(V*I))
    *100%
17 eff = ((V*I - (Ia*Ia*Ra) - (If*V) - C)/(V*I))*100 //
    in percent
18
19 printf("\n\n Result \n\n")
20 printf("\n efficiency is %.1f", eff)

```

---

#### Scilab code Exa 21.25 Example 25

```

1 //Problem 21.25: A 250 V series motor draws a
    current of 40 A. The armature resistance is 0.15
    ohm and the field resistance is 0.05ohm .
    Determine the maximum efficiency of the motor.
2
3 //initializing the variables:
4 I = 40; // in Amperes
5 Rf = 0.05; // in ohms
6 Ra = 0.15; // in ohm
7 V = 250; // in Volts
8
9 //calculation:
10 //However for a series motor, If = 0 and the Ia*Ia*
    Ra loss needs to be I*I*(Ra + Rf)
11 //For maximum efficiency I*I*(Ra + Rf) = C
12 //Efficiency =((V*I -2*Ia*Ia*Ra)/(V*I))*100%
13 eff = ((V*I - (2*I*I*(Ra + Rf)))/(V*I))*100 // in

```

```

    percent
14
15 printf("\n\n Result \n\n")
16 printf("\n efficiency is %.1f",eff)

```

---

### Scilab code Exa 21.26 Example 26

```

1 //Problem 21.26: A 200 V d.c. motor develops a shaft
   torque of 15 Nm at 1200 rev/min. If the
   efficiency is 80%, determine the current supplied
   to the motor.
2
3 //initializing the variables:
4 T = 15; // in Nm
5 n = 1200/60; // in rev/sec
6 eff = 0.8;
7 V = 200; // in Volts
8
9 //calculation:
10 //The efficiency of a motor = (output power/input
   power)*100 %
11 //The output power of a motor is the power available
   to do work at its shaft and is given by  $T\omega$  or  $T$ 
   proportional to  $(2\pi n)$  watts, where  $T$  is the
   torque in Nm and  $n$  is the speed of rotation in
   rev/s. The input power is the electrical power in
   watts supplied to the motor, i.e.  $VI$  watts.
12 //Thus for a motor, efficiency =  $(T*2\pi*$ 
13  $n/(V*I))\%$ 
14  $I = T*2*\pi*n/(V*eff)$ 
15
16 printf("\n\n Result \n\n")
17 printf("\n current supplied , I is %.1f A",I)

```

---

**Scilab code Exa 21.27** Example 27

```
1 //Problem 21.27: A d.c. series motor drives a load
   at 30 rev/s and takes a current of 10 A when the
   supply voltage is 400 V. If the total resistance
   of the motor is 2 ohm and the iron, friction and
   windage losses amount to 300 W, determine the
   efficiency of the motor.
2
3 //initializing the variables:
4 R = 2; // in ohm
5 n = 30; // in rev/sec
6 I = 10; // in A
7 C = 300; // in Watt
8 V = 400; // in Volts
9
10 //calculation:
11 //Efficiency =((V*I - I*I*R - C)/(V*I))*100%
12 eff = ((V*I - (I*I*R) - C)/(V*I))*100 // in percent
13
14 printf("\n\n Result \n\n")
15 printf("\n efficiency is %.1f percent",eff)
```

---

**Scilab code Exa 21.28** Example 28

```
1 //Problem 21.28: A 500 V shunt motor runs at its
   normal speed of 10 rev/s when the armature
   current is 120 A. The armature resistance is 0.2
   ohm. (a) Determine the speed when the current is
   60 A and a resistance of 0.5 ohm is connected in
   series with the armature, the shunt field
   remaining constant. (b) Determine the speed when
```

the current is 60 A and the shunt field is reduced to 80% of its normal value by increasing resistance in the field circuit.

```

2
3 //initializing the variables:
4 Ia1 = 120; // in A
5 Ia2 = 60; // in A
6 Ra = 0.2; // in ohm
7 n1 = 10; // in rev/sec
8 R = 0.5; // in ohm
9 x = 0.8;
10 V = 500; // in Volts
11
12 //calculation:
13 //back e.m.f. at Ia1
14 E1 = V - Ia1*Ra
15 //at Ia2
16 E2 = V - Ia2*(Ra + R)
17 //E1/E2 = Phi1*n1/Phi2*n2
18 Phi2 = Phi1
19 n2 = Phi1*n1*E2/(Phi2*E1)
20 //Back e.m.f. when Ia2
21 E3 = V - Ia2*Ra
22 Phi3 = x*Phi1
23 n3 = Phi1*n1*E3/(Phi3*E1)
24
25 printf("\n\n Result \n\n")
26 printf("\n (a) speed n2 is %.2f rev/sec", n2)
27 printf("\n (b) speed n3 is %.2f rev/sec", n3)

```

---

#### Scilab code Exa 21.29 Example 29

```

1 //Problem 21.29: On full-load a 300 V series motor
  takes 90 A and runs at 15 rev/s. The armature
  resistance is 0.1 ohm and the series winding

```

resistance is 50 mohm. Determine the speed when developing full load torque but with a 0.2 ohm diverter in parallel with the field winding. ( Assume that the flux is proportional to the field current.)

```

2
3 //initializing the variables:
4 Ia1 = 90; // in Amperes
5 Ra = 0.1; // in ohm
6 Rse = 0.05; // in ohm
7 Rd = 0.2; // in Ohm
8 n1 = 15; // in rev/sec
9 V = 300; // in Volts
10
11 //calculation:
12 //e.m.f. E1
13 E1 = V - Ia1*(Ra + Rse)
14 //With the Rd diverter in parallel with Rse
15 //equivalent resistance , Re
16 Re = Rd*Rse/(Rd+Rse)
17 //Torque, T proprtional to Ia*Phi and for full load
    torque, Ia1*Phi1 = Ia2*Phi2
18 //Since flux is proportional to field current Phi1
    proportional to Ia1 and Phi2 Proportional to Ia2
19 I1 = (Ia1*Ia2*0.8)^0.5
20 //By current division , current I1
21 Ia2 = I1/(Rd/(Rd + Rse))
22 //Hence e.m.f. E2
23 E2 = V - Ia2*(Ra + Re)
24 //E1/E2 = Phi1*n1/Phi2*n2
25 n2 = E2*Ia1*n1/(I1*E1)
26
27 printf("\n\n Result \n\n")
28 printf("\n speed n2 is %.2f rev/sec", n2)

```

---

Scilab code Exa 21.30 Example 30

```
1 //Problem 21.30: A series motor runs at 800 rev/min
   when the voltag is 400 V and the current is 25 A.
   The armature resistance is 0.4 ohm and the
   series field resistance is 0.2 ohm. Determine the
   resistance to be connected in series to reduce
   the speed to 600 rev/min with the same current.
2
3 //initializing the variables:
4 Ia1 = 25; // in Amperes
5 Ra = 0.4; // in ohm
6 Rse = 0.2; // in ohm
7 n1 = 800/60; // in rev/sec
8 n2 = 600/60; // in rev/sec
9 V = 400; // in Volts
10
11 //calculation:
12 //e.m.f. E1
13 E1 = V - Ia1*(Ra + Rse)
14 //At n2, since the current is unchanged, the flux is
   unchanged.
15 //E1/E2 = n1/n2
16 E2 = E1*n2/n1
17 //and E2 = V - Ia1(Ra + Rse + R)
18 R = (V - E2)/Ia1 - Ra - Rse
19
20 printf("\n\n Result \n\n")
21 printf("\n Resistance is %.2f ohm", R)
```

---

# Chapter 22

## Three phase induction motors

Scilab code Exa 22.01 Example 1

```
1 //Problem 22.01: A three-phase two-pole induction
   motor is connected to a 50 Hz supply. Determine
   the synchronous speed of the motor in rev/min.
2
3 //initializing the variables:
4 f = 50; // in Hz
5 p = 2/2; // number of pairs of poles
6
7 //calculation:
8 //ns is the synchronous speed, f is the frequency in
   hertz of the supply to the stator and p is the
   number of pairs of poles.
9 ns = f/p
10 nsrpm = ns*60
11
12 printf("\n\n Result \n\n")
13 printf("\nsynchronous speed of the motor is %.0f rev
   /min", nsrpm)
```

---



### Scilab code Exa 22.02 Example 2

```
1 //Problem 22.02: A stator winding supplied from a
   three-phase 60 Hz system is required to produce a
   magnetic flux rotating at 900 rev/min. Determine
   the number of poles.
2
3 //initializing the variables:
4 f = 60; // in Hz
5 ns = 900/60; // in rev/sec
6
7 //calculation:
8 //ns is the synchronous speed, f is the frequency in
   hertz of the supply to the stator and p is the
   number of pairs of poles.
9 p = f/ns
10 np = p*2
11
12 printf("\n\n Result \n\n")
13 printf("\nnumber of poles is %.0f", np)
```

---

### Scilab code Exa 22.03 Example 3

```
1 //Problem 22.03: A three-phase 2-pole motor is to
   have a synchronous speed of 6000 rev/min.
   Calculate the frequency of the supply voltage.
2
3 //initializing the variables:
4 p = 2/2; // number of pairs of poles
5 ns = 6000/60; // in rev/sec
6
7 //calculation:
8 //ns is the synchronous speed, f is the frequency in
   hertz of the supply to the stator and p is the
   number of pairs of poles.
```

```

9 f = p*ns
10
11 printf("\n\n Result \n\n")
12 printf("\nfrequency is %.0f Hz",f)

```

---

#### Scilab code Exa 22.04 Example 4

```

1 //Problem 22.04: The stator of a 3-phase, 4-pole
   induction motor is connected to a 50 Hz supply.
   The rotor runs at 1455 rev/min at full load.
   Determine (a) the synchronous speed and (b) the
   slip at full load.
2
3 //initializing the variables:
4 p = 4/2; // number of pairs of poles
5 f = 50; // in Hz
6 nr = 1455/60; // in rev/sec
7
8 //calculation:
9 //ns is the synchronous speed, f is the frequency in
   hertz of the supply to the stator and p is the
   number of pairs of poles.
10 ns = f/p
11 //The slip, s
12 s = ((ns - nr)/ns)*100 // in percent
13
14 printf("\n\n Result \n\n")
15 printf("\n(a) synchronous speed is %.0f rev/sec",ns)
16 printf("\n(b) slip is %.0f percent",s)

```

---

#### Scilab code Exa 22.05 Example 5

```

1 //Problem 22.05: A 3-phase, 60 Hz induction motor
   has 2 poles. If the slip is 2% at a certain load,
   determine (a) the synchronous speed, (b) the
   speed of the rotor and (c) the frequency of the
   induced e.m.f. s in the rotor.
2
3 //initializing the variables:
4 p = 2/2; // number of pairs of poles
5 f = 60; // in Hz
6 s = 0.02; // slip
7
8 //calculation:
9 //ns is the synchronous speed, f is the frequency in
   hertz of the supply to the stator and p is the
   number of pairs of poles.
10 ns = f/p
11 //The the rotor runs at
12 nr = ns*(1 - s)
13 //frequency of the e.m.f. s induced in the rotor
   bars is
14 fr = ns - nr
15
16 printf("\n\n Result \n\n")
17 printf("\n(a) synchronous speed is %.0f rev/sec",ns)
18 printf("\n(b) rotor speed is %.1f rev/sec",nr)
19 printf("\n(c) frequency of the e.m.f. s induced in
   the rotor bars is is %.1f Hz",fr)

```

---

#### Scilab code Exa 22.06 Example 6

```

1 //Problem 22.06: A three-phase induction motor is
   supplied from a 50 Hz supply and runs at 1200 rev
   /min when the slip is 4%. Determine the
   synchronous speed.
2

```

```

3 //initializing the variables:
4 f = 50; // in Hz
5 nr = 1200/60; // in rev/min
6 s = 0.04; // slip
7
8 //calculation:
9 //the synchronous speed.
10 ns = nr/(1 - s)
11 nsrpm = ns*60
12 printf("\n\n Result \n\n")
13 printf("\n synchronous speed is %.0f rev/min",nsrpm)

```

---

**Scilab code Exa 22.07** Example 7

```

1 //Problem 22.07: The frequency of the supply to the
   stator of an 8- pole induction motor is 50 Hz and
   the rotor frequency is 3 Hz. Determine (a) the
   slip , and (b) the rotor speed.
2
3 //initializing the variables:
4 p = 8/2; // number of pairs of poles
5 f = 50; // in Hz
6 fr = 3; // in Hz
7
8 //calculation:
9 //ns is the synchronous speed, f is the frequency in
   hertz of the supply to the stator and p is the
   number of pairs of poles.
10 ns = f/p
11 //fr = s*f
12 s = (fr/f)
13 //the rotor speed.
14 nr = ns*(1 - s)
15 nrrpm = nr*60
16

```

```

17 printf("\n\n Result \n\n")
18 printf("\n(a) slip is %.0f percent",s*100)
19 printf("\n (b) rotor speed is %.0f rev/min",nrrpm)

```

---

### Scilab code Exa 22.08 Example 8

```

1 //Problem 22.08: The power supplied to a three-phase
   induction motor is 32 kW and the stator losses
   are 1200 W. If the slip is 5%, determine (a) the
   rotor copper loss , (b) the total mechanical power
   developed by the rotor , (c) the output power of
   the motor if friction and windage losses are 750
   W, and (d) the efficiency of the motor ,
   neglecting rotor iron loss .
2
3 //initializing the variables :
4 Psi = 32000; // in Watts
5 Psl = 1200; // in Watts
6 s = 0.05; // slip
7 Pfl = 750; // in Watts
8
9 //calculation :
10 //Input power to rotor = stator input power - stator
   losses
11 Pi = Psi - Psl
12 //slip = rotor copper loss/rotor input
13 Pl = s*Pi
14 //Total mechanical power developed by the rotor =
   rotor input power - rotor losses
15 Pr = Pi - Pl
16 //Output power of motor = power developed by the
   rotor - friction and windage losses
17 Po = Pr - Pfl
18 //Efficiency of induction motor = (output power/
   input power)*100

```

```

19 eff = (Po/Psi)*100 // in percent
20
21 printf("\n\n Result \n\n")
22 printf("\n(a) rotor copper loss is %.0f Watt",P1)
23 printf("\n(b) Total mechanical power developed by
    the rotor is %.0f W",Pr)
24 printf("\n(c) Output power of motor is %.0f Watt",Po
    )
25 printf("\n(d) efficiency of induction motor is %.2f
    percent",eff)

```

---

#### Scilab code Exa 22.09 Example 9

```

1 //Problem 22.09: The speed of the induction motor of
    Problem 22.08 is reduced to 35% of its
    synchronous speed by using external rotor
    resistance. If the torque and stator losses are
    unchanged, determine (a) the rotor copper loss ,
    and (b) the efficiency of the motor.
2
3 //initializing the variables:
4 Psi = 32000; // in Watts
5 Psl = 1200; // in Watts
6 Pfl = 750; // in Watts
7 x = 0.35;
8
9 //calculation:
10 nr = x*ns
11 //The slip , s
12 s = ((ns - nr)/ns)
13 //Input power to rotor = stator input power - stator
    losses
14 Pi = Psi - Psl
15 //slip = rotor copper loss/rotor input
16 P1 = s*Pi

```

```

17 //Total mechanical power developed by the rotor =
    rotor input power - rotor losses
18 Pr = Pi - P1
19 //Output power of motor = power developed by the
    rotor - friction and windage losses
20 Po = Pr - Pfl
21 //Efficiency of induction motor = (output power/
    input power)*100
22 eff = (Po/Psi)*100 // in percent
23
24 printf("\n\n Result \n\n")
25 printf("\n(a) rotor copper loss is %.0f Watt",P1)
26 printf("\n(b) efficiency of induction motor is %.2f
    percent",eff)

```

---

#### Scilab code Exa 22.10 Example 10

```

1 //Problem 22.10: A 415 V, three-phase, 50 Hz, 4 pole
    , star-connected induction motor runs at 24 rev/s
    on full load. The rotor resistance and reactance
    per phase are 0.35 ohm and 3.5 ohm respectively,
    and the effective rotor-stator turns ratio is
    0.85:1. Calculate (a) the synchronous speed, (b)
    the slip, (c) the full load torque, (d) the power
    output if mechanical losses amount to 770 W, (e)
    the maximum torque, (f) the speed at which
    maximum torque occurs and (g) the starting torque
    .
2
3 //initializing the variables:
4 V = 415; // in Volts
5 f = 50 ; // in Hz
6 nr = 24; // in rev/sec
7 p = 4/2; // no. of pole pairs
8 R2 = 0.35; // in Ohms

```

```

 9 X2 = 3.5; // in Ohms
10 tr = 0.85; // turn ratio N2/N1
11 P1 = 770; // in Watt
12 m = 3; // no. of phases
13
14 //calculation:
15 //ns is the synchronous speed, f is the frequency in
    hertz of the supply to the stator and p is the
    number of pairs of poles.
16 ns = f/p
17 //The slip, s
18 s = ((ns - nr)/ns)*100 // in percent
19 //Phase voltage, E1 = V/(3^0.5)
20 E1 = V/(3^0.5)
21 //Full load torque
22 T = [m*(tr^2)/(2*pi*ns)]*[(s/100)*E1*E1*R2/(R2*R2 +
    (X2*(s/100))^2)]
23 //Output power, including friction losses
24 Pm = 2*pi*nr*T
25 //power output
26 Po = Pm - P1
27 //Maximum torque occurs when R2 = Xr = 0.35 ohm
28 //Slip
29 sm = R2/X2
30 //maximum torque, Tm
31 Tm = [m*(tr^2)/(2*pi*ns)]*[sm*E1*E1*R2/(R2*R2 + (X2
    *sm)^2)]
32 //speed at which maximum torque occurs
33 nrm = ns*(1 - sm)
34 nrmrpm = nrm*60
35 //At the start, i.e., at standstill, slip, s=1
36 ss = 1
37 //starting torque
38 Ts = [m*(tr^2)/(2*pi*ns)]*[ss*E1*E1*R2/(R2*R2 + (X2
    *ss)^2)]
39
40 printf("\n\n Result \n\n")
41 printf("\n(a) Synchronous speed is %.0f rev/sec",ns)

```



```

42 printf("\n(b) Slip is %.0f percent",s)
43 printf("\n(c) Full load torque is %.2f Nm",T)
44 printf("\n(d) power output is %.2E W",Po)
45 printf("\n(e) maximum torque is %.2f Nm",Tm)
46 printf("\n(f) speed at which maximum torque occurs is
    %.0f rev/min",nrmpm)
47 printf("\n(g) starting torque is %.2f Nm",Ts)

```

---

### Scilab code Exa 22.11 Example 11

```

1 //Problem 22.11: Determine for the induction motor
  in problem 22.10 at full load, (a) the rotor
  current, (b) the rotor copper loss, and (c) the
  starting current.
2
3 //initializing the variables:
4 V = 415; // in Volts
5 f = 50 ; // in Hz
6 nr = 24; // in rev/sec
7 p = 4/2; // no. of pole pairs
8 R2 = 0.35; // in Ohms
9 X2 = 3.5; // in Ohms
10 tr = 0.85; // turn ratio N2/N1
11 m = 3; // no. of phases
12
13 //calculation:
14 //ns is the synchronous speed, f is the frequency in
  hertz of the supply to the stator and p is the
  number of pairs of poles.
15 ns = f/p
16 //The slip, s
17 s = ((ns - nr)/ns)*100 // in percent
18 //Phase voltage, E1 = V/(3^0.5)
19 E1 = V/(3^0.5)
20 //rotor current,

```

```

21 Ir = (s/100)*E1*tr/((R2^2 + (X2*(s/100))^2)^0.5)
22 //Rotor copper loss
23 Pcl = m*R2*(Ir^2)
24 //starting current ,
25 ss =1
26 I2 = ss*tr*E1/((R2^2 + (X2*ss)^2)^0.5)
27
28 printf("\n\n Result \n\n")
29 printf("\n(a)rotor current is %.2f A",Ir)
30 printf("\n(b)Total copper loss is %.2f W",Pcl)
31 printf("\n(c)starting current is %.2f A",I2)

```

---

#### Scilab code Exa 22.12 Example 12

```

1 //Problem 22.12: For the induction motor in problems
   22.10 and 22.11, if the stator losses are 650 W,
   determine (a) the power input at full load , (b)
   the efficiency of the motor at full load and (c)
   the current taken from the supply at full load ,
   if the motor runs at a power factor of 0.87
   lagging.
2
3 //initializing the variables:
4 V = 415; // in Volts
5 Psl = 650; // in Watt
6 pf = 0.87; // power factor
7
8 //calculation:
9 Pm = 11770; // watts from part (d), Problem 22.10
10 Pcl = 490.35; // watts, Rotor copper loss , from part
   (b), Problem 22.11
11 //Stator input power
12 P1 = Pm + Pcl + Psl
13 Po = 11000 // watts , Net power output , from part (d)
   , Problem 22.10

```

```

14 //efficiency = (output/input) *100
15 eff = (Po/P1)*100 // in percent
16 //Power input , P1 = (3^0.5)*VL*IL*cos(phi)
17 // pf = cos(phi)
18 //supply current , IL
19 I = P1/((3^0.5)*V*pf)
20
21 printf("\n\n Result \n\n")
22 printf("\n(a)Stator input power is %.2E W",P1)
23 printf("\n(b) efficiency is %.2f percent",eff)
24 printf("\n(c) supply current is %.2f A",I)

```

---

### Scilab code Exa 22.13 Example 13

```

1 //Problem 22.13: For the induction motor of Problems
   22.10 to 22.12, determine the resistance of the
   rotor winding required for maximum starting
   torque.
2
3 //initializing the variables:
4 V = 415; // in Volts
5 f = 50 ; // in Hz
6 nr = 24; // in rev/sec
7 p = 4/2; // no. of pole pairs
8 R2 = 0.35; // in Ohms
9 X2 = 3.5; // in Ohms
10
11 //calculation:
12 //At the moment of starting , slip ,
13 s = 1
14 //Maximum torque occurs when rotor reactance equals
   rotor resistance
15 //for maximum torque
16 R2 = s*X2
17

```

```
18 printf("\n\n Result \n\n")
19 printf("\nresistance of the rotor is %.1f Ohm",R2)
```

---

# Chapter 23

## Revision of complex numbers

Scilab code Exa 23.01 Example 1

```
1 //Problem 23.01: In an electrical circuit the total
  impedance ZT is given by  $ZT = (Z1*Z2/(Z1 + Z2)) + Z3$ .
  Determine ZT in (a + jb) form, correct to
  two decimal places, when  $Z1 = 5 - j3$ ,  $Z2 = 4 - j7$ 
  and  $Z3 = 3.9 - j6.7$ .
2
3 //initializing the variables:
4 Z1 = 5 - 3*i;
5 Z2 = 4 + 7*i;
6 Z3 = 3.9 - 6.7*i;
7
8 //calculation:
9 ZT = (Z1*Z2/(Z1 + Z2)) + Z3
10 y = imag(ZT)
11 x = real(ZT)
12
13 printf("\n\n Result \n\n")
14 printf("\n ZT is %.2f + (%.2f)i", x,y)
```

---

### Scilab code Exa 23.02 Example 2

```
1 //Problem 23.02: Given  $Z1 = 3 + i4$ ,  $Z2 = 2 - i5$ 
   determine in cartesian form correct to three
   decimal places:
2 //(a)  $1/Z1$ , (b)  $1/Z2$ , (c)  $1/Z1 + 1/Z2$ , (d)  $1/(1/Z1 +$ 
    $1/Z2)$ 
3
4 //initializing the variables:
5 Z1 = 3 + 4*i;
6 Z2 = 2 - 5*i;
7
8 //calculation:
9 za = 1/Z1
10 zb = 1/Z2
11 zc = za + zb
12 zd = 1/zc
13 zax = real(za)
14 zay = imag(za)
15 zbx = real(zb)
16 zby = imag(zb)
17 zcx = real(zc)
18 zcy = imag(zc)
19 zdx = real(zd)
20 zdy = imag(zd)
21
22 printf("\n\n Result \n\n")
23 printf("\n (a)  $1/Z1$  is %.3f + (%.3f)i", zax, zay)
24 printf("\n (b)  $1/Z2$  is %.3f + (%.3f)i", zbx, zby)
25 printf("\n (c)  $1/Z1 + 1/Z2$  is %.3f + (%.3f)i", zcx,
   zcy)
26 printf("\n (d)  $1/(1/Z1 + 1/Z2)$  is %.3f + (%.3f)i",
   zdx, zdy)
```

---

### Scilab code Exa 23.03 Example 3

```

1 //Problem 23.03: Solve the following complex
  equations:
2 //(a)  $3(a + ib) = 9 - i2$ 
3 //(b)  $(2+i)(-2+i) = x+iy$ 
4 //(c)  $(a-i(2b))+(b-i3a) = 5+i2$ 
5
6 //initializing the variables:
7 Z1 = 9 - 2*i;
8 Z2 = 2 + 1*i;
9 Z3 = -2 + 1*i;
10 Z4 = 5 + 2*i;
11
12 //calculation:
13 za = Z1/3
14 zb = Z2*Z3
15 zca = (2*real(Z4) + imag(Z4))/-1
16 zcb = real(Z4) - zca
17 zaa = real(za)
18 zab = imag(za)
19 zbx = real(zb)
20 zby = imag(zb)
21
22 printf("\n\n Result \n\n")
23 printf("\n (a) a and b are %.0f and %.2f resp.", zaa,
  zab)
24 printf("\n (b) x and y are %.0f and %.0f resp.", zbx,
  zby)
25 printf("\n (c) a and b are %.0f and %.0f resp.", zca,
  zcb)

```

---

#### Scilab code Exa 23.05 Example 5

```

1 //Problem 23.05: Convert  $(5, -132)$  into  $a + ib$  form
  correct to four significant figures.
2

```

```

3 //initializing the variables:
4 r = 5; // magnitude
5 theta = -132; // in degree
6
7 //calculation:
8 x = r*sin(theta*pi/180)
9 y = r*cos(theta*pi/180)
10 z = x+i*y
11
12 printf("\n\n Result \n\n")
13 printf("\n Z is %.3f + (%.3f)i", x,y)

```

---

#### Scilab code Exa 23.06 Example 6

```

1 //Problem 23.06: Two impedances in an electrical
   network are given by  $Z1 = (4.7, 35)$  and  $Z2 =$ 
    $(7.3, -48)$  . Determine in polar form the total
   impedance  $ZT$  given that  $ZT = Z1*Z2/(Z1 + Z2)$ 
2
3 //initializing the variables:
4 r1 = 4.7; // magnitude
5 theta1 = 35; // in degree
6 r2 = 7.3; // magnitude
7 theta2 = -48; // in degree
8
9 //calculation:
10 x1 = r1*cos(theta1*pi/180)
11 y1 = r1*sin(theta1*pi/180)
12 z1 = x1+i*y1
13 x2 = r2*cos(theta2*pi/180)
14 y2 = r2*sin(theta2*pi/180)
15 z2 = x2+i*y2
16 z3 = z1*z2/(z1 + z2)
17 x3 = real(z3)
18 y3 = imag(z3)

```



```

19 r3 = (x3^2 + y3^2)^0.5
20 theta3 = atan(y3/x3)*180/%pi
21
22 printf("\n\n Result \n\n")
23 printf("\n ZT is (%.2 f/_%.2 f )", r3,theta3)

```

---

### Scilab code Exa 23.07 Example 7

```

1 //Problem 23.07: Determine  $(-2 + i3)^5$  in polar and
  in cartesian form.
2
3 //initializing the variables:
4 z = -2 + %i*3;
5
6 //calculation:
7 zc = z^5
8 x = real(zc)
9 y = imag(zc)
10 r = (x^2 + y^2)^0.5
11 theta = atan(y/x)*180/%pi
12 if ((x<0)&(y<0)) then
13     theta = theta -180;
14 elseif ((x<0)&(y>0)) then
15     theta = theta +180;
16 end
17
18 printf("\n\n Result \n\n")
19 printf("\n Z is %.0 f + (%.0 f)i", x,y)
20 printf("\n ZT is (%.1 f/_%.2 f )", r,theta)

```

---

### Scilab code Exa 23.08 Example 8

```

1 //Problem 23.08: Determine the two square roots of
   the complex number (12 + i5) in cartesian and
   polar form, correct to three significant figures.
   Show the roots on an Argand diagram.
2
3 //initializing the variables:
4 z = 12 + %i*5;
5
6 //calculation:
7 x = real(z)
8 y = imag(z)
9 r = (x^2 + y^2)^0.5
10 theta1 = atan(y/x)*180/%pi
11 if ((x<0)&(y<0)) then
12     theta1 = theta1 -180;
13 elseif ((x<0)&(y>0)) then
14     theta1 = theta1 +180;
15 end
16 theta2 = theta1 + 360
17 rtheta1 = theta1/2
18 rtheta2 = theta2/2
19 if (rtheta2 > 180) then
20     rtheta2 = rtheta2 -360;
21 elseif ((x<0)&(y>0)) then
22     rtheta2 = rtheta2 +360;
23 end
24 rr = r^0.5
25 x1 = rr*cos(rtheta1*%pi/180)
26 y1 = rr*sin(rtheta1*%pi/180)
27 z1 = x1 + %i*y1
28 x2 = rr*cos(rtheta2*%pi/180)
29 y2 = rr*sin(rtheta2*%pi/180)
30 z2 = x2 + %i*y2
31
32 printf("\n\n Result \n\n")
33 printf("\n two roots are (%.2f + (%.2f)i) and (%.2f
   + (%.2f)i)", x1,y1,x2,y2)
34 printf("\n two roots are (%.1f/-%.2f ) and (%.1f/-%.2f)

```

.2 f )", rr,rtheta1, rr,rtheta2)

---

# Chapter 24

## Application of complex numbers to series ac circuits

Scilab code Exa 24.01 Example 1

```
1 //Problem 24.01: Determine the values of the
   resistance and the series-connected inductance or
   capacitance for each of the following impedances
   :(a)(12 + i5)ohm (b)-i40 ohm (c)30/_60 ohm (d)
   2.20 x 10^6 /_-30 ohm. Assume for each a
   frequency of 50 Hz.
2
3 //initializing the variables:
4 z1 = 12 + %i*5;
5 z2 = -40*%i;
6 r3 = 30;
7 theta3 = 60; // in degrees
8 r4 = 2.20E6;
9 theta4 = -30; // in degrees
10 f = 50; // in Hz
11
12 //calculation:
13 //for an R L series circuit , impedance
14 // Z = R + iXL
```

```

15 Ra = real(z1)
16 XLa = imag(z1)
17 La = XLa/(2*%pi*f)
18 //for a purely capacitive circuit , impedance Z = -
    iXc
19 Xcb = abs(imag(z2))
20 Cb = 1/(2*%pi*f*Xcb)
21 z3 = r3*cos(theta3*%pi/180) + %i*(r3*sin(theta3*%pi
    /180))
22 Rc = real(z3)
23 XLc = imag(z3)
24 Lc = XLc/(2*%pi*f)
25 z4 = r4*cos(theta4*%pi/180) + %i*(r4*sin(theta4*%pi
    /180))
26 Rd = real(z4)
27 Xcd = abs(imag(z4))
28 Cd = 1/(2*%pi*f*Xcd)
29
30 printf("\n\n Result \n\n")
31 printf("\n (a)an impedance (12 + i5)ohm represents a
    resistance of %.0f ohm in series with an
    inductance of %.2E", Ra,La)
32 printf("\n (b)an impedance -i40 ohm represents a
    pure capacitor of capacitance %.2E", Cb)
33 printf("\n (c)an impedance 30/_60 ohm represents a
    resistance of %.0f ohm in series with an
    inductance of %.2E", Rc,Lc)
34 printf("\n (d)an impedance 2.20 x 10^6 /_-30 ohm
    represents a resistance of %.2E ohm in series
    with a capacitor of capacitance %.2E",Rd, Cd)

```

---

#### Scilab code Exa 24.02 Example 2

```

1 //Problem 24.02: Determine , in polar and rectangular
    forms , the current flowing in an inductor of

```

```

    negligible resistance and inductance 159.2 mH
    when it is connected to a 250 V, 50 Hz supply.
2
3 //initializing the variables:
4 L = 0.1592 ; // in Henry
5 V = 250; // in Volts
6 f = 50; // in Hz
7 R = 0; // in ohms
8
9 //calculation:
10 //for an R L series circuit , impedance
11 // Z = R + iXL
12 XL = 2*%pi*f*L
13 Z = R + %i*XL
14 I = V/Z
15 x = real(I)
16 y = imag(I)
17 r = (x^2 + y^2)^0.5
18 if ((x==0)&(y<0)) then
19     theta = -90
20 elseif ((x==0)&(y>0)) then
21     theta = +90
22 else
23     theta = atan(y/x)*180/%pi
24 end
25
26 printf("\n\n Result \n\n")
27 printf("\n current is (%.0f/_.%.0f ) A", r, theta)

```

---

### Scilab code Exa 24.03 Example 3

```

1 //Problem 24.03: A 3 F capacitor is connected to a
  supply of frequency 1 kHz and a current of 2.83/
  _90 A flows. Determine the value of the supply
  p.d.

```

```

2
3 //initializing the variables:
4 C = 3E-6 ; // in farad
5 f = 1000; // in Hz
6 ri = 2.83;
7 thetai = 90; // in degrees
8
9 //calculation:
10 //Capacitive reactance Xc
11 Xc = 1/(2*%pi*f*C)
12 // circuit impedance Z
13 Z = -1*%i*Xc
14 I = ri*cos(thetai*%pi/180) + %i*ri*sin(thetai*%pi
    /180)
15 V = I*Z
16 x = real(V)
17 y = imag(V)
18
19 printf("\n\n Result \n\n")
20 printf("\n supply p.d. is %.0f + (%.0f) V", x,y)

```

---

#### Scilab code Exa 24.04 Example 4

```

1 //Problem 24.04: The impedance of an electrical
    circuit is  $(30 - i50)$  ohms. Determine (a) the
    resistance, (b) the capacitance, (c) the modulus
    of the impedance, and (d) the current flowing and
    its phase angle, when the circuit is connected
    to a 240 V, 50 Hz supply.
2
3 //initializing the variables:
4 V = 240; // in Volts
5 f = 50; // in Hz
6 Z = 30 - %i*50;
7

```

```

8 //calculation :
9 //Since impedance Z = 30 - i50 ,
10 //resistance
11 R = real(Z)
12 //capacitive reactance
13 Xc = abs(imag(Z))
14 //capacitance
15 C = 1/(2*%pi*f*Xc)
16 //modulus of impedance
17 modZ = (R^2 + Xc^2)^0.5
18 I = V/Z
19 x = real(I)
20 y = imag(I)
21 r = (x^2 + y^2)^0.5
22 if ((x==0)&(y<0)) then
23     theta = -90
24 elseif ((x==0)&(y>0)) then
25     theta = +90
26 else
27     theta = atan(y/x)*180/%pi
28 end
29
30 printf("\n\n Result \n\n")
31 printf("\n (a)resistance is %.0f ohm", R)
32 printf("\n (b)capacitance is %.2E Farad", C)
33 printf("\n (c)modulus of impedance is %.2f ohm",
    modZ)
34 printf("\n (d)current flowing and its phase angle is
    (%.2f/-.2f ) A", r, theta)

```

---

#### Scilab code Exa 24.05 Example 5

```

1 //Problem 24.05: A 200 V, 50 Hz supply is connected
  across a coil of negligible resistance and
  inductance 0.15 H connected in series with a 32

```



ohm resistor. Determine (a) the impedance of the circuit, (b) the current and circuit phase angle, (c) the p.d. across the 32 ohm resistor, and (d) the p.d. across the coil.

```

2
3 //initializing the variables:
4 V = 200; // in Volts
5 f = 50; // in Hz
6 R = 32; // in ohms
7 L = 0.15; // in Henry
8
9 //calculation:
10 //Inductive reactance XL
11 XL = 2*%pi*f*L
12 //impedance, Z
13 Z = R + %i*XL
14 //Current I
15 I = V/Z
16 xi = real(I)
17 yi = imag(I)
18 ri = (xi^2 + yi^2)^0.5
19 if ((xi==0)&(yi<0)) then
20     thetai = -90
21 elseif ((xi==0)&(yi>0)) then
22     thetai = +90
23 else
24     thetai = atan(yi/xi)*180/%pi
25 end
26 //P.d. across the resistor
27 VR = I*R
28 xr = real(VR)
29 yr = imag(VR)
30 rr = (xr^2 + yr^2)^0.5
31 thetar = atan(yr/xr)*180/%pi
32 //P.d. across the coil, VL
33 VL = I*%i*XL
34 x1 = real(VL)
35 y1 = imag(VL)

```

```

36 r1 = (x1^2 + y1^2)^0.5
37 thetai = atan(y1/x1)*180/%pi
38
39 printf("\n\n Result \n\n")
40 printf("\n (a)impedance is %.0f + (%.1f)i ohm", real
    (Z), imag(Z))
41 printf("\n (b)current flowing and its phase angle is
    (%.2f/-.%.2f ) A", ri, thetai)
42 printf("\n (c)P.d. across the resistor is (%.2f/-.%.2
    f ) V", rr, thetar)
43 printf("\n (d)P.d. across the coil, VL is (%.2f/-.%.2
    f ) V", r1, thetai)

```

---

#### Scilab code Exa 24.06 Example 6

```

1 //Problem 24.06: Determine the value of impedance if
    a current of (7+i16)A flows in a circuit when
    the supply voltage is (120+i200)V. If the
    frequency of the supply is 5 MHz, determine the
    value of the components forming the series
    circuit.
2
3 //initializing the variables:
4 V = 120 + %i*200; // in Volts
5 f = 5E6; // in Hz
6 I = 7 + %i*16; // in amperes
7
8 //calculation:
9 //impedance, Z
10 Z = V/I
11 R = real(Z)
12 X = imag(Z)
13 if ((R>0)&(X<0)) then
14     printf("\n\n Result \n\n")
15     C = -1/(2*%pi*f*X)

```

```

16     printf("\n The series circuit thus consists of a
           resistor of resistance %.2f ohm and a
           capacitor of capacitance %.2E Farad\n",R,C)
17 elseif ((R>0)&(X>0)) then
18     printf("\n\n Result \n\n")
19     L = 2*pi*f*X
20     printf("\n The series circuit thus consists of a
           resistor of resistance %.2f ohm and a
           inductor of insuctance %.2E Henry\n",R,L)
21 end

```

---

#### Scilab code Exa 24.07 Example 7

```

1 //Problem 24.07: For the circuit shown in Figure
   24.11, determine the value of impedance Z2.
2
3 //initializing the variables:
4 rv = 70; // in volts
5 thetav = 30; // in degrees
6 ri = 3.5; // in amperes
7 thetai = -20; // in degrees
8 //z1 consist of two resistance
9 R1 = 4.36; // in ohms
10 R2 = -2.1*i; // in ohms
11
12 //calculation:
13 V = rv*cos(thetav*pi/180) + %i*rv*sin(thetav*pi
   /180)
14 I = ri*cos(thetai*pi/180) + %i*ri*sin(thetai*pi
   /180)
15 //impedance, Z
16 Z = V/I
17 //Total impedance Z = z1 + z2
18 Z1 = R1 + R2
19 Z2 = Z - Z1

```

```

20 x = real(Z2)
21 y = imag(Z2)
22
23 printf("\n\n Result \n\n")
24 printf("\n impedance Z2 is %.2f + (%.2f) ohm\n",x,y)

```

---

#### Scilab code Exa 24.08 Example 8

```

1 //Problem 24.08: A circuit comprises a resistance of
  90 ohm in series with an inductor of inductive
  reactance 150 ohm. If the supply current is (1.35/
  -0 )A, determine (a) the supply voltage , (b) the
  voltage across the 90 ohm resistance , (c) the
  voltage across the inductance , and (d) the
  circuit phase angle. Draw the phasor diagram.
2
3 //initializing the variables :
4 R = 90; // in ohms
5 XL = 150; // in ohms
6 ri = 1.35; // in amperes
7 thetai = 0; // in degrees
8
9 //calculation :
10 I = ri*cos(thetai*pi/180) + %i*ri*sin(thetai*pi
    /180)
11 //Circuit impedance Z
12 Z = R + %i*XL
13 //Supply voltage , V
14 V = I*Z
15 //Voltage across 90 ohm resistor
16 VR = real(V)
17 //Voltage across inductance , VL
18 VL = imag(V)
19 xv = real(V)
20 yv = imag(V)

```

```

21 rv = (xv^2 + yv^2)^0.5
22 thetav = atan(yv/xv)*180/%pi
23 phi = thetav - thetai
24
25 printf("\n\n Result \n\n")
26 printf("\n (a) Supply voltage , V is %.2f + (%.2f)i V"
, xv, yv)
27 printf("\n (b) Voltage across 90 ohm resistor , VR is
%.2f V", VR)
28 printf("\n (c) Voltage across inductance , VL is %.2f
V", VL)
29 printf("\n (d) Circuit phase angle is %.2f ", phi)

```

---

#### Scilab code Exa 24.09 Example 9

```

1 //Problem 24.09: A coil of resistance 25 ohm and
inductance 20 mH has an alternating voltage given
by  $v = 282.8\sin(628.4t + \pi/3)$  volts applied
across it. Determine (a) the rms value of voltage
(in polar form), (b) the circuit impedance, (c)
the rms current flowing, and (d) the circuit
phase angle.
2
3 //initializing the variables:
4 R = 25; // in ohms
5 L = 0.02; // in henry
6 Vm = 282.8; // in volts
7 w = 628.4; // in rad/sec
8 phiv = %pi/3; // phase angle
9
10 //calculation:
11 //rms voltage
12 Vrms = 0.707*Vm*cos(phiv) + %i*0.707*Vm*sin(phiv)
13 //frequency
14 f = w/(2*%pi)

```

```

15 //Inductive reactance XL
16 XL = 2*%pi*f*L
17 //Circuit impedance Z
18 Z = R + %i*XL
19 //Rms current
20 Irms = Vrms/Z
21 phii = atan(imag(Irms)/real(Irms))*180/%pi
22 phi = phiv*180/%pi - phii
23
24 printf("\n\n Result \n\n")
25 printf("\n (a)the rms value of voltage is %.2f + (%
    .2f)i V ",real(Vrms), imag(Vrms))
26 printf("\n (b)the circuit impedance is %.2f + (%.2f)
    i ohm ",R, XL)
27 printf("\n (c)the rms current flowing is %.2f + (%.2
    f)i A ",real(Irms), imag(Irms))
28 printf("\n (d)Circuit phase angle is %.2f ",phi)

```

---

#### Scilab code Exa 24.10 Example 10

```

1 //Problem 24.10: A 240 V, 50 Hz voltage is applied
    across a series circuit comprising a coil of
    resistance 12 ohm and inductance 0.10 H, and 120
    F capacitor. Determine the current flowing in
    the circuit.
2
3 //initializing the variables:
4 R = 12; // in ohms
5 L = 0.10; // in henry
6 C = 120E-6; // in Farads
7 f = 50; // in Hz
8 V = 240; // in volts
9
10 //calculation:
11 //Inductive reactance, XL

```

```

12 XL = 2*%pi*f*L
13 //Capacitive reactance , Xc
14 Xc = 1/(2*%pi*f*C)
15 //Circuit impedance Z
16 Z = R + %i*(XL - Xc)
17 I = V/Z
18 phii = atan(imag(I)/real(I))*180/%pi
19 phiv = 0 // in degrees
20 phi = phiv - phii
21
22 printf("\n\n Result \n\n")
23 printf("\n the current flowing is %.2f + (%.2f)i A\n
      ",real(I), imag(I))
24 printf("and Circuit phase angle is %.2f \n",phi)

```

---

### Scilab code Exa 24.11 Example 11

```

1 //Problem 24.11:A coil of resistance R ohms and
  inductance L henrys is connected in series with a
  50 F capacitor. If the supply voltage is 225 V
  at 50 Hz and the current flowing in the circuit
  is 1.56/−30 A, determine the values of R and L
  . Determine also the voltage across the coil and
  the voltage across the capacitor.
2
3 //initializing the variables :
4 C = 50E-6; // in Farads
5 f = 50; // in Hz
6 V = 225; // in volts
7 ri = 1.5; // in Amperes
8 thetai = -30; // in degrees
9
10 //calculation :
11 I = ri*cos(thetai*%pi/180) + %i*ri*sin(thetai*%pi
      /180)

```

```

12 //Capacitive reactance , Xc
13 Xc = 1/(2*%pi*f*C)
14 //Circuit impedance Z
15 Z = V/I
16 R = real(Z)
17 XL = imag(Z) + Xc
18 //inductance L
19 L = XL/(2*%pi*f)
20 //Voltage across coil
21 Zcoil = R + %i*XL
22 Vcoil = I*Zcoil
23 //Voltage across capacitor ,
24 Vc = -1*I*Xc*%i
25
26 printf("\n\n Result \n\n")
27 printf("\n (a)resistance is %.2f ohm and inductance
    is %.2f H ",R, L)
28 printf("\n (b)voltage across the coil is %.2f + (%.2
    f)i V ",real(Vcoil), imag(Vcoil))
29 printf("\n (c)voltage across the capacitor is %.2f +
    (%.2f)i V ",real(Vc), imag(Vc))

```

---

#### Scilab code Exa 24.12 Example 12

```

1 //Problem 24.12: For the circuit shown in Figure
    24.17, determine the values of voltages V1 and V2
    if the supply frequency is 4 kHz. Determine also
    the value of the supply voltage V and the
    circuit phase angle. Draw the phasor diagram.
2
3 //initializing the variables:
4 C = 2.653E-6; // in Farads
5 R1 = 8; // in ohms
6 R2 = 5; // in ohms
7 L = 0.477E-3; // in Henry

```



```

8 f = 4000; // in Hz
9 ri = 6; // in Amperes
10 thetai = 0; // in degrees
11
12 //calculation :
13 I = ri*cos(thetai*pi/180) + %i*ri*sin(thetai*pi
    /180)
14 //Capacitive reactance , Xc
15 Xc = 1/(2*pi*f*C)
16 //impedance Z1
17 Z1 = R1 - %i*Xc
18 //inductive reactance XL
19 XL = 2*pi*f*L
20 //impedance Z2,
21 Z2 = R2 + %i*XL
22 //voltage V1
23 V1 = I*Z1
24 //voltage V2
25 V2 = I*Z2
26 //Supply voltage , V
27 V = V1 + V2
28 phiv = atan(imag(V)/real(V))*180/%pi
29 phi = phiv - thetai
30
31 printf("\n\n Result \n\n")
32 printf("\n supply voltage is %.2f + (%.2f)i V\n",
    real(V), imag(V))
33 printf("and Circuit phase angle is %.2 f \n",phi)

```

---

# Chapter 25

## Application of complex numbers to parallel ac networks

Scilab code Exa 25.01 Example 1

```
1 //Problem 25.01: Determine the admittance ,
   conductance and susceptance of the following
   impedances: (a)-i5 ohm, (b)25+i40 ohm, (c)3-i2
   ohm, (d)50/_40 ohm .
2
3 //initializing the variables:
4 Z1 = 0 - %i*5; // in ohms
5 Z2 = 25 + %i*40; // in ohms
6 Z3 = 3 - %i*2; // in ohms
7 r4 = 50; // in ohms
8 theta4 = 40; // in degrees
9
10 //calculation:
11 //admittance Y
12 Y1 = 1/Z1
13 //conductance , G
14 G1 = real(Y1)
15 //Susceptance , Bc
16 Bc1 = abs(imag(Y1))
```

```

17 //admittance Y
18 Y2 = 1/Z2
19 //conductance , G
20 G2 = real(Y2)
21 //Susceptance , Bc
22 Bc2 = abs(imag(Y2))
23 //admittance Y
24 Y3 = 1/Z3
25 //conductance , G
26 G3 = real(Y3)
27 //Susceptance , Bc
28 Bc3 = abs(imag(Y3))
29 Z4 = r4*cos(theta4*pi/180) + %i*r4*sin(theta4*pi
    /180)
30 //admittance Y
31 Y4 = 1/Z4
32 //conductance , G
33 G4 = real(Y4)
34 //Susceptance , Bc
35 Bc4 = abs(imag(Y4))
36
37 printf("\n\n Result \n\n")
38 printf("\n (a)admittance Y is (%.0f + (%.1f)i) S,
    conductance , G is %.0f S, susceptance ,Bc is %.1f
    S ",real(Y1), imag(Y1),G1,Bc1)
39 printf("\n (b)admittance Y is (%.4f + (%.4f)i) S,
    conductance , G is %.4f S, susceptance ,Bc is %.4f
    S ",real(Y2), imag(Y2),G2, Bc2)
40 printf("\n (c)admittance Y is (%.3f + (%.3f)i) S,
    conductance , G is %.3f S, susceptance ,Bc is %.3f
    S ",real(Y3), imag(Y3),G3,Bc3)
41 printf("\n (d)admittance Y is (%.4f + (%.4f)i) S,
    conductance , G is %.4f S, susceptance ,Bc is %.4f
    S ",real(Y4), imag(Y4),G4,Bc4)

```

---

### Scilab code Exa 25.02 Example 2

```
1 //Problem 25.02: Determine expressions for the
   impedance of the following admittances: (a)  $0.004/$ 
    $-30^\circ$  S (b)  $(0.001 - i0.002)$  S (c)  $(0.05 + i0.08)$  S
2
3 //initializing the variables:
4 Y2 = 0.001 - %i*0.002; // in S
5 Y3 = 0.05 + %i*0.08; // in S
6 r1 = 0.004; // in S
7 theta1 = 30; // in degrees
8
9 //calculation:
10 //impedance, Z
11 Z2 = 1/Y2
12 Z3 = 1/Y3
13 Y1 = r1*cos(theta1*pi/180) + %i*r1*sin(theta1*pi
   /180)
14 Z1 = 1/Y1
15
16 printf("\n\n Result \n\n")
17 printf("\n (a) Impedance, Z is (%.1f + (%.0f)i) ohm ",
   real(Z1), imag(Z1))
18 printf("\n (b) Impedance, Z is (%.0f + (%.0f)i) ohm ",
   real(Z2), imag(Z2))
19 printf("\n (c) Impedance, Z is (%.2f + (%.2f)i) ohm ",
   real(Z3), imag(Z3))
```

---

### Scilab code Exa 25.03 Example 3

```
1 //Problem 25.03: The admittance of a circuit is
    $(0.040 + i0.025)$  S. Determine the values of the
   resistance and the capacitive reactance of the
   circuit if they are connected (a) in parallel, (b
   ) in series. Draw the phasor diagram for each of
```

```

        the circuits.
2
3 //initializing the variables:
4 Y = 0.040 - %i*0.025; // in S
5
6 //calculation:
7 //impedance, Z
8 Z = 1/Y
9 //conductance, G
10 G = real(Y)
11 //Susceptance, Bc
12 Bc = abs(imag(Y))
13 //parallrl
14 //resistance, R
15 Rp = 1/G
16 //capacitive reactance
17 Xcp = 1/Bc
18 //series
19 //resistance, R
20 Rs = real(Z)
21 //capacitive reactance
22 Xcs = abs(imag(Z))
23
24 printf("\n\n Result \n\n")
25 printf("\n (a)for parallel, resistance ,R is %.0f ohm
        and capacitive reactance, Xc is %.0f ohm ",Rp,
        Xcp)
26 printf("\n (b)forseries, resistance ,R is %.2f ohm
        and capacitive reactance, Xc is %.2f ohm ",Rs,Xcs
        )

```

---

#### Scilab code Exa 25.04 Example 4

```

1 //Problem 25.04: Determine the values of currents I,
  I1 and I2 shown in the network of Figure 25.5.

```

```

2
3 //initializing the variables:
4 R1 = 8; // in ohm
5 R = 5; // in ohm
6 R2 = 6; // ohm
7 rv = 50; // in volts
8 thetav = 0; // in degrees
9
10 //calculation:
11 //voltage ,V
12 V = rv*cos(thetav*pi/180) + %i*rv*sin(thetav*pi
    /180)
13 //circuit impedance , ZT
14 ZT = R + (R1*%i*R2/(R1 + %i*R2))
15 //Current I
16 I = V/ZT
17 //current , I1
18 I1 = I*(%i*R2/(R1 + %i*R2))
19 //current , I2
20 I2 = I*(R1/(R1 + %i*R2))
21
22 printf("\n\n Result \n\n")
23 printf("\n current , I is (%.2f + (%.2f)i) A, current ,
    I1 is (%.2f + (%.2f)i) A, current , I2 is (%.2f +
    (%.2f)i) A ", real(I), imag(I), real(I1), imag(I1),
    real(I2), imag(I2))

```

---

### Scilab code Exa 25.05 Example 5

```

1 //Problem 25.05: For the parallel network shown in
    Figure 25.6, determine the value of supply
    current I and its phase relative to the 40 V
    supply.
2
3 //initializing the variables:

```

```

4 R1 = 5; // in ohm
5 R2 = 3; // in ohm
6 R3 = 8; // ohm
7 Xc = 4; // in ohms
8 XL = 12; // in Ohms
9 V = 40; // in volts
10 f = 50; // in Hz
11
12 // calculation :
13 Z1 = R1 + %i*XL
14 Z2 = R2 - %i*Xc
15 Z3 = R3
16 //circuit admittance, YT = 1/ZT
17 YT = (1/Z1) + (1/Z2) + (1/Z3)
18 //Current I
19 I = V*YT
20 I1 = V/Z1
21 I2 = V/Z2
22 I3 = V/Z2
23 thetav = 0
24 thetai = atan(imag(I)/real(I))*180/%pi
25 phi = thetav - thetai
26 if (phi>0) then
27     a = "lagging"
28 else
29     a = "leading"
30 end
31
32 printf("\n\n Result \n\n")
33 printf("\n current, I is (%.2f + (%.2f)i) A, and its
    phase relative to the 40 V supply is %s by %.2 f
    \n", real(I), imag(I), a, abs(phi))

```

---

Scilab code Exa 25.06 Example 6

```

1 //Problem 25.06: An a.c. network consists of a coil ,
  of inductance 79.58 mH and resistance 18 ohm, in
  parallel with a capacitor of capacitance 64.96
  F. If the supply voltage is 250/_0 V at 50 Hz
  , determine (a) the total equivalent circuit
  impedance, (b) the supply current, (c) the
  circuit phase angle, (d) the current in the coil ,
  and (e) the current in the capacitor.
2
3 //initializing the variables:
4 L = 0.07958; // in Henry
5 R = 18; // in ohm
6 C = 64.96E-6; // in Farad
7 rv = 250; // in volts
8 thetav = 0; // in degrees
9 f = 50; // in Hz
10
11 //calculation:
12 //Inductive reactance
13 XL = 2*%pi*f*L
14 //capacitive reactance
15 Xc = 1/(2*%pi*f*C)
16 //impedance of the coil ,
17 Zcoil = R + %i*XL
18 //impedance presented by the capacitor ,
19 Zc = -1*%i*Xc
20 //Total equivalent circuit impedance ,
21 ZT = Zcoil*Zc/(Zcoil + Zc)
22 //voltage
23 V = rv*cos(thetav*%pi/180) + %i*rv*sin(thetav*%pi
  /180)
24 //current , I
25 I = V/ZT
26 thetai = atan(imag(I)/real(I))*180/%pi
27 phi = thetav - thetai
28 if (phi>0) then
29     a = "lagging"
30 else

```



```

31     a = "leading"
32 end
33 //Current in the coil , ICOIL
34 Icoil = V/Zcoil
35 //Current in the capacitor , IC
36 Ic = V/Zc
37
38 printf("\n\n Result \n\n")
39 printf("\n (a)the circuit impedance is %.2f + (%.2f)
    i ohm ",real(ZT), imag(ZT))
40 printf("\n (b)supply current , I is %.2f + (%.2f)i A
    ",real(I), imag(I))
41 printf("\n (c)circuit phase relative is %s by %.2f
    ",a,abs(phi))
42 printf("\n (d)current in coil , Icoil is %.2f + (%.2f
    )i A ",real(Icoil), imag(Icoil))
43 printf("\n (e)current in capacitor , Ic is %.2f + (%
    .2f)i A ",real(Ic), imag(Ic))

```

---

#### Scilab code Exa 25.07 Example 7

```

1 //Problem 25.07: (a) For the network diagram of
    Figure 25.8, determine the value of impedance Z1
    (b) If the supply frequency is 5 kHz, determine
    the value of the components comprising impedance
    Z1.
2
3 //initializing the variables:
4 RL = %i*6; // in ohm
5 R2 = 8; // in ohm
6 Z3 = 10; // in ohm
7 rv = 50; // in volts
8 thetav = 30; // in degrees
9 ri = 31.4; // in amperes
10 thetai = 52.48; // in degrees

```

```

11 f = 5000; // in Hz
12
13 // calculation :
14 //impedance , Z2
15 Z2 = R2 + RL
16 //voltage
17 V = rv*cos(thetav*pi/180) + %i*rv*sin(thetav*pi
    /180)
18 //current , I
19 I = ri*cos(thetai*pi/180) + %i*ri*sin(thetai*pi
    /180)
20 //Total circuit admittance ,
21 YT = I/V
22 //admittance , Y3
23 Y3 = 1/Z3
24 //admittance , Y2
25 Y2 = 1/Z2
26 //admittance , Y1
27 Y1 = YT - Y2 - Y3
28 //impedance , Z1
29 Z1 = 1/Y1
30
31 printf("\n\n Result \n\n")
32 printf("\n (a)the impedance Z1 is %.2f + (%.2f)i ohm
    ",real(Z1), imag(Z1))
33
34 //resistance , R1
35 R1 = real(Z1)
36 X1 = imag(Z1)
37 if ((R1>0)&(X1<0)) then
38     C1 = -1/(2*pi*f*X1)
39     printf("\n (b)The series circuit thus consists
        of a resistor of resistance %.2f ohm and a
        capacitor of capacitance %.2E Farad\n",R1,C1)
40 elseif ((R1>0)&(X1>0)) then
41     L1 = 2*pi*f*X1
42     printf("\n (b)The series circuit thus consists
        of a resistor of resistance %.2f ohm and a

```

```

                                inductor of insuctance %.2E Henry\n",R1,L1)
43 end

```

---

### Scilab code Exa 25.08 Example 8

```

1 //Problem 25.08: For the series-parallel arrangement
  shown in Figure 25.9, determine (a) the
  equivalent series circuit impedance, (b) the
  supply current I, (c) the circuit phase angle, (d
  ) the values of voltages V1 and V2, and (e) the
  values of currents IA and IB.
2
3 //initializing the variables:
4 RL1 = %i*1.02; // in ohm
5 R1 = 1.65; // in ohm
6 RLa = %i*7; // in ohm
7 Ra = 5; // in ohm
8 Rcb = -1*%i*15; // in ohm
9 Rb = 4; // in ohm
10 rv = 91; // in volts
11 thetav = 0; // in degree
12
13 //calculation:
14 //voltage
15 V = rv*cos(thetav*%pi/180) + %i*rv*sin(thetav*%pi
  /180)
16 //impedance, Z1
17 Z1 = R1 + RL1
18 //impedance, Za
19 Za = Ra + RLa
20 //impedance, Zb
21 Zb = Rb + Rcb
22 //impedance, Z, of the two branches connected in
  parallel
23 Z = Za*Zb/(Za + Zb)

```

```

24 //Total circuit impedance
25 ZT = Z1 + Z
26 //Supply current , I
27 I = V/ZT
28 thetai = atan(imag(I)/real(I))*180/%pi
29 phi = thetav - thetai
30 if (phi>0) then
31     a = "lagging"
32 else
33     a = "leading"
34 end
35 //Voltage V1
36 V1 = I*Z1
37 //Voltage V2
38 V2 = I*Z
39 //current Ia
40 Ia = V2/Za
41 //Current Ib
42 Ib = V2/Zb
43
44 printf("\n\n Result \n\n")
45 printf("\n (a)equivalent series circuit impedance is
    %.2f + (%.2f)i ohm ",real(ZT), imag(ZT))
46 printf("\n (b)supply current , I is %.2f + (%.2f)i A
    ",real(I), imag(I))
47 printf("\n (c)circuit phase relative is %s by %.2 f
    ",a,abs(phi))
48 printf("\n (d)voltage , V1 is (%.2f + (%.2f)i) V and
    V2 is (%.2f + (%.2f)i) V ",real(V1), imag(V1),real
    (V2), imag(V2))
49 printf("\n (e)current , Ia is (%.2f + (%.2f)i) A and
    Ib is (%.2f + (%.2f)i) A ",real(Ia), imag(Ia),real
    (Ib), imag(Ib))

```

---

# Chapter 26

## Power in ac circuits

Scilab code Exa 26.01 Example 1

```
1 //Problem 26.01: A coil of resistance 5 ohm and
   inductive reactance 12 ohm is connected across a
   supply voltage of 526/_30volts. Determine the
   active power in the circuit.
2
3 //initializing the variables:
4 RL = %i*12; // in ohm
5 R = 5; // in ohm
6 rv = 52; // in volts
7 thetav = 30; // in degree
8
9 //calculation:
10 //voltage
11 V = rv*cos(thetav*%pi/180) + %i*rv*sin(thetav*%pi
   /180)
12 //impedance, Z
13 Z = R + RL
14 //current
15 I = V/Z
16 //Active power, P
17 Pa = real(V)*real(I) + imag(V)*imag(I)
```

```

18
19 printf("\n\n Result \n\n")
20 printf("\n the active power in the circuit %.0f W\n",
    Pa)

```

---

### Scilab code Exa 26.02 Example 2

```

1 //Problem 26.02: A current of (15+i8)A flows in a
    circuit whose supply voltage is (120+i200)V.
    Determine (a) the active power, and (b) the
    reactive power.
2
3 //initializing the variables:
4 V = 120 + %i*200; // in volts
5 I = 15 + %i*8; // in amperes
6
7 //calculation:
8 //Active power, P
9 Pa = real(V)*real(I) + imag(V)*imag(I)
10 //Reactive power, Q
11 Q = imag(V)*real(I) - real(V)*imag(I)
12
13 printf("\n\n Result \n\n")
14 printf("\n (a) the active power in the circuit %.0f
    W",Pa)
15 printf("\n (b) the reactive power in the circuit %.0
    f var ",Q)

```

---

### Scilab code Exa 26.03 Example 3

```

1 //Problem 26.03: A series circuit possesses
    resistance R and capacitance C. The circuit
    dissipates a power of 1.732 kW and has a power

```

factor of 0.866 leading. If the applied voltage is given by  $v = 141.4 \sin(10000t + \pi/9)$  volts, determine (a) the current flowing and its phase, (b) the value of resistance R, and (c) the value of capacitance C.

```

2
3 //initializing the variables:
4 Vm = 141.4; // in volts
5 w = 10000; // in rad/sec
6 phiv = %pi/9; // in radian
7 Pd = 1732; // in Watts
8 pf = 0.866; // power fctr
9
10 //calculation:
11 //the rms voltage ,
12 Vrms = 0.707*Vm
13 //Power P = V*I*cos(phi)
14 //current magnitude, Irms
15 Irms = Pd/(Vrms*pf)
16 phid = acos(pf)
17 //current phase angle
18 phii = phiv + phid
19 phiid = phii*180/%pi // in degrees
20 //Voltage, V
21 V = Vrms*cos(phiv) + %i*Vrms*sin(phiv)
22 //current, I
23 I = Irms*cos(phii) + %i*Irms*sin(phii)
24 //Impedance, Z
25 Z = V/I
26 //resistance, R
27 R = real(Z)
28 //capacitive reactance, Xc
29 Xc = abs(imag(Z))
30 //capacitance, C
31 C = 1/ (w*Xc)
32
33 printf("\n\n Result \n\n")
34 printf("\n (a)the current flowing and Circuit phase

```

```

    angle is %.0f/-%.2f A ",Irms,phiid)
35 printf("\n (b) the resistance is %.2f ohm ",R)
36 printf("\n (c) the capacitance is %.2E farad ",C)

```

---

#### Scilab code Exa 26.04 Example 4

```

1 //Problem 26.04:For the circuit shown in Figure
   26.8, determine the active power developed
   between points (a) A and B, (b) C and D, (c) E
   and F.
2
3 //initializing the variables:
4 rv = 100; // in volts
5 thetav = 0; // in degrees
6 R = 5; // in ohm
7 R1 = 3; // in ohms
8 RL = %i*4; // in ohm
9 Rc = -10*%i; // in ohms
10
11 //calculation:
12 //impedance, Z1
13 Z1 = R1 + RL
14 //impedance, Zc
15 Zc = Rc
16 //Circuit impedance, Z
17 Z = R + (Z1*Zc/(Z1 + Zc))
18 //voltage
19 V = rv*cos(thetav*%pi/180) + %i*rv*sin(thetav*%pi
   /180)
20 I = V/Z
21 Imag = ((real(I))^2 + (imag(I))^2)^0.5
22 //Active power developed between points A and B
23 Pab = (Imag^2)*R
24 //Active power developed between points C and D
25 Pcd = (Imag^2)*real(Zc)

```



```

26 //Current, I1
27 I1 = I*Zc/(Zc + Z1)
28 I1mag = ((real(I1))^2 + (imag(I1))^2)^0.5
29 //active power developed between points E and F
30 Pef = (I1mag^2)*real(Z1)
31
32 printf("\n\n Result \n\n")
33 printf("\n (a)Active power developed between points
    A and B is %.2f W ",Pab)
34 printf("\n (b)Active power developed between points
    C and D is %.2f W ",Pcd)
35 printf("\n (c)Active power developed between points
    E and F is %.2f W ",Pef)

```

---

#### Scilab code Exa 26.05 Example 5

```

1 //Problem 26.05:The circuit shown in Figure 26.9
    dissipates an active power of 400 Wand has a
    power factor of 0.766 lagging. Determine (a) the
    apparent power, (b) the reactive power, (c) the
    value and phase of current I, and (d) the value
    of impedance Z.
2
3 //initializing the variables:
4 Pa = 400; // in Watts
5 rv = 100; // in volts
6 thetav = 30; // in degrees
7 R = 4; // in ohm
8 pf = 0.766; // power factor
9
10 //calculation:
11 V = rv*cos(thetav*pi/180) + %i*rv*sin(thetav*pi
    /180)
12 //magnitude of apparent power,S = V*I
13 S = Pa/pf

```

```

14 phi = acos(pf)
15 theta = phi*180/%pi // in degrees
16 //Reactive power Q
17 Q = S*sin(phi)
18 //magnitude of current
19 Imag = S/rv
20 thetai = thetav - theta
21 I = Imag*cos(thetai*%pi/180) + %i*Imag*sin(thetai*
    %pi/180)
22 //Total circuit impedance ZT
23 ZT = V/I
24 //impedance Z
25 Z = ZT - R
26
27 printf("\n\n Result \n\n")
28 printf("\n (a)apparent power is %.2f VA ",S)
29 printf("\n (b)reactive power is %.2f var ",Q)
30 printf("\n (c)the current flowing and Circuit phase
    angle is %.2f/_.0 f A ",Imag,thetai)
31 printf("\n (d)impedance, Z is %.2f + (%.2f)i ohm ",
    real(Z), imag(Z))

```

---

#### Scilab code Exa 26.06 Example 6

```

1 //Problem 26.06: A 300 kVA transformer is at full
    load with an overall power factor of 0.70 lagging
    . The power factor is improved by adding
    capacitors in parallel with the transformer until
    the overall power factor becomes 0.90 lagging.
    Determine the rating (in kilovars) of the
    capacitors required.
2
3 //initializing the variables:
4 S = 300000; // in VA
5 pf1 = 0.70; // in power factor

```

```

6 pf2 = 0.90; // in power factor
7
8 //calculation:
9 //active power, P
10 Pa = S*pf1
11 phi1 = acos(pf1)
12 phi1d = phi1*180/%pi
13 //Reactive power, Q
14 Q = S*sin(phi1)
15 phi2 = acos(pf2)
16 phi2d = phi2*180/%pi
17 //The capacitor rating needed to improve the power
    factor to 0.90
18 //the capacitor rating,
19 Pr = Q - (Pa*tan(phi2))
20
21 printf("\n\n Result \n\n")
22 printf("\n the rating (in kilovars) of the
    capacitors is %.1f kvar\n", (Pr/1E3))

```

---

### Scilab code Exa 26.07 Example 7

```

1 //Problem 26.07: A circuit has an impedance  $Z = (3 + i4)$  ohm and a source p.d. of  $50 \angle -30^\circ$  V at a
    frequency of 1.5 kHz. Determine (a) the supply
    current, (b) the active, apparent and reactive
    power, (c) the rating of a capacitor to be
    connected in parallel with impedance Z to improve
    the power factor of the circuit to 0.966 lagging
    , and (d) the value of capacitance needed to
    improve the power factor to 0.966 lagging.
2
3 //initializing the variables:
4 Z = 3 + %i*4; // in ohms
5 rv = 50; // in volts

```

```

6 thetav = 30; // in Degrees
7 f = 1500; // in Hz
8 pf1 = 0.966; // in power factor
9
10 //calculation :
11 V = rv*cos(thetav*pi/180) + %i*rv*sin(thetav*pi
    /180)
12 //Supply current , I
13 I = V/Z
14 Istr = real(I) - %i*imag(I)
15 //Apparent power , S
16 S = V*Istr
17 //active power , Pa
18 Pa = real(S)
19 //reactive power , Q
20 Q = abs(imag(S))
21 //apparent power , S
22 S = (real(S)^2 + imag(S)^2)^0.5
23 phi1 = acos(pf1)
24 phi1d = phi1*180/%pi
25 //rating of the capacitor
26 Pr = Q - Pa*tan(phi1)
27 //Current in capacitor , Ic
28 Ic = Pr/rv
29 //Capacitive reactance , Xc
30 Xc = rv/Ic
31 C = 1/(2*pi*f*Xc)
32
33 printf("\n\n Result \n\n")
34 printf("\n (a)supply current , I is %.2f + (%.2f)i A
    ",real(I), imag(I))
35 printf("\n (b)active power is %.0f W, apparent power
    is %.0f W and reactive power is %.0f W ",Pa, S,
    Q)
36 printf("\n (c)the rating of the capacitors is %.1f
    var\n",Pr)
37 printf(" (d)value of capacitance needed to improve
    the power factor to 0.966 lagging is %.3E F\n", C

```

)

---

# Chapter 27

## AC bridges

Scilab code Exa 27.02 Example 2

```
1 //Problem 27.02: For the Wien bridge shown in Figure
   27.9, R2 = R3 = 30 kohm, R4 = 1 kohm and C2 = C3
   = 1 nF. Determine, when the bridge is balanced,
   (a) the value of resistance R1, and (b) the
   frequency of the bridge.
2
3 //initializing the variables:
4 R2 = 30000; // in ohms
5 R3 = 30000; // in ohms
6 R4 = 1000; // in ohms
7 C2 = 1e-9; // IN FARADS
8 C3 = 1e-9; // IN FARADS
9
10 //calculation:
11 //the bridge is balanced
12 R1 = R4/((R3/R2) + (C2/C3))
13 //frequency, f
14 f = 1/(2*pi*((C2*C3*R2*R3)^0.5))
15
16 printf("\n\n Result \n\n")
17 printf("\n (a) Resistance R1 = %.0f ohm",R1)
```

```
18 printf("\n (b) frequency , f is %.2E Hz ",f)
```

---

### Scilab code Exa 27.03 Example 3

```
1 //Problem 27.03: A Schering bridge network is as
  shown in Figure 27.7. Given C2 = 0.2 F , R4 =
  200 ohm, R3 = 600 ohm, C3 = 4000 pF and the
  supply frequency is 1.5 kHz, determine, when the
  bridge is balanced, (a) the value of resistance
  Rx, (b) the value of capacitance Cx, (c) the
  phase angle of the unknown arm, (d) the power
  factor of the unknown arm and (e) its loss angle.
2
3 //initializing the variables:
4 R3 = 600; // in ohms
5 R4 = 200; // in ohms
6 C2 = 0.2e-6; // IN FARADS
7 C3 = 4000e-12; // IN FARADS
8 f = 1500; //in Hz
9
10 //calculation:
11 //the bridge is balanced
12 //Resistance , Rx
13 Rx = R4*C3/C2
14 //Capacitance , Cx
15 Cx = C2*R3/R4
16 //Phase angle
17 phi = atan(1/(2*pi*f*Cx*Rx))
18 phid = phi*180/pi // in degrees
19 //Power factor of capacitor
20 Pc = cos(phi)
21 //Loss angle ,
22 del = 90 - phid
23
24 printf("\n\n Result \n\n")
```

```
25 printf("\n (a) Resistance Rx = %.0f ohm ",Rx)
26 printf("\n (b) capacitance , Cx is %.2E Farad ",Cx)
27 printf("\n (c) phasor diagram = %.2 f ",phid)
28 printf("\n (d) power factor is %.4f ",Pc)
29 printf("\n (e) Loss angle = %.2 f ",del)
```

---



# Chapter 28

## Series resonance and Q factor

Scilab code Exa 28.01 Example 1

```
1 //Problem 28.01: A coil having a resistance of 10
   ohm and an inductance of 75 mH is connected in
   series with a 40 F capacitor across a 200 V a.c
   . supply. Determine at what frequency resonance
   occurs, and (b) the current flowing at resonance.
2
3 //initializing the variables:
4 R = 10; // in ohms
5 C = 40e-6; // IN FARADS
6 L = 0.075; // IN Henry
7 V = 200; // in Volts
8
9 //calculation:
10 //Resonant frequency,
11 fr = 1/(2*pi*((L*C)^0.5))
12 //Current at resonance, I
13 I = V/R
14
15 printf("\n\n Result \n\n")
16 printf("\n (a)Resonant frequency = %.1f Hz ",fr)
17 printf("\n (b)Current at resonance, I is %.0f A ",I)
```

---

**Scilab code Exa 28.02** Example 2

```
1 //Problem 28.02: An R L C series circuit is
   comprised of a coil of inductance 10 mH and
   resistance 8 ohm and a variable capacitor C. The
   supply frequency is 1 kHz. Determine the value of
   capacitor C for series resonance.
2
3 //initializing the variables:
4 R = 8; // in ohms
5 L = 0.010; // IN Henry
6 f = 1000; // in Hz
7
8 //calculation:
9 //At resonance
10 //capacitance C
11 C = 1/(L*(2*%pi*f)^2)
12
13 printf("\n\n Result \n\n")
14 printf("\n capacitance , C is %.2E F\n",C)
```

---

**Scilab code Exa 28.03** Example 3

```
1 //Problem 28.03: A coil having inductance L is
   connected in series with a variable capacitor C.
   The circuit possesses stray capacitance CS which
   is assumed to be constant and effectively in
   parallel with the variable capacitor C. When the
   capacitor is set to 1000 pF the resonant
   frequency of the circuit is 92.5 kHz, and when
   the capacitor is set to 500 pF the resonant
```

frequency is 127.8 kHz Determine the values of (a) the stray capacitance CS, and (b) the coil inductance L.

```

2
3 //initializing the variables:
4 C1 = 1000e-12; // IN FARADS
5 C2 = 500e-12; // IN FARADS
6 fr1 = 92500; // in Hz
7 fr2 = 127800; // in Hz
8
9 //calculation:
10 //For a series R L C circuit the resonant
    frequency fr is given by:
11 //fr = 1/(2pi*(L*C)^2)
12 Cs = ((C1 - C2)/((fr2/fr1)^2 - 1)) - C2
13 L = 1/((C1 + Cs)*(2*pi*fr1)^2)
14
15 printf("\n\n Result \n\n")
16 printf("\n (a)stray capacitance , Cs is %.2E F ",Cs)
17 printf("\n (b)inductance , L is %.2E H ",L)

```

---

#### Scilab code Exa 28.04 Example 4

```

1 //Problem 28.04: A series circuit comprises a 10 ohm
    resistance , a 5 F capacitor and a variable
    inductance L. The supply voltage is 20/_0 volts
    at a frequency of 318.3 Hz. The inductance is
    adjusted until the p.d. across the 10 ohm
    resistance is a maximum. Determine for this
    condition (a) the value of inductance L, (b) the
    p.d. across each component and (c) the Q-factor.
2
3 //initializing the variables:
4 R = 10; // in ohms
5 C = 5e-6; // IN FARADS

```

```

6 rv = 20; //in volts
7 thetav = 0; // in degrees
8 f = 318.3; // in Hz
9
10 //calculation:
11 wr = 2*%pi*f
12 //The maximum voltage across the resistance occurs
    at resonance when the current is a maximum. At
    resonance ,L = 1/c*wr^2
13 L = 1/(C*wr^2)
14 //voltage
15 V = rv*cos(thetav*%pi/180) + %i*rv*sin(thetav*%pi
    /180)
16 //Current at resonance Ir
17 Ir = V/R
18 //p.d. across resistance , VR
19 VR = Ir*R
20 //inductive reactance , XL
21 XL = wr*L
22 //p.d. across inductance , VL
23 VL = Ir*(%i*XL)
24 //capacitive reactance , Xc
25 Xc = 1/(wr*C)
26 //p.d. across capacitor , Vc
27 Vc = Ir*(-1*%i*Xc)
28 //Q-factor at resonance , Qr
29 Qr = imag(VL)/V
30
31 printf("\n\n Result \n\n")
32 printf("\n (a)inductance , L is %.2E H ",L)
33 printf("\n (b)p.d. across resistance , VR is %.2f V,
    p.d. across inductance , VL %.0fi V and p.d.
    across capacitor , VC %.0fi V ",VR, imag(VL), imag
    (Vc))
34 printf("\n (c)Q-factor at resonance , Qr is %.0f ",
    Qr)

```

---

### Scilab code Exa 28.05 Example 5

```
1 //Problem 28.05: A series L R C circuit has a
  sinusoidal input voltage of maximum value 12 V.
  If inductance , L = 20 mH, resistance , R = 80 ohm,
  and capacitance , C = 400 nF, determine (a) the
  resonant frequency , (b) the value of the p.d.
  across the capacitor at the resonant frequency , (
  c) the frequency at which the p.d. across the
  capacitor is a maximum, and (d) the value of the
  maximum voltage across the capacitor.
2
3 //initializing the variables:
4 R = 80; // in ohms
5 C = 0.4e-6; // IN FARADS
6 L = 0.020; // IN Henry
7 Vm = 12; //in volts
8
9 //calculation:
10 //Resonant frequency ,
11 fr = 1/(2*%pi*((L*C)^0.5))
12 wr = 2*%pi*fr
13 //Q = wr*L/R
14 Q = wr*L/R
15 Vc = Q*Vm
16 //the frequency f at which VC is a maximum value ,
17 f = fr*(1 - (1/(2*Q*Q)))^0.5
18 //the maximum value of the p.d. across the capacitor
  is given by:
19 Vcm = Vc/(1 - (1/(2*Q))^2)^0.5
20
21 printf("\n\n Result \n\n")
22 printf("\n (a)The resonant frequency is %.1f Hz ",fr
  )
```

```

23 printf("\n (b)the value of the p.d. across the
    capacitor at the resonant frequency %.2f V ",Vc)
24 printf("\n (c)the frequency f at which Vc is a
    maximum value , is %.1f Hz ",f)
25 printf("\n (d)the maximum value of the p.d. across
    the capacitor is %.1f V ",Vcm)

```

---

#### Scilab code Exa 28.06 Example 6

```

1 //Problem 28.06: An inductor of Q-factor 60 is
    connected in series with a capacitor having a Q-
    factor of 390. Determine the overall Q-factor of
    the circuit.
2
3 //initializing the variables:
4 QL = 60; // Q-factor
5 Qc = 390; // Q-factor
6
7 //calculation:
8 QT = QL*Qc/(QL + Qc)
9
10 printf("\n\n Result \n\n")
11 printf("\n the overall Q-factor is %.0f \n",QT)

```

---

#### Scilab code Exa 28.07 Example 7

```

1 //Problem 28.07: A filter in the form of a series
    L R C circuit is designed to operate at a
    resonant frequency of 10 kHz. Included within the
    filter is a 10 mH inductance and 5 ohm
    resistance. Determine the bandwidth of the filter
    .
2

```

```

3 //initializing the variables:
4 R = 5; // in ohms
5 L = 0.010; // IN Henry
6 fr = 10000; // in Hz
7
8 //calculation:
9 wr = 2*%pi*fr
10 //Q-factor at resonance is given by
11 Qr = wr*L/R
12 //Since  $Q_r = f_r / (f_2 - f_1)$ ,
13 bw = fr/Qr
14
15 printf("\n\n Result \n\n")
16 printf("\n bandwidth of the filter is %.1f Hz\n",bw)

```

---

#### Scilab code Exa 28.08 Example 8

```

1 //Problem 28.08: An R L C series circuit has a
  resonant frequency of 1.2 kHz and a Q-factor at
  resonance of 30. If the impedance of the circuit
  at resonance is 50 ohm determine the values of (a
  ) the inductance, and (b) the capacitance. Find
  also (c) the bandwidth, (d) the lower and upper
  half-power frequencies and (e) the value of the
  circuit impedance at the half-power frequencies.
2
3 //initializing the variables:
4 Zr = 50; // in ohms
5 fr = 1200; // in Hz
6 Qr = 30; // Q-factor
7
8 //calculation:
9 //At resonance the circuit impedance, Z
10 R = Zr
11 wr = 2*%pi*fr

```

```

12 //Q-factor at resonance is given by  $Q_r = \omega_r L/R$ ,
    then L is
13 L = Qr*R/wr
14 //At resonance  $r*L = 1/(\omega_r*C)$ 
15 //capacitance , C
16 C = 1/(L*wr*wr)
17 //bandwidth ,.( f2      f1)
18 bw = fr/Qr
19 //upper half-power frequency , f2
20 f2 = (bw + ((bw^2) + 4*(fr^2))^0.5)/2
21 //lower half-power frequency , f1
22 f1 = f2 - bw
23 //At the half-power frequencies , current I
24 //I = 0.707*Ir
25 //Hence impedance
26 Z = (2^0.5)*R
27
28 printf("\n\n Result \n\n")
29 printf("\n (a) inductance , L is %.3f H ",L)
30 printf("\n (b) capacitance , C is %.2E F ",C)
31 printf("\n (c) bandwidth is %.0f Hz ",bw)
32 printf("\n (d) the upper half-power frequency , f2 is
    %.0f Hz and the lower half-power frequency , f1 is
    %.0f Hz ",f2,f1)
33 printf("\n (e) impedance at the half-power
    frequencies is %.2f ohm ",Z)

```

---

### Scilab code Exa 28.09 Example 9

```

1 //Problem 28.09: A series R L C circuit is
    connected to a 0.2 V supply and the current is at
    its maximum value of 4 mA when the supply
    frequency is adjusted to 3 kHz. The Q-factor of
    the circuit under these conditions is 100.
    Determine the value of (a) the circuit resistance

```



```

    , (b) the circuit inductance, (c) the circuit
    capacitance, and (d) the voltage across the
    capacitor
2
3 //initializing the variables:
4 V = 0.2; // in Volts
5 I = 0.004; // in Amperes
6 fr = 3000; // in Hz
7 Qr = 100; // Q-factor
8
9 //calculation:
10 wr = 2*%pi*fr
11 //At resonance , impedance
12 Z = V/I
13 //At resonance the circuit impedance, Z
14 R = Z
15 //Q-factor at resonance is given by  $Q_r = \omega_r L/R$ ,
    then L is
16 L = Qr*R/wr
17 //At resonance  $r*L = 1/(\omega_r*C)$ 
18 //capacitance, C
19 C = 1/(L*wr*wr)
20 //Q-factor at resonance in a series circuit
    represents the voltage magnification  $Q_r = V_c/V$ ,
    then Vc is
21 Vc = Qr*V
22
23 printf("\n\n Result \n\n")
24 printf("\n (a)the circuit resistance is %.0f ohm ",R
    )
25 printf("\n (b)inductance , L is %.3f H ",L)
26 printf("\n (c)capacitance , C is %.2E F ",C)
27 printf("\n (d)the voltage across the capacitor is %
    .0f V ",Vc)

```

---

### Scilab code Exa 28.10 Example 10

```
1 //Problem 28.10: A coil of inductance 351.8 mH and
   resistance 8.84 ohm is connected in series with a
   20 F capacitor. Determine (a) the resonant
   frequency, (b) the Q-factor at resonance, (c) the
   bandwidth, and (d) the lower and upper -3dB
   frequencies.
2
3 //initializing the variables:
4 R = 8.84; // in ohms
5 L = 0.3518; // IN Henry
6 C = 20e-6; // IN FARADS
7
8 //calculation:
9 //Resonant frequency,
10 fr = 1/(2*pi*((L*C)^0.5))
11 wr = 2*pi*fr
12 //Q-factor at resonance, Q = wr*L/R
13 Qr = wr*L/R
14 //bandwidth,.(f2 f1)
15 bw = fr/Qr
16 //the lower 3 dB frequency
17 f1 = fr - bw/2
18 //the upper 3 dB frequency
19 f2 = fr + bw/2
20
21 printf("\n\n Result \n\n")
22 printf("\n (a)Resonant frequency, fr is %.0f Hz",fr)
23 printf("\n (b)Q-factor at resonance is %.0f",Qr)
24 printf("\n (c)Bandwidth is %.0f Hz ",bw)
25 printf("\n (d)the lower -3dB frequency, f1 is %.0f
   Hz and the upper -3dB frequency, f2 is %.0f Hz ",
   f1,f2)
```

---

### Scilab code Exa 28.11 Example 11

```
1 //Problem 28.11: In an L R C series network, the
   inductance, L = 8 mH, the capacitance, C = 0.3
   F, and the resistance, R = 15 ohm. Determine
   the current flowing in the circuit when the input
   voltage is 7.56/_0 V and the frequency is (a)
   the resonant frequency, (b) a frequency 3% above
   the resonant frequency. Find also (c) the
   impedance of the circuit when the frequency is 3%
   above the resonant frequency.
2
3 //initializing the variables:
4 R = 15; // in ohms
5 L = 0.008; // IN Henry
6 C = 0.3e-6; // IN FARADS
7 rv = 7.56; //in volts
8 thetav = 0; // in degrees
9 x = 0.03;
10
11 //calculation:
12 //Resonant frequency,
13 fr = 1/(2*pi*((L*C)^0.5))
14 wr = 2*pi*fr
15 //At resonance,
16 Zr = R
17 //voltage
18 V = rv*cos(thetav*pi/180) + %i*rv*sin(thetav*pi
   /180)
19 //Current at resonance
20 Ir = V/Zr
21 //Q-factor at resonance, Q = wr*L/R
22 Qr = wr*L/R
23 //If the frequency is 3% above fr, then
24 del = x
25 I = Ir/(1 + (2*del*Qr*i))
26 Z = V/I
27
```

```
28 printf("\n\n Result \n\n")
29 printf("\n (a)Current at resonance , Ir is %.2f A ",
    Ir)
30 printf("\n (b)current flowing in the circuit when
    frequency 3 percent above the resonant frequency
    is %.4f + (%.4f)i A ",real(I), imag(I))
31 printf("\n (c)impedance of the circuit when the
    frequency is 3 percent above the resonant
    frequency is %.0f + (%.2f)i A ",real(Z), imag(Z))
```

---

# Chapter 29

## Parallel resonance and Q factor

Scilab code Exa 29.01 Example 1

```
1 //Problem 29.01: A coil of inductance 5 mH and
   resistance 10 ohm is connected in parallel with a
   250 nF capacitor across a 50 V variable-
   frequency supply. Determine (a) the resonant
   frequency, (b) the dynamic resistance, (c) the
   current at resonance, and (d) the circuit Q-
   factor at resonance.
2
3 //initializing the variables:
4 R = 10; // in ohms
5 L = 0.005; // IN Henry
6 C = 0.25e-6; // IN FARADS
7 V = 50; //in volts
8
9 //calculation:
10 //Resonant frequency, for parallel
11 fr = ((1/(L*C) - ((R^2)/(L^2)))^0.5)/(2*%pi)
12 //dynamic resistance
13 Rd = L/(C*R)
14 //Current at resonance
15 Ir = V/Rd
```

```

16 wr = 2*%pi*fr
17 //Q-factor at resonance , Q = wr*L/R
18 Qr = wr*L/R
19
20 printf("\n\n Result \n\n")
21 printf("\n (a)Resonance frequency is %.0f Hz ",fr)
22 printf("\n (b)dynamic resistance %.0f ohm ",Rd)
23 printf("\n (c)Current at resonance , Ir is %.3f A ",
    Ir)
24 printf("\n (d)Q-factor at resonance is %.1f ",Qr)

```

---

#### Scilab code Exa 29.02 Example 2

```

1 //Problem 29.02: In the parallel network of Figure
    29.6, inductance , L = 100 mH and capacitance , C =
    40 F . Determine the resonant frequency for the
    network if (a) RL = 0 and (b) RL = 30 ohm.
2
3 //initializing the variables:
4 RL1 = 0; // in ohms
5 RL2 = 30; // in ohms
6 L = 0.100; // IN Henry
7 C = 40e-6; // IN FARADS
8 V = 50; //in volts
9
10 //calculation :
11 //for RL1
12 //Resonant frequency ,
13 wr1 = (1/(L*C))^0.5
14 fr1 = wr1/(2*%pi)
15 //for RL2
16 //Resonant frequency ,
17 wr2 = (1/(L*C) - ((RL2^2)/(L^2)))^0.5
18 fr2 = wr2/(2*%pi)
19

```

```

20 printf("\n\n Result \n\n")
21 printf("\n (a)Resonance frequency at RL = 0 is %.1f
    Hz",fr1)
22 printf("\n (b)Resonance frequency at RL = 30 ohm is
    %.1f Hz\n",fr2)

```

---

### Scilab code Exa 29.03 Example 3

```

1 //Problem 29.03: A coil of inductance 120 mH and
  resistance 150 ohm is connected in parallel with
  a variable capacitor across a 20 V, 4 kHz supply.
  Determine for the condition when the supply
  current is a minimum, (a) the capacitance of the
  capacitor, (b) the dynamic resistance, (c) the
  supply current, (d) the Q-factor, (e) the band-
  width, (f) the upper and lower -3 dB frequencies,
  and (g) the value of the circuit impedance at
  the -3 dB frequencies.
2
3 //initializing the variables:
4 R = 150; // in ohms
5 L = 0.120; // IN Henry
6 V = 20; //in volts
7 fr = 4000; // in Hz
8
9 //calculation:
10 //capacitance, C
11 C = 1/(L*[(2*%pi*fr)^2 + ((R^2)/(L^2))])
12 Rd = L/(C*R)
13 //Current at resonance
14 Ir = V/Rd
15 wr = 2*%pi*fr
16 //Q-factor at resonance, Q = wr*L/R
17 Qr = wr*L/R
18 //bandwidth,.( f2      f1)

```

```

19 bw = fr/QR
20 //upper half-power frequency , f2
21 f2 = (bw + ((bw^2) + 4*(fr^2))^0.5)/2
22 //lower half-power frequency , f1
23 f1 = f2 - bw
24 //impedance at the 3 dB frequencies
25 Z = Rd/(2^0.5)
26
27 printf("\n\n Result \n\n")
28 printf("\n (a)the capacitance of the capacitor ,C is
    %.2E F",C)
29 printf("\n (b)dynamic resistance %.2E ohm ",Rd)
30 printf("\n (c)Current at resonance , Ir is %.3E A ",
    Ir)
31 printf("\n (d)Q-factor at resonance is %.2f ",QR)
32 printf("\n (e)bandwidth is %.0f Hz ",bw)
33 printf("\n (f)the upper half-power frequency , f2 is
    %.0f Hz and the lower half-power frequency , f1 is
    %.0f Hz ",f2,f1)
34 printf("\n (g)impedance at the 3 dB frequencies
    is %.3E ohm",Z)

```

---

#### Scilab code Exa 29.04 Example 4

```

1 //Problem 29.03: A two-branch parallel network is
    shown in Figure 29.8. Determine the resonant
    frequency of the network.
2
3 //initializing the variables:
4 RL = 5; // in ohms
5 L = 0.002; // IN Henry
6 C = 25e-6; // IN FARADS
7 Rc = 3; // in ohms
8
9 //calculation:

```



```

10 //Resonant frequency, for parallel
11 fr = (1/(2*%pi*((L*C)^0.5)))*((RL^2 - (L/C))/(Rc^2 -
    (L/C)))^0.5
12
13 printf("\n\n Result \n\n")
14 printf("\n resonant frequency , fr is %.2f Hz",fr)

```

---

### Scilab code Exa 29.05 Example 5

```

1 //Problem 29.05: Determine for the parallel network
  shown in Figure 29.9 the values of inductance L
  for which the network is resonant at a frequency
  of 1 kHz.
2
3 //initializing the variables:
4 RL = 3; // in ohms
5 fr = 1000; // in Hz
6 Xc = 10; // IN ohms
7 Rc = 4; // in ohms
8
9 //calculation:
10 XL1 = (((Rc^2 + Xc^2)/Xc) + (((Rc^2 + Xc^2)/Xc)^2)
    - 4*(RL^2))^0.5)/2
11 XL2 = (((Rc^2 + Xc^2)/Xc) - (((Rc^2 + Xc^2)/Xc)^2)
    - 4*(RL^2))^0.5)/2
12 wr = 2*%pi*fr
13 //inductance
14 L1 = XL1/wr
15 L2 = XL2/wr
16
17 printf("\n\n Result \n\n")
18 printf("\n inductance is either %.2E H or %.2E H",L1
    , L2)

```

---

**Scilab code Exa 29.06** Example 6

```
1 //Problem 29.06: A capacitor having a Q-factor of
   300 is connected in parallel with a coil having a
   Q-factor of 60. Determine the overall Q-factor
   of the parallel combination.
2
3 //initializing the variables:
4 QL = 60; // Q-factor
5 Qc = 300; // Q-factor
6
7 //calculation:
8 QT = QL*Qc/(QL + Qc)
9
10 printf("\n\n Result \n\n")
11 printf("\n the overall Q-factor is %.0f \n",QT)
```

---

**Scilab code Exa 29.07** Example 7

```
1 //Problem 29.07: In an LR C network, the
   capacitance is 10.61 nF, the bandwidth is 500 Hz
   and the resonant frequency is 150 kHz. Determine
   for the circuit (a) the Q-factor, (b) the dynamic
   resistance, and (c) the magnitude of the
   impedance when the supply frequency is 0.4%
   greater than the tuned frequency.
2
3 //initializing the variables:
4 C = 10.61E-9; // in Farad
5 bw = 500; // in Hz
6 fr = 150000; // in Hz
7 x = 0.004
```

```

8
9 //calculation:
10 //Q-factor
11 Q = fr/bw
12 wr = 2*%pi*fr
13 //dynamic resistance , RD
14 Rd = L*Q/(C*wr*L)
15 del = x
16 Z = Rd/(1 + (2*del*Q*%i))
17 Zmag = (real(Z)^2 + imag(Z)^2)^0.5
18
19 printf("\n\n Result \n\n")
20 printf("\n (a)Q-factor %.2f",Q)
21 printf("\n (b)dynamic resistance %.2E ohm",Rd)
22 printf("\n (c)magnitude of the impedance %.2E ohm",
    Zmag)

```

---

# Chapter 30

## Introduction to network analysis

Scilab code Exa 30.01 Example 1

```
1 //Problem 30.01: Use Kirchhoff s laws to find the
   current flowing in each branch of the network
   shown in Figure 30.3.
2
3 //initializing the variables:
4 rv1 = 100; // in volts
5 rv2 = 50; // in volts
6 thetav1 = 0; // in degrees
7 thetav2 = 90; // in degrees
8 R1 = 25; // in ohm
9 R2 = 20; // in ohm
10 R3 = 10; // in ohm
11
12 //calculation:
13 //voltage
14 V1 = rv1*cos(thetav1*%pi/180) + %i*rv1*sin(thetav1*
   %pi/180)
15 V2 = rv2*cos(thetav2*%pi/180) + %i*rv2*sin(thetav2*
   %pi/180)
```

```

16 //The branch currents and their directions are
    labelled as shown in Figure 30.4
17 //Two loops are chosen. loop ABEF, and loop BCDE
18 //using kirchoff rule in 3 loops
19 //two eqns obtained
20 //(R1 + R2)*I1 + R2*I2 = V1
21 //R2*I1 + (R2 + R3)*I2 = V2
22 I1 = (3*V1 - 2*V2)/(3*(R1 + R2) - 2*(R2))
23 I2 = (V2 - R2*I1)/(R2 + R3)
24 I = I1 + I2
25
26 printf("\n\n Result \n\n")
27 printf("\n current, I1 is %.2f + (%.2f)i A, current,
    I2 is %.2f + (%.2f)i A and total current, I is
    %.2f + (%.2f)i A", real(I1), imag(I1), real(I2),
    imag(I2), real(I), imag(I))

```

---

### Scilab code Exa 30.02 Example 2

```

1 //Problem 30.02: Determine the current flowing in
    the 2 ohm resistor of the circuit shown in Figure
    30.5 using Kirchoff s laws. Find also the
    power dissipated in the 3 ohm resistance.
2
3 //initializing the variables:
4 V = 8; // in volts
5 R1 = 1; // in ohm
6 R2 = 2; // in ohm
7 R3 = 3; // in ohm
8 R4 = 4; // in ohm
9 R5 = 5; // in ohm
10 R6 = 6; // in ohm
11
12 //calculation:
13 //Currents and their directions are assigned as

```

shown in Figure 30.6.

```

14 //Three loops are chosen since three unknown
    currents are required. The choice of loop
    directions is arbitrary. loop ABCDE, and loop
    EDGF and loop DCHG
15 //using kirchoff rule in 3 loops
16 //three eqns obtained
17 //R5*I1 + (R6 + R4)*I2 - R4*I3 = V
18 //-1*R1*I1 + (R6 + R1)*I2 + R2*I3 = 0
19 // R3*I1 - (R3 + R4)*I2 + (R2 + R3 + R4)*I3 = 0
20 //using determinants
21 d1 = [V (R6 + R4) -1*R4; 0 (R6 + R1) R2; 0 (-1*(R3 +
    R4)) (R2 + R3 + R4)]
22 D1 = det(d1)
23 d2 = [R5 V -1*R4; -1*R1 0 R2; R3 0 (R2 + R3 + R4)]
24 D2 = det(d2)
25 d3 = [R5 (R6 + R4) V; -1*R1 (R6 + R1) 0; R3 (-1*(R3
    + R4)) 0]
26 D3 = det(d3)
27 d = [R5 (R6 + R4) -1*R4; -1*R1 (R6 + R1) R2; R3
    (-1*(R3 + R4)) (R2 + R3 + R4)]
28 D = det(d)
29 I1 = D1/D
30 I2 = D2/D
31 I3 = D3/D
32 //Current in the 2 ohm resistance
33 I = I1 - I2 + I3
34 //power dissipated in the 3 ohm resistance
35 P3 = R3*I^2
36
37 printf("\n\n Result \n\n")
38 printf("\n (a)current through 2 ohm resistor is %.2f
    A", I2)
39 printf("\n (b)power dissipated in the 3 ohm resistor
    is %.2f W", P3)

```

---

### Scilab code Exa 30.03 Example 3

```
1 //Problem 30.03: For the a.c. network shown in
   Figure 30.7, determine the current flowing in
   each branch using Kirchhoff s laws.
2
3 //initializing the variables:
4 E1 = 5 + %i*0; // in volts
5 E2 = 2 + %i*4; // in volts
6 Z1 = 3 + %i*4; // in ohm
7 Z2 = 2 - %i*5; // in ohm
8 Z3 = 6 + %i*8; // in ohm
9
10 //calculation:
11 //Currents I1 and I2 with their directions are shown
   in Figure 30.8.
12 //Two loops are chosen with their directions both
   clockwise.loop ABEF and loop BCDE,
13 //using kirchoff rule in 3 loops
14 //two eqns obtained
15 //(Z1 + Z3)*I1 - Z3*I2 = E1
16 // -1*Z3*I1 + (Z2 + Z3)*I2 = E2
17 I1 = ((Z2 + Z3)*E1 + Z3*E2)/((Z2 + Z3)*(Z1 + Z3) -
   Z3*Z3)
18 I2 = -1*(E1 - (Z1 + Z3)*I1)/Z3
19 I3 = I1 - I2
20
21 printf("\n\n Result \n\n")
22 printf("\n current , I1 is %.2f + (%.2f)i A, current ,
   I2 is  %.2f + (%.2f)i A and current in Z3, I3 is
   %.3f + (%.3f)i A", real(I1), imag(I1), real(I2),
   imag(I2), real(I3), imag(I3))
```

---

#### Scilab code Exa 30.04 Example 4

```
1 //Problem 30.04: For the network shown in Figure
   30.9, use Kirchhoff s laws to determine the
   magnitude of the current in the (4 + i3)ohm
   impedance.
2
3 //initializing the variables:
4 rv1 = 10; // in volts
5 rv2 = 12; // in volts
6 rv3 = 15; // in volts
7 thetav1 = 0; // in degrees
8 thetav2 = 0; // in degrees
9 thetav3 = 0; // in degrees
10 R1 = 4; // in ohm
11 R2 = -1*5*i; // in ohm
12 R3 = 8; // in ohm
13 R4 = 4; // in ohm
14 R5 = %i*3; // in ohm
15
16 //calculation:
17 //voltages
18 V1 = rv1*cos(thetav1*pi/180) + %i*rv1*sin(thetav1*
   pi/180)
19 V2 = rv2*cos(thetav2*pi/180) + %i*rv2*sin(thetav2*
   pi/180)
20 V3 = rv3*cos(thetav3*pi/180) + %i*rv3*sin(thetav3*
   pi/180)
21 //Currents I1, I2 and I3 with their directions are
   shown in Figure 30.10.
22 //Three loops are chosen. The choice of loop
   directions is arbitrary. loop ABGH, and loopBCFG
   and loop CDEF
23 Z4 = R4 + R5
```



```

24 //using kirchoff rule in 3 loops
25 //three eqns obtained
26 //R1*I1 + R2*I2 = V1 + V2
27 //-1*R3*I1 + (R3 + R2)*I2 + R3*I3 = V2 + V3
28 // -1*R3*I1 + R3*I2 + (R3 + Z4)*I3 = V3
29 //using determinants
30 d1 = [(V1 + V2) R2 0; (V2 + V3) (R3 + R2) R3; V3 R3
      (R3 + Z4)]
31 D1 = det(d1)
32 d2 = [R1 (V1 + V2) 0; -1*R3 (V2 + V3) R3; -1*R3 V3 (
      R3 + Z4)]
33 D2 = det(d2)
34 d3 = [R1 R2 (V1 + V2); -1*R3 (R3 + R2) (V2 + V3);
      -1*R3 R3 V3]
35 D3 = det(d3)
36 d = [R1 R2 0; -1*R3 (R3 + R2) R3; -1*R3 R3 (R3 + Z4)
      ]
37 D = det(d)
38 I1 = D1/D
39 I2 = D2/D
40 I3 = D3/D
41 I3mag = (real(I3)^2 + imag(I3)^2)^0.5
42
43 printf("\n\n Result \n\n")
44 printf("\n magnitude of the current through (4 + i3)
      ohm impedance is %.2f A",I3mag)

```

---

# Chapter 31

## Mesh current and nodal analysis

Scilab code Exa 31.01 Example 1

```
1 //Problem 31.01: Use mesh-current analysis to
   determine the current flowing in (a) the 5 ohm
   resistance , and (b) the 1ohm resistance of the d
   .c. circuit shown in Figure 31.2.
2
3 //initializing the variables:
4 V1 = 4; // in volts
5 V2 = 5; // in volts
6 R1 = 3; // in ohm
7 R2 = 5; // in ohm
8 R3 = 4; // in ohm
9 R4 = 1; // in ohm
10 R5 = 6; // in ohm
11 R6 = 8; // in ohm
12
13 //calculation:
14 //The mesh currents I1, I2 and I3 are shown in
   Figure 31.2. Using Kirchhoff s voltage law in 3
   loops
```

```

15 //three eqns obtained
16 //(R1 + R2)*I1 - R2*I2 = V1
17 //-1*R2*I1 + (R2 + R3 + R4 + R5)*I2 - R4*I3 = 0
18 // -1*R4*I2 + (R4 + R6)*I3 = -1*V2
19 //using determinants
20 d1 = [V1 -1*R2 0; 0 (R2 + R3 + R4 + R5) -1*R4; -1*V2
        -1*R4 (R4 + R6)]
21 D1 = det(d1)
22 d2 = [(R1 + R2) V1 0; -1*R2 0 -1*R4; 0 -1*V2 (R4 +
        R6)]
23 D2 = det(d2)
24 d3 = [(R1 + R2) -1*R2 V1; -1*R2 (R2 + R3 + R4 + R5)
        0; 0 -1*R4 -1*V2]
25 D3 = det(d3)
26 d = [(R1 + R2) -1*R2 0; -1*R2 (R2 + R3 + R4 + R5)
        -1*R4; 0 -1*R4 (R4 + R6)]
27 D = det(d)
28 I1 = D1/D
29 I2 = D2/D
30 I3 = D3/D
31 IR2 = I1 - I2
32 IR4 = I2 - I3
33
34 printf("\n\n Result \n\n")
35 printf("\n (a) current in the 5 ohm resistance is %.2
        f A",IR2)
36 printf("\n (b) current in the 1 ohm resistance is %.2
        f A",IR4)

```

---

### Scilab code Exa 31.02 Example 2

```

1 //Problem 31.02: For the a.c. network shown in
  Figure 31.3 determine, using mesh-current
  analysis, (a) the mesh currents I1 and I2 (b) the
  current flowing in the capacitor, and (c) the

```

```

    active power delivered by the 100/_0 V voltage
    source.

2
3 //initializing the variables:
4 rv = 100; // in volts
5 thetav = 0; // in degrees
6 R1 = 5; // in ohm
7 R2 = -1*4*%i; // in ohm
8 R3 = 4; // in ohm
9 R4 = %i*3; // in ohm
10
11 //calculation:
12 //voltages
13 V = rv*cos(thetav*%pi/180) + %i*rv*sin(thetav*%pi
    /180)
14 //Currents I1, I2 with their directions are shown in
    Figure 31.03.
15 //Two loops are chosen. The choice of loop
    directions is arbitrary.
16 //using kirchoff rule in 2 loops
17 //two eqns obtained
18 //(R1 + R2)*I1 - R2*I2 = V
19 //-1*R2*I1 + (R3 + R2 + R4)*I2 = 0
20 //using determinants
21 d1 = [V -1*R2; 0 (R3 + R2 + R4)]
22 D1 = det(d1)
23 d2 = [(R1 + R2) V; -1*R2 0]
24 D2 = det(d2)
25 d = [(R1 + R2) -1*R2; -1*R2 (R3 + R2 + R4)]
26 D = det(d)
27 I1 = D1/D
28 I2 = D2/D
29 I1mag = (real(I1)^2 + imag(I1)^2)^0.5
30 //Current flowing in capacitor
31 Ic = I1 - I2
32 //Source power P
33 phi = atan(imag(I1)/real(I1))
34 P = V*I1mag*cos(phi)

```

```

35 Icmag = (real(Ic)^2 + imag(Ic)^2)^0.5
36
37 printf("\n\n Result \n\n")
38 printf("\n (a) current, I1 is %.2f + (%.2f)i A,
      current, I2 is  %.2f + (%.2f)i A",real(I1), imag(
      I1),real(I2), imag(I2))
39 printf("\n (b) current in the capacitor is %.2f A",
      Icmag)
40 printf("\n (c) Source power P is %.2f W",P)

```

---

### Scilab code Exa 31.03 Example 3

```

1 //Problem 31.03: A balanced star-connected 3-phase
      load is shown in Figure 31.4. Determine the value
      of the line currents IR, IY and IB using mesh-
      current analysis.
2
3 //initializing the variables:
4 rv1 = 415; // in volts
5 rv2 = 415; // in volts
6 thetav1 = 120; // in degrees
7 thetav2 = 0; // in degrees
8 R = 3 + %i*4; // in ohm
9
10 //calculation:
11 //voltages
12 V1 = rv1*cos(thetav1*%pi/180) + %i*rv1*sin(thetav1*
      %pi/180)
13 V2 = rv2*cos(thetav2*%pi/180) + %i*rv2*sin(thetav2*
      %pi/180)
14 //Two mesh currents I1 and I2 are chosen as shown in
      Figure 31.4.
15 //Two loops are chosen. The choice of loop
      directions is arbitrary.
16 //using kirchoff rule in 2 loops

```

```

17 //two eqns obtained
18 //2*R*I1 - R*I2 = V1
19 //-1*R*I1 + 2*R*I2 = V2
20 //using determinants
21 d1 = [V1 -1*R; V2 2*R]
22 D1 = det(d1)
23 d2 = [2*R V1; -1*R V2]
24 D2 = det(d2)
25 d = [2*R -1*R; -1*R 2*R]
26 D = det(d)
27 I1 = D1/D
28 I2 = D2/D
29 I1mag = (real(I1)^2 + imag(I1)^2)^0.5
30 //line current IR
31 IR = I1
32 //line current IB
33 IB = -1*I2
34 //line current IY
35 IY = I2 - I1
36
37 printf("\n\n Result \n\n")
38 printf("\n current , IR is %.2f + (%.2f)i A, current ,
      IB is %.2f + (%.2f)i A and current , IY is %.2f
      + (%.2f)i A",real(IR), imag(IR),real(IB), imag(IB)
      ),real(IY), imag(IY))

```

---

#### Scilab code Exa 31.04 Example 4

```

1 //Problem 31.04: For the network shown in Figure
  31.8, determine the voltage VAB, by using nodal
  analysis.
2
3 //initializing the variables:
4 ri = 20; // in amperes
5 thetai = 0; // in degrees

```

```

6 R1 = 10; // in ohm
7 R2 = %i*3; // in ohm
8 R3 = 4; // in ohm
9 R4 = 16; // in ohm
10
11 //calculation:
12 //current
13 I = ri*cos(thetai*pi/180) + %i*ri*sin(thetai*pi
    /180)
14 //Figure 31.8 contains two principal nodes (at 1 and
    B) and thus only one nodal equation is required.
    B is taken as the reference node and the
    equation for node 1 is obtained as follows.
    Applying Kirchhoff s current law to node 1
    gives:
15 //IX + IY = I
16 V1 = I/((1/R4) +(1/(R2 +R3)))
17 IY = V1/(R2 + R3)
18 VAB = IY*R3
19
20 printf("\n\n Result \n\n")
21 printf("\n voltage VAB is %.2f + (%.2f)i V",real(VAB
    ), imag(VAB))

```

---

### Scilab code Exa 31.05 Example 5

```

1 //Problem 31.05: Determine the value of voltage VXY
    shown in the circuit of Figure 31.9.
2
3 //initializing the variables:
4 rv1 = 8; // in volts
5 rv2 = 8; // in volts
6 thetav1 = 0; // in degrees
7 thetav2 = 90; // in degrees
8 R1 = 5; // in ohm

```

```

 9 R2 = %i*6; // in ohm
10 R3 = 4; // in ohm
11 R4 = 3; // in ohm
12
13 // calculation :
14 // voltages
15 V1 = rv1*cos(thetav1*%pi/180) + %i*rv1*sin(thetav1*
    %pi/180)
16 V2 = rv2*cos(thetav2*%pi/180) + %i*rv2*sin(thetav2*
    %pi/180)
17 //The circuit contains no principal nodes. However,
    if point Y is chosen as the reference node then
    an equation may be written for node X assuming
    that current leaves point X by both branches
18 VX = [(V1/(R1 + R3) + V2/(R2 + R4))/(1/(R1 + R3) +
    1/(R2 + R4))]
19 VXY = VX
20
21 printf("\n\n Result \n\n")
22 printf("\n voltage VXY is %.2f + (%.2f)i V", real(VXY
    ), imag(VXY))

```

---

### Scilab code Exa 31.06 Example 6

```

1 //Problem 31.06: Use nodal analysis to determine the
    current flowing in each branch of the network
    shown in Figure 31.10.
2
3 //initializing the variables:
4 rv1 = 100; // in volts
5 rv2 = 50; // in volts
6 thetav1 = 0; // in degrees
7 thetav2 = 90; // in degrees
8 R1 = 25; // in ohm
9 R2 = 20; // in ohm

```



```

10 R3 = 10; // in ohm
11
12 // calculation :
13 // voltages
14 V1 = rv1*cos(thetav1*%pi/180) + %i*rv1*sin(thetav1*
    %pi/180)
15 V2 = rv2*cos(thetav2*%pi/180) + %i*rv2*sin(thetav2*
    %pi/180)
16 //There are only two principal nodes in Figure 31.10
    so only one nodal equation is required. Node 2
    is taken as the reference node.
17 //The equation at node 1 is I1 + I2 + I3 = 0
18 Vn1 = [(V1/R1 + V2/R3)/(1/R1 + 1/R2 + 1/R3)]
19 I1 = (Vn1 - V1)/R1
20 I2 = Vn1/R2
21 I3 = (Vn1 - V2)/R3
22
23 printf("\n\n Result \n\n")
24 printf("\n current , I1 is %.2f + (%.2f)i A, current ,
    I2 is %.2f + (%.2f)i A and current , I3 is %.2f
    + (%.2f)i A",real(I1), imag(I1),real(I2), imag(I2)
    ),real(I3), imag(I3))

```

---

### Scilab code Exa 31.07 Example 7

```

1 //Problem 31.07: In the network of Figure 31.11 use
    nodal analysis to determine (a) the voltage at
    nodes 1 and 2, (b) the current in the j4 ohm
    inductance, (c) the current in the 5 ohm
    resistance, and (d) the magnitude of the active
    power dissipated in the 2.5 ohm resistance.
2
3 //initializing the variables:
4 rv1 = 25; // in volts
5 rv2 = 25; // in volts

```

```

6 thetav1 = 0; // in degrees
7 thetav2 = 90; // in degrees
8 R1 = 2; // in ohm
9 R2 = -1*i*4; // in ohm
10 R3 = 5; // in ohm
11 R4 = %i*4; // in ohm
12 R5 = 2.5; // in ohm
13
14 //calculation:
15 //voltages
16 V1 = rv1*cos(thetav1*pi/180) + %i*rv1*sin(thetav1*
    %pi/180)
17 V2 = rv2*cos(thetav2*pi/180) + %i*rv2*sin(thetav2*
    %pi/180)
18 //The equation at node 1
19 //Vn1*(1/R1 + 1/R2 + 1/R3) - Vn2/R3 = V1/R1
20 //The equation at node 2
21 //Vn1*(-1/R3) + Vn2*(1/R4 + 1/R5 + 1/R3) = V2/R5
22 //using determinants
23 d1 = [V1/R1 -1/R3; V2/R5 (1/R4 + 1/R5 + 1/R3)]
24 D1 = det(d1)
25 d2 = [(1/R1 + 1/R2 + 1/R3) V1/R1; -1/R3 V2/R5]
26 D2 = det(d2)
27 d = [(1/R1 + 1/R2 + 1/R3) -1/R3; -1/R3 (1/R4 + 1/R5
    + 1/R3)]
28 D = det(d)
29 Vn1 = D1/D
30 Vn2 = D2/D
31 //current in the j4 ohm inductance is given by:
32 I4 = Vn2/R4
33 //current in the 5 ohm resistance is given by:
34 I3 = (Vn1 - Vn2)/R3
35 //active power dissipated in the 2.5 ohm resistor is
    given by
36 P5 = R5*((Vn2 - V2)/R5)^2
37 //magnitude of the active power dissipated
38 P5mag = (real(P5)^2 + imag(P5)^2)^0.5
39

```

```

40 printf("\n\n Result \n\n")
41 printf("\n (a) the voltage at nodes 1 and 2 is %.2f
    + (%.2f)i V and %.2f + (%.2f)i V",real(Vn1), imag
    (Vn1),real(Vn2), imag(Vn2))
42 printf("\n (b)the current in the j4 ohm inductance
    is %.2f + (%.2f)i A",real(I4), imag(I4))
43 printf("\n (c)the current in the 5 ohm resistance is
    %.2f + (%.2f)i A",real(I3), imag(I3))
44 printf("\n (d) magnitude of the active power
    dissipated in the 2.5 ohm resistance is %.2f W",
    P5mag)

```

---

#### Scilab code Exa 31.08 Example 8

```

1 //Problem 31.08: In the network shown in Figure
    31.12 determine the voltage VXY using nodal
    analysis
2
3 //initializing the variables:
4 ri = 25; // in amperes
5 thetai = 0; // in degrees
6 R1 = 4; // in ohm
7 R2 = %i*3; // in ohm
8 R3 = 5; // in ohm
9 R4 = %i*10; // in ohm
10 R5 = %i*20; // in ohm
11
12 //calculation:
13 //current
14 I = ri*cos(thetai*pi/180) + %i*ri*sin(thetai*pi
    /180)
15 //Node 3 is taken as the reference node.
16 //At node 1,
17 //V1*(1/(R1 + R2) + 1/R3) - V2/R3 = I
18 //The equation at node 2

```

```

19 //V1*(-1/R3) + V2*(1/R4 + 1/R5 + 1/R3) = 0
20 //using determinants
21 d1 = [I -1/R3; 0 (1/R4 + 1/R5 + 1/R3)]
22 D1 = det(d1)
23 d2 = [(1/(R1 + R2) + 1/R3) I; -1/R3 0]
24 D2 = det(d2)
25 d = [(1/(R1 + R2) + 1/R3) -1/R3; -1/R3 (1/R4 + 1/R5
      + 1/R3)]
26 D = det(d)
27 V1 = D1/D
28 V2 = D2/D
29 //the voltage between point X and node 3 is
30 VX = V1*R2/(R1 + R2)
31 //Thus the voltage
32 VY = V2
33 VXY = VX - VY
34
35 printf("\n\n Result \n\n")
36 printf("\n voltage VXY is %.2f + (%.2f)i V", real(VXY
      ), imag(VXY))

```

---

### Scilab code Exa 31.09 Example 9

```

1 //Problem 31.09: Use nodal analysis to determine the
  voltages at nodes 2 and 3 in Figure 31.13 and
  hence determine the current flowing in the 2 ohm
  resistor and the power dissipated in the 3 ohm
  resistor.
2
3 //initializing the variables:
4 V = 8; // in volts
5 R1 = 1; // in ohm
6 R2 = 2; // in ohm
7 R3 = 3; // in ohm
8 R4 = 4; // in ohm

```

```

9 R5 = 5; // in ohm
10 R6 = 6; // in ohm
11
12 //calculation:
13 //In Figure 31.13, the reference node is shown at
    point A.
14 //At node 1,
15 //V1*(1/R1 + 1/R6 + 1/R5) - V2/R1 - V3/R5 = V/R5
16 //The equation at node 2
17 //V1*(-1/R1) + V2*(1/R2 + 1/R1 + 1/R3) - V3/R3 = 0
18 //At node 3
19 // - V1/R5 - V2/R3 + V3*(1/R4 + 1/R3 + 1/R5) = -1*V/
    R5
20 //using determinants
21 d1 = [V/R5 -1/R1 -1/R5; 0 (1/R2 + 1/R1 + 1/R3) -1/R3
    ; -1*V/R5 -1/R3 (1/R4 + 1/R3 + 1/R5)]
22 D1 = det(d1)
23 d2 = [(1/R1 + 1/R6 + 1/R5) V/R5 -1/R5; -1/R1 0 -1/R3
    ; -1/R5 -1*V/R5 (1/R4 + 1/R3 + 1/R5)]
24 D2 = det(d2)
25 d3 = [(1/R1 + 1/R6 + 1/R5) -1/R1 V/R5; -1/R1 (1/R2 +
    1/R1 + 1/R3) 0; -1/R5 -1/R3 -1*V/R5]
26 D3 = det(d3)
27 d = [(1/R1 + 1/R6 + 1/R5) -1/R1 -1/R5; -1/R1 (1/R2 +
    1/R1 + 1/R3) -1/R3; -1/R5 -1/R3 (1/R4 + 1/R3 +
    1/R5)]
28 D = det(d)
29 Vn1 = D1/D
30 Vn2 = D2/D
31 Vn3 = D3/D
32 //the current in the 2 ohm resistor
33 I2 = Vn2/R2
34 //power dissipated in the 3 ohm resistance
35 P3 = R3*((Vn2 - Vn3)/R3)^2
36
37 printf("\n\n Result \n\n")
38 printf("\n voltage at node 2 is %.2f V",Vn2)
39 printf("\n voltage at node 3 is %.2f V",Vn3)

```

```
40 printf("\n (a) current through 2 ohm resistor is %.2f
    A", I2)
41 printf("\n (b) power dissipated in the 3 ohm resistor
    is %.2f W", P3)
```

---

# Chapter 32

## The superposition theorem

Scilab code Exa 32.01 Example 1

```
1 //Problem 32.01:A.c. sources of 100/_0 V and
   internal resistance 25 ohm and 50/_90 V and
   internal resistance 10 ohm, are connected in
   parallel across a 20 ohm load. Determine using
   the superposition theorem, the current in the 20
   ohm load and the current in each voltage source
2
3 //initializing the variables:
4 rv1 = 100; // in volts
5 rv2 = 50; // in volts
6 thetav1 = 0; // in degrees
7 thetav2 = 90; // in degrees
8 r1 = 25; // in ohm
9 R = 20; // in ohm
10 r2 = 10; // in ohm
11
12 //calculation:
13 //voltage
14 V1 = rv1*cos(thetav1*%pi/180) + %i*rv1*sin(thetav1*
   %pi/180)
15 V2 = rv2*cos(thetav2*%pi/180) + %i*rv2*sin(thetav2*
```

```

    %pi/180)
16 //The circuit diagram is shown in Figure 32.7.
    Following the above procedure:
17 //The network is redrawn with the 50/_90 V source
    removed as shown in Figure 32.8
18 //Currents I1, I2 and I3 are labelled as shown in
    Figure 32.8.
19 I1 = V1/(r1 + r2*R/(R + r2))
20 I2 = (r2/(r2 + R))*I1
21 I3 = (R/(r2 + R))*I1
22 //The network is redrawn with the 100/_0 V source
    removed as shown in Figure 32.9
23 //Currents I4, I5 and I6 are labelled as shown in
    Figure 32.9.
24 I4 = V2/(r2 + r1*R/(r1 + R))
25 I5 = (r1/(r1 + R))*I4
26 I6 = (R/(r1 + R))*I4
27 //Figure 32.10 shows Figure 32.9 superimposed on
    Figure 32.8, giving the currents shown.
28 //Current in the 20 ohm load ,
29 I20 = I2 + I5
30 //Current in the 100/_0 V source
31 IV1 = I1 - I6
32 //Current in the 50/_90 V source
33 IV2 = I4 - I3
34
35 printf("\n\n Result \n\n")
36 printf("\n (a) current in the 20 ohm load is %.3f + (
    %.3f)i A", real(I20), imag(I20))
37 printf("\n (b) Current in the 100/_0 V source is %
    .3f + (%.3f)i A", real(IV1), imag(IV1))
38 printf("\n (b) Current in the 50/_90 V source is %
    .3f + (%.3f)i A", real(IV2), imag(IV2))

```

---

Scilab code Exa 32.02 Example 2



```

1 //Problem 32.02:Use the superposition theorem to
   determine the current in the 4 ohm resistor of
   the network shown in Figure 32.11.
2
3 //initializing the variables:
4 V1 = 12; // in volts
5 V2 = 20; // in volts
6 R1 = 5; // in ohm
7 R2 = 4; // in ohm
8 R3 = 2.5; // in ohm
9 R4 = 6; // in ohm
10 R5 = 2; // in ohm
11
12 //calculation:
13 //Removing the 20 V source gives the network shown
   in Figure 32.12.
14 //Currents I1 and I2 are shown labelled in Figure
   32.12
15 Re1 = (R4*R5/(R4 + R5)) + R3
16 Re2 = Re1*R2/(Re1 + R2) + R1
17 I1 = V1/Re2
18 I2 = (R2/(Re1 + R2))*I1
19 //Removing the 12 V source from the original network
   gives the network shown in Figure 32.14.
20 //Currents I3, I4 and I5 are shown labelled in
   Figure 32.14.
21 Re3 = (R1*R2/(R1 + R2)) + R3
22 Re4 = Re3*R4/(Re3 + R4) + R5
23 I3 = V2/Re4
24 I4 = (R4/(Re3 + R4))*I3
25 I5 = (R1/(R1 + R2))*I4
26 //Superimposing Figure 32.14 on Figure 32.12 shows
   that the current flowing in the 4 ohm resistor is
   given by
27 Ir4 = I5 - I2
28
29 printf("\n\n Result \n\n")
30 printf("\ncurrent in the 4 ohm resistor of the

```

network is %.3f A",Ir4)

---

### Scilab code Exa 32.03 Example 3

```
1 //Problem 32.03: Use the superposition theorem to
  obtain the current flowing in the (4 + i3) ohm
  impedance of Figure 32.16.
2
3 //initializing the variables:
4 rv1 = 30; // in volts
5 rv2 = 30; // in volts
6 thetav1 = 45; // in degrees
7 thetav2 = -45; // in degrees
8 R1 = 4; // in ohm
9 R2 = 4; // in ohm
10 R3 = %i*3; // in ohm
11 R4 = -1*%i*10; // in ohm
12
13 //calculation:
14 //voltage
15 V1 = rv1*cos(thetav1*%pi/180) + %i*rv1*sin(thetav1*
  %pi/180)
16 V2 = rv2*cos(thetav2*%pi/180) + %i*rv2*sin(thetav2*
  %pi/180)
17 //The network is redrawn with V2 removed, as shown
  in Figure 32.17.
18 //Current I1 and I2 are shown in Figure 32.17. From
  Figure 32.17,
19 Re1 = R4*(R2 + R3)/(R4 + R3 + R2)
20 Re2 = Re1 + R1
21 //current
22 I1 = V1/Re2
23 I2 = (R4/(R2 + R3 + R4))*I1
24 //The original network is redrawn with V1 removed,
  as shown in Figure 32.18
```

```

25 //Currents I3 and I4 are shown in Figure 32.18. From
    Figure 32.18,
26 Re3 = R1*(R2 + R3)/(R1 + R3 + R2)
27 Re4 = Re3 + R4
28 I3 = V2/Re4
29 I4 = (R1/(R2 + R3 + R1))*I3
30 //If the network of Figure 32.18 is superimposed on
    the network of Figure 32.17, it can be seen that
    the current in the (4+i3) ohm impedance is given
    by
31 Ir4i3 = I2 - I4
32
33 printf("\n\n Result \n\n")
34 printf("\ncurrent in the (4 + i3) ohm impedance of
    the network is %.3f + (%.3f)i A",real(Ir4i3),
    imag(Ir4i3))

```

---

#### Scilab code Exa 32.04 Example 4

```

1 //Problem 32.04: For the a.c. network shown in
    Figure 32.19 determine, using the superposition
    theorem, (a) the current in each branch, (b) the
    magnitude of the voltage across the(6 + i8) ohm
    impedance, and (c) the total active power
    delivered to the network.
2
3 //initializing the variables:
4 E1 = 5 + %i*0; // in volts
5 E2 = 2 + %i*4; // in volts
6 Z1 = 3 + %i*4; // in ohm
7 Z2 = 2 - %i*5; // in ohm
8 Z3 = 6 + %i*8; // in ohm
9
10 //calculation:
11 //The original network is redrawn with E2 removed,

```

```

    as shown in Figure 32.20.
12 //Currents I1, I2 and I3 are labelled as shown in
    Figure 32.20.
13 Ze1 = Z3*Z2/(Z3 + Z2)
14 Ze2 = Ze1 + Z1
15 //current
16 I1 = E1/Ze2
17 I2 = (Z2/(Z3 + Z2))*I1
18 I3 = (Z3/(Z3 + Z2))*I1
19 //The original network is redrawn with E1 removed,
    as shown in Figure 32.22
20 //Currents I4, I5 and I6 are shown labelled in
    Figure 32.22 with I4 flowing away from the
    positive terminal of the E2 source.
21 Ze3 = Z3*Z1/(Z3 + Z1)
22 Ze4 = Ze3 + Z2
23 I4 = E2/Ze4
24 I5 = (Z1/(Z3 + Z1))*I4
25 I6 = (Z3/(Z3 + Z1))*I4
26 //If the network of Figure 32.18 is superimposed on
    the network of Figure 32.17, it can be seen that
    the current in the (4+i3) ohm impedance is given
    by
27 i1 = I1 + I6
28 i2 = I3 + I4
29 i3 = I2 - I5
30 //magnitude
31 i1mag = (real(i1)^2 + imag(i1)^2)^0.5
32 i2mag = (real(i2)^2 + imag(i2)^2)^0.5
33 E1mag = (real(E1)^2 + imag(E1)^2)^0.5
34 E2mag = (real(E2)^2 + imag(E2)^2)^0.5
35 //phase
36 phi1 = atan(imag(i1)/real(i1))
37 phi2 = atan(imag(i2)/real(i2))
38 //voltage across the(6 + i8) ohm impedance
39 V6i8 = i3*Z3
40 V6i8m = (real(V6i8)^2 + imag(V6i8)^2)^0.5
41 //power

```

```

42 P = (E1mag*i1mag*cos(phi1)) + (E2mag*i2mag*cos(phi2
    - atan(imag(E2)/real(E2)))
43
44 printf("\n\n Result \n\n")
45 printf("\n(b) current in the (6 + i8) ohm resistor of
    the network is %.3f V",V6i8m)
46 printf("\n(c) the total active power delivered to the
    network is %.3f W",P)

```

---

### Scilab code Exa 32.05 Example 5

```

1 //Problem 32.05: Use the superposition theorem to
    determine , for the network shown in Figure 32.25 ,
    (a) the magnitude of the current flowing in the
    capacitor , (b) the p.d. across the 5 ohm
    resistance , (c) the active power dissipated in
    the 20 ohm resistance and (d) the total active
    power taken from the supply .
2
3 //initializing the variables :
4 rv1 = 50; // in volts
5 rv2 = 30; // in volts
6 thetav1 = 0; // in degrees
7 thetav2 = 90; // in degrees
8 R1 = 20; // in ohm
9 R2 = 5; // in ohm
10 R3 = -1*i*3; // in ohm
11 R4 = 8; // in ohm
12 R5 = 8; // in ohm
13
14 //calculation :
15 //voltage
16 V1 = rv1*cos(thetav1*pi/180) + %i*rv1*sin(thetav1*
    pi/180)
17 V2 = rv2*cos(thetav2*pi/180) + %i*rv2*sin(thetav2*

```

```

    %pi/180)
18 //The network is redrawn with the V2 source removed,
    as shown in Figure 32.26.
19 //Currents I1 to I5 are shown labelled in Figure
    32.26.
20 //current
21 Re1 = R4*R5/(R5 + R4) + R3
22 Re2 = Re1*R2/(R2 + Re1)
23 I1 = V1/(Re2 + R1)
24 I2 = (Re1/(R2 + Re1))*I1
25 I3 = (R2/(Re1 + R2))*I1
26 I4 = (R4/(R4 + R5))*I3
27 I5 = I3 - I4
28 //The original network is redrawn with the V1 source
    removed, as shown in Figure 32.27.
29 //Currents I6 to I10 are shown labelled in Figure
    32.27
30 Re3 = R1*R2/(R1 + R2)
31 Re4 = Re3 + R3
32 Re5 = Re4*R4/(Re4 + R4)
33 Re6 = Re5 + R5
34 I6 = V2/Re6
35 I7 = (Re4/(Re4 + R4))*I6
36 I8 = (R4/(Re4 + R4))*I6
37 I9 = (R1/(R1 + R2))*I8
38 I10 = (R2/(R1 + R2))*I8
39 //current flowing in the capacitor is given by
40 Ic = I3 - I8
41 //magnitude of the current in the capacitor
42 Icmag = (real(Ic)^2 + imag(Ic)^2)^0.5
43 //
44 i1 = I2 + I9
45 i1mag = (real(i1)^2 + imag(i1)^2)^0.5
46 //magnitude of the p.d. across the 5 ohm resistance
    is given by
47 Vr5m = i1mag*R2
48 //Active power dissipated in the 20 ohm resistance
    is given by

```

```

49 i2 = I1 - I10
50 i2mag = (real(i2)^2 + imag(i2)^2)^0.5
51 phii2 = atan(imag(i2)/real(i2))
52 Pr20 = R1*(i2mag)^2
53 //Active power developed by the V1
54 P1 = rv1*i2mag*cos(phii2)
55 //Active power developed by V2 source
56 i3 = I6 - I5
57 i3mag = (real(i3)^2 + imag(i3)^2)^0.5
58 phii3 = atan(imag(i3)/real(i3))
59 if ((imag(i3)>0) & (real(i3)<0)) then
60     phii3 = phii3 + %pi
61 end
62 P2 = rv2*i3mag*cos(phii3 - (thetav2*%pi/180))
63 //Total power developed
64 P = P1 + P2
65
66 printf("\n\n Result \n\n")
67 printf("\n(a)the magnitude of the current flowing in
        the capacitor is %.2f A",Icmag)
68 printf("\n(b) the p.d. across the 5 ohm resistance
        is %.3f V",Vr5m)
69 printf("\n(c)the active power dissipated in the 20
        ohm resistance is %.0f W",Pr20)
70 printf("\n(d)the total active power taken from the
        supply is %.1f W",P)

```

---

# Chapter 33

## Thevenins and Nortons theorems

Scilab code Exa 33.01 Example 1

```
1 //Problem 33.01: For the circuit shown in Figure
   33.12, use Th evenin s theorem to determine (a
   ) the current flowing in the capacitor, and (b)
   the p.d. across the 150 kohm resistor.
2
3 //initializing the variables:
4 rv = 200; // in volts
5 thetav = 0; // in degrees
6 R1 = 5000; // in ohm
7 R2 = 20000; // in ohm
8 R3 = -1*%i*120000; // in ohm
9 R4 = 150000; // in ohm
10
11 //calculation:
12 //voltage
13 V = rv*cos(thetav*%pi/180) + %i*rv*sin(thetav*%pi
   /180)
14 //Initially the (150-i120)kohm impedance is removed
   from the circuit as shown in Figure 33.13.
```



```

15 //Note that, to find the current in the capacitor ,
    only the capacitor need have been initially
    removed from the circuit. However, removing each
    of the components from the branch through which
    the current is required will often result in a
    simpler solution .
16 //From Figure 33.13,
17 //current , I1
18 I1 = V/(R1 + R2)
19 //The open-circuit e.m.f. E is equal to the p.d.
    across the 20 kohm resistor , i.e.
20 E = I1*R2
21 //Removing the V1 source gives the network shown in
    Figure 33.14.
22 //The impedance, z, looking in at the open-
    circuited terminals is given by
23 z = R1*R2/(R1 + R2)
24 //The Th evenin equivalent circuit is shown in
    Figure 33.15, where current iL is given by
25 ZL = R3 + R4
26 IL = E/(ZL + z)
27 ILMag = (real(IL)^2 + imag(IL)^2)^0.5
28 //current flowing in the capacitor
29 Ic = ILMag
30 //P.d. across the 150 kohm resistor ,
31 Vr150 = ILMag*R4
32
33 printf("\n\n Result \n\n")
34 printf("\n(a)the current flowing in the capacitor is
    %.1E A",Ic)
35 printf("\n(b) the p.d. across the 150 ohm resistance
    is %.0f V",Vr150)

```

---

Scilab code Exa 33.02 Example 2

```

1 //Problem 33.02: Determine , for the network shown in
   Figure 33.16, the value of current I. Each of
   the voltage sources has a frequency of 2 kHz.
2
3 //initializing the variables:
4 V1 = 20; // in volts
5 V2 = 10; // in volts
6 R1 = 2; // in ohm
7 R2 = 1.5; // in ohm
8 L = 235E-6; // in Henry
9 R4 = 3; // in ohm
10 f = 2000; // in Hz
11
12 //calculation:
13 //The impedance through which current I is flowing
   is initially removed from the network, as shown
   in Figure 33.17.
14 //From Figure 33.17,
15 //current, I1
16 I1 = (V1 - V2)/(R1 + R4)
17 //the open circuit e.m.f. E
18 E = V1 - I1*R1
19 //When the sources of e.m.f. are removed from the
   circuit, the impedance, z, looking in at
   the break is given by
20 z = R1*R4/(R1 + R4)
21 //The Thevenin equivalent circuit is shown in
   Figure 33.18, where inductive reactance,
22 XL = 2*%pi*f*L
23 R3 = %i*XL
24 //Hence current
25 I = E/(R2 + R3 + z)
26
27 printf("\n\n Result \n\n")
28 printf("\n the current I is %.2f + (%.2f)i A",real(I
   ), imag(I))

```

---

### Scilab code Exa 33.03 Example 3

```
1 //Problem 33.03: Use Thevenin's theorem to
   determine the power dissipated in the 48 ohm
   resistor of the network shown in Figure 33.19
2
3 //initializing the variables:
4 rv = 50; // in volts
5 thetav = 0; // in degrees
6 R1 = -1*i*400; // in ohm
7 R2 = 300; // in ohm
8 R3 = %i*144; // in ohm
9 R4 = 48; // in ohm
10
11 //calculation:
12 //voltage
13 V = rv*cos(thetav*pi/180) + %i*rv*sin(thetav*pi
   /180)
14 //The R3 and R4 impedance is initially removed from
   the network as shown in Figure 33.20.
15 //From Figure 33.20,
16 //current, I
17 i = V/(R1 + R2)
18 //the open circuit e.m.f. E
19 E = i*R2
20 //When the V is removed from the circuit, the
   impedance, z, looking in at the break is
   given by
21 z = R1*R2/(R1 + R2)
22 //The Thevenin equivalent circuit is shown in
   Figure 33.21 connected to R# and R4,
23 //Hence current
24 I = E/(R4 + R3 + z)
25 Imag = (real(I)^2 + imag(I)^2)^0.5
```

```

26 //the power dissipated in the 48 ohm resistor
27 Pr48 = R4*Imag^2
28
29 printf("\n\n Result \n\n")
30 printf("\n the power dissipated in the 48 ohm
    resistor is %.2f W",Pr48)

```

---

#### Scilab code Exa 33.04 Example 4

```

1 //Problem 33.04:For the network shown in Figure
  33.22, use Th evenin s theorem to determine
  the current flowing in the 80 ohm resistor.
2
3 //initializing the variables:
4 V = 100; // in volts
5 R1 = 5; // in ohm
6 R2 = 20; // in ohm
7 R3 = 46; // in ohm
8 R4 = 50; // in ohm
9 R5 = 15; // in ohm
10 R6 = 60; // in ohm
11 R7 = 16; // in ohm
12 R8 = 80; // in ohm
13
14 //calculation:
15 //One method of analysing a multi-branch network as
  shown in Figure 33.22 is to use Th evenin s
  theorem on one part of the network at a time. For
  example, the part of the circuit to the left of
  AA may be reduced to a Th evenin equivalent
  circuit.
16 //From Figure 33.23,
17 E1 = (R2/(R1 + R2))*V
18 z1 = R1*R2/(R1 + R2)
19 //Thus the network of Figure 33.22 reduces to that

```

```

of Figure 33.24. The part of the network shown in
Figure 33.24 to the left of BB may be reduced to
a Th evenin equivalent circuit , where
20 E2 = (R4/(R3 + R4 + z1))*E1
21 z2 = R4*(z1 + R3)/(R4 + z1 + R3)
22 //Thus the original network reduces to that shown in
Figure 33.25. The part of the network shown in
Figure 33.25 to the left of CC may be reduced to
a Th evenin equivalent circuit , where
23 E3 = (R6/(R5 + R6 + z2))*E2
24 z3 = R6*(z2 + R5)/(R5 + z2 + R6)
25 //Thus the original network reduces to that of
Figure 33.26, from which the current in the 80
ohm resistor is given by
26 I = E3/(z3 + R7 + R8)
27
28 printf("\n\n Result \n\n")
29 printf("\n the current flowing in the 80 ohm
resistor is %.2f A",I)

```

---

### Scilab code Exa 33.05 Example 5

```

1 //Problem 33.05:Determine the Th evenin equivalent
circuit with respect to terminals AB of the
circuit shown in Figure 33.27. Hence determine (a
) the magnitude of the current flowing in a (3.75
+ i11) ohm impedance connected across terminals
AB, and (b) the magnitude of the p.d. across the(
3.75 + i11)ohm impedance.
2
3 //initializing the variables:
4 rv = 24; // in volts
5 thetav = 0; // in degrees
6 R1 = -1*i*3; // in ohm
7 R2 = 4; // in ohm

```

```

8 R3 = %i*3; // in ohm
9
10 // calculation :
11 // voltage
12 V = rv*cos(thetav*%pi/180) + %i*rv*sin(thetav*%pi
    /180)
13 //Current I1 shown in Figure 33.27 is given by
14 I1 = V/(R1 + R2 + R3)
15 //The Th evenin equivalent voltage , i.e., the open-
    circuit voltage across terminals AB, is given by
16 E = I1*(R2 + R3)
17 //When the voltage source is removed, the impedance
    z looking in at AB is given by
18 z = (R2 + R3)*R1/(R1 + R2 + R3)
19 //Thus the Th evenin equivalent circuit is as shown
    in Figure 33.28.
20 //when (3.75 + i11) ohm impedance connected across
    terminals AB, the current I flowing in the
    impedance is given by
21 R = 3.75 + %i*11; // in ohms
22 I = E/(R + z)
23 Imag = (real(I)^2 + imag(I)^2)^0.5
24 //the p.d. across the( 3.75 + i11)ohm impedance.
25 VR = I*R
26 VRmag = (real(VR)^2 + imag(VR)^2)^0.5
27
28 printf("\n\n Result \n\n")
29 printf("\n (a) the current I flowing in the (3.75 +
    i11) impedance is given by is %.0f A",Imag)
30 printf("\n (b) the magnitude of the p.d. across the
    impedance is %.1f V",VRmag)

```

---

### Scilab code Exa 33.06 Example 6

```

1 //Problem 33.06: Use Th evenin s theorem to

```

```

    determine the current flowing in the capacitor of
    the network shown in Figure 33.29.
2
3 //initializing the variables:
4 rv = 16.55; // in volts
5 thetav = -22.62; // in degrees
6 R1 = 4; // in ohm
7 R2 = %i*2; // in ohm
8 R3 = %i*6; // in ohm
9 R4 = 3; // in ohm
10 R5 = 5; // in ohm
11 R6 = -1*%i*8; // in ohm
12
13 //calculation:
14 //voltage
15 V = rv*cos(thetav*%pi/180) + %i*rv*sin(thetav*%pi
    /180)
16 //The capacitor is removed from branch AB, as shown
    in Figure 33.30.
17 //Impedance, Z
18 Z1 = R3 + R4 + R5
19 Z = R1 + (Z1*R2/(R2 + Z1))
20 I1 = V/Z
21 I2 = (R2/(R2 +Z1))*I1
22 //The open-circuit voltage, E
23 E = I2*R5
24 //If the voltage source is removed from Figure
    33.30, the impedance, z, looking in at AB
    is given by
25 z = R5*((R1*R2/(R1 + R2)) + R3 + R4)/(R5 + ((R1*R2/(
    R1 + R2)) + R3 + R4))
26 //The Thevenin equivalent circuit is shown in
    Figure 33.31, where the current flowing in the
    capacitor, I, is given by
27 I = E/(z + R6)
28 Imag = (real(I)^2 + imag(I)^2)^0.5
29 phiid = (atan(imag(I)/real(I)))*180/%pi
30 printf("\n\n Result \n\n")

```

```
31 printf("\n the current flowing in the capacitor of
    the network is %.2f/-%.2f A",Imag,phiid)
```

---

### Scilab code Exa 33.07 Example 7

```
1 //Problem 33.07: For the network shown in Figure
    33.32, derive the Thevenin equivalent circuit
    with respect to terminals PQ, and hence determine
    the power dissipated by a 2 ohm resistor
    connected across PQ.
2
3 //initializing the variables:
4 rv1 = 5; // in volts
5 rv2 = 10; // in volts
6 thetav1 = 45; // in degrees
7 thetav2 = 0; // in degrees
8 R1 = 8; // in ohm
9 R2 = 5; // in ohm
10 R3 = %i*3; // in ohm
11 R4 = 4; // in ohm
12
13 //calculation:
14 //voltage
15 V1 = rv1*cos(thetav1*%pi/180) + %i*rv1*sin(thetav1*
    %pi/180)
16 V2 = rv2*cos(thetav2*%pi/180) + %i*rv2*sin(thetav2*
    %pi/180)
17 //Current I1 shown in Figure 33.32 is given by
18 I1 = V2/(R2 + R3 + R4)
19 //Hence the voltage drop across the 5 ohm resistor
    is given by Vx is in the direction shown in
    Figure 33.32,
20 Vx = I1*R2
21 //The open-circuit voltage E across PQ is the phasor
    sum of V1, Vx and V2, as shown in Figure 33.33.
```



```

22 E = V2 - V1 - Vx
23 //The impedance, z, looking in at terminals PQ
    with the voltage sources removed is given by
24 z = R1 + R2*(R3 + R4)/(R2 + R3 + R4)
25 //The Th evenin equivalent circuit is shown in
    Figure 33.34 with the 2 ohm resistance connected
    across terminals PQ.
26 //The current flowing in the 2 ohm resistance is
    given by
27 R = 2; // in ohms
28 I = E/(z + R)
29 Imag = (real(I)^2 + imag(I)^2)^0.5
30 //power P dissipated in the 2 ohm resistor is given
    by
31 Pr2 = R*Imag^2
32
33 printf("\n\n Result \n\n")
34 printf("\n power P dissipated in the 2 ohm resistor
    is %.4 f W",Pr2)

```

---

### Scilab code Exa 33.08 Example 8

```

1 //Problem 33.08: For the a.c. bridge network shown
    in Figure 33.35, determine the current flowing in
    the capacitor, and its direction, by using
    Th evenin s theorem. Assume the 306/_0 V
    source to have negligible internal impedance.
2
3 //initializing the variables:
4 rv = 30; // in volts
5 thetav = 0; // in degrees
6 R1 = 15; // in ohm
7 R2 = 40; // in ohm
8 R3 = %i*20; // in ohm
9 R4 = 20; // in ohm

```

```

10 R5 = %i*5; // in ohm
11 R6 = 5; // in ohm
12 R7 = -1*%i*25; // in ohm
13
14 //calculation :
15 //voltage
16 V = rv*cos(thetav*%pi/180) + %i*rv*sin(thetav*%pi
    /180)
17 //The R7 is initially removed from the network , as
    shown in Figure 33.36
18 Z1 = R1
19 Z2 = R2
20 Z3 = R3 + R4
21 Z4 = R5 + R6
22 //P.d. between A and C,
23 Vac = (Z1/(Z1 + Z4))*V
24 //P.d. between B and C,
25 Vbc = (Z2/(Z2 + Z3))*V
26 //Assuming that point A is at a higher potential
    than point B, then the p.d. between A and B is
27 Vab = Vac - Vbc
28 //the open-circuit voltage across AB is given by
29 E = Vab
30 //Point C is at a potential of V . Between C and A
    is a volt drop of Vac. Hence the voltage at point
    A is
31 Va = V - Vac
32 //Between points C and B is a voltage drop of Vbc.
    Hence the voltage at point B
33 Vb = V - Vbc
34 //Replacing the V source with a short-circuit (i.e.,
    zero internal impedance) gives the network shown
    in Figure 33.37(a). The network is shown redrawn
    in Figure 33.37(b) and simplified in Figure
    33.37(c). Hence the impedance, z, looking
    in at terminals AB is given by
35 z = Z1*Z4/(Z1 + Z4) + Z2*Z3/(Z2 + Z3)
36 //The Th evenin equivalent circuit is shown in

```

Figure 33.38, where current  $I$  is given by

```

37 I = E/(z + R7)
38 Imag = (real(I)^2 + imag(I)^2)^0.5
39
40 printf("\n\n Result \n\n")
41 printf("\n the current flowing in the capacitor is
    %.3f A in direction from B to A.",Imag)

```

---

### Scilab code Exa 33.09 Example 9

```

1 //Problem 33.09: Use Norton s theorem to determine
    the value of current I in the circuit shown in
    Figure 33.47.
2
3 //initializing the variables:
4 V = 5; // in volts
5 R1 = 2; // in ohm
6 R2 = 3; // in ohm
7 R3 = -1*i*3; // in ohm
8 R4 = 2.8; // in ohm
9
10 //calculation:
11 //The branch containing the R4 is short-circuited ,
    as shown in Figure 33.48.
12 //The R2 in parallel with a short-circuit is the
    same as R2 in parallel with 0 ohm giving an
    equivalent impedance of
13 Z1 = R2*0/(R3 + 0)
14 //Hence the network reduces to that shown in Figure
    33.49, where
15 Isc = V/R1
16 //If the Voltage source is removed from the network
    the input impedance, z, looking-in at a
    break made in AB of Figure 33.48 gives
17 z = R1*R2/(R1 + R2)

```

```

18 //The Norton equivalent network is shown in Figure
    33.51, where current I is given by
19 I = (z/(z + R4 + R3))*Isc
20
21 printf("\n\n Result \n\n")
22 printf("\n the current flowing in the capacitor is
    %.2f + (%.2f)i A",real(I), imag(I))

```

---

### Scilab code Exa 33.10 Example 10

```

1 //Problem 33.10: For the circuit shown in Figure
    33.52 determine the current flowing in the
    inductive branch by using Norton s theorem.
2
3 //initializing the variables:
4 V1 = 20; // in volts
5 V2 = 10; // in volts
6 R1 = 2; // in ohm
7 R2 = 1.5; // in ohm
8 R3 = %i*2.95; // in ohm
9 R4 = 3; // in ohm
10
11 //calculation:
12 //The inductive branch is initially short-circuited ,
    as shown in Figure 33.53.
13 //From Figure 33.53,
14 I1 = V1/R1
15 I2 = V2/R4
16 Isc = I1 + I2
17 //If the voltage sources are removed, the impedance,
    z, looking in at a break made in AB is
    given by
18 z = R1*R4/(R1 + R4)
19 //The Norton equivalent network is shown in Figure
    33.54, where current I is given by

```

```

20 I = (z/(z + R2 + R3))*Isc
21
22 printf("\n\n Result \n\n")
23 printf("\n the current flowing in the inductive
    branch is %.2f + (%.2f)i A",real(I), imag(I))

```

---

### Scilab code Exa 33.11 Example 11

```

1 //Problem 33.11: Use Norton s theorem to determine
    the magnitude of the p.d. across the 1 ohm
    resistance of the network shown in Figure 33.55.
2
3 //initializing the variables:
4 V = 10; // in volts
5 R1 = 4; // in ohm
6 R2 = 4; // in ohm
7 R3 = -1*i*2; // in ohm
8 R4 = 1; // in ohm
9
10 //calculation:
11 //The branch containing the R4 is initially short-
    circuited , as shown in Figure 33.56.
12 //R2 in parallel with R3 in parallel with 0 ohm (i.e
    ., the short-circuit) is equivalent 0 ohm giving
    the equivalent circuit of Figure 33.57. Hence Isc
13 Isc = V/R1
14 //The voltage source is removed from the network of
    Figure 33.55, as shown in Figure 33.58, and the
    impedance z, looking in at a break made in
    AB is given by
15 z = 1/(1/R1 + 1/R2 + 1/R3)
16 //The Norton equivalent network is shown in Figure
    33.59, from which current I is given by
17 I = (z/(z + R4))*Isc
18 Imag = (real(I)^2 + imag(I)^2)^0.5

```

```

19 Vr1 = Imag*R4
20
21 printf("\n\n Result \n\n")
22 printf("\n the magnitude of the p.d. across the 1
    ohm resistor is %.2f V", Vr1)

```

---

### Scilab code Exa 33.12 Example 12

```

1 //Problem 33.12:For the network shown in Figure
    33.60, obtain the Norton equivalent network at
    terminals AB. Hence determine the power
    dissipated in a 5 ohm resistor connected between
    A and B.
2
3 //initializing the variables:
4 rv = 20; // in volts
5 thetav = 0; // in degrees
6 R1 = 2; // in ohm
7 R2 = 4; // in ohm
8 R3 = %i*3; // in ohm
9 R4 = -1*%i*3; // in ohm
10
11 //calculation:
12 //voltage
13 V = rv*cos(thetav*%pi/180) + %i*rv*sin(thetav*%pi
    /180)
14 //Terminals AB are initially short-circuited, as
    shown in Figure 33.61.
15 //The circuit impedance Z presented to the voltage
    source is given by
16 Z = R1 + R4*(R2 + R3)/(R2 + R3 + R4)
17 //Thus current I in Figure 33.61 is given by
18 I = V/Z
19 Isc = ((R2 + R3)/(R2 + R3 + R4))*I
20 //Removing the voltage source of Figure 33.60 gives

```

```

    the network Figure 33.62 of Figure 33.62.
    Impedance, z, looking in at terminals AB is
    given by
21 z = R4 + R1*(R2 + R3)/(R2 + R3 + R1)
22 //The Norton equivalent network is shown in Figure
    33.63.
23 R = 5; // in ohms
24 //Current IL
25 IL = (z/(z + R))*Isc
26 IImag = (real(IL)^2 + imag(IL)^2)^0.5
27 //the power dissipated in the 5 ohm resistor is
28 Pr5 = R*IImag^2
29
30 printf("\n\n Result \n\n")
31 printf("\n the power dissipated in the 5 ohm
    resistor is %.2f W", Pr5)

```

---

### Scilab code Exa 33.13 Example 13

```

1 //Problem 33.13: Derive the Norton equivalent network
    with respect to terminals PQ for the network
    shown in Figure 33.64 and hence determine the
    magnitude of the current flowing in a 2 ohm
    resistor connected across PQ.
2
3 //initializing the variables:
4 rv1 = 5; // in volts
5 rv2 = 10; // in volts
6 thetav1 = 45; // in degrees
7 thetav2 = 0; // in degrees
8 R1 = 8; // in ohm
9 R2 = 5; // in ohm
10 R3 = %i*3; // in ohm
11 R4 = 4; // in ohm
12

```

```

13 // calculation :
14 // voltage
15 V1 = rv1*cos(thetav1*%pi/180) + %i*rv1*sin(thetav1*
    %pi/180)
16 V2 = rv2*cos(thetav2*%pi/180) + %i*rv2*sin(thetav2*
    %pi/180)
17 //Terminals PQ are initially short-circuited , as
    shown in Figure 33.65.
18 //Currents I1 and I2 are shown labelled.
    Kirchhoff s laws are used.
19 //For loop ABCD, and moving anticlockwise ,
20 //I1*(R2 + R3 + R4) + I2*(R3 + R4) = V2
21 //For loop DPQC, and moving clockwise ,
22 //R2*I1 - R1*I2 = V2 - V1
23 //Solving Equations by using determinants gives
24 d1 = [V2 (R3 + R4); (V2 - V1) -1*R1]
25 D1 = det(d1)
26 d2 = [(R2 + R3 + R4) V2; R2 (V2 - V1)]
27 D2 = det(d2)
28 d = [(R2 + R3 + R4) (R3 + R4); R2 -1*R1]
29 D = det(d)
30 I1 = D1/D
31 I2 = D2/D
32 //the short-circuit current Isc
33 Isc = I2
34 //The impedance, z, looking in at a break made
    between P and Q is given by
35 z = R1 + R2*(R3 + R4)/(R2 + R3 + R4)
36 //The Norton equivalent circuit is shown in Figure
    33.66, where current I is given by
37 R = 2; //in ohm
38 I = (z/(z + R))*Isc
39 Imag = (real(I)^2 + imag(I)^2)^0.5
40
41 printf("\n\n Result \n\n")
42 printf("\n the magnitude of the current flowing 5
    ohm resistor is %.2f A", Imag)

```

---



**Scilab code Exa 33.15** Example 15

```
1 //Problem 33.15: (a) Convert the circuit to the left
  of terminals AB in Figure 33.72 to an equivalent
  Th evenin circuit by initially converting to a
  Norton equivalent circuit. (b) Determine the
  magnitude of the current flowing in the (1.8+i4)
  ohm impedance connected between terminals A and B
  of Figure 33.72.
2
3 //initializing the variables:
4 E1 = 12; // in volts
5 E2 = 24; // in volts
6 Z1 = 3; // in ohm
7 Z2 = 2; // in ohm
8 R1 = %i*4; // in ohm
9 R2 = 1.8; // in ohm
10
11 //calculation:
12 Z3 = R1 + R2
13 //For the branch containing the E1 source ,
  conversion to a Norton equivalent network gives
14 Isc1 = E1/Z1
15 //For the branch containing the E2 source ,
  conversion to a Norton equivalent circuit gives
16 Isc2 = E2/Z2
17 //Thus Figure 33.73 shows a network equivalent to
  Figure 33.72. From Figure 33.73, the total short-
  circuit current
18 Isc = Isc1 + Isc2
19 //the total impedance is given by
20 z = Z1*Z2/(Z1 + Z2)
21 //Thus Figure 33.73 simplifies to Figure 33.74.
22 //The open-circuit voltage across AB of Figure
```

```

33.74, E
23 E = Isc*z
24 //the impedance looking in at AB, is z
25 //the Thevenin equivalent circuit is as shown in
    Figure 33.75.
26 R = 1.8 + %i*4; // in ohm
27 //when R impedance is connected to terminals AB of
    Figure 33.75, the current I flowing is given by
28 I = E/(z + R)
29 Imag = (real(I)^2 + imag(I)^2)^0.5
30
31 printf("\n\n Result \n\n")
32 printf("\n the magnitude of the current flowing (1.8
    + i4) ohm resistor is %.2f A", Imag)

```

---

### Scilab code Exa 33.16 Example 16

```

1 //Problem 33.16: Determine, by successive
    conversions between Thevenin's and Norton's
    equivalent networks, a Thevenin equivalent
    circuit for terminals AB of Figure 33.76. Hence
    determine the magnitude of the current flowing in
    the capacitive branch connected to terminals AB.
2
3 //initializing the variables:
4 V1 = 5; // in volts
5 V2 = 10; // in volts
6 i = 0.001; // in Amperes
7 R1 = 1000; // in ohm
8 R2 = 4000; // in ohm
9 R3 = 2000; // in ohm
10 R4 = 200; // in ohm
11 R5 = -1*%i*4000; // in ohm
12
13 //calculation:

```

```

14 //For the branch containing the V1 source ,
    conversion to a Norton equivalent network gives
15 Isc1 = V1/R1
16 z1 = R1
17 //For the branch containing the V2 source ,
    conversion to a Norton equivalent circuit gives
18 Isc2 = V2/R2
19 z2 = R2
20 //Thus the circuit of Figure 33.76 converts to that
    of Figure 33.77.
21 //The above two Norton equivalent networks shown in
    Figure 33.77 may be combined, since the total
    short-circuit current is
22 Isc = Isc1 + Isc2
23 //the total impedance is given by
24 Z1 = z1*z2/(z1 + z2)
25 //Both of the Norton equivalent networks shown in
    Figure 33.78 may be converted to Th evenin
    equivalent circuits. Open-circuit voltage across
    CD is
26 Ecd = Isc*Z1
27 //the impedance looking in at CD is Z1
28 //Open-circuit voltage across EF
29 Eef = i*R3
30 //the impedance looking in Figure 33.79 at EF
31 Z2 = R3
32 //Thus Figure 33.78 converts to Figure 33.79.
33 //Combining the two Th evenin circuits gives e.m.f.
34 E = Ecd - Eef
35 //impedance z
36 z = Z1 + Z2
37 //the Th evenin equivalent circuit for terminals AB
    of Figure 33.76 is as shown in Figure 33.80.
38 Z3 = R4 + R5
39 //If an impedance Z3 is connected across terminals
    AB, then the current I flowing is given by
40 I = E/(z + Z3)
41 Imag = (real(I)^2 + imag(I)^2)^0.5

```

```

42
43 printf("\n\n Result \n\n")
44 printf("\n the current in the capacitive branch is %
    .2E A", Imag)

```

---

**Scilab code Exa 33.17** Example 17

```

1 //Problem 33.17: (a) Determine an equivalent
  Th evenin circuit for terminals AB of the
  network shown in Figure 33.81. (b) Calculate the
  power dissipated in a (600 - i800)ohm impedance
  connected between A and B of Figure 33.81.
2
3 //initializing the variables:
4 V = 5; // in volts
5 i = 0.004; // in Amperes
6 R1 = 2000; // in ohm
7 R2 = %i*1000; // in ohm
8
9 //calculation:
10 //Converting the Th evenin circuit to a Norton
    network gives
11 Isc1 = V/R2
12 //Thus Figure 33.81 converts to that shown in Figure
    33.82. The two Norton equivalent networks may be
    combined, giving
13 Isc = Isc1 + i
14 z = R1*R2/(R1 + R2)
15 //This results in the equivalent network shown in
    Figure 33.83. Converting to an equivalent
    Th evenin circuit gives open circuit e.m.f.
    across AB,
16 E = Isc*z
17 //Thus the The venin equivalent circuit is as shown
    in Figure 33.84.

```

```
18 R = 600 - %i*800; // in ohms
19 //When a R impedance is connected across AB, the
    current I flowing is given by
20 I = E/(z + R)
21 Imag = (real(I)^2 + imag(I)^2)^0.5
22 //the power dissipated in the R resistor is
23 PR = R*Imag^2
24
25 printf("\n\n Result \n\n")
26 printf("\n the power dissipated in the (600 - i800)
    ohm resistor is %.2E W", PR)
```

---

# Chapter 34

## Delta star and star delta transformations

Scilab code Exa 34.02 Example 2

```
1 //Problem 34.02: For the network shown in Figure
   // 34.7, determine (a) the equivalent circuit
   // impedance across terminals AB, (b) supply current
   // I and (c) the power dissipated in the 10 ohm
   // resistor.
2
3 //initializing the variables:
4 rv = 40; // in volts
5 thetav = 0; // in degrees
6 ZA = %i*10; // in ohm
7 ZB = %i*15; // in ohm
8 ZC = %i*25; // in ohm
9 ZD = -1*%i*8; // in ohm
10 ZE = 10; // in ohm
11
12 //calculation:
13 //voltage
14 V = rv*cos(thetav*%pi/180) + %i*rv*sin(thetav*%pi
   //180)
```

```

15 //The network of Figure 34.7 is redrawn, as in
    Figure 34.8, showing more clearly the part of the
    network 1, 2, 3 forming a delta connection This
    may be transformed into a star connection as
    shown in Figure 34.9.
16 Z1 = ZA*ZB/(ZA + ZB + ZC)
17 Z2 = ZC*ZB/(ZA + ZB + ZC)
18 Z3 = ZA*ZC/(ZA + ZB + ZC)
19 //The equivalent network is shown in Figure 34.10
    and is further simplified in Figure 34.11
20 //((ZE + Z3) in parallel with (Z1 + ZD) gives an
    equivalent impedance of
21 z = (ZE + Z3)*(Z1 + ZD)/(Z1 + ZD + ZE + Z3)
22 //Hence the total circuit equivalent impedance
    across terminals AB is given by
23 Zab = z + Z2
24 //Supply current I
25 I = V/Zab
26 I1 = ((Z1 + ZD)/(Z1 + ZD + ZE + Z3))*I
27 I1mag = (real(I1)^2 + imag(I1)^2)^0.5
28 //Power P dissipated in the 10 ohm resistance of
    Figure 34.7 is given by
29 Pr10 = ZE*I1mag^2
30
31 printf("\n\n Result \n\n")
32 printf("\n (a)the equivalent circuit impedance
    across terminals AB is %.2f + (%.2f)i ohm",real(
    Zab), imag(Zab))
33 printf("\n (b)supply current I is %.2f + (%.2f)i A",
    real(I), imag(I))
34 printf("\n (c)power P dissipated in the 10 ohm
    resistor is %.2f W",Pr10)

```

---

Scilab code Exa 34.03 Example 3

```

1 //Problem 34.03: Determine , for the bridge network
   shown in Figure 34.12, (a) the value of the
   single equivalent resistance that replaces the
   network between terminals A and B, (b) the
   current supplied by the 52 V source , and (c) the
   current flowing in the 8 ohm resistance .
2
3 //initializing the variables :
4 V = 52; // in volts
5 ZA = 8; // in ohm
6 ZB = 16; // in ohm
7 ZC = 40; // in ohm
8 ZD = 1; // in ohm
9 ZE = 4; // in ohm
10
11 //calculation :
12 //In Figure 34.12, no resistances are directly in
   parallel or directly in series with each other .
   However, ACD and BCD are both delta connections
   and either may be converted into an equivalent
   star connection . The delta network BCD is redrawn
   in Figure 34.13(a) and is transformed into an
   equivalent star connection as shown in Figure
   34.13(b) , where
13 Z1 = ZA*ZB/(ZA + ZB + ZC)
14 Z2 = ZC*ZB/(ZA + ZB + ZC)
15 Z3 = ZA*ZC/(ZA + ZB + ZC)
16 //The network of Figure 34.12 may thus be redrawn as
   shown in Figure 34.14. The Z1 and ZE are in
   series with each other , as are the ZD and Z3
   resistors . Hence the equivalent network is as
   shown in Figure 34.15. The total equivalent
   resistance across terminals A and B is given by
17 Zab = (Z1 + ZE)*(ZD + Z3)/(Z1 + ZE + ZD + Z3) + Z2
18 //Current supplied by the source , i.e. , current I in
   Figure 34.15, is given by
19 I = V/Zab
20 //From Figure 34.15, current I1

```



```

21 I1 = ((ZD + Z3)/(Z1 + ZE + ZD + Z3))*I
22 //current I2
23 I2 = I - I1
24 //From Figure 34.14, p.d. across AC,
25 Vac = I1*ZE
26 //p.d. across AD
27 Vad = I2*ZD
28 //Hence p.d. between C and D is given
29 Vcd = Vac - Vad
30 //current in the 8 ohm resistance
31 Ir8 = Vcd/ZA
32
33 printf("\n\n Result \n\n")
34 printf("\n (a)the equivalent circuit impedance
    across terminals AB is %.2f ohm",Zab)
35 printf("\n (b)the current supplied by the 52 V
    source is %.2f A",I)
36 printf("\n (c)the current flowing in the 8 ohm
    resistance is %.2f A",Ir8)

```

---

#### Scilab code Exa 34.05 Example 5

```

1 //Problem 34.05: For the network shown in Figure
    34.20, determine (a) the current flowing in the
    (0+i10) ohm impedance, and (b) the power
    dissipated in the (20 + i0) ohm impedance.
2
3 //initializing the variables:
4 rv = 120; // in volts
5 thetav = 0; // in degrees
6 ZA = 25 - %i*5; // in ohm
7 ZB = 15 + %i*10; // in ohm
8 ZC = 20 - %i*30; // in ohm
9 ZD = 20 + %i*0; // in ohm
10 ZE = 0 + %i*10; // in ohm

```

```

11 ZF = 2.5 - %i*5; // in ohm
12
13 // calculation :
14 // voltage
15 V = rv*cos(thetav*%pi/180) + %i*rv*sin(thetav*%pi
    /180)
16 //The network may initially be simplified by
    transforming the delta PQR to its equivalent star
    connection as represented by impedances Z1, Z2
    and Z3 in Figure 34.21. From equation (34.7),
17 Z1 = ZA*ZB/(ZA + ZB + ZC)
18 Z2 = ZC*ZB/(ZA + ZB + ZC)
19 Z3 = ZA*ZC/(ZA + ZB + ZC)
20 //The network is shown redrawn in Figure 34.22 and
    further simplified in Figure 34.23, from which,
21 Zab = ((Z3 + ZE)*(ZD + Z2)/(Z2 + ZE + ZD + Z3)) + (
    Z1 + ZF)
22 //Current I1
23 I1 = V/Zab
24 //current I2
25 I2 = ((ZE + Z3)/(Z2 + ZE + ZD + Z3))*I1
26 //current I3
27 I3 = I1 - I2
28 //The power P dissipated in the ZD impedance of
    Figure 34.20 is given by
29 Pzd = ZD*I2^2
30
31 printf("\n\n Result \n\n")
32 printf("\n (a)the current flowing in the (0+i10) ohm
    impedance is %.2f A",I3)
33 printf("\n (b) the power dissipated in the (20 + i0)
    ohm impedance is %.2f W",Pzd)

```

---

## Chapter 35

# Maximum power transfer theorems and impedance matching

Scilab code Exa 35.01 Example 1

```
1 //Problem 35.01: For the circuit shown in Figure
   35.2 the load impedance Z is a pure resistance .
   Determine (a) the value of R for maximum power to
   be transferred from the source to the load , and
   (b) the value of the maximum power delivered to R
   .
2
3 //initializing the variables :
4 rv = 120; // in volts
5 thetav = 0; // in degrees
6 Z = 15 + %i*20; // in ohm
7
8 //calculation :
9 //voltage
10 V = rv*cos(thetav*%pi/180) + %i*rv*sin(thetav*%pi
   /180)
11 //maximum power transfer occurs when R = mod(Z)
```

```

12 R = (real(Z)^2 + imag(Z)^2)^0.5
13 //the total circuit impedance
14 ZT = Z + R
15 //Current I flowing in the load is given by
16 I = V/ZT
17 Imag = (real(I)^2 + imag(I)^2)^0.5
18 //maximum power delivered
19 P = R*Imag^2
20
21 printf("\n\n Result \n\n")
22 printf("\n (a)maximum power transfer occurs when R
    is %.0f ohm",R)
23 printf("\n (b) maximum power delivered is %.0f W",P)

```

---

#### Scilab code Exa 35.02 Example 2

```

1 //Problem 35.02: If the load impedance Z in Figure
    35.2 of problem 35.01 consists of variable
    resistance R and variable reactance X, determine
    (a) the value of Z that results in maximum power
    transfer, and (b) the value of the maximum power.
2
3 //initializing the variables:
4 rv = 120; // in volts
5 thetav = 0; // in degrees
6 Z = 15 + %i*20; // in ohm
7
8 //calculation:
9 //voltage
10 V = rv*cos(thetav*pi/180) + %i*rv*sin(thetav*pi
    /180)
11 //maximum power transfer occurs when X = -1*imag(Z)
    and R = real(Z)
12 z = real(Z) - %i*imag(Z)
13 //Total circuit impedance at maximum power transfer

```

```

        condition ,
14 ZT = Z + z
15 //Current I flowing in the load is given by
16 I = V/ZT
17 Imag = (real(I)^2 + imag(I)^2)^0.5
18 //maximum power delivered
19 P = real(Z)*I^2
20
21 printf("\n\n Result \n\n")
22 printf("\n (a)maximum power transfer occurs when Z
        is %.0f + (%.0f)i ohm",real(z), imag(z))
23 printf("\n (b) maximum power delivered is %.0f W",P)

```

---

### Scilab code Exa 35.03 Example 3

```

1 //Problem 35.03: For the network shown in Figure
    35.3, determine (a) the value of the load
    resistance R required for maximum power transfer ,
    and (b) the value of the maximum power
    transferred.
2
3 //initializing the variables:
4 rv = 200; // in volts
5 thetav = 0; // in degrees
6 R1 = 100; // in ohm
7 C = 1E-6; // in farad
8 f = 1000; // in Hz
9
10 //calculation:
11 //voltage
12 V = rv*cos(thetav*pi/180) + %i*rv*sin(thetav*pi
    /180)
13 //Capacitive reactance , Xc
14 Xc = 1/(2*pi*f*C)
15 //Hence source impedance ,

```

```

16 z = R1*(%i*Xc)/(R1 + %i*Xc)
17 //maximum power transfer is achieved when R = mod(z)
18 R = (real(z)^2 + imag(z)^2)^0.5
19 //Total circuit impedance at maximum power transfer
   condition ,
20 ZT = z + R
21 //Current I flowing in the load is given by
22 I = V/ZT
23 Imag = (real(I)^2 + imag(I)^2)^0.5
24 //maximum power transferred ,
25 P = R*Imag^2
26
27 printf("\n\n Result \n\n")
28 printf("\n (a)maximum power transfer occurs when R
   is %.2f ohm",R)
29 printf("\n (b) maximum power delivered is %.0f W",P)

```

---

#### Scilab code Exa 35.04 Example 4

```

1 //Problem 35.04: In the network shown in Figure 35.4
   the load consists of a fixed capacitive
   reactance of 7 ohm and a variable resistance R.
   Determine (a) the value of R for which the power
   transferred to the load is a maximum, and (b) the
   value of the maximum power.
2
3 //initializing the variables:
4 rv = 60; // in volts
5 thetav = 0; // in degrees
6 R1 = 4; // in ohm
7 XL = 10; // in ohm
8 Xc = 7; // in ohm
9 R2 = %i*XL; // in ohm
10 R3 = -1*%i*Xc; // in ohm
11

```

```

12 //calculation :
13 //voltage
14 V = rv*cos(thetav*pi/180) + %i*rv*sin(thetav*pi
    /180)
15 //maximum power transfer is achieved when
16 R = (R1^2 + (XL - Xc)^2)^0.5
17 //Hence source impedance ,
18 ZT = R1 + R2 + R3 + R
19 //Current I flowing in the load is given by
20 I = V/ZT
21 Imag = (real(I)^2 + imag(I)^2)^0.5
22 //maximum power transferred ,
23 P = R*Imag^2
24
25 printf("\n\n Result \n\n")
26 printf("\n (a)maximum power transfer occurs when R
    is %.2 f ohm",R)
27 printf("\n (b) maximum power delivered is %.0f W",P)

```

---

#### Scilab code Exa 35.05 Example 5

```

1 //Problem 35.05: Determine the value of the load
    resistance R shown in Figure 35.5 that gives
    maximum power dissipation and calculate the value
    of this power.
2
3 //initializing the variables:
4 V = 20; // in volts
5 R1 = 5; // in ohm
6 R2 = 15; // in ohm
7
8 //calculation :
9 //R is removed from the network as shown in Figure
    35.6
10 //P.d. across AB, E

```

```

11 E = (R2/(R1 + R2))*V
12 //Impedance looking -in at terminals AB with
    the source removed is given by
13 r = R1*R2/(R1 + R2)
14 //The equivalent Th evenin circuit supplying
    terminals AB is shown in Figure 35.7. From
    condition (2), for maximum power transfer
15 R = r
16 //Current I flowing in the load is given by
17 I = E/(R + r)
18 //maximum power transferred ,
19 P = R*I^2
20
21 printf("\n\n Result \n\n")
22 printf("\n (a)maximum power transfer occurs when R
    is %.2f ohm",R)
23 printf("\n (b) maximum power delivered is %.0f W",P)

```

---

### Scilab code Exa 35.06 Example 6

```

1 //Problem 35.06: Determine, for the network shown in
    Figure 35.8, (a) the values of R and X that will
    result in maximum power being transferred across
    terminals AB, and (b) the value of the maximum
    power.
2
3 //initializing the variables:
4 rv = 100; // in volts
5 thetav = 30; // in degrees
6 R1 = 5; // in ohm
7 R2 = 5; // in ohm
8 R3 = %i*10; // in ohm
9
10 //calculation:
11 //voltage

```



```

12 V = rv*cos(thetav*pi/180) + %i*rv*sin(thetav*pi
    /180)
13 //Resistance R and reactance X are removed from the
    network as shown in Figure 35.9
14 //P.d. across AB,
15 E = ((R2 + R3)/(R1 + R2 + R3))*V
16 //With the source removed the impedance, z,
    looking in at terminals AB is given by:
17 z = (R2 + R3)*R1/(R1 + R2 + R3)
18 //The equivalent Th evenin circuit is shown in
    Figure 35.10. From condition 3, maximum power
    transfer is achieved when X = -1*imag(z) and R =
    real(z)
19 X = -1*imag(z)
20 R = real(z)
21 Z = R + %i*X
22 //Current I flowing in the load is given by
23 I = E/(z + Z)
24 Imag = (real(I)^2 + imag(I)^2)^0.5
25 //maximum power transferred ,
26 P = R*Imag^2
27
28 printf("\n\n Result \n\n")
29 printf("\n (a)maximum power transfer occurs when R
    is %.2f ohm and X is %.2f ohm",R, X)
30 printf("\n (b) maximum power delivered is %.0f W",P)

```

---

### Scilab code Exa 35.07 Example 7

```

1 //Problem 35.07: Determine the optimum value of load
    resistance for maximum power transfer if the
    load is connected to an amplifier of output
    resistance 448 ohm through a transformer with a
    turns ratio of 8:1.
2

```

```

3 //initializing the variables:
4 Ro = 448; // in ohm
5 tr = 8; // turn ratio N1/N2
6
7 //calculation:
8 //The equivalent input resistance r of the
   transformer must be Ro for maximum power transfer
   .
9 r = Ro
10 RL = r*(1/tr)^2
11
12 printf("\n\n Result \n\n")
13 printf("\n the optimum value of load resistance is %
   .0 f ohm",RL)

```

---

#### Scilab code Exa 35.08 Example 8

```

1 //Problem 35.08: A generator has an output impedance
   of (450 + i60) ohm. Determine the turns ratio of
   an ideal transformer necessary to match the
   generator to a load of (40 + i19) ohm for maximum
   transfer of power.
2
3 //initializing the variables:
4 Zo = 450 + %i*60; // in ohm
5 ZL = 40 + %i*19; // in ohm
6
7 //calculation:
8 //transformer turns ratio tr = (N1/N2)
9 Zomag = (real(Zo)^2 + imag(Zo)^2)^0.5
10 ZLmag = (real(ZL)^2 + imag(ZL)^2)^0.5
11 tr = (Zomag/ZLmag)^0.5
12
13 printf("\n\n Result \n\n")
14 printf("\n the transformer turns ratio is %.2 f",tr)

```

---

**Scilab code Exa 35.09** Example 9

```
1 //Problem 35.09: A single-phase, 240 V/1920 V ideal
  transformer is supplied from a 240 V source
  through a cable of resistance 5 ohm. If the load
  across the secondary winding is 1.60 kohm
  determine (a) the primary current flowing, and (b
  ) the power dissipated in the load resistance.
2
3 //initializing the variables:
4 V1 = 240; // in volts
5 V2 = 1920; // in volts
6 R1 = 5; // in ohms
7 R2 = 1600; // in ohms
8
9 //calculation:
10 //The network is shown in Figure 35.12.
11 //turn ratio  $N1/N2 = V1/V2$ 
12 tr = V1/V2
13 //Equivalent input resistance of the transformer,
14 RL = R2
15 r = RL*tr^2
16 //Total input resistance,
17 Rin = R1 + r
18 //primary current, I1
19 I1 = V1/Rin
20 //For an ideal transformer  $V1/V2 = I2/I1$ 
21 I2 = I1*(V1/V2)
22 //Power dissipated in the load resistance
23 P = RL*I2^2
24
25 printf("\n\n Result \n\n")
26 printf("\n (a) primary current flowing is %.0f A",I1
  )
```

```
27 printf("\n (b) Power dissipated in the load
    resistance is %.0fW",P)
```

---

### Scilab code Exa 35.10 Example 10

```
1 //Problem 35.10: An ac. source of 30/_0 V and
    internal resistance 20 kohm is matched to a load
    by a 20:1 ideal transformer. Determine for
    maximum power transfer (a) the value of the load
    resistance , and (b) the power dissipated in the
    load.
2
3 //initializing the variables:
4 rv = 30; // in volts
5 thetav = 0; // in degrees
6 r = 20000; // in ohms
7 tr = 20; // turn ratio
8
9 //calculation:
10 //voltage
11 V = rv*cos(thetav*pi/180) + %i*rv*sin(thetav*pi
    /180)
12 //The network diagram is shown in Figure 35.13.
13 //For maximum power transfer , r1 must be equal to
14 r1 = r
15 //load resistance RL
16 RL = r1/tr^2
17 //The total input resistance when the source is
    connected to the matching transformer is
18 RT = r + r1
19 //Primary current
20 I1 = V/RT
21 //N1/N2 = I2/I1
22 I2 = I1*tr
23 //Power dissipated in load resistance RL is given by
```

```
24 P = RL*I2^2
25
26 printf("\n\n Result \n\n")
27 printf("\n (a)the value of the load resistance is %
    .0 f ohm",RL)
28 printf("\n (b) Power dissipated in the load
    resistance is %.2E W",P)
```

---

# Chapter 36

## Complex Waveforms

Scilab code Exa 36.03 Example 3

```
1 //Problem 36.03: Determine the rms value of the
   current waveform represented by  $i = 100\sin\omega t + 20\sin(3\omega t + \pi/6) + 10\sin(5\omega t + 2\pi/3)$  mA
2
3 //initializing the variables:
4 A1 = 0.100; // in amperes
5 A3 = 0.020; // in amperes
6 A5 = 0.010; // in amperes
7
8 //calculation:
9 //the rms value of current is given by
10 Irms = ((A1^2 + A3^2 + A5^2)/2)^0.5
11
12 printf("\n\n Result \n\n")
13 printf("\n the rms value of current is %.5f A", Irms)
```

---

Scilab code Exa 36.04 Example 4

```

1 //Problem 36.04: A complex voltage is represented by
2 // v = 10sinwt + 3sin(3wt) + 2sin(5wt) Volts
3 //Determine for the voltage , (a) the rms value , (b)
   the mean value and (c) the form factor.
4
5 //initializing the variables:
6 A1 = 10; // in volts
7 A3 = 3; // in volts
8 A5 = 2; // in volts
9
10 //calculation:
11 //the rms value of voltage is given by
12 Vrms = ((A1^2 + A3^2 + A5^2)/2)^0.5
13 //the mean value of voltage is given by
14 //x = wt
15 function [Y]=f(x)
16     Y = (10*sin(x) + 3*sin(3*x) + 2*sin(5*x));
17 endfunction
18 Vav = (1/%pi)*(integrate('f', 'x', 0, %pi))
19 //form factor is given by
20 ff = Vrms/Vav
21
22 printf("\n\n Result \n\n")
23 printf("\n (a)the rms value of voltage is %.2f V",
   Vrms)
24 printf("\n (b)the mean value of voltage is %.2f V",
   Vav)
25 printf("\n (c)form factor is %.3f ",ff)

```

---

#### Scilab code Exa 36.06 Example 6

```

1 //Problem 36.06: Determine the average power in a 20
   # resistance if the current i flowing through it
   is of the form
2 // i = 12sinwt + 5sin(3wt) + 2sin(5wt) A

```

```

3
4 //initializing the variables:
5 A1 = 12; // in amperes
6 A3 = 5; // in amperes
7 A5 = 2; // in amperes
8 R = 20; // in ohms
9
10 //calculation:
11 //rms current
12 Irms = ((A1^2 + A3^2 + A5^2)/2)^0.5
13 //average power
14 P = R*Irms^2
15
16 printf("\n\n Result \n\n")
17 printf("\n average power %.0f W",P)

```

---

#### Scilab code Exa 36.07 Example 7

```

1 //Problem 36.07: A complex voltage v given by
2 // v = 60sinwt + 15sin(3wt + pi/4) + 10sin(5wt - pi
  /2) Volts
3 //is applied to a circuit and the resulting current
  i is given by
4 // i = 2sin(wt - pi/6) + 0.30sin(3wt - pi/12) + 0.1
  sin(5wt - 8pi/9) A
5 //Determine (a) the total active power supplied to
  the circuit, and (b) the overall power factor.
6
7 //initializing the variables:
8 Ia1 = 2; // in amperes
9 Ia3 = 0.3; // in amperes
10 Ia5 = 0.1; // in amperes
11 Va1 = 60; // in volts
12 Va3 = 15; // in volts
13 Va5 = 10; // in volts

```



```

14 Phii1 = -1*%pi/6; // in radians
15 Phii3 = -1*%pi/12; // in radians
16 Phii5 = -8*%pi/9; // in radians
17 Phiv1 = 0; // in radians
18 Phiv3 = %pi/4; // in radians
19 Phiv5 = -1*%pi/2; // in radians
20
21
22 //calculation:
23 //rms values;
24 I1 = Ia1/(2^0.5); // in amperes
25 I3 = Ia3/(2^0.5); // in amperes
26 I5 = Ia5/(2^0.5); // in amperes
27 V1 = Va1/(2^0.5); // in volts
28 V3 = Va3/(2^0.5); // in volts
29 V5 = Va5/(2^0.5); // in volts
30 //total power supplied,
31 P = V1*I1*cos(Phiv1 - Phii1) + V3*I3*cos(Phiv3 -
    Phii3) + V5*I5*cos(Phiv5 - Phii5)
32 //rms current
33 Irms = ((I1^2 + I3^2 + I5^2))^0.5
34 //rms voltage
35 Vrms = ((V1^2 + V3^2 + V5^2))^0.5
36 //overall power factor
37 pf = P/(Vrms*Irms)
38
39 printf("\n\n Result \n\n")
40 printf("\n(a)the total active power supplied to the
    circuit %.2f W",P)
41 printf("\n(b)overall power factor %.3f",pf)

```

---

### Scilab code Exa 36.09 Example 9

```

1 //Problem 36.09: A supply voltage v given by
2 // v = 240sin314t + 40sin942t + 30sin1570t Volts

```

```

3 //is applied to a circuit comprising a resistance of
   12 ohm connected in series with a coil of
   inductance 9.55 mH. Determine (a) an expression
   to represent the instantaneous value of the
   current, (b) the rms voltage, (c) the rms current
   , (d) the power dissipated, and (e) the overall
   power factor.
4
5 //initializing the variables:
6 V1m = 240; // in volts
7 V3m = 40; // in volts
8 V5m = 30; // in volts
9 w1 = 314; // fundamental
10 R = 12; // in ohm
11 L = 0.00955; // in Henry
12
13 //calculation:
14 //fundamental or first harmonic
15 //inductive reactance,
16 XL1 = w1*L
17 //impedance at the fundamental frequency,
18 Z1 = R + %i*XL1
19 //Maximum current at fundamental frequency
20 I1m = V1m/Z1
21 I1mag = (real(I1m)^2 + imag(I1m)^2)^0.5
22 phii1 = atan(imag(I1m)/real(I1m))
23 //Third harmonic
24 XL3 = 3*XL1
25 //impedance at the third harmonic frequency,
26 Z3 = R + %i*XL3
27 //Maximum current at third harmonic frequency
28 I3m = V3m/Z3
29 I3mag = (real(I3m)^2 + imag(I3m)^2)^0.5
30 phii3 = atan(imag(I3m)/real(I3m))
31 //fifth harmonic
32 XL5 = 5*XL1
33 //impedance at the third harmonic frequency,
34 Z5 = R + %i*XL5

```

```

35 //Maximum current at third harmonic frequency
36 I5m = V5m/Z5
37 I5mag = (real(I5m)^2 + imag(I5m)^2)^0.5
38 phii5 = atan(imag(I5m)/real(I5m))
39 //rms voltage
40 Vrms = ((V1m^2 + V3m^2 + V5m^2)/2)^0.5
41 //rms current
42 Irms = ((I1mag^2 + I3mag^2 + I5mag^2)/2)^0.5
43 //power dissipated
44 P = R*Irms^2
45 //overall power factor
46 pf = P/(Vrms*Irms)
47
48 printf("\n\n Result \n\n")
49 printf("\n(b)the rms value of current is %.2f A",
        Irms)
50 printf("\n(c)the rms value of voltage is %.2f V",
        Vrms)
51 printf("\n(d)the total power dissipated %.0f W",P)
52 printf("\n(e)overall power factor %.3f",pf)

```

---

### Scilab code Exa 36.10 Example 10

```

1 //Problem 36.10: An e.m.f. is represented by
2 // e = 50 + 200sinwt + 40sin(2wt - pi/2) + 5sin(4wt
  + pi/4) Volts
3 //the fundamental frequency being 50 Hz. The e.m.f.
  is applied across a circuit comprising a 100 F
  capacitor connected in series with a 50 ohm
  resistor. Obtain an expression for the current
  flowing and hence determine the rms value of
  current.
4
5 //initializing the variables:
6 Vom = 50; // in volts

```

```

7 V1m = 200; // in volts
8 V2m = 40; // in volts
9 V4m = 5; // in volts
10 f = 50; // in Hz
11 R = 50; // in ohm
12 C = 100E-6; // in farad
13 phiv1 = 0; // in rad
14 phiv2 = -1*%pi/2; // in rad
15 phiv4 = %pi/4; // in rad
16
17 //calculation:
18 //voltage
19 V1 = V1m*cos(phiv1) + %i*V1m*sin(phiv1)
20 V2 = V2m*cos(phiv2) + %i*V2m*sin(phiv2)
21 V4 = V4m*cos(phiv4) + %i*V4m*sin(phiv4)
22 //Inductance has no effect on a steady current.
    Hence the d.c. component of the current, i0, is
    given by
23 Iom = 0
24 //fundamental or first harmonic
25 w1 = 2*%pi*f
26 //inductive reactance,
27 Xc1 = 1/(w1*C)
28 //impedance at the fundamental frequency,
29 Z1 = R + %i*Xc1
30 //Maximum current at fundamental frequency
31 I1m = V1/Z1
32 I1mag = (real(I1m)^2 + imag(I1m)^2)^0.5
33 phii1 = atan(imag(I1m)/real(I1m))
34 //second harmonic
35 Xc2 = Xc1/2
36 //impedance at the third harmonic frequency,
37 Z2 = R + %i*Xc2
38 //Maximum current at third harmonic frequency
39 I2m = V2/Z2
40 I2mag = (real(I2m)^2 + imag(I2m)^2)^0.5
41 phii2 = atan(imag(I2m)/real(I2m))
42 //fourth harmonic

```

```

43 Xc4 = Xc1/4
44 //impedance at the third harmonic frequency ,
45 Z4 = R + %i*Xc4
46 //Maximum current at third harmonic frequency
47 I4m = V4/Z4
48 I4mag = (real(I4m)^2 + imag(I4m)^2)^0.5
49 phi4 = atan(imag(I4m)/real(I4m))
50 //rms current
51 Irms = (Iom^2 + (I1mag^2 + I2mag^2 + I4mag^2)/2)^0.5
52
53 printf("\n\n Result \n\n")
54 printf("\n(b)the rms value of current is %.2f A",
        Irms)

```

---

#### Scilab code Exa 36.11 Example 11

```

1 //Problem 36.11: A supply voltage v given by
2 // v = 25 + 100sinwt + 40sin(3wt + pi/6) + 20sin(5wt
   // + pi/12) Volts
3 //where w = 10000 rad/s. The voltage is applied to a
   // series circuit comprising a 5.0 ohm resistance
   // and a 500 H inductance. Determine (a) an
   // expression to represent the current flowing in
   // the circuit , (b) the rms value of current ,
   // correct to two decimal places , and (c) the power
   // dissipated in the circuit , correct to three
   // significant figures .
4
5 //initializing the variables:
6 Vom = 25; // in volts
7 V1m = 100; // in volts
8 V3m = 40; // in volts
9 V5m = 20; // in volts
10 w1 = 10000; // fundamental
11 R = 5; // in ohm

```

```

12 L = 500E-6; // in Henry
13 phiv1 = 0; // in rad
14 phiv3 = %pi/6; // in rad
15 phiv5 = %pi/12; // in rad
16
17 //calculation:
18 //voltage
19 V1 = V1m*cos(phiv1) + %i*V1m*sin(phiv1)
20 V3 = V3m*cos(phiv3) + %i*V3m*sin(phiv3)
21 V5 = V5m*cos(phiv5) + %i*V5m*sin(phiv5)
22 //Inductance has no effect on a steady current.
    Hence the d.c. component of the current,  $i_0$ , is
    given by
23 Iom = Vom/R
24 //fundamental or first harmonic
25 //inductive reactance,
26 XL1 = w1*L
27 //impedance at the fundamental frequency,
28 Z1 = R + %i*XL1
29 //Maximum current at fundamental frequency
30 I1m = V1/Z1
31 I1mag = (real(I1m)^2 + imag(I1m)^2)^0.5
32 phii1 = atan(imag(I1m)/real(I1m))
33 //Third harmonic
34 XL3 = 3*XL1
35 //impedance at the third harmonic frequency,
36 Z3 = R + %i*XL3
37 //Maximum current at third harmonic frequency
38 I3m = V3/Z3
39 I3mag = (real(I3m)^2 + imag(I3m)^2)^0.5
40 phii3 = atan(imag(I3m)/real(I3m))
41 //fifth harmonic
42 XL5 = 5*XL1
43 //impedance at the third harmonic frequency,
44 Z5 = R + %i*XL5
45 //Maximum current at third harmonic frequency
46 I5m = V5/Z5
47 I5mag = (real(I5m)^2 + imag(I5m)^2)^0.5

```

```

48 phi_i5 = atan(imag(I5m)/real(I5m))
49 //rms current
50 Irms = (Iom^2 + (I1mag^2 + I3mag^2 + I5mag^2)/2)^0.5
51 //power dissipated
52 P = R*Irms^2
53
54 printf("\n\n Result \n\n")
55 printf("\n(b)the rms value of current is %.2f A",
        Irms)
56 printf("\n(c)the total power dissipated %.0f W",P)

```

---

#### Scilab code Exa 36.12 Example 12

```

1 //Problem 36.12: The voltage applied to a particular
    circuit comprising two components connected in
    series is given by
2 // v = 30 + 40sinwt + 25sin(2wt) + 15sin(4wt) Volts
3 //and the resulting current is given by
4 // v = 0.743sin(wt + 1.19) + 0.78sin(2wt + 0.896) +
    0.636sin(4wt + 0.559) A
5 //Determine (a) the average power supplied , (b) the
    type of components present , and (c) the values of
    the components.
6
7 //initializing the variables:
8 Vom = 30; // in volts
9 V1m = 40; // in volts
10 V2m = 25; // in volts
11 V4m = 15; // in volts
12 Iom = 0; // in amperes
13 I1m = 0.743; // in Amperes
14 I2m = 0.781; // in Amperes
15 I4m = 0.636; // in Amperes
16 phi_i1 = 1.190; // in rad
17 phi_i2 = 0.896; // in rad

```

```

18 phi14 = 0.559; // in rad
19 w = 1000; // in rad
20
21 //calculation:
22 //the average power P is given by
23 P = Vom*Iom + (0.707*V1m)*(0.707*I1m)*cos(phi11) + +
      (0.707*V2m)*(0.707*I2m)*cos(phi12) + (0.707*V4m)
      *(0.707*I4m)*cos(phi14)
24 //rms current
25 Irms = (Iom^2 + (I1m^2 + I2m^2 + I4m^2)/2)^0.5
26 //resistance R
27 R = P/(Irms^2)
28 //impedance
29 Z1 = V1m/I1m
30 //Xc1
31 Xc1 = (Z1^2 - R^2)^0.5
32 //capacitance
33 C = 1/(w*Xc1)
34
35 printf("\n\n Result \n\n")
36 printf("\n(a)the average power P is %.2f W",P)
37 printf("\n(c)the resistance R %.0f ohm and
      capacitance %.2E F",R,C)

```

---

### Scilab code Exa 36.13 Example 13

```

1 //Problem 36.13: In the circuit shown in Figure
  36.17 the supply voltage v is given by  $v = 300 \sin 314t + 120 \sin(942t + 0.698)$  Volts. Determine (a
  ) an expression for the supply current, i, (b)
  the percentage harmonic content of the supply
  current, (c) the total power dissipated, (d) an
  expression for the p.d. shown as v1, and (e) an
  expression for current ic.

```

2



```

3 //initializing the variables:
4 V1m = 300; // in volts
5 V3m = 120; // in volts
6 phiv1 = 0; // in rad
7 phiv2 = 0.698; // in rad
8 w1 = 314; // in rad
9 C = 2.123E-6; // in farads
10 R1 = 560; // in ohms
11 R2 = 2000; // in Ohm
12
13 //calculation:
14 //voltage
15 V1 = V1m*cos(phiv1) + %i*V1m*sin(phiv1)
16 V3 = V3m*cos(phiv3) + %i*V3m*sin(phiv3)
17 //capacitive reactance,
18 Xc1 = 1/(w1*C)
19 //impedance at the fundamental frequency,
20 Z1 = R1 + %i*Xc1*R2/(R2 + %i*Xc1)
21 //Maximum current at fundamental frequency
22 I1m = V1/Z1
23 I1mag = (real(I1m)^2 + imag(I1m)^2)^0.5
24 phii1 = atan(imag(I1m)/real(I1m))
25 //Third harmonic
26 Xc3 = Xc1/3
27 //impedance at the third harmonic frequency,
28 Z3 = R1 + %i*Xc3*R2/(R2 + %i*Xc3)
29 //Maximum current at third harmonic frequency
30 I3m = V3/Z3
31 I3mag = (real(I3m)^2 + imag(I3m)^2)^0.5
32 phii3 = atan(imag(I3m)/real(I3m))
33 //Percentage harmonic content of the supply current
    is given by
34 percent = I3mag*100/I1mag
35 //total active power
36 P = (0.707*V1m)*(0.707*I1mag)*cos(phiv1 - phii1) +
    (0.707*V3m)*(0.707*I3m)*cos(phiv3 - phii3)
37
38 printf("\n\n Result \n\n")

```

```

39 printf("\n(b)Percentage harmonic content of the
    supply current is %.0f percent",percent)
40 printf("\n(c)total active power is %.2f W",P)

```

---

### Scilab code Exa 36.14 Example 14

```

1 //Problem 36.14: A voltage waveform having a
    fundamental of maximum value 400 V and a third
    harmonic of maximum value 10 V is applied to the
    circuit shown in Figure 36.18. Determine (a) the
    fundamental frequency for resonance with the
    third harmonic, and (b) the maximum value of the
    fundamental and third harmonic components of
    current.
2
3 //initializing the variables:
4 V1m = 400; // in volts
5 V3m = 10; // in volts
6 C = 0.2E-6; // in farads
7 R = 2; // in ohms
8 L = 0.5; // in Henry
9
10 //calculation:
11 //Resonance with the third harmonic means that
12 w = (1/(9*L*C))^0.5
13 //fundamental frequency, f
14 f = w/(2*pi)
15 //At the fundamental frequency,
16 //impedance Z1
17 Z1 = R + %i*(w*L - 1/(w*C))
18 Z1mag = (real(Z1)^2 + imag(Z1)^2)^0.5
19 phiZ1 = atan(imag(Z1)/real(Z1))
20 //Maximum value of current at the fundamental
    frequency,
21 I1m = V1m/Z1mag

```

```

22 //At the third harmonic frequency ,
23 Z3 = R + %i*(3*w*L - 1/(3*w*C))
24 Z3mag = (real(Z3)^2 + imag(Z3)^2)^0.5
25 phiZ3 = atan(imag(Z3)/real(Z3))
26 //Maximum value of current at the third harmonic
    frequency ,
27 I3m = V3m/Z3
28
29 printf("\n\n Result \n\n")
30 printf("\n(a)fundamental frequency for resonance
    with the third harmonic is %.2f Hz",f)
31 printf("\n(b)Maximum value of current at the
    fundamental frequency is %.3f A and at the third
    harmonic frequency %.2f A",I1m, I3m)

```

---

### Scilab code Exa 36.15 Example 15

```

1 //Problem 36.15: A voltage wave has an amplitude of
    800 V at the fundamental frequency of 50 Hz and
    its nth harmonic has an amplitude 1.5% of the
    fundamental. The voltage is applied to a series
    circuit containing resistance 5 ohm, inductance
    0.369 H and capacitance 0.122 F . Resonance
    occurs at the nth harmonic. Determine (a) the
    value of n, (b) the maximum value of current at
    the nth harmonic, (c) the p.d. across the
    capacitor at the nth harmonic and (d) the maximum
    value of the fundamental current.
2
3 //initializing the variables:
4 V1m = 800; // in volts
5 f = 50; // in Hz
6 x = 0.015;
7 C = 0.122E-6; // in farads
8 R = 5; // in ohms

```

```

9 L = 0.369; // in Henry
10
11 //calculation:
12 //voltage at nth harmonic
13 Vnm = x*V1m
14 w = 2*%pi*f
15 //For resonance at the nth harmonic  $n\omega L = 1/n\omega C$ 
16 n = 1/(w*(L*C)^0.5)
17 //At resonance, impedance
18 Zn = R
19 //the maximum value of current at the nth harmonic
20 Inm = Vnm/Zn
21 //capacitive reactance, at nth harmonic
22 Xcn = 1/(n*w*C)
23 //the p.d. across the capacitor at the nth harmonic
24 Vcn = Inm*Xcn
25 //At the fundamental frequency, inductive reactance,
26 XL1 = w*L
27 //capacitive reactance
28 Xc1 = 1/(w*C)
29 //Impedance at the fundamental frequency,
30 Z1 = R + %i*(XL1 - Xc1)
31 Z1mag = (real(Z1)^2 + imag(Z1)^2)^0.5
32 phiZ1 = atan(imag(Z1)/real(Z1))
33 //Maximum value of current at the fundamental
    frequency,
34 I1m = V1m/Z1mag
35
36 printf("\n\n Result \n\n")
37 printf("\n(a)n = %.0 f",n)
38 printf("\n(b)the maximum value of current at the nth
    harmonic %.2 f A",Inm)
39 printf("\n(c)the p.d. across the capacitor at the
    nth harmonic is %.2 f",Vcn)
40 printf("\n(d)the maximum value of the fundamental
    current. %.2 f A",I1m)

```

---

# Chapter 38

## Magnetic materials

Scilab code Exa 38.01 Example 1

```
1 //Problem 38.01: The area of a hysteresis loop
   obtained from a ferromagnetic specimen is 12.5
   cm2. The scales used were: horizontal axis 1 cm =
   500 A/m; vertical axis 1 cm = 0.2 T. Determine (
   a) the hysteresis loss per m3 per cycle , and (b)
   the hysteresis loss per m3 at a frequency of 50
   Hz.
2
3 //initializing the variables:
4 A = 12.5; // in cm2
5 x = 500; // horizontal axis 1 cm = 500 A/m
6 y = 0.2; // vertical axis 1 cm = 0.2 T
7 f = 50; // in Hz
8
9 //calculation:
10 //hysteresis loss per cycle
11 HL = A*x*y
12 //At 50 Hz frequency , hysteresis loss
13 HLf = HL*f
14
15 printf("\n\n Result \n\n")
```

```

16 printf("\n(a) hysteresis loss per cycle is = %.0f J/
    m3",HL)
17 printf("\n(b) At 50 Hz frequency, hysteresis loss %.0
    f W/m3",HLf)

```

---

### Scilab code Exa 38.02 Example 2

```

1 //Problem 38.02: If in problem 38.01, the maximum
    flux density is 1.5 T at a frequency of 50 Hz,
    determine the hysteresis loss per m3 for a
    maximum flux density of 1.1 T and frequency of 25
    Hz. Assume the Steinmetz index to be 1.6
2
3 //initializing the variables:
4 n = 1.6; // the Steinmetz index
5 f1 = 50; // in Hz
6 f2 = 25; // in Hz
7 Bm1 = 1.5; // in Tesla
8 Bm2 = 1.1; // in Tesla
9 Ph1 = 62500; // in W/m3
10 v = 1;
11
12 //calculation:
13 //hysteresis loss Ph = kh*v*f*(Bm)^n
14 kh = Ph1/(v*f1*(Bm1)^n)
15 //When f = 25 Hz and Bm = 1.1 T,
16 Ph2 = kh*v*f2*(Bm2)^n
17
18 printf("\n\n Result \n\n")
19 printf("\n hysteresis loss When f = 25 Hz and Bm =
    1.1 T, is = %.0f W/m3",Ph2)

```

---

### Scilab code Exa 38.03 Example 3

```

1 //Problem 38.03: A ferromagnetic ring has a uniform
  cross-sectional area of 2000 mm2 and a mean
  circumference of 1000 mm. A hysteresis loop
  obtained for the specimen is plotted to scales of
  10 mm = 0.1 T and 10 mm = 400 A/m and is found
  to have an area of 104 mm2. Determine the
  hysteresis loss at a frequency of 80 Hz.
2
3 //initializing the variables:
4 csa = 0.002; // in m2
5 l = 1; // in m
6 a = 400/0.01; // 10 mm = 400 A/m
7 b = 0.1/0.01; // 10 mm = 0.1 T
8 A = 0.01; // in m2
9 f = 80; // in Hz
10
11 //calculation:
12 //hysteresis loss per cycle
13 HL = A*a*b
14 //At a frequency of 80 Hz,
15 //hysteresis loss
16 HLf = HL*f
17 //Volume of ring
18 v = csa*l
19 //hysteresis loss
20 Ph = HLf*v
21
22 printf("\n\n Result \n\n")
23 printf("\n the hysteresis loss at a frequency of 80
  Hz is %.0f W",Ph)

```

---

#### Scilab code Exa 38.04 Example 4

```

1 //Problem 38.04: The cross-sectional area of a
  transformer limb is 80 cm2 and the volume of the

```

transformer core is 5000 cm<sup>3</sup>. The maximum value of the core flux is 10 mWb at a frequency of 50 Hz. Taking the Steinmetz constant as 1.7, the hysteresis loss is found to be 100 W. Determine the value of the hysteresis loss when the maximum core flux is 8 mWb and the frequency is 50 Hz.

```

2
3 //initializing the variables:
4 Phi1 = 0.01; // in Wb
5 Phi2 = 0.008; // in Wb
6 csa = 0.008; // in m2
7 v = 0.005; // in m3
8 f = 50; // in Hz
9 n = 1.7; // the Steinmetz constant
10 Ph1 = 100; // in Watt
11
12 //calculation:
13 //maximum flux density
14 Bm1 = Phi1/csa
15 //hysteresis loss Ph1 = kh*v*f*(Bm1)^n
16 kh = Ph1/(v*f*(Bm1)^n)
17 //When the maximum core flux is 8 mWb,
18 Bm2 = Phi2/csa
19 //hysteresis loss, Ph2
20 Ph2 = kh*v*f*(Bm2)^n
21
22 printf("\n\n Result \n\n")
23 printf("\nthe value of the hysteresis loss when the
    maximum core flux is 8 mWb and the frequency is
    50 Hz is %.1f W",Ph2)

```

---

#### Scilab code Exa 38.05 Example 5

```

1 //Problem 38.05: The eddy current loss in a
    particular magnetic circuit is 10 W/m3. If the

```



```

    frequency of operation is reduced from 50 Hz to
    30 Hz with the flux density remaining unchanged,
    determine the new value of eddy current loss per
    cubic metre.
2
3 //initializing the variables:
4 Pe1 = 10; // in W/m3
5 f1 = 50; // in Hz
6 f2 = 30; // in Hz
7
8 //calculation:
9 //When the eddy current loss is 10 W/m3, frequency f
    is 50 Hz.
10 //constant k
11 k = Pe1/(f1^2)
12 //When the frequency is 30 Hz, eddy current loss ,
13 Pe2 = k*(f2^2)
14
15 printf("\n\n Result \n\n")
16 printf("\neddy current loss per cubic metre is %.1f
    W/m3",Pe2)

```

---

#### Scilab code Exa 38.06 Example 6

```

1 //Problem 38.06: The core of a transformer operating
    at 50 Hz has an eddy current loss of 100 W/m3
    and the core laminations have a thickness of 0.50
    mm. The core is redesigned so as to operate with
    the same eddy current loss but at a different
    voltage and at a frequency of 250 Hz. Assuming
    that at the new voltage the maximum flux density
    is one-third of its original value and the
    resistivity of the core remains unaltered,
    determine the necessary new thickness of the
    laminations.

```

```

2
3 //initializing the variables:
4 Pe = 100; // in W/m3
5 f1 = 50; // in Hz
6 t1 = 0.0005; // in m
7 x = 1/3;
8 f2 = 250; // in Hz
9
10 //calculation:
11 //Pe = ke*(Bm1*f1*t1)^2
12 //Hence, at 50 Hz frequency
13 ke = Pe/(Bm1*f1*t1)^2
14 //At 250 Hz frequency
15 Bm2 = x*Bm1
16 t2 = ((Pe/ke)^0.5)/(Bm2*f2)
17
18 printf("\n\n Result \n\n")
19 printf("\nlamination thickness is %.2Em",t2)

```

---

### Scilab code Exa 38.07 Example 7

```

1 //Problem 38.07: The core of an inductor has a
  hysteresis loss of 40 W and an eddy current loss
  of 20 W when operating at 50 Hz frequency. (a)
  Determine the values of the losses if the
  frequency is increased to 60 Hz. (b) What will be
  the total core loss if the frequency is 50 Hz
  and the lamination are made one-half of their
  original thickness? Assume that the flux density
  remains unchanged in each case
2
3 //initializing the variables:
4 Ph1 = 40; // in W
5 Pe1 = 20; // in W
6 f1 = 50; // in Hz

```

```

7 x = 1/2;
8 f2 = 60; // in Hz
9 t1 = 1;
10 //calculation:
11 //hysteresis loss  $Ph = kh*v*f*(Bm)^n = k1*f$ 
12 //Thus when the hysteresis is 40 W and the frequency
    50 Hz,
13 k1 = Ph1/f1
14 //If the frequency is increased to 60 Hz,
15 Ph2 = k1*f2
16 //eddy current loss ,  $Pe = ke*(Bm1*f1*t1)^2 = k2*f^2$ 
17 //since the flux density and lamination thickness
    are constant.
18 //When the eddy current loss is 20 W the frequency
    is 50 Hz. Thus
19 k2 = Pe1/(f1^2)
20 //If the frequency is increased to 60 Hz,
21 Pe2 = k2*(f2^2)
22 //hysteresis loss  $Ph = kh*v*f*(Bm)^n$ , is independent
    of the thickness of the laminations. Thus, if
    the thickness of the laminations is halved, the
    hysteresis loss remains at
23 Phb2 = Ph1
24 //eddy current loss ,  $Pe = ke*(Bm1*f1*t1)^2 = k2*t^3$ 
25 k3 = Pe1/(t1^3)
26 t2 = 0.5*t1
27 Peb2 = k3*t2^3
28 //total core loss when the thickness of the
    laminations is halved is given by
29 TL = Phb2 + Peb2
30
31 printf("\n\n Result \n\n")
32 printf("\n(a)If the frequency is increased to 60 Hz,
    hysteresis loss is %.0f W and eddy current loss %
    .1f W",Ph2, Pe2)
33 printf("\n(b)the total core loss when the thickness
    of the laminations is halved %.1f W",TL)

```

---

### Scilab code Exa 38.08 Example 8

```
1 //Problem 38.08: When a transformer is connected to
  a 500 V, 50 Hz supply , the hysteresis and eddy
  current losses are 400 W and 150 W respectively .
  The applied voltage is increased to 1 kV and the
  frequency to 100 Hz. Assuming the Steinmetz index
  to be 1.6, determine the new total core loss.
2
3 //initializing the variables:
4 V1 = 500; // in Volts
5 V2 = 1000; // in Volts
6 Ph1 = 400; // in W
7 Pe1 = 150; // in W
8 f1 = 50; // in Hz
9 n = 1.6; // Steinmetz index
10 f2 = 100; // in Hz
11
12 //calculation:
13 //hysteresis loss  $Ph = k1*f*(E/f)^n$ 
14 //At 500 V and 50 Hz
15 k1 = Ph1/(f1*(V1/f1)^1.6)
16 //At 1000 V and 100 Hz,
17 Ph2 = k1*f2*(V2/f2)^1.6
18 //eddy current loss ,  $Pe = k2*E^2$ 
19 //At 500 V,
20 k2 = Pe1/(V1^2)
21 //At 1000 V,
22 Pe2 = k2*(V2^2)
23 //the new total core loss
24 TL = Ph2 + Pe2
25
26 printf("\n\n Result \n\n")
27 printf("\n the new total core loss %.0f W", TL)
```

---

**Scilab code Exa 38.10** Example 10

```
1 //Problem 38.10: The core of a synchrogenerator has
   total losses of 400 W at 50 Hz and 498W at 60 Hz,
   the flux density being constant for the two
   tests. (a) Determine the hysteresis and eddy
   current losses at 50 Hz (b) If the flux density
   is increased by 25% and the lamination thickness
   is increased by 40%, determine the hysteresis and
   eddy current losses at 50 Hz. Assume the
   Steinmetz index to be 1.7.
2
3 //initializing the variables:
4 TL1 = 400; // in Watt
5 TL2 = 498; // in Watt
6 x = 0.25;
7 y = 0.4;
8 f1 = 50; // in Hz
9 n = 1.7; // Steinmetz index
10 f2 = 60; // in Hz
11
12 //calculation:
13 //if volume v and the maximum flux density are
   constant
14 //hysteresis loss  $Ph = kh*v*f*(Bm)^n = k1*f$ 
15 //(if the maximum flux density and the lamination
   thickness are constant)
16 //eddy current loss,  $Pe = ke*(Bm1*f1*t1)^2 = k2*f^2$ 
17 //At 50 Hz frequency,  $TL1 = k1*f1 + k2*f1^2$ 
18 //At 60 Hz frequency,  $TL2 = k1*f2 + k2*f2^2$ 
19 //Solving equations gives the values of k1 and k2.
20  $k2 = (5*TL2 - 6*TL1)/(5*(f2^2) - 6*(f1^2))$ 
21  $k1 = (TL1 - k2*f1^2)/f1$ 
22 //hysteresis loss  $Ph = k1*f$ 
```

```

23 Ph1 = k1*f1
24 //eddy current loss
25 Pe1 = k2*f1^2
26 //Since at 50 Hz the flux density is increased by 25
    %, the new hysteresis loss is
27 Ph2 = Ph1*(1 + x)^1.7
28 //Since at 50 Hz the flux density is increased by 25
    %, and the lamination thickness is increased by
    40%, the new eddy current loss is
29 Pe2 = Pe1*((1 + x)^2)*(1 + y)^3
30
31 printf("\n\n Result \n\n")
32 printf("\n (a)the hysteresis and eddy current losses
    at 50 Hz are %.0f W and %.0f W resp.",Ph1, Pe1)
33 printf("\n (b)the hysteresis and eddy current losses
    at 50 Hz after increement are %.1f W and %.1f W
    resp.",Ph2, Pe2)

```

---

# Chapter 39

## Dielectrics and dielectric loss

Scilab code Exa 39.01 Example 1

```
1 //Problem 39.01: The equivalent series circuit for a
   particular capacitor consists of a 1.5 ohm
   resistance in series with a 400 pF capacitor.
   Determine for the capacitor, at a frequency of 8
   MHz, (a) the loss angle, (b) the power factor, (c
   ) the Q-factor, and (d) the dissipation factor.
2
3 //initializing the variables:
4 Rs = 1.5; // in ohms
5 Cs = 400E-12; // in Farads
6 f = 8E6; // in Hz
7
8 //calculation:
9 //for a series equivalent circuit,
10 //tan(delta) = Rs*w*Cs
11 //loss angle,
12 delta = atan(Rs*Cs*(2*%pi*f))
13 //power factor
14 pf = cos(delta)
15 //the Q-factor
16 Q = 1/tan(delta)
```

```

17 //dissipation factor ,
18 D = 1/Q
19
20 printf("\n\n Result \n\n")
21 printf("\n (a)loss angle %.3f rad.",del)
22 printf("\n (b)power factor %.3f rad.",del)
23 printf("\n (c)Q-factor is %.2f ",Q)
24 printf("\n (d)dissipation factor %.3f rad.",D)

```

---

### Scilab code Exa 39.02 Example 2

```

1 //Problem 39.02: A capacitor has a loss angle of
   0.025 rad, and when it is connected across a 5 kV
   , 50 Hz supply, the power loss is 20 .W Determine
   the component values of the equivalent parallel
   circuit.
2
3 //initializing the variables:
4 del = 0.025; // in rad.
5 V = 5000; // in Volts
6 PL = 20; // power loss
7 f = 50; // in Hz
8
9 //calculation:
10 //power loss = w*C*V^2*tan(del)
11 Cp = PL/(2*%pi*f*V*V*tan(del))
12 //for a parallel equivalent circuit ,
13 //tan(del) = 1/(Rp*w*Cp)
14 Rp = 1/(2*%pi*f*Cp*tan(del))
15
16 printf("\n\n Result \n\n")
17 printf("\n capacitance C %.2E F and parallel
   resistance %.2E ohm.",Cp, Rp)

```

---



### Scilab code Exa 39.03 Example 3

```
1 //Problem 39.03: A 2000 pF capacitor has an
   alternating voltage of 20 V connected across it
   at a frequency of 10 kHz. If the power dissipated
   in the dielectric is 500 W , determine (a) the
   loss angle , (b) the equivalent series loss
   resistance , and (c) the equivalent parallel loss
   resistance .
2
3 //initializing the variables :
4 P = 500E-6; // in Watt
5 C = 2000E-12; // in Farads
6 V = 20; // in Volts
7 f = 10000; // in Hz
8
9 //calculation :
10 //power loss = w*C*V^2*tan(del)
11 //loss angle
12 del = atan(P/(2*pi*f*V*V*C))
13 //for an equivalent series circuit ,
14 //tan(del) = (Rs*w*Cs)
15 Cs = C
16 Rs = (tan(del))/(2*pi*f*Cp)
17 //for an equivalent parallel circuit
18 //tan(del) = 1/(Rp*w*Cp)
19 Cp = C
20 Rp = 1/(2*pi*f*Cp*tan(del))
21
22 printf("\n\n Result \n\n")
23 printf("\n (a) loss angle %.6f rad.",del)
24 printf("\n (b) series resistance %.2f ohm.",Rs)
25 printf("\n (c) parallel resistance %.2E ohm.",Rp)
```

---

# Chapter 40

## Field theory

Scilab code Exa 40.01 Example 1

```
1 //Problem 40.01: A field plot between two metal
   plates is shown in Figure 40.9. The relative
   permeability of the dielectric is 2.8. Determine
   the capacitance per metre length of the system.
2
3 //initializing the variables:
4 e0 = 8.85E-12;
5 er = 2.8;
6 l = 1; // in m
7
8 //calculation:
9 //From Figure 40.9
10 m = 16; // number of parallel squares measured along
   each equipotential
11 n = 6; // the number of series squares measured
   along each line of force
12 C = e0*er*l*m/n
13
14 printf("\n\n Result \n\n")
15 printf("\n capacitance is %.3E Farad.",C)
```

---

### Scilab code Exa 40.02 Example 2

```
1 //Problem 40.02: A field plot for a cross-section of
   a concentric cable is shown in Figure 40.10. If
   the relative permeability of the dielectric is
   3.4, determine the capacitance of a 100 m length
   of the cable.
2
3 //initializing the variables:
4 e0 = 8.85E-12;
5 er = 3.4;
6 l = 100; // in m
7
8 //calculation:
9 //From Figure 40.10
10 m = 13; // number of parallel squares measured along
    each equipotential
11 n = 4; // the number of series squares measured
    along each line of force
12 C = e0*er*l*m/n
13
14 printf("\n\n Result \n\n")
15 printf("\n capacitance is %.3E Farad.",C)
```

---

### Scilab code Exa 40.03 Example 3

```
1 //Problem 40.03: A coaxial cable has an inner core
   radius of 0.5 mm and an outer conductor of
   internal radius 6.0 mm. Determine the capacitance
   per metre length of the cable if the dielectric
   has a relative permittivity of 2.7.
2
```

```

3 //initializing the variables:
4 e0 = 8.85E-12;
5 er = 2.7;
6 ri = 0.0005; // in m
7 ro = 0.006; // in m
8
9 //calculation:
10 //capacitance C
11 C = 2*%pi*e0*er/(log(ro/ri))
12
13 printf("\n\n Result \n\n")
14 printf("\n capacitance is %.3E Farad.",C)

```

---

#### Scilab code Exa 40.04 Example 4

```

1 //Problem 40.04: A single-core concentric cable has
   a capacitance of 80 pF per metre length. The
   relative permittivity of the dielectric is 3.5
   and the core diameter is 8.0 mm. Determine the
   internal diameter of the sheath.
2
3 //initializing the variables:
4 C = 80E-12; // in Farads
5 e0 = 8.85E-12;
6 er = 3.5;
7 d0 = 0.008; // in m
8
9 //calculation:
10 //internal diameter
11 di = d0*(%e^(2*%pi*e0*er/C))
12
13 printf("\n\n Result \n\n")
14 printf("\n internal diameter is %.5 f m.",di)

```

---

### Scilab code Exa 40.05 Example 5

```
1 //Problem 40.05: A concentric cable has a core
   diameter of 32 mm and an inner sheath diameter of
   80 mm. The core potential is 40 kV and the
   relative permittivity of the dielectric is 3.5.
   Determine (a) the capacitance per kilometre
   length of the cable, (b) the dielectric stress at
   a radius of 30 mm, and (c) the maximum and
   minimum values of dielectric stress.
2
3 //initializing the variables:
4 e0 = 8.85E-12;
5 er = 3.5;
6 di = 0.08; // in m
7 d0 = 0.032; // in m
8 r = 0.03; // in m
9 V = 40000; // in Volts
10
11 //calculation:
12 //capacitance C
13 C = 2*pi*e0*er/(log(di/d0))
14 //dielectric stress at radius r,
15 E = V/(r*log(di/d0))
16 //maximum dielectric stress,
17 Emax = V/((d0/2)*(log((di/d0))))
18 //minimum dielectric stress,
19 Emin = V/((di/2)*(log((di/d0))))
20
21 printf("\n\n Result \n\n")
22 printf("\n capacitance is %.2E F/km",C*1E3)
23 printf("\n dielectric stress at radius r is %.2E V/m
   ",E)
24 printf("\n maximum dielectric stress, is %.2E V/m
```

minimum dielectric stress  $0.2E \text{ V/m}$ ,  $E_{\max}$ ,  $E_{\min}$ )

---

### Scilab code Exa 40.06 Example 6

```
1 //Problem 40.06: A single-core concentric cable is
  to be manufactured for a 60 kV, 50 Hz
  transmission system. The dielectric used is paper
  which has a maximum permissible safe dielectric
  stress of 10 MV/m rms and a relative permittivity
  of 3.5. Calculate (a) the core and inner sheath
  radii for the most economical cable, (b) the
  capacitance per metre length, and (c) the
  charging current per kilometre run.
2
3 //initializing the variables:
4 e0 = 8.85E-12;
5 er = 3.5;
6 V = 60000; // in Volts
7 f = 50; // in Hz
8 Em = 10E6; // in V/m
9
10
11 //calculation:
12 //core radius, a
13 a = V/Em
14 //internal sheath radius,
15 b = a*e^1
16 //capacitance
17 C = 2*pi*e0*er/(log(b/a))
18 //Charging current
19 I = V*2*pi*f*C
20 //charging current per kilometre
21 Ipkm = I*1000
22
23 printf("\n\n Result \n\n")
```

```

24 printf("\n core radius is %.2E m and internal sheath
      radius %.2E m",a,b)
25 printf("\n capacitance is %.2E F/m",C)
26 printf("\n the charging current per kilometre %.2f A
      ",Ipkm)

```

---

### Scilab code Exa 40.07 Example 7

```

1 //Problem 40.07: A concentric cable has a core
  diameter of 25 mm and an inside sheath diameter
  of 80 mm. The relative permittivity of the
  dielectric is 2.5, the loss angle is  $3.5 \times 10^{-3}$ 
  rad and the working voltage is 132 kV at 50 Hz
  frequency. Determine for a 1 km length of the
  cable (a) the capacitance, (b) the charging
  current and (c) the power loss.
2
3 //initializing the variables:
4 e0 = 8.85E-12;
5 er = 2.5;
6 di = 0.08; // in m
7 d0 = 0.025; // in m
8 r = 1000; // in m
9 V = 132000; // in Volts
10 f = 50; // in Hz
11 del = 3.5E-3; // rad.
12
13 //calculation:
14 //core radius, a
15 a = d0/2
16 //internal sheath radius,
17 b = di/2
18 //capacitance
19 C = 2*pi*e0*er*1E3/(log(b/a))
20 //Charging current

```

```

21 I = V*2*%pi*f*C
22 //power loss
23 P = (2*%pi*f*C*tan(del))*V^2
24
25 printf("\n\n Result \n\n")
26 printf("\n (a) capacitance for a 1 km length is %.2E
    F",C)
27 printf("\n (b) the charging current %.2E A/km",I)
28 printf("\n (c) power loss %.0f W",P)

```

---

#### Scilab code Exa 40.08 Example 8

```

1 //Problem 40.08: A concentric cable has a core
    diameter of 20 mm and a sheath inside diameter of
    60 mm. The permittivity of the dielectric is
    3.2. Using three equipotential surfaces within
    the dielectric , determine the capacitance of the
    cable per metre length by the method of
    curvilinear squares. Draw the field plot for the
    cable.
2
3 //initializing the variables:
4 e0 = 8.85E-12;
5 er = 3.2;
6 di = 0.06; // in m
7 d0 = 0.020; // in m
8
9 //calculation:
10 //core radius, a
11 a = d0/2
12 //internal sheath radius,
13 b = di/2
14 //capacitance
15 C = 2*%pi*e0*er/(log(b/a))
16

```



```
17 printf("\n\n Result \n\n")
18 printf("\n capacitance per m of length is %.2E F",C)
```

---

#### Scilab code Exa 40.09 Example 9

```
1 //Problem 40.09: Two parallel wires , each of
   diameter 5 mm, are uniformly spaced in air at a
   distance of 50 mm between centres . Determine the
   capacitance of the line if the total length is
   200 m.
2
3 //initializing the variables:
4 e0 = 8.85E-12;
5 er = 1;
6 D = 0.05; // in m
7 d = 0.005; // in m
8 l = 200; // in m
9
10 //calculation:
11 //capacitance
12 C = %pi*e0*er/(log(D/(d/2)))
13 //capacitance of a 200 m length
14 C200 = C*l
15
16 printf("\n\n Result \n\n")
17 printf("\n capacitance of a 200 m length is %.2E F",
   C200)
```

---

#### Scilab code Exa 40.10 Example 10

```
1 //Problem 40.10: A single-phase circuit is composed
   of two parallel conductors , each of radius 4 mm,
   spaced 1.2 m apart in air . The p.d. between the
```

conductors at a frequency of 50 Hz is 15 kV. Determine, for a 1 km length of line, (a) the capacitance of the conductors, (b) the value of charge carried by each conductor, and (c) the charging current.

```

2
3 //initializing the variables:
4 e0 = 8.85E-12;
5 er = 1;
6 D = 1.2; // in m
7 r = 0.004; // in m
8 f = 50; // in Hz
9 V = 15000; // in Volts
10 l = 1000; // in m
11
12 //calculation:
13 //capacitance
14 C = %pi*e0*er/(log(D/r))
15 //capacitance of a 1 km length
16 Cpkm = C*l
17 //Charge Q
18 Q = Cpkm*V
19 //Charging current
20 I = V*2*%pi*f*Cpkm
21
22 printf("\n\n Result \n\n")
23 printf("\n capacitance per 1km length is %.2E F",
        Cpkm)
24 printf("\n Charge Q is %.2E C",Q)
25 printf("\n Charging current is %.3f A",I)

```

---

#### Scilab code Exa 40.11 Example 11

```

1 //Problem 40.11:The charging current for an 800 m
  run of isolated twin line is not to exceed 15 mA.

```

The voltage between the lines is 10 kV at 50 Hz.  
 If the line is air-insulated, determine (a) the maximum value required for the capacitance per metre length, and (b) the maximum diameter of each conductor if their distance between centres is 1.25 m.

```

2
3 //initializing the variables:
4 e0 = 8.85E-12;
5 er = 1;
6 I = 0.015; // in Amperes
7 d = 1.25; // in m
8 r = 800; // in m
9 f = 50; // in Hz
10 V = 10000; // in Volts
11
12 //calculation:
13 //capacitance
14 C = I/(2*pi*f*V)
15 //required maximum value of capacitance
16 Cmax = C/r
17 //maximum diameter of each conductor
18 D = 2*d/(%e^(%pi*e0*er/Cmax))
19
20 printf("\n\n Result \n\n")
21 printf("\n required maximum value of capacitance is
    %.2E F/m", Cmax)
22 printf("\nthe maximum diameter of each conductor is
    %.4 f m", D)

```

---

#### Scilab code Exa 40.12 Example 12

```

1 //Problem 40.12: Determine the energy stored in a 10
    nF capacitor when charged to 1 kV, and the
    average power developed if this energy is

```

```

        dissipated in 10 s .
2
3 //initializing the variables:
4 e0 = 8.85E-12;
5 er = 1;
6 C = 10E-9; // in Farad
7 V = 1000; // in Volts
8 t = 10E-6; // in sec
9
10 //calculation:
11 //energy stored ,Wf
12 Wf = C*V*V/2
13 //average power developed
14 Pav = Wf/t
15
16 printf("\n\n Result \n\n")
17 printf("\n the energy stored is %.2E J",Wf)
18 printf("\nthe average power developed is %.0f W",Pav
    )

```

---

### Scilab code Exa 40.13 Example 13

```

1 //Problem 40.13: A capacitor is charged with 5 mC.
   If the energy stored is 625 mJ, determine (a) the
   voltage across the plates and (b) the
   capacitance of the capacitor.
2
3 //initializing the variables:
4 e0 = 8.85E-12;
5 er = 1;
6 Q = 5E-3; // in Coulomb
7 W = 0.625; // in Joules
8
9 //calculation:
10 //voltage across the plates

```

```

11 V = 2*W/Q
12 //Capacitance C
13 C = Q/V
14
15 printf("\n\n Result \n\n")
16 printf("\n voltage across the plates is %.0f V",V)
17 printf("\n Capacitance C is %.2E F",C)

```

---

#### Scilab code Exa 40.14 Example 14

```

1 //Problem 40.14: A ceramic capacitor is to be
   constructed to have a capacitance of 0.01 F and
   to have a steady working potential of 2.5 kV
   maximum. Allowing a safe value of field stress of
   10 MV/m, determine (a) the required thickness of
   the ceramic dielectric , (b) the area of plate
   required if the relative permittivity of the
   ceramic is 10, and (c) the maximum energy stored
   by the capacitor.
2
3 //initializing the variables:
4 e0 = 8.85E-12;
5 er = 10;
6 C = 0.01E-6; // in Farad
7 E = 10E6; // in V/m
8 V = 2500; // in Volts
9
10 //calculation:
11 //thickness of ceramic dielectric ,
12 d = V/E
13 //cross-sectional area of plate
14 A = C*d/(e0*er)
15 //Maximum energy stored ,
16 W = C*V*V/2
17

```

```

18 printf("\n\n Result \n\n")
19 printf("\n thickness of ceramic dielectric is %.2E m
    ",d)
20 printf("\n cross-sectional area of plate , is %.4f m2
    ",A)
21 printf("\n Maximum energy stored is %.4f J",W)

```

---

#### Scilab code Exa 40.15 Example 15

```

1 //Problem 40.15: A 400 pF capacitor is charged to a
  p.d. of 100 V. The dielectric has a cross-
  sectional area of 200 cm2 and a relative
  permittivity of 2.3. Calculate the energy stored
  per cubic metre of the dielectric.
2
3 //initializing the variables:
4 e0 = 8.85E-12;
5 er = 2.3;
6 A = 0.02; // in m2
7 C = 400E-12; // in Farad
8 V = 100; // in Volts
9
10 //calculation:
11 //energy stored per unit volume of dielectric ,
12 W = ((C*V)^2)/(2*e0*er*A^2)
13
14 printf("\n\n Result \n\n")
15 printf("\n energy stored per unit volume of
    dielectric is %.4f J/m3",W)

```

---

#### Scilab code Exa 40.16 Example 16

```

1 //Problem 40.16: A coaxial cable has an inner core
  of radius 1.0 mm and an outer sheath of internal
  radius 4.0 mm. Determine the inductance of the
  cable per metre length. Assume that the relative
  permeability is unity.
2
3 //initializing the variables:
4 u0 = 4*%pi*1E-7;
5 ur = 1;
6 a = 0.001; // in m
7 b = 0.004; // in m
8
9 //calculation:
10 //inductance L
11 L = (u0*ur/(2*%pi))*(0.25 + log(b/a))
12
13 printf("\n\n Result \n\n")
14 printf("\n inductance L is %.2E H/m" ,L)

```

---

#### Scilab code Exa 40.17 Example 17

```

1 //Problem 40.17: A concentric cable has a core
  diameter of 10 mm. The inductance of the cable is
   $4 \times 10^{-7}$  H/m. Ignoring inductance due to
  internal linkages, determine the diameter of the
  sheath. Assume that the relative permeability is
  1.
2
3 //initializing the variables:
4 u0 = 4*%pi*1E-7;
5 ur = 1;
6 da = 0.010; // in m
7 L = 4E-7; // in H/m
8
9 //calculation:

```

```

10 //diameter of the sheath
11 db = da*(%e^(L/(u0*ur/(2*%pi))))
12
13 printf("\n\n Result \n\n")
14 printf("\n diameter of the sheath is %.4f m",db)

```

---

### Scilab code Exa 40.18 Example 18

```

1 //Problem 40.18: A coaxial cable 7.5 km long has a
   core 10 mm diameter and a sheath 25 mm diameter ,
   the sheath having negligible thickness. Determine
   for the cable (a) the inductance , assuming
   nonmagnetic materials , and (b) the capacitance ,
   assuming a dielectric of relative permittivity 3.
2
3 //initializing the variables:
4 u0 = 4*%pi*1E-7;
5 ur = 1;
6 e0 = 8.85E-12;
7 er = 3;
8 da = 0.010; // in m
9 db = 0.025; // in m
10 l = 7500; // in m
11
12 //calculation:
13 //inductance per metre length
14 L = (u0*ur/(2*%pi))*(0.25 + log(db/da))
15 //Since the cable is 7500 m long ,
16 L7500 = L*7500
17 //capacitance C
18 C = 2*%pi*e0*er/(log(db/da))
19 ////Since the cable is 7500 m long ,
20 C7500 = C*7500
21
22 printf("\n\n Result \n\n")

```



```
23 printf("\ninductance is %.5f H",L7500)
24 printf("\ncapCItance is %.2E F",C7500)
```

---

#### Scilab code Exa 40.19 Example 19

```
1 //Problem 40.19: A single-phase power line comprises
    two conductors each with a radius 8.0 mm and
    spaced 1.2 m apart in air. Determine the
    inductance of the line per metre length ignoring
    internal linkages. Assume the relative
    permeability  $\mu_r = 1$ .
2
3 //initializing the variables:
4  $\mu_0 = 4 * \pi * 1E-7$ ;
5  $\mu_r = 1$ ;
6  $\epsilon_0 = 8.85E-12$ ;
7  $\epsilon_r = 3$ ;
8  $D = 1.2$ ; // in m
9  $a = 0.008$ ; // in m
10
11 //calculation:
12 //inductance per metre length
13  $L = (\mu_0 * \mu_r / (\pi)) * (\log(D/a))$ 
14
15 printf("\n\n Result \n\n")
16 printf("\ninductance is %.2E H/m",L)
```

---

#### Scilab code Exa 40.20 Example 20

```
1 //Problem 40.20: Determine (a) the loop inductance ,
    and (b) the capacitance of a 1 km length of
    single-phase twin line having conductors of
    diameter 10 mm and spaced 800 mm apart in air.
```

```

2
3 //initializing the variables:
4 u0 = 4*%pi*1E-7;
5 ur = 1;
6 e0 = 8.85E-12;
7 er = 1;
8 l = 1000; // in m
9 D = 0.8; // in m
10 a = 0.01/2; // in m
11
12 //calculation:
13 //inductance per metre length
14 L = (u0*ur/(%pi))*(0.25 + log(D/a))
15 //Since the cable is 1000 m long ,
16 L1k = L*l
17 //capacitance C
18 C = %pi*e0*er/(log(D/a))
19 ////Since the cable is 1000 m long ,
20 C1k = C*l
21
22 printf("\n\n Result \n\n")
23 printf("\ninductance is %.5f H" ,L1k)
24 printf("\ncapcitanace is %.2E F" ,C1k)

```

---

#### Scilab code Exa 40.21 Example 21

```

1 //Problem 40.21: The total loop inductance of an
   isolated twin power line is 2.185 H/m. The
   diameter of each conductor is 12 mm. Determine
   the distance between their centres.
2
3 //initializing the variables:
4 L = 2.185E-6; // in H/m
5 u0 = 4*%pi*1E-7;
6 ur = 1;

```

```

7 a = 0.012/2; // in m
8
9 //calculation:
10 //distance D
11 D = a*e^((L*pi)/(u0*ur) - 0.25)
12
13 printf("\n\n Result \n\n")
14 printf("\ndistance D is %.2f m",D)

```

---

#### Scilab code Exa 40.22 Example 22

```

1 //Problem 40.22: Calculate the value of the energy
   stored when a current of 50 mA is flowing in a
   coil of inductance 200 mH. What value of current
   would double the energy stored?
2
3 //initializing the variables:
4 L = 0.2; // in H
5 I = 0.05; // in Amperes
6 u0 = 4*pi*1E-7;
7 ur = 1;
8
9 //calculation:
10 //energy stored in inductor
11 W = L*I*I/2
12 //current I
13 I = (2*2*W/L)^0.5
14
15 printf("\n\n Result \n\n")
16 printf("\nenergy stored in inductor is %.2E J",W)
17 printf("\ncurrent I is %.2E A",I)

```

---

#### Scilab code Exa 40.23 Example 23

```

1 //Problem 40.23: The airgap of a moving coil
   instrument is 2.0 mm long and has a cross-
   sectional area of 500 mm2. If the flux density is
   50 mT, determine the total energy stored in the
   magnetic field of the airgap.
2
3 //initializing the variables:
4 B = 0.05; // in Tesla
5 A = 500E-6; // in m2
6 l = 0.002; // in m
7 u0 = 4*%pi*1E-7;
8
9 //calculation:
10 //energy stored
11 W = (B^2)/(2*u0)
12 //Volume of airgap
13 v = A*l
14 //energy stored in airgap
15 W = W*v
16
17 printf("\n\n Result \n\n")
18 printf("\nenergy stored in the airgap is %.2E J",W)

```

---

#### Scilab code Exa 40.24 Example 24

```

1 //Problem 40.24: Determine the strength of a uniform
   electric field if it is to have the same energy
   as that established by a magnetic field of flux
   density 0.8 T. Assume that the relative
   permeability of the magnetic field and the
   relative permittivity of the electric field are
   both unity.
2
3 //initializing the variables:
4 B = 0.8; // in Tesla

```

```
5 A = 500E-6; // in m2
6 l = 0.002; // in m
7 u0 = 4*%pi*1E-7;
8 ur = 1;
9 e0 = 8.85E-12;
10 er = 1;
11
12 //calculation:
13 //energy stored in mag. field
14 W = (B^2)/(2*u0)
15 //electric field
16 E = (2*W/(e0*er))^0.5
17
18 printf("\n\n Result \n\n")
19 printf("\nelectric field strength is %.2E V/m",E)
```

---

# Chapter 41

## Attenuators

Scilab code Exa 41.01 Example 1

```
1 //Problem 41.01: The ratio of output power to input
  power in a system is
2 //(a)2 (b) 25 (c) 1000 and (d) 0.01
3 //Determine the power ratio in each case (i) in
  decibels and (ii) in nepers.
4
5 //initializing the variables:
6 //ratio of output power to input power
7 rp1 = 2;
8 rp2 = 25;
9 rp3 = 1000;
10 rp4 = 0.01;
11
12 //calculation:
13 //power ratio in decibels
14 rpd1 = 10*log10(rp1)
15 rpd2 = 10*log10(rp2)
16 rpd3 = 10*log10(rp3)
17 rpd4 = 10*log10(rp4)
18 //power ratio in nepers
19 rpn1 = (log(rp1))/2
```

```

20 rpn2 = (log(rp2))/2
21 rpn3 = (log(rp3))/2
22 rpn4 = (log(rp4))/2
23
24 printf("\n\n Result \n\n")
25 printf("\n power ratio in decibels are (a)%0f dB (b
    )%0f dB (c) %0f dB and (d) %0f dB", rpd1, rpd2,
    rpd3, rpd4)
26 printf("\n power ratio in nepers are (a)%0.3f Np (b)%
    0.3f Np (c) %0.3f Np and (d) %0.3f Np", rpn1, rpn2,
    rpn3, rpn4)

```

---

#### Scilab code Exa 41.02 Example 2

```

1 //Problem 41.02: 5% of the power supplied to a cable
    appears at the output terminals. Determine the
    attenuation in decibels.
2
3 //initializing the variables:
4 rp = 0.05; // power ratio P2/P1
5
6 //calculation:
7 //power ratio in decibels
8 rpd = 10*log10(rp)
9
10 printf("\n\n Result \n\n")
11 printf("\nthe attenuation is %0f dB", abs(rpd))

```

---

#### Scilab code Exa 41.03 Example 3

```

1 //Problem 41.03: An amplifier has a gain of 15 dB.
    If the input power is 12 mW, determine the output
    power.

```

```

2
3 //initializing the variables:
4 gain = 1.5; // in dB
5 Pi = 0.012; // in Watt
6
7 //calculation:
8 //output power
9 Po = Pi*10^gain
10
11 printf("\n\n Result \n\n")
12 printf("\noutput power is %.4f W",Po)

```

---

#### Scilab code Exa 41.04 Example 4

```

1 //Problem 41.04: The current output of an attenuator
   is 50 mA. If the current ratio of the attenuator
   is 1.32 Np, determine (a) the current input and
   (b) the current ratio expressed in decibels.
   Assume that the input and load resistances of the
   attenuator are equal.
2
3 //initializing the variables:
4 I2 = 0.05; // in Amperes
5 rin = 1.32; // in Np
6
7 //calculation:
8 //current input, I1
9 I1 = I2*%e^(rin)
10 //current ratio in decibels
11 rid = 20*log10(I2/I1)
12
13 printf("\n\n Result \n\n")
14 printf("\ncurrent input, I1 is %.4f A",I1)
15 printf("\ncurrent ratio in decibels is %.2f dB",rid)

```

---



**Scilab code Exa 41.05** Example 5

```
1 //Problem 41.05: Determine the characteristic
   impedance of each of the attenuator sections
   shown in Figure 41.9.
2
3 //initializing the variables:
4 R1a = 8; // in ohm
5 R2a = 21; // in ohm
6 R1b = 10; // in ohm
7 R2b = 15; // in ohm
8 R1c = 200; // in ohm
9 R2c = 56.25; // in ohm
10
11 //calculation:
12 //for a T-section attenuator the characteristic
   impedance
13 Roa = (R1a^2 + 2*R1a*R2a)^0.5
14 Rob = (R1b^2 + 2*R1b*R2b)^0.5
15 Roc = (R1c^2 + 2*R1c*R2c)^0.5
16
17 printf("\n\n Result \n\n")
18 printf("\nfor a T-sections attenuator the
   characteristic impedances are (a) %.0f ohm, (b) %
   .0f ohm and (c)%.0f ohm",Roa,Rob,Roc)
```

---

**Scilab code Exa 41.06** Example 6

```
1 //Problem 41.06: A symmetrical pi-attenuator pad has
   a series arm of 500 ohm resistance and each
   shunt arm of 1 kohm resistance. Determine (a) the
```

```

        characteristic impedance, and (b) the
        attenuation (in dB) produced by the pad.
2
3 //initializing the variables:
4 R1 = 500; // in ohm
5 R2 = 1000; // in ohm
6 I1 = 1; // in ampere (lets say)
7
8 //calculation:
9 // for symmetrical pi-attenuator section
10 //characteristic impedance, R0
11 R0 = (R1*(R2^2)/(R1 + 2*R2))^0.5
12 //current Ix
13 Ix = (R2/(R2 + R1 + (R2*R0/(R2 + R0))))*I1
14 //current I2
15 I2 = (R2/(R2 + R0))*Ix
16 ri = I1/I2; // retio of currents
17 //attenuation
18 attn = 20*log10(ri)
19
20 printf("\n\n Result \n\n")
21 printf("\n the characteristic impedance is %.0f ohm"
        ,R0)
22 printf("\n attenuation is %.2f dB",attn)

```

---

#### Scilab code Exa 41.07 Example 7

```

1 //Problem 41.07: For each of the attenuator networks
    shown in Figure 41.11, determine (a) the input
    resistance when the output port is open-circuited
    , (b) the input resistance when the output port
    is short-circuited , and (c) the characteristic
    impedance.
2
3 //initializing the variables:

```

```

4 R1 = 15; // in ohm
5 R2 = 10; // in ohm
6 R3 = 5; // in ohm
7
8 //calculation:
9 //For the T-network shown in Figure 41.11(i):
10 Roct = R1 + R2
11 Rsct = R1 + R1*R2/(R1 + R2)
12 Rot = (Roct*Rsct)^0.5
13 //For the Pi-network shown in Figure 41.11(ii):
14 Rocpi = R3*(R1 + R3)/(R3 + R1 + R3)
15 Rscpi = R3*R1/(R3 + R1)
16 Ropi = (R1*(R3^2)/(R1 + 2*R3))^0.5
17
18 printf("\n\n Result \n\n")
19 printf("\n the input resistance when the output port
    is open-circuited is (a) %.0f ohm (b) %.0f ohm",
    Roct, Rocpi)
20 printf("\n the input resistance when the output port
    is short-circuited is (a) %.0f ohm (b) %.2f ohm"
    ,Rsct, Rscpi)
21 printf("\n the characteristic impedance is (a) %.1f
    ohm (b) %.2f ohm", Rot, Ropi)

```

---

#### Scilab code Exa 41.10 Example 10

```

1 //Problem 41.10: The attenuator shown in Figure
    41.15 feeds a matched load. Determine (a) the
    characteristic impedance R0, and (b) the
    insertion loss in decibels.
2
3 //initializing the variables:
4 R1 = 300; // in ohm
5 R2 = 450; // in ohm
6 I1 = 1; // in ampere (lets say)

```

```

7
8 //calculation:
9 //the characteristic impedance of a symmetric T-pad
  attenuator is given by
10 R0 = (R1^2 + 2*R1*R2)^0.5
11 //By current division
12 //current I2
13 I2 = (R2/(R2 + R1+ R0))*I1
14 ri = I1/I2; // ratio of currents
15 //insertion loss
16 il = 20*log10(ri)
17
18 printf("\n\n Result \n\n")
19 printf("\n the characteristic impedance is %.0f ohm"
  ,R0)
20 printf("\n insertion loss is %.2f dB",il)

```

---

#### Scilab code Exa 41.11 Example 11

```

1 //Problem 41.11: A 0 3 kohm rheostat is connected
  across the output of a signal generator of
  internal resistance 500 ohm. If a load of 2 kohm
  is connected across the rheostat , determine the
  insertion loss at a tapping of (a) 2 kohm, (b) 1
  kohm.
2
3 //initializing the variables:
4 r = 500; // in ohm
5 Rhm = 3000; // in ohm
6 RL = 2000; // in ohm
7 r1 = 2000; // in ohm
8 r2 = 1000; // in ohm
9 E = 1; // in volts (lets say)
10
11 //calculation:

```

```

12 //Without the rheostat in the circuit the voltage
    across the 2 kohm load , VL
13 VL = (RL/(RL + r))*E
14 //voltage V2 with 2kohm tapping
15 V2 = ((RL*r1/(r1 + RL))/((RL*r1/(r1 + RL)) + Rhm -
    r1 + r))*E
16 rv1 = VL/V2; // ratio of currents
17 //insertion loss
18 il1 = 20*log10(rv1)
19 //voltage V1 with 1kohm tapping
20 V1 = ((RL*r2/(r2 + RL))/((RL*r2/(r2 + RL)) + Rhm -
    r2 + r))*E
21 rv2 = VL/V1; // ratio of currents
22 //insertion loss
23 il2 = 20*log10(rv2)
24
25 printf("\n\n Result \n\n")
26 printf("\n insertion loss for 2kohm tap is %.2f dB",
    il1)
27 printf("\n insertion loss for 1kohm tap is %.2f dB",
    il2)

```

---

### Scilab code Exa 41.12 Example 12

```

1 //Problem 41.12: A symmetrical pi-attenuator pad has
    a series arm of resistance 1000 ohm and shunt
    arms each of 500ohm . Determine (a) its
    characteristic impedance, and (b) the insertion
    loss (in decibels) when feeding a matched load..
2
3 //initializing the variables:
4 R1 = 1000; // in ohm
5 R2 = 500; // in ohm
6 I1 = 1; // in amperes (lets say)
7

```

```

8 //calculation:
9 //characteristic impedance of a symmetrical
  attenuator
10 R0 = (R1*(R2^2)/(R1 + 2*R2))^0.5
11 //current Ix
12 Ix = (R2/(R2 + R1 + (R2*R0/(R2 + R0))))*I1
13 //current I2
14 I2 = (R2/(R2 + R0))*Ix
15 ri = I1/I2; // retio of currents
16 //insertion loss
17 il = 20*log10(ri)
18
19 printf("\n\n Result \n\n")
20 printf("\n characteristic impedance is %.0f ohm",R0)
21 printf("\n insertion loss is %.2f dB",il)

```

---

#### Scilab code Exa 41.13 Example 13

```

1 //Problem 41.13: An asymmetrical T-section
  attenuator is shown in Figure 41.24. Determine
  for the section (a) the image impedances, and (b)
  the iterative impedances.
2
3 //initializing the variables:
4 R1 = 100; // in ohm
5 R2 = 200; // in ohm
6 R3 = 300; // in ohm
7 I1 = 1; // in amperes (lets say)
8
9 //calculation:
10 //image impedance Roa
11 Roa = ((R1 + R2)*(R2 + (R1*R3/(R1 + R3))))^0.5
12 //image impedance Rob
13 Rob = ((R1 + R3)*(R3 + (R1*R2/(R1 + R2))))^0.5
14 //The iterative impedance at port 1

```

```

15 Ri1 = (-1*R1 + (R1^2 - (-1*4*((R2*(R1 + R3)) + (R3*
    R1))))^0.5)/2
16 //The iterative impedance at port 2
17 Ri2 = (R1 + (R1^2 - (-1*4*((R3*(R1 + R2)) + (R2*R1))
    ))^0.5)/2
18
19 printf("\n\n Result \n\n")
20 printf("\n image impedance are %.1f ohm and %.0f ohm
    ",Roa,Rob)
21 printf("\n iterative impedances are %.1f ohm and %.1
    f ohm ",Ri1,Ri2)

```

---

#### Scilab code Exa 41.14 Example 14

```

1 //Problem 41.14: An asymmetrical pi-section
    attenuator is shown in Figure 41.28. Determine
    for the section (a) the image impedances, and (b)
    the iterative impedances.
2
3 //initializing the variables:
4 R1 = 1000; // in ohm
5 R2 = 2000; // in ohm
6 R3 = 3000; // in ohm
7 I1 = 1; // in amperes (lets say)
8
9 //calculation:
10 //image impedance Roa
11 Roa = (((R3 + R2)*R1/(R1 + R2 + R3))*(R1*R3/(R1 + R3
    )))^0.5
12 //image impedance Rob
13 Rob = (((R3 + R1)*R2/(R1 + R2 + R3))*(R2*R3/(R2 + R3
    )))^0.5
14 //The iterative impedance at port 1
15 Ri1 = (-1*R1 + ((R1^2) - (-1*4*2*R2*R1))^0.5)/(2*2)
16 //The iterative impedance at port 2

```

```

17 Ri2 = (R1 + ((-1*R1)^2 - (-1*4*2*R2*R1))^0.5)/(2*2)
18
19 printf("\n\n Result \n\n")
20 printf("\n image impedance are %.0f ohm and %.0f ohm
    ",Roa,Rob)
21 printf("\n iterative impedances are %.0f ohm and %.0
    f ohm ",Ri1,Ri2)

```

---

### Scilab code Exa 41.15 Example 15

```

1 //Problem 41.15: A generator having an internal
    resistance of 500 ohm is connected to a 100 ohm
    load via an impedance–matching resistance pad as
    shown in Figure 41.33. Determine (a) the values
    of resistance R1 and R2, (b) the attenuation of
    the pad in decibels , and (c) its insertion loss.
2
3 //initializing the variables:
4 r = 500; // in ohm
5 RL = 100; // in ohm
6 E = 1; // in volts (lets say)
7
8 //calculation:
9 //res.
10 R1 = (r*(r - RL))^0.5
11 R2 = (r*RL^2/(r - RL))^0.5
12 //current I1
13 I1 = E/(r + R1 + R2*RL/(RL + R2))
14 //current I2
15 I2 = (R2/(R2 + RL))*I1
16 //input power
17 P1 = r*I1^2
18 //output power
19 P2 = RL*I2^2
20 //attenuation

```



```

21 attn = 10*log10(P1/P2)
22 //Load current , IL
23 IL = E/(r + RL)
24 //voltage , VL
25 VL = IL*RL
26 //voltage , V1
27 V1 = E - I1*r
28 //voltage , V2
29 V2 = V1 - I1*R1
30 //insertion loss
31 il = 20*log10(VL/V2)
32
33 printf("\n\n Result \n\n")
34 printf("\n R1 = %.1f ohm and R2 = %.1f ohm ",R1,R2)
35 printf("\n attenuation is %.2f dB ",attn)
36 printf("\n In decibels , the insertion loss is %.2f
    dB ",il)

```

---

#### Scilab code Exa 41.16 Example 16

```

1 //Problem 41.16: Five identical attenuator sections
  are connected in cascade. The overall attenuation
  is 70 dB and the voltage input to the first
  section is 20 mV. Determine (a) the attenuation
  of eac individual attenuation section , (b) the
  voltage output of the fina stage , and (c) the
  voltage output of the third stage.
2
3 //initializing the variables:
4 attn0 = 70; // in dB
5 n = 5; // numbers of identical atteneurs
6 V1 = 0.02; // in Volts
7
8 //calculation:
9 //attenuation of each section

```

```
10 attn = attn0/n
11 //output of the final stage
12 Vo = V1/(10^(attn0/20))
13 //voltage output of the third stage
14 V3 = V1/(10^(3*attn/20))
15
16 printf("\n\n Result \n\n")
17 printf("\n attenuation of each section = %.0f dB ",
    attn)
18 printf("\n output of the final stage is %.2E V ",Vo)
19 printf("\n voltage output of the third stage is %.2E
    V ",V3)
```

---

# Chapter 42

## Filter networks

Scilab code Exa 42.01 Example 1

```
1 //Problem 42.01: Determine the cut-off frequency and
   the nominal impedance of each of the low-pass
   filter sections shown in Figure 42.19.
2
3 //initializing the variables:
4 L1 = 2*100E-3; // in Henry
5 C1 = 0.2E-6; // in Fareads
6 L2 = 0.4; // in Henry
7 C2 = 2*200E-12; // in Fareads
8
9 //calculation:
10 //cut-off frequency
11 fc1 = 1/(%pi*(L1*C1)^0.5)
12 //nominal impedance
13 R01 = (L1/C1)^0.5
14 //cut-off frequency
15 fc2 = 1/(%pi*(L2*C2)^0.5)
16 //nominal impedance
17 R02 = (L2/C2)^0.5
18
19 printf("\n\n Result \n\n")
```

```
20 printf("\n cut-off frequency %.0f Hz and the nominal
    impedance is %.0f ohm ",fc1, R01)
21 printf("\n cut-off frequency %.0f Hz and the nominal
    impedance is %.0f ohm ",fc2, R02)
```

---

### Scilab code Exa 42.02 Example 2

```
1 //Problem 42.02: A filter section is to have a
    characteristic impedance at zero frequency of 600
    ohm and a cut-off frequency at 5 MHz. Design (a)
    a low-pass T section filter , and (b) a low-pass
    pi section filter to meet these requirements.
2
3 //initializing the variables:
4 R0 = 600; // in ohm
5 fc = 5E6; // in Hz
6
7 //calculation:
8 //capacitance
9 C = 1/(%pi*R0*fc)
10 //inductance
11 L = R0/(%pi*fc)
12
13 printf("\n\n Result \n\n")
14 printf("\n A low-pass T section filter capcitanace is
    %.2E farad and inductance is%.2E Henry",C, L/2)
15 printf("\n A low-pass pi section filter capcitanace
    is %.2E farad and inductance is%.2E Henry",C/2, L
    )
```

---

### Scilab code Exa 42.03 Example 3

```

1 //Problem 42.03: The nominal impedance of a low-pass
  pi section filter is 500 ohm and its cut-off
  frequency is at 100 kHz. Determine (a) the value
  of the characteristic impedance of the section at
  a frequency of 90 kHz, and (b) the value of the
  characteristic impedance of the equivalent low-
  pass T section filter.
2
3 //initializing the variables:
4 R0 = 500; // in ohm
5 fc = 100000; // in Hz
6 f = 90000; // in Hz
7
8 //calculation:
9 //characteristic impedance of the pi section
10 Zpi = R0/(1 - (f/fc)^2)^0.5
11 //characteristic impedance of the T section
12 Zt = R0*(1 - (f/fc)^2)^0.5
13
14 printf("\n\n Result \n\n")
15 printf("\ncharacteristic impedance of the pi section
  is %.0f ohm",Zpi)
16 printf("\ncharacteristic impedance of the T section
  is %.0f ohm",Zt)

```

---

#### Scilab code Exa 42.04 Example 4

```

1 //Problem 42.04: A low-pass section filter has a
  nominal impedanc of 600 ohm and a cut-off
  frequency of 2 MHz. Determine the frequency at
  which the characteristic impedance of the section
  is (a) 600 ohm (b) 1 kohm (c) 10kohm.
2
3 //initializing the variables:
4 R0 = 600; // in ohm

```

```

5 fc = 2E6; // in Hz
6 Z1 = 600; // in ohm
7 Z2 = 1000; // in ohm
8 Z3 = 10000; // in ohm
9
10 //calculation:
11 //frequency
12 f1 = fc*(1 - (R0/Z1)^2)^0.5
13 f2 = fc*(1 - (R0/Z2)^2)^0.5
14 f3 = fc*(1 - (R0/Z3)^2)^0.5
15
16 printf("\n\n Result \n\n")
17 printf("\nfrequency at which the characteristic
    impedance of the section is 600 ohm is %.0f Hz
    and 1000 Ohm is %.2E Hz and 10000 ohm is %.3E Hz
    ",f1,f2,f3)

```

---

#### Scilab code Exa 42.05 Example 5

```

1 //Problem 42.05: Determine for each of the high-pass
    filter sections shown in Figure 42.27 (i) the
    cut-off frequency , and (ii) the nominal impedance
    .
2
3 //initializing the variables:
4 L1 = 100E-3; // in Henry
5 C1 = 0.2E-6/2; // in Fareads
6 L2 = 200E-6/2; // in Henry
7 C2 = 4000E-12; // in Fareads
8
9 //calculation:
10 //cut-off frequency
11 fc1 = 1/(4*pi*(L1*C1)^0.5)
12 //nominal impedance
13 R01 = (L1/C1)^0.5

```

```

14 //cut-off frequency
15 fc2 = 1/(4*pi*(L2*C2)^0.5)
16 //nominal impedance
17 R02 = (L2/C2)^0.5
18
19 printf("\n\n Result \n\n")
20 printf("\n cut-off frequency %.0f Hz and the nominal
    impedance is %.0f ohm",fc1, R01)
21 printf("\n cut-off frequency %.0f Hz and the nominal
    impedance is %.0f ohm ",fc2, R02)

```

---

#### Scilab code Exa 42.07 Example 7

```

1 //Problem 42.07: A low-pass T section filter having
    a cut-off frequency of 15 kHz is connected in
    series with a high-pass T section filter having a
    cut-off frequency of 10 kHz. The terminating
    impedance of the filter is 600 ohm.(a) Determine
    the values of the components comprising the
    composite filter.
2
3 //initializing the variables:
4 R0 = 600; // in ohm
5 fc1 = 15000; // in Hz
6 fc2 = 10000; // in Hz
7
8 //calculation:
9 //capacitance
10 C1 = 1/(%pi*R0*fc1)
11 //inductance
12 L1 = R0/(%pi*fc1)
13 //capacitance
14 C2 = 1/(4*pi*R0*fc2)
15 //inductance
16 L2 = R0/(4*pi*fc2)

```

```

17
18 printf("\n\n Result \n\n")
19 printf("\n A low-pass T section filter capacitance is
    %.2E farad and inductance is%.2E Henry",C1, L1
    /2)
20 printf("\n A high-pass pi section filter capacitance
    is %.2E farad and inductance is%.2E Henry",2*C2,
    L2)

```

---

#### Scilab code Exa 42.08 Example 8

```

1 //Problem 42.08: A high-pass T section filter has a
    cut-off frequency of 500 Hz and a nominal
    impedance of 600 ohm. Determine the frequency at
    which the characteristic impedance of the section
    is (a) zero , (b) 300 ohm, (c) 590 ohm.
2
3 //initializing the variables:
4 R0 = 600; // in ohm
5 fc = 500; // in Hz
6 Z1 = 0; // in ohm
7 Z2 = 300; // in ohm
8 Z3 = 590; // in ohm
9
10 //calculation:
11 //frequency
12 f1 = fc
13 f2 = fc/(1 - (Z2/R0)^2)^0.5
14 f3 = fc/(1 - (Z3/R0)^2)^0.5
15
16 printf("\n\n Result \n\n")
17 printf("\n frequency at which the characteristic
    impedance of the section is 0 ohm is %.0f Hz and
    300 Ohm is %.1f Hz and 590 ohm is %.0f Hz ",f1,f2
    ,f3)

```



---

**Scilab code Exa 42.09** Example 9

```
1 //Problem 42.09: The propagation coefficients of two
  filter networks are given by (a)  $r = (1.25 + i0.52)$  (b)  $r = 1.794/_{-39.4}$  Determine for each (i
  ) the attenuation coefficient , and (ii) the phase
  shift coefficient .
2
3 //initializing the variables:
4 r1 = 1.25 + %i*0.52; // propagation coefficients
5 rr = 1.794; // propagation coefficients
6 thetar = -39.4; // in ddegrees
7
8 //calculation:
9 //r
10 r2 = rr*cos(thetar*%pi/180) + %i*rr*sin(thetar*%pi
  /180)
11 //attenuation coefficient
12 a1 = real(r1)
13 a2 = real(r2)
14 //phase shift coefficient
15 b1 = imag(r1)
16 b2 = imag(r2)
17
18 printf("\n\n Result \n\n")
19 printf("\nattenuation coefficient are for (a) is %.2
  f N and for (b) is %.3f N ",a1,a2)
20 printf("\nphase shift coefficient are for (a) is %.2
  f rad and for (b) is %.3f rad ",b1,b2)
```

---

**Scilab code Exa 42.10** Example 10

```

1 //Problem 42.10: The current input to a filter
   section is 24/_10 mA and the current output is
   8/_-45 mA. Determine for the section (a) the
   attenuation coefficient , (b) the phase shift
   coefficient , and (c) the propagation coefficient.
   (d) If five such sections are cascaded determine
   the output current of the fifth stage and the
   overall propagation constant of the network.
2
3 //initializing the variables:
4 ri1 = 0.024; // in amperes
5 ri2 = 0.008; // in amperes
6 thetai1 = 10; // in ddegrees
7 thetai2 = -45; // in ddegrees
8
9 //calculation:
10 //currents
11 I1 = ri1*cos(thetai1*%pi/180) + %i*ri1*sin(thetai1*
   %pi/180)
12 I2 = ri2*cos(thetai2*%pi/180) + %i*ri2*sin(thetai2*
   %pi/180)
13 //ir
14 ir = I1/I2
15 irmag = ri1/ri2
16 thetai = thetai1-thetai2
17 //attenuation coefficient
18 a = log(irmag)
19 //phase shift coefficient
20 b = thetai*%pi/180
21 //propagation coefficient
22 r = a + %i*b
23 //output current of the fifth stage
24 I6 = I1/(ir^5)
25 x = ir^5
26 xmg = (real(x)^2 + imag(x)^2)^0.5
27 //overall attenuation coefficient
28 ad = log(xmg)
29 //overall phase shift coefficient

```

```

30 bd = atan(imag(x)/real(x)) + 2*%pi
31
32 printf("\n\n Result \n\n")
33 printf("\nattenuation coefficient is %.3f N ",a)
34 printf("\nphase shift coefficient is %.3f rad ",b)
35 printf("\npropagation coefficient is %.3f + (%.3f)i
    ",a,b)
36 printf("\nthe output current of the fifth stage is %
    .2E + (%.2E)i A and the overall propagation
    coefficient is %.2f + (%.2f)i",real(I6),imag(I6),
    ad,bd)

```

---

#### Scilab code Exa 42.11 Example 11

```

1 //Problem 42.11: For the low-pass T section filter
  shown in Figure 42.34 determine (a) the
  attenuation coefficient , (b) the phase shift
  coefficient and (c) the propagation coefficient r
  .
2
3 //initializing the variables:
4 XL = %i*5; // in ohms
5 Xc = -1*%i*10; // in ohms
6 RL = 12; // in ohms
7 I1 = 1; // in amperes (lets say)
8
9 //calculation:
10 //current I2
11 I2 = (Xc/(Xc + XL + RL))*I1
12 //current ratio
13 Ir = I1/I2
14 Irmg = (real(Ir)^2 + imag(Ir)^2)^0.5
15 //attenuation coefficient
16 a = log(Irmg)
17 //phase shift coefficient

```

```

18 b = atan(imag(Ir)/real(Ir))
19 //propagation coefficient
20 r = a + %i*b
21
22 printf("\n\n Result \n\n")
23 printf("\nattenuation coefficient is %.3f N ",a)
24 printf("\nphase shift coefficient is %.3f rad ",b)
25 printf("\npropagation coefficient is %.3f + (%.3f)i
    ",a,b)

```

---

#### Scilab code Exa 42.12 Example 12

```

1 //Problem 42.12: Determine for the filter section
  shown in Figure 42.40, (a) the time delay for the
  signal to pass through the filter , assuming the
  phase shift is small, and (b) the time delay for
  a signal to pass through the section at the cut-
  off frequency .
2
3 //initializing the variables:
4 L = 2*0.5; // in Henry
5 C = 2E-9; // in Farad
6
7 //calculation:
8 //time delay
9 t = (L*C)^0.5
10 //time delay at the cut-off frequency
11 tfc = t*pi/2
12
13 printf("\n\n Result \n\n")
14 printf("\n time delay is %.2E sec ",t)
15 printf("\ntime delay at the cut-off frequency is %.2
    E sec",tfc)

```

---

### Scilab code Exa 42.13 Example 13

```
1 //Problem 42.13: A filter network comprising n
   identical sections passes signals of all
   frequencies up to 500 kHz and provides a total
   delay of 9.55 s . If the nominal impedance of
   the circuit into which the filter is inserted is
   1 kohm, determine (a) the values of the elements
   in each section , and (b) the value of n.
2
3 //initializing the variables:
4 fc = 500000; // in Hz
5 t1 = 9.55E-6; // in secs
6 R0 = 1000; // in ohm
7
8 //calculation:
9 //for a low-pass filter section , capacitance
10 C = 1/(%pi*R0*fc)
11 //inductance
12 L = R0/(%pi*fc)
13 //time delay
14 t2 = (L*C)^0.5
15 //number of cascaded sections required
16 n = t1/t2
17
18 printf("\n\n Result \n\n")
19 printf("\n for low-pass T section inductance is %.2E
   H and capacitance is %.2E F",L/2,C)
20 printf("\n for low-pass pi section inductance is %.2
   E H and capacitance is %.2E F",L,C/2)
21 printf("\nnumber of cascaded sections required is %
   .0 f",n)
```

---

Scilab code Exa 42.14 Example 14

```
1 //Problem 42.14: A filter network consists of 8
   sections in cascade having a nominal impedance of
   1 kohm. If the total delay time is 4 s ,
   determine the component values for each section
   if the filter is (a) a low-pass T network, and (b
   ) a high-pass pi network.
2
3 //initializing the variables:
4 n = 8; // sections in cascade
5 R0 = 1000; // in ohm
6 t1 = 4E-6; // in secs
7
8
9 //calculation:
10 //time delay
11 t2 = t1/n
12 //capacitance
13 C = t2/R0
14 //inductance
15 L = t2*R0
16
17 printf("\n\n Result \n\n")
18 printf("\n for low-pass T section inductance is %.2E
   H and capacitance is %.2E F",L/2,C)
19 printf("\n for high-pass pi section inductance is %
   .2E H and capacitance is %.2E F",2*L,C)
```

---

# Chapter 43

## Magnetically coupled circuits

Scilab code Exa 43.01 Example 1

```
1 //Problem 43.01: A and B are two coils in close
   proximity. A has 1200 turns and B has 1000 turns.
   When a current of 0.8 A flows in coil A a flux
   of 100 Wb links with coil A and 75% of this
   flux links coil B. Determine (a) the self
   inductance of coil A, and (b) the mutual
   inductance.
2
3 //initializing the variables:
4 Na = 1200;
5 Nb = 1000;
6 Ia = 0.8; // in amperes
7 Phia = 100E-6; // in Wb
8 xb = 0.75;
9
10 //calculation:
11 //self inductance of coil A
12 La = Na*Phia/Ia
13 //mutual inductance, M
14 Phib = xb*Phia
15 M = Nb*Phib/Ia
```

```
16
17 printf("\n\n Result \n\n")
18 printf("\n self inductance of coil A is %.2f H",La)
19 printf("\n mutual inductance , M is %.2E H",M)
```

---

### Scilab code Exa 43.02 Example 2

```
1 //Problem 43.02: Two circuits have a mutual
   inductance of 600 mH. A current of 5 A in the
   primary is reversed in 200 ms. Determine the e.m.
   f. induced in the secondary , assuming the current
   changes at a uniform rate.
2
3 //initializing the variables:
4 M = 600E-3; // in Henry
5 Ia = 5; // in amperes
6 dt = 0.2; // in secs
7
8 //calculation:
9 //change of current
10 dIa = 2*Ia
11 dIadt = dIa/dt
12 //secondary induced e.m.f., E2
13 E2 = -1*M*dIadt
14
15 printf("\n\n Result \n\n")
16 printf("\n secondary induced e.m.f., E2 is %.0f V",
   E2)
```

---

### Scilab code Exa 43.03 Example 3



```

1 //Problem 43.03: Two coils have self inductances of
   250 mH and 400 mH respectively. Determine the
   magnetic coupling coefficient of the pair of
   coils if their mutual inductance is 80 mH.
2
3 //initializing the variables:
4 La = 250E-3; // in Henry
5 Lb = 400E-3; // in Henry
6 M = 80E-3; // in Henry
7
8 //calculation:
9 //coupling coefficient ,
10 k = M/(La*Lb)^0.5
11
12 printf("\n\n Result \n\n")
13 printf("\n coupling coefficient , is %.3f",k)

```

---

#### Scilab code Exa 43.04 Example 4

```

1 //Problem 43.04: Two coils , X and Y, having self
   inductances of 80 mH and 60 mH respectively , are
   magnetically coupled. Coil X has 200 turns and
   coil Y has 100 turns. When a current of 4A flows
   in coil X the change of flux in coil Y is 5 mWb.
   Determine (a) the mutual inductance between the
   coils , and (b) the coefficient of coupling.
2
3 //initializing the variables:
4 Lx = 80E-3; // in Henry
5 Ly = 60E-3; // in Henry
6 Nx = 200; // turns
7 Ny = 100; // turns
8 Ix = 4; // in Amperes
9 Phiy = 0.005; // in Wb
10

```

```

11 //calculation :
12 //mutual inductance , M
13 M = Ny*Phiy/(2*Ix)
14 //coupling coefficient ,
15 k = M/(Lx*Ly)^0.5
16
17 printf("\n\n Result \n\n")
18 printf("\n mutual inductance , M is %.2E H",M)
19 printf("\n coupling coefficient , is %.3f",k)

```

---

#### Scilab code Exa 43.05 Example 5

```

1 //Problem 43.05: Two coils connected in series have
  self inductance of 40 mH and 10 mH respectively.
  The total inductance of the circuit is found to
  be 60 mH. Determine (a) the mutual inductance
  between the two coils , and (b) the coefficient of
  coupling.
2
3 //initializing the variables:
4 La = 40E-3; // in Henry
5 Lb = 10E-3; // in Henry
6 L = 60E-3; // in Henry
7
8 //calculation :
9 //mutual inductance , M
10 M = (L - La - Lb)/2
11 //coupling coefficient ,
12 k = M/(La*Lb)^0.5
13
14 printf("\n\n Result \n\n")
15 printf("\n mutual inductance , M is %.2E H",M)
16 printf("\n coupling coefficient , is %.3f",k)

```

---

**Scilab code Exa 43.06** Example 6

```
1 //Problem 43.06: Two mutually coupled coils X and Y
  are connected in series to a 240 V d.c. supply.
  Coil X has a resistance of 5 ohm and an
  inductance of 1 H. Coil Y has a resistance of 10
  ohm and an inductance of 5 H. At a certain
  instant after the circuit is connected, the
  current is 8 A and increasing at a rate of 15 A/s
  . Determine (a) the mutual inductance between the
  coils and (b) the coefficient of coupling.
2
3 //initializing the variables:
4 V = 240; // in Volts
5 Ra = 5; // in Ohm
6 La = 1; // in Henry
7 Rb = 10; // in Ohm
8 Lb = 5; // in Henry
9 I = 8; // in amperes
10 dIdt = 15; // in A/sec
11
12 //calculation:
13 //Kirchhoff s voltage law
14 L = (V - I*(Ra + Rb))/dIdt
15 //mutual inductance , M
16 M = (L - La - Lb)/2
17 //coupling coefficient ,
18 k = M/(La*Lb)^0.5
19
20 printf("\n\n Result \n\n")
21 printf("\n mutual inductance , M is %.0f H",M)
22 printf("\n coupling coefficient , is %.3f",k)
```

---

### Scilab code Exa 43.07 Example 7

```
1 //Problem 43.07: Two coils are connected in series
   and their effective inductance is found to be 15
   mH. When the connection to one coil is reversed ,
   the effective inductance is found to be 10 mH. If
   the coefficient of coupling is 0.7, determine (a
   ) the self inductance of each coil , and (b) the
   mutual inductance .
2
3 //initializing the variables :
4 k = 0.7; // coefficient of coupling
5 L1 = 15E-3; // in Henry
6 L2 = 10E-3; // in Henry
7
8 //calculation :
9 //L1 = La + Lb + 2*k*(La*Lb)^0.5
10 //L2 = La + Lb - 2*k*(La*Lb)^0.5
11 //self inductance of coils
12 a = ((L1 - (L1 + L2)/2)/(2*k))^2
13 La1 =((L1 + L2)/2 + (((L1 + L2)/2)^2 - 4*a)^0.5)/2
14 La2 =((L1 + L2)/2 - (((L1 + L2)/2)^2 - 4*a)^0.5)/2
15 Lb1 = (L1 + L2)/2 - La1
16 Lb2 = (L1 + L2)/2 - La2
17 //mutual inductance , M
18 M = (L1 - L2)/4
19
20 printf("\n\n Result \n\n")
21 printf("\nself inductance of coils are %.2E H and %
   .2E H",La1, Lb1)
22 printf("\n mutual inductance , M is %.2E H",M)
```

---

### Scilab code Exa 43.08 Example 8

```
1 //Problem 43.08: For the circuit shown in Figure
   43.7, determine the p.d. E2 which appears across
   the open-circuited secondary winding, given that
   E1 D 8 sin 2500t volts.
2
3 //initializing the variables:
4 E1 = 8; // in Volts
5 thetae1 = 0; // in degrees
6 w = 2500; // in rad/sec
7 R = 15; // in ohm
8 L = 5E-3; // in Henry
9 M = 0.1E-3; // in Henry
10
11 //calculation:
12 //voltage
13 E1 = E1*cos(thetae1*pi/180) + %i*E1*sin(thetae1*pi
   /180)
14 //Impedance of primary
15 Z1 = R + %i*w*L
16 //Primary current I1
17 I1 = E1/Z1
18 //E2
19 E2 = %i*w*M*I1
20
21 printf("\n\n Result \n\n")
22 printf("\nE2 is %.2f + (%.2f)i V",real(E2), imag(E2)
   )
```

---

### Scilab code Exa 43.09 Example 9

```
1 //Problem 43.09: Two coils x and y, with negligible
   resistance, have self inductances of 20 mH and 80
   mH respectively, and the coefficient of coupling
```

between them is 0.75. If a sinusoidal alternating p.d. of 5 V is applied to x, determine the magnitude of the open circuit e.m.f. induced in y.

```

2
3 //initializing the variables:
4 Lx = 20E-3; // in Henry
5 Ly = 80E-3; // in Henry
6 k = 0.75; // coupling coeff.
7 Ex = 5; // in Volts
8
9 //calculation:
10 //mutual inductance
11 M = k*(Lx*Ly)^0.5
12 //magnitude of the open circuit e.m.f. induced
13 Ey = M*Ex/Lx
14
15 printf("\n\n Result \n\n")
16 printf("\n mutual inductance is %.2f H",M)
17 printf("\n magnitude of the open circuit e.m.f.
    induced is %.2f V",Ey)

```

---

#### Scilab code Exa 43.10 Example 10

```

1 //Problem 43.10: For the circuit shown in Figure
    43.9, determine the value of the secondary
    current I2 if E1 = 2∠0 volts and the frequency
    is 1000/π Hz.
2
3 //initializing the variables:
4 E1 = 2; // in Volts
5 thetae1 = 0; // in degrees
6 f = 1000/%pi; // in Hz
7 R1 = 4; // in ohm
8 R2 = 16; // in ohm

```

```

 9 R3 = 16; // in ohm
10 R4 = 50; // in ohm
11 L = 10E-3; // in Henry
12 M = 2E-3; // in Henry
13
14 //calculation:
15 w = 2*%pi*f
16 //voltage
17 E1 = E1*cos(thetae1*%pi/180) + %i*E1*sin(thetae1*%pi
    /180)
18 //R1e is the real part of Z1e
19 R1e = R1 + R2 + ((R3 + R4)*(M^2)*(w^2))/((R3 + R4)^2
    + (w*L)^2)
20 //X1e is the imaginary part of Z1e
21 X1e = w*L - (L*(M^2)*(w^3))/((R3 + R4)^2 + (w*L)^2)
22 Z1e = R1e + %i*X1e
23 Z2e = R3 + R4 + %i*w*L
24 //primary current, I1
25 I1 = E1/Z1e
26 //E2
27 E2 = %i*w*M*I1
28 //secondary current I2
29 I2 = E2/Z2e
30
31 printf("\n\n Result \n\n")
32 printf("\n secondary current I2 is %.2E +(%.2E)i A",
    real(I2), imag(I2))

```

---

### Scilab code Exa 43.11 Example 11

```

1 //Problem 43.11: For the coupled circuit shown in
    Figure 43.10, calculate (a) the self impedance of
    the primary circuit, (b) the self impedance of
    the secondary circuit, (c) the impedance
    reflected into the primary circuit, (d) the

```

```

    effective primary impedance, (e) the primary
    current, and (f) the secondary current
2
3 //initializing the variables:
4 E1 = 50; // in Volts
5 thetae1 = 0; // in degrees
6 w = 500; // in rad/sec
7 R1 = 300; // in ohm
8 L1 = 0.2; // in Henry
9 L2 = 0.5; // in Henry
10 L3 = 0.3; // in Henry
11 R2 = 500; // in ohm
12 C = 5E-6; // in farad
13 M = 0.2; // in Henry
14
15 //calculation:
16 //voltage
17 E1 = E1*cos(thetae1*pi/180) + %i*E1*sin(thetae1*pi
    /180)
18 // Self impedance of primary circuit
19 Z1 = R1 + %i*w*(L1 + L2)
20 //Self impedance of secondary circuit ,
21 Z2 = R2 + %i*(w*L3 - 1/(w*C))
22 //reflected impedance, Zr
23 Zr = (w*M)^2/Z2
24 //Effective primary impedance,
25 Z1e = Z1 + Zr
26 //Primary current I1
27 I1 = E1/Z1e
28 //Secondary current I2
29 E2 = %i*w*M*I1
30 I2 = E2/Z2
31
32 printf("\n\n Result \n\n")
33 printf("\n Self impedance of primary circuit , Z1 is
    %.0f + (%.0f)i ohm",real(Z1), imag(Z1))
34 printf("\n Self impedance of secondary circuit , Z2
    is %.0f + (%.0f)i ohm",real(Z2), imag(Z2))

```



```

35 printf("\n reflected impedance, Zr is %.0f +(%0.0f)i
    ohm",real(Zr), imag(Zr))
36 printf("\n Effective primary impedance Z1(eff) is %
    .0f +(%0.0f)i ohm",real(Z1e), imag(Z1e))
37 printf("\n primary current I1 is %.2f +(%0.2f)i A",
    real(I1), imag(I1))
38 printf("\n secondary current I2 is %.2f +(%0.2f)i A",
    real(I2), imag(I2))

```

---

### Scilab code Exa 43.12 Example 12

```

1 //Problem 43.12:For the circuit shown in Figure
    43.12 each winding is tuned to resonate at the
    same frequency. Determine (a) the reso-nant
    frequency, (b) the value of capacitor C2 , (c)
    the effective primary impedance, (d) the primary
    current, (e) the voltage across capacitor C2 and
    (f) the coefficient of coupling.
2
3 //initializing the variables:
4 E1 = 20; // in Volts
5 thetai1 = 0; // in degrees
6 R1 = 15; // in ohm
7 C1 = 400E-12; // in farad
8 R2 = 30; // in ohm
9 L1 = 0.001; // in Henry
10 L2 = 0.0002; // in Henry
11 R3 = 50; // in ohm
12 M = 10E-6; // in Henry
13
14 //calculation:
15 //voltage
16 E1 = E1*cos(thetai1*%pi/180) + %i*E1*sin(thetai1*%pi
    /180)
17 //the resonant frequency, fr

```

```

18 fr = 1/(2*pi*(L1*C1)^0.5)
19 w = 2*pi*fr
20 //The secondary is also tuned to a resonant
    frequency
21 //capacitance ,C2
22 C2 = 1/(L2*(2*pi*fr)^2)
23 //the effective primary impedance Z1eff
24 Z1e = R1 + R2 + ((w*M)^2)/R3
25 //Primary current I1
26 I1 = E1/Z1e
27 //Secondary current I2
28 E2 = %i*w*M*I1
29 I2 = E2/R3
30 //voltage across capacitor C2
31 Vc2 = I2*-1*i/(w*C2)
32 //coefficient of coupling , k
33 k = M/(L1*L2)^0.5
34
35 printf("\n\n Result \n\n")
36 printf("\n the resonant frequency ,fr is %.0f Hz",fr)
37 printf("\n capacitance ,C2 is %.2E F",C2)
38 printf("\n Effective primary impedance Z1(eff) is %
    .0f +(%0f)i ohm",real(Z1e), imag(Z1e))
39 printf("\n primary current I1 is %.2f +(%0.2f)i A",
    real(I1), imag(I1))
40 printf("\n voltage across capacitor C2 is %.0f +(%0.0
    f)i V",real(Vc2), imag(Vc2))
41 printf("\n coefficient of coupling , k is %.4f",k)

```

---

### Scilab code Exa 43.13 Example 13

```

1 //Problem 43.13:For the coupled circuit shown in
    Figure 43.16, determine the values of currents
    I1 and I2.
2

```

```

3 //initializing the variables:
4 E1 = 250; // in Volts
5 thetae1 = 0; // in degrees
6 R1 = %i*50; // in ohm
7 R2 = 10; // in ohm
8 R3 = 10; // in ohm
9 R4 = %i*50; // in ohm
10 R5 = 50; // in ohm
11 M = %i*10; // in ohm
12
13 //calculation:
14 //voltage
15 E1 = E1*cos(thetae1*%pi/180) + %i*E1*sin(thetae1*%pi
    /180)
16 //Applying Kirchhoff s voltage law to the primary
    circuit gives
17 //(R1 + R2)*I1 - M*I2 = E1
18 //Applying Kirchhoff s voltage law to the
    secondary circuit gives
19 //-1*M*I1 + ( R3 + R4 + R5)*I2 = 0
20 //solving these two
21 I2 = E1/((R1 + R2)*(R3 + R4 + R5)/(M) + (-1*M))
22 I1 = I2*(R3 + R4 + R5)/(M)
23
24 printf("\n\n Result \n\n")
25 printf("\n primary current I1 is %.2f +(%i.2f)i A",
    real(I1), imag(I1))
26 printf("\n secondary current I2 is %.2f +(%i.2f)i A",
    real(I2), imag(I2))

```

---

#### Scilab code Exa 43.14 Example 14

```

1 //Problem 43.14:The circuit diagram of an air-cored
    transformer winding is shown in Figure 43.17. The
    coefficient of coupling between primary and

```

secondary windings is 0.70. Determine for the circuit (a) the mutual inductance M, (b) the primary current I1 and (c) the secondary terminal p.d.

```

2
3 //initializing the variables:
4 re = 40; // in Volts
5 thetae1 = 0; // in degrees
6 R1 = 5; // in ohm
7 L1 = 0.001; // in Henry
8 L2 = 0.006; // in Henry
9 R2 = 40; // in ohm
10 rzl = 200; // in ohm
11 thetazl = -60; // in degrees
12 k = 0.70
13 f = 20000; // in Hz
14
15 //calculation:
16 w = 2*%pi*f
17 //voltage
18 E1 = re*cos(thetae1*%pi/180) + %i*re*sin(thetae1*%pi
    /180)
19 //impedance
20 ZL = rzl*cos(thetazl*%pi/180) + %i*rzl*sin(thetazl*
    %pi/180)
21 //mutual inductance , M
22 M = k*(L1*L2)^0.5
23 //Applying Kirchhoff s voltage law to the primary
    circuit gives
24 //(R1 + %i*w*L1)*I1 - %i*w*M*I2 = E1
25 //Applying Kirchhoff s voltage law to the
    secondary circuit gives
26 //-1*%i*w*M*I1 + ( R2 + ZL + %i*w*L2)*I2 = 0
27 //solving these two
28 I1 = E1/((R1 +%i*w*L1) - (%i*w*M)^2/(R2 + ZL + %i*w*
    L2))
29 //secondary terminal p.d.
30 pd = I2*ZL

```

```

31
32 printf("\n\n Result \n\n")
33 printf("\n mutual induction M is %.2E H",M)
34 printf("\n primary current I1 is %.2f +(%.2f)i A",
    real(I1), imag(I1))
35 printf("\n secondary terminal p.d. is %.2f +(%.2f)i
    V",real(pd), imag(pd))

```

---

### Scilab code Exa 43.15 Example 15

```

1 //Problem 43.15:A mutual inductor is used to couple
  a 20 ohm resistive load to a 50/_0 V generator
  as shown in Figure 43.18. The generator has an
  internal resistance of 5 ohm and the mutual
  inductor parameters are R1 = 20 ohm , L1 = 0.2 H,
  R2 = 25 ohm , L2 = 0.4 H and M = 0.1 H. The
  supply frequency is 75/pi Hz. Determine (a) the
  generator current I1 and (b) the load current I2
  .
2
3 //initializing the variables:
4 E1 = 50; // in Volts
5 thetae1 = 0; // in degrees
6 r = 5; // in ohm
7 R1 = 20; // in ohm
8 L1 = 0.2; // in Henry
9 L2 = 0.4; // in Henry
10 R2 = 25; // in ohm
11 RL = 20; // in ohm
12 M = 0.1; // in Henry
13 f = 75/%pi; // in Hz
14
15 //calculation:
16 w = 2*%pi*f
17 //voltage

```

```

18 E1 = E1*cos(thetae1*pi/180) + %i*E1*sin(thetae1*pi
    /180)
19 //Applying Kirchhoff s voltage law to the primary
    circuit gives
20 //(r + R1 + %i*w*L1)*I1 - %i*w*M*I2 = E1
21 //Applying Kirchhoff s voltage law to the
    secondary circuit gives
22 //-1*%i*w*M*I1 + ( R2 + RL + %i*w*L2)*I2 = 0
23 //solving these two
24 I2 = E1/((r + R1 + %i*w*L1)*(R2 + RL + %i*w*L2)/(%i*
    w*M) + (-1*%i*w*M))
25 I1 = I2*(R2 + RL + %i*w*L2)/(%i*w*M)
26
27 printf("\n\n Result \n\n")
28 printf("\n primary current I1 is %.2f +(%0.2f)i A",
    real(I1), imag(I1))
29 printf("\n load current I2 is %.2f +(%0.2f)i A",real(
    I2), imag(I2))

```

---

### Scilab code Exa 43.16 Example 16

```

1 //Problem 43.16:The mutual inductor of problem 43.15
    is connected to the circuit of Figure 43.19.
    Determine the source and load currents for (a)
    the windings as shown (i.e. with the dots
    adjacent), and (b) with one winding reversed (i.e
    . with the dots at opposite ends).
2
3 //initializing the variables:
4 E1 = 50; // in Volts
5 thetae1 = 0; // in degrees
6 r = 5; // in ohm
7 R1 = 20; // in ohm
8 L1 = 0.2; // in Henry
9 R = 8; // in ohm

```

```

10 L = 0.1; // in Henry
11 L2 = 0.4; // in Henry
12 R2 = 25; // in ohm
13 RL = 20; // in ohm
14 M = 0.1; // in Henry
15 f = 75/%pi; // in Hz
16
17 // calculation :
18 w = 2*%pi*f
19 // voltage
20 E1 = E1*cos(thetae1*%pi/180) + %i*E1*sin(thetae1*%pi
    /180)
21 //Applying Kirchhoff s voltage law to the primary
    circuit gives
22 //(r + R1 + %i*w*L1 + R + %i*w*L)*I1 - (%i*w*M + R +
    %i*w*L)*I2 = E1
23 //Applying Kirchhoff s voltage law to the
    secondary circuit gives
24 //-1*(%i*w*M + R + %i*w*L)*I1 + (R2 + RL + %i*w*L2 +
    R + %i*w*L)*I2 = 0
25 //solving these two
26 I2 = E1/((r + R1 + %i*w*L1 + R + %i*w*L)*(R2 + RL +
    %i*w*L2 + R + %i*w*L)/((%i*w*M + R + %i*w*L)) +
    (-1*(%i*w*M + R + %i*w*L)))
27 I1 = I2*(R2 + RL + %i*w*L2 + R + %i*w*L)/(%i*w*M + R
    + %i*w*L)
28 //reversing
29 //Applying Kirchhoff s voltage law to the primary
    circuit gives
30 //(r + R1 + %i*w*L1 + R + %i*w*L)*I1r - (-1*%i*w*M +
    R + %i*w*L)*I2r = E1
31 //Applying Kirchhoff s voltage law to the
    secondary circuit gives
32 //-1*(-1*%i*w*M + R + %i*w*L)*I1r + (R2 + RL + %i*w*
    L2 + R + %i*w*L)*I2r = 0
33 //solving these two
34 I2r = E1/((r + R1 + %i*w*L1 + R + %i*w*L)*(R2 + RL +
    %i*w*L2 + R + %i*w*L)/((-1*%i*w*M + R + %i*w*L))

```

```

    + (-1*(-1*i*w*M + R + %i*w*L))
35 I1r = I2r*(R2 + RL + %i*w*L2 + R + %i*w*L)/((-1*i*w
    *M + R + %i*w*L))
36
37 printf("\n\n Result \n\n")
38 printf("\n primary current I1 is %.2f +(%.2f)i A",
    real(I1), imag(I1))
39 printf("\n load current I2 is %.2f +(%.2f)i A",real(
    I2), imag(I2))
40 printf("\n reversed primary current I1r is %.2f +(%.
    2f)i A",real(I1r), imag(I1r))
41 printf("\n reversed load current I2r is %.2f +(%0.2f)
    i A",real(I2r), imag(I2r))

```

---



# Chapter 44

## Transmission lines

Scilab code Exa 44.01 Example 1

```
1 //Problem 44.01:A parallel-wire air-spaced
   transmission line operating at 1910 Hz has a
   phase shift of 0.05 rad/km. Determine (a) the
   wavelength on the line , and (b) the speed of
   transmission of a signal.
2
3 //initializing the variables:
4 f = 1910; // in Hz
5 b = 0.05; // in rad/km
6
7 //calculation:
8 w = 2*pi*f
9 //wavelength
10 Y = 2*pi/b
11 //speed of transmission
12 u = f*Y
13
14 printf("\n\n Result \n\n")
15 printf("\n wavelength Y is %.1f km",Y)
16 printf("\n speed of transmission %.2E km/sec",u)
```

---

### Scilab code Exa 44.02 Example 2

```
1 //Problem 44.02:A transmission line has an
   inductance of 4 mH/loop km and a capacitance of
   0.004 F /km. Determine, for a frequency of
   operation of 1 kHz, (a) the phase delay, (b) the
   wavelength on the line , and (c) the velocity of
   propagation (in metres per second) of the signal.
2
3 //initializing the variables:
4 L = 0.004; // in Henry/loop
5 C = 0.004E-6; // in F/loop
6 f = 1000; // in Hz
7
8 //calculation:
9 w = 2*%pi*f
10 //phase delay
11 b = w*(L*C)^0.5
12 //wavelength
13 Y = 2*%pi/b
14 //speed of transmission
15 u = f*Y
16
17 printf("\n\n Result \n\n")
18 printf("\n phase delay is %.3f rad/km",b)
19 printf("\n wavelength Y is %.1f km",Y)
20 printf("\n speed of transmission %.2E km/sec",u)
```

---

### Scilab code Exa 44.03 Example 3

```
1 //Problem 44.03: When operating at a frequency of 2
   kHz, a cable has an attenuation of 0.25 Np/km and
```

a phase shift of 0.20 rad/km. If a 5 V rms signal is applied at the sending end, determine the voltage at a point 10 km down the line, assuming that the termination is equal to the characteristic impedance of the line.

```

2
3 //initializing the variables:
4 a = 0.25; // in Np/km
5 b = 0.20; // in rad/km
6 Vs = 5; // in Volts
7 n = 10; // in km
8 f = 2000; // in Hz
9
10 //calculation:
11 w = 2*%pi*f
12 //the voltage 10 km down the line
13 r = a + %i*b
14 VR = Vs*%e^(-1*n*r)
15
16 printf("\n\n Result \n\n")
17 printf("\n the voltage 10 km down the line is %.2f
    +(%i A",real(VR), imag(VR))

```

---

#### Scilab code Exa 44.04 Example 4

```

1 //Problem 44.04: A transmission line 5 km long has a
    characteristic impedance of  $800\sqrt{-25}$  ohm. At a
    particular frequency, the attenuation
    coefficient of the line is 0.5 Np/km and the
    phase shift coefficient is 0.25 rad/km. Determine
    the magnitude and phase of the current at the
    receiving end, if the sending end voltage is  $2.0\sqrt{-0}$ 
    V r.m.s.
2
3 //initializing the variables:

```

```

4 a = 0.5; // in Np/km
5 b = 0.25; // in rad/km
6 rvs = 2; // in Volts
7 thetavs = 0; // in degrees
8 rzo = 800; // in ohm
9 thetazo = -25; // in degrees
10 n = 5; // in km
11
12 //calculation:
13 //voltage
14 Vs = rvs*cos(thetavs*%pi/180) + %i*rvs*sin(thetavs*
    %pi/180)
15 //characteristic impedance
16 Zo = rzo*cos(thetazo*%pi/180) + %i*rzo*sin(thetazo*
    %pi/180)
17 // receiving end voltage
18 r = a + %i*b
19 VR = Vs*%e^(-1*n*r)
20 //Receiving end current ,
21 IR = VR/Zo
22
23 printf("\n\n Result \n\n")
24 printf("\n Receiving end current , IR is %.2E +(%i.2E)
    i A",real(IR), imag(IR))

```

---

#### Scilab code Exa 44.05 Example 5

```

1 //Problem 44.05: The voltages at the input and at
    the output of a transmission line properly
    terminated in its characteristic impedance are
    8.0 V and 2.0 V rms respectively. Determine the
    output voltage if the length of the line is
    doubled.
2
3 //initializing the variables:

```

```

4 Vs = 8; // in Volts
5 VR = 2; // in Volts
6 x = 2;
7
8 //calculation:
9 // receiving end voltage VR = Vs*e^(-nr)
10 //e^-nr = p
11 p = VR/Vs
12 //If the line is doubled in length, then
13 VR = Vs*(p)^2
14
15 printf("\n\n Result \n\n")
16 printf("\n Receiving end voltage If the line is
    doubled in length, VR is %.2f +(%i.2f)i V",real(VR
    ), imag(VR))

```

---

#### Scilab code Exa 44.06 Example 6

```

1 //Problem 44.06: At a frequency of 1.5 kHz the open-
    circuit impedance of a length of transmission
    line is 800/_-50 ohm and the short-circuit
    impedance is 413/_-20 ohm. Determine the
    characteristic impedance of the line at this
    frequency.
2
3 //initializing the variables:
4 rzoc = 800; // in ohm
5 thetazoc = -50; // in degrees
6 rzsc = 413; // in ohm
7 thetazsc = -20; // in degrees
8 f = 1500; // in Hz
9
10 //calculation:
11 //open circuit impedance
12 Zoc = rzoc*cos(thetazoc*pi/180) + %i*rzoc*sin(

```

```

    thetazoc*%pi/180)
13 //short circuit impedance
14 Zsc = rzsc*cos(thetazsc*%pi/180) + %i*rzsc*sin(
    thetazsc*%pi/180)
15 //characteristic impedance Zo
16 Zo = (Zoc*Zsc)^0.5
17
18 printf("\n\n Result \n\n")
19 printf("\n characteristic impedance Zo is %.0f +(%0.0
    f)i ohm",real(Zo), imag(Zo))

```

---

#### Scilab code Exa 44.07 Example 7

```

1 //Problem 44.07: A transmission line has the
    following primary constants: resistance R = 15
    ohm/loop km, inductance L = 3.4 mH/loop km,
    conductance G = 3 S/km and capacitance C = 10
    nF/km. Determine the characteristic impedance of
    the line when the frequency is 2 kHz.
2
3 //initializing the variables:
4 R = 15; // in ohm/loop km
5 L = 0.0034; // in H/loop km
6 C = 10E-9; // in F/km
7 G = 3E-6; // in S/km
8 f = 2000; // in Hz
9
10 //calculation:
11 w = 2*%pi*f
12 //characteristic impedance Zo
13 Zo = ((R + %i*w*L)/(G + %i*w*C))^0.5
14
15 printf("\n\n Result \n\n")
16 printf("\n characteristic impedance Zo is %.1f +(%0.1
    f)i ohm",real(Zo), imag(Zo))

```

---

**Scilab code Exa 44.08** Example 8

```
1 //Problem 44.08: A transmission line having
   negligible losses has primary line constants of
   inductance  $L = 0.5$  mH/loop km and capacitance  $C =$ 
    $0.12$  F/km. Determine, at an operating
   frequency of  $400$  kHz, (a) the characteristic
   impedance, (b) the propagation coefficient, (c)
   the wavelength on the line, and (d) the velocity
   of propagation, in metres per second, of a signal
   .
2
3 //initializing the variables:
4 L = 0.0005; // in H/loop km
5 C = 0.12E-6; // in F/km
6 f = 400000; // in Hz
7
8 //calculation:
9 w = 2*%pi*f
10 //characteristic impedance Zo
11 Zo = (L/C)^0.5
12 //the propagation coefficient
13 r = %i*w*(L*C)^0.5
14 //the attenuation coefficient
15 a = real(r)
16 //the phaseshift coefficient
17 b = imag(r)
18 //wavelength
19 Y = 2*%pi/b
20 //velocity of propagation
21 u = f*Y
22
23 printf("\n\n Result \n\n")
24 printf("\n characteristic impedance Zo is %.1f +(%1
```

```

    f)i ohm",real(Zo), imag(Zo))
25 printf("\n propagation coefficient is %.2f +(%i.2f)i"
    ,a,b)
26 printf("\n wavelength Y is %.3f km",Y)
27 printf("\n speed of transmission %.2E km/sec",u)

```

---

#### Scilab code Exa 44.09 Example 9

```

1 //Problem 44.09: At a frequency of 1 kHz the primary
    constants of a transmission line are resistance
    R = 25 ohm/loop km, inductance L = 5 mH/loop km,
    capacitance C = 0.04 F/km and conductance G =
    80 S/km. Determine for the line (a) the
    characteristic impedance, (b) the propagation
    coefficient, (c) the attenuation coefficient and
    (d) the phase-shift coefficient.
2
3 //initializing the variables:
4 R = 25; // in ohm/loop km
5 L = 0.005; // in H/loop km
6 C = 0.04E-6; // in F/km
7 G = 80E-6; // in S/km
8 f = 1000; // in Hz
9
10 //calculation:
11 w = 2*%pi*f
12 //characteristic impedance Zo
13 Zo = ((R + %i*w*L)/(G + %i*w*C))^0.5
14 //the propagation coefficient
15 r =((R + %i*w*L)*(G + %i*w*C))^0.5
16 //the attenuation coefficient
17 a = real(r)
18 //the phaseshift coefficient
19 b = imag(r)
20

```



```

21 printf("\n\n Result \n\n")
22 printf("\n characteristic impedance Zo is %.1f +(%0.1
    f)i ohm",real(Zo), imag(Zo))
23 printf("\n propagation coefficient is %.4f +(%0.4f)i"
    ,a,b)
24 printf("\n attenuation coefficient is %.4f Np/km",a)
25 printf("\n the phaseshift coefficient %.4f rad/km",b
    )

```

---

#### Scilab code Exa 44.10 Example 10

```

1 //Problem 44.10: An open wire line is 300 km long
    and is terminated in its characteristic impedance
    . At the sending end is a generator having an
    open-circuit e.m.f. of 10.0 V, an internal
    impedance of  $(400 + j0)$  ohmand a frequency of 1
    kHz. If the line primary constants are  $R = 8$  ohm/
    loop km,  $L = 3$  mH/loop km,  $C = 7500$  pF/km and  $G =$ 
    0.25 S /km, determine (a) the characteristic
    impedance, (b) the propagation coefficient, (c)
    the attenuation and phase-shift coefficients, (d)
    the sending-end current, (e) the receiving-end
    current, (f) the wavelength on the line, and (g)
    the speed of transmission of signal.
2
3 //initializing the variables:
4 R = 8; // in ohm/loop km
5 L = 0.003; // in H/loop km
6 C = 7500E-12; // in F/km
7 G = 0.25E-6; // in S/km
8 f = 1000; // in Hz
9 n = 300; // in km
10 Zg = 400 + %i*0; // in ohm
11 Vg = 10; // in Volts
12

```

```

13 //calculation :
14 w = 2*%pi*f
15 //characteristic impedance Zo
16 Zo = ((R + %i*w*L)/(G + %i*w*C))^0.5
17 //the propagation coefficient
18 r = ((R + %i*w*L)*(G + %i*w*C))^0.5
19 //the attenuation coefficient
20 a = real(r)
21 //the phaseshift coefficient
22 b = imag(r)
23 //the sending-end current ,
24 Is = Vg/(Zg + Zo)
25 //the receiving-end current ,
26 IR = Is*%e^(-1*n*r)
27 //wavelength
28 Y = 2*%pi/b
29 //velocity of propagation
30 u = f*Y
31
32 printf("\n\n Result \n\n")
33 printf("\n characteristic impedance Zo is %.1f +(%.1
    f)i ohm",real(Zo), imag(Zo))
34 printf("\n propagation coefficient is %.2f +(%.2f)i"
    ,a,b)
35 printf("\n attenuation coefficient is %.4f Np/km and
    the phaseshift coefficient %.4f rad/km",a,b)
36 printf("\n sending-end current Is is %.3E +(%.3E)i A
    ",real(Is), imag(Is))
37 printf("\n receiving-end current IR is %.3E +(%.3E)i
    A",real(IR), imag(IR))
38 printf("\n wavelength Y is %.3f km",Y)
39 printf("\n speed of transmission %.2E km/sec",u)

```

---

Scilab code Exa 44.11 Example 11

```

1 //Problem 44.11: An underground cable has the
  following primary constants: resistance R = 10
  ohm/loop km, inductance L = 1.5 mH/loop km,
  conductance G = 1.2 S/km and capacitance C =
  0.06 F/km. Determine by how much the inductance
  should be increased to satisfy the condition for
  minimum distortion.
2
3 //initializing the variables:
4 R = 10; // in ohm/loop km
5 L = 0.0015; // in H/loop km
6 C = 0.06E-6; // in F/km
7 G = 1.2E-6; // in S/km
8
9 //calculation:
10 //the condition for minimum distortion is given by
    LG = CR, from which,
11 Lm = C*R/G
12 dL = Lm - L
13
14 printf("\n\n Result \n\n")
15 printf("\n inductance should be increased by %.2E H/
    loop km for minimum distortion",dL)

```

---

**Scilab code Exa 44.12** Example 12

```

1 //Problem 44.12: A cable has the following primary
  constants: resistance R = 80 ohm/loop km,
  conductance, G = 2 S/km, and capacitance C = 5
  nF/km. Determine, for minimum distortion at a
  frequency of 1.5 kHz (a) the value of inductance
  per loop kilometre required, (b) the propagation
  coefficient, (c) the velocity of propagation of
  signal, and (d) the wavelength on the line
2

```

```

3 //initializing the variables:
4 R = 80; // in ohm/loop km
5 C = 5E-9; // in F/km
6 G = 2E-6; // in S/km
7 f = 1500; // in Hz
8
9 //calculation:
10 w = 2*%pi*f
11 //the condition for minimum distortion is given by
    LG = CR, from which, inductance
12 L = C*R/G
13 //attenuation coefficient ,
14 a = (R*G)^0.5
15 //phase shift coefficient ,
16 b = w*(L*C)^0.5
17 //propagation coefficient ,
18 r = a + %i*b
19 //velocity of propagation ,
20 u = 1/(L*C)^0.5
21 //wavelength
22 Y = u/f
23
24 printf("\n\n Result \n\n")
25 printf("\n inductance is %.2f H",L)
26 printf("\n propagation coefficient is %.4f +(%0.4f)i"
    ,a,b)
27 printf("\n wavelength Y is %.2f km",Y)
28 printf("\n speed of transmission %.2E km/sec",u)

```

---

### Scilab code Exa 44.13 Example 13

```

1 //Problem 44.13: A cable which has a characteristic
    impedance of 75 ohm is terminated in a 250 ohm
    resistive load. Assuming that the cable has
    negligible losses and the voltage measured across

```

the terminating load is 10 V, calculate the value of (a) the reflection coefficient for the line, (b) the incident current, (c) the incident voltage, (d) the reflected current, and (e) the reflected voltage.

```

2
3 //initializing the variables:
4 Zo = 75; // in ohm
5 ZR = 250; // in ohm
6 VR = 10; // in Volts
7
8 //calculation:
9 //reflection coefficient
10 p = (Zo - ZR)/(Zo + ZR)
11 //Current flowing in the terminating load
12 IR = VR/ZR
13 //incident current, Ii
14 Ii = IR/(1 + p)
15 //incident voltage, Vi
16 Vi = Ii*Zo
17 //reflected current, Ir
18 Ir = IR - Ii
19 //reflected voltage, Vr
20 Vr = -1*Ir*Zo
21
22 printf("\n\n Result \n\n")
23 printf("\n reflection coefficient is %.3f",p)
24 printf("\n incident current, Ii is %.4f A",Ii)
25 printf("\n incident voltage, Vi is %.2f V",Vi)
26 printf("\n reflected current, Ir is %.4f A",Ir)
27 printf("\n reflected voltage, Vr is %.2f V",Vr)

```

---

#### Scilab code Exa 44.14 Example 14

```

1 //Problem 44.14: A long transmission line has a

```

characteristic impedance of  $500 - j40$  ohm and is terminated in an impedance of (a)  $500 + j40$  ohm and (b)  $600 + j20$  ohm. Determine the magnitude of the reflection coefficient in each case.

```

2
3 //initializing the variables:
4 Zo = 500 - %i*40; // in ohm
5 ZR1 = 500 + %i*40; // in ohm
6 ZR2 = 600 + %i*20; // in ohm
7
8 //calculation:
9 //reflection coefficient
10 p1 = (Zo - ZR1)/(Zo + ZR1)
11 p2 = (Zo - ZR2)/(Zo + ZR2)
12 p1mag = (real(p1)^2 + imag(p1)^2)^0.5
13 p2mag = (real(p2)^2 + imag(p2)^2)^0.5
14
15 printf("\n\n Result \n\n")
16 printf("\n reflection coefficient (a)%.3f and (b)%.3
    f",p1mag, p2mag)

```

---

#### Scilab code Exa 44.15 Example 15

```

1 //Problem 44.15: A loss-free transmission line has a
    characteristic impedance of 500/_0 and is
    connected to an aerial of impedance 320 + j240
    ohm. Determine (a) the magnitude of the ratio of
    the reflected to the incident voltage wave, and (
    b) the incident voltage if the reflected voltage
    is 20/_35 V
2
3 //initializing the variables:
4 rzo = 500; // in ohm
5 thetazo = 0; // in degrees
6 ZR = 320 + %i*240; // in ohm

```

```

7 rvr = 20; // in volts
8 thetavr = 35; // in degrees
9
10 //calculation:
11 //voltage
12 VR = rvr*cos(thetavr*pi/180) + %i*rvr*sin(thetavr*
    %pi/180)
13 //characteristic impedance
14 Zo = rzo*cos(thetazo*pi/180) + %i*rzo*sin(thetazo*
    %pi/180)
15 //the ratio of the reflected to the incident voltage
16 //vr = VR/Vi
17 vr = (ZR - Zo)/(Zo + ZR)
18 vrmag = (real(vr)^2 + imag(vr)^2)^0.5
19 //incident voltage, Vi
20 Vi = VR/vr
21
22 printf("\n\n Result \n\n")
23 printf("\n the magnitude of the ratio Vr : Vi is %.3
    f",vrmag)
24 printf("\n incident voltage, Vi is %.2f +(%i.2f)i V",
    real(Vi), imag(Vi))

```

---

#### Scilab code Exa 44.16 Example 16

```

1 //Problem 44.16: A transmission line has a
    characteristic impedance of 600/_0 and
    negligible loss. If the terminating impedance of
    the line is 400 + j250 ohm, determine (a) the
    reflection coefficient and (b) the standing-wave
    ratio.
2
3 //initializing the variables:
4 rzo = 600; // in ohm
5 thetazo = 0; // in degrees

```

```

6 ZR = 400 + %i*250; // in ohm
7
8 //calculation:
9 //characteristic impedance
10 Zo = rzo*cos(thetazo*%pi/180) + %i*rzo*sin(thetazo*
    %pi/180)
11 //reflection coefficient
12 p = (Zo - ZR)/(Zo + ZR)
13 pmag = (real(p)^2 + imag(p)^2)^0.5
14 //standing-wave ratio,
15 s = (1 + pmag)/(1 - pmag)
16
17 printf("\n\n Result \n\n")
18 printf("\n reflection coefficient , is %.4f +(%i.4f)i
    V",real(p), imag(p))
19 printf("\n standing-wave ratio , s is %.3f",s)

```

---

#### Scilab code Exa 44.17 Example 17

```

1 //Problem 44.17: A low-loss transmission line has a
    mismatched load such that the reflection
    coefficient at the termination is  $0.2/\angle -120^\circ$ .
    The characteristic impedance of the line is 80
    ohm. Calculate (a) the standing-wave ratio, (b)
    the load impedance, and (c) the incident current
    flowing if the reflected current is 10 mA.
2
3 //initializing the variables:
4 rp = 0.2;
5 thetap = -120; // in degrees
6 Zo = 80; // in ohm
7 Ir = 0.01; // in Amperes
8
9 //calculation:
10 //reflection coefficient

```



```

11 p = rp*cos(thetap*pi/180) + %i*rp*sin(thetap*pi
    /180)
12 //standing-wave ratio ,
13 s = (1 + rp)/(1 - rp)
14 //load impedance ZR
15 ZR = Zo*(1 - p)/(1 + p)
16 //incident current
17 Ii = Ir*(s + 1)/(s - 1)
18
19 printf("\n\n Result \n\n")
20 printf("\n standing-wave ratio , s is %.1f",s)
21 printf("\n load impedance ZR is %.2f +(%0.2f)i ohm",
    real(ZR), imag(ZR))
22 printf("\n incident current is %.3f A",Ii)

```

---

#### Scilab code Exa 44.18 Example 18

```

1 //Problem 44.18: The standing-wave ratio on a
    mismatched line is calculated as 1.60. If the
    incident power arriving at the termination is 200
    mW, determine the value of the reflected power.
2
3 //initializing the variables:
4 s = 1.6;
5 Pi = 0.2; // in Watts
6
7 //calculation:
8 //reflected power, Pr
9 Pr = Pi*((s - 1)/(s + 1))^2
10
11 printf("\n\n Result \n\n")
12 printf("\n reflected power, Pr is %.5f W",Pr)

```

---

# Chapter 45

## Transients and Laplace transforms

Scilab code Exa 45.01 Example 1

```
1 //Problem 45.01: A 500 nF capacitor is connected in
   series with a 100 kohm resistor and the circuit
   is connected to a 50 V, d.c. supply. Calculate (a
   ) the initial value of current flowing, (b) the
   value of current 150 ms after connection, (c) the
   value of capacitor voltage 80 ms after
   connection, and (d) the time after connection
   when the resistor voltage is 35 V.
2
3 //initializing the variables:
4 C = 500E-9; // in Farad
5 R = 100000; // in Ohm
6 V = 50; // in VOLts
7 ti = 0.15; // in sec
8 tc = 0.08; // in sec
9 Vrt = 35; // in Volts
10
11 //calculation:
12 //Initial current,
```

```

13 i0 = (V/R)
14 //when time t = 150ms current is
15 i150 = (V/R)*%e^(-1*ti/(R*C))
16 //capacitor voltage , Vc
17 Vc = V*(1 - %e^(-1*tc/(R*C)))
18 //time , t
19 tvr = -1*R*C*log(Vrt/V)
20
21 printf("\n\n Result \n\n")
22 printf("\n initial value of current flowing is %.2E
    A",i0)
23 printf("\n current flowing at t = 150ms is %.2E A",
    i150)
24 printf("\n value of capacitor voltage at t = 80ms
    is %.2f V",Vc)
25 printf("\n the time after connection when the
    resistor voltage is 35 V is %.4f sec",tvr)

```

---

### Scilab code Exa 45.02 Example 2

```

1 //Problem 45.02: A d.c. voltage supply of 200 V is
    connected across a 5 F capacitor as shown in
    Figure 45.5. When the supply is suddenly cut by
    opening switch S, the capacitor is left isolated
    except for a parallel resistor of 2 Mohm.
    Calculate the p.d. across the capacitor after 20
    s.
2
3 //initializing the variables:
4 C = 5E-6; // in Farad
5 R = 2000000; // in Ohm
6 V = 200; // in VOLts
7 tc = 20; // in sec
8
9 //calculation:

```

```

10 //capacitor voltage , Vc
11 Vc = V*(%e^(-1*tc/(R*C)))
12
13 printf("\n\n Result \n\n")
14 printf("\n value of capacitor voltage at t = 20s is
    %.2f V" ,Vc)

```

---

### Scilab code Exa 45.03 Example 3

```

1 //Problem 45.03: A coil of inductance 50 mH and
  resistance 5 ohm is connected to a 110 V, d.c.
  supply. Determine (a) the final value of current ,
  (b) the value of current after 4 ms, (c) the
  value of the voltage across the resistor after 6
  ms, (d) the value of the voltage across the
  inductance after 6 ms, and (e) the time when the
  current reaches 15 A.
2
3 //initializing the variables:
4 L = 0.05; // in Henry
5 R = 5; // in Ohm
6 V = 110; // in VOLts
7 ti = 0.004; // in sec
8 tvr = 0.006; // in sec
9 tvl = 0.006; // in sec
10 it = 15; // in amperes
11
12 //calculation:
13 //steady state current i
14 i = V/R
15 //when time t = 4ms current is
16 i4 = (V/R)*(1 - %e^(-1*ti*R/L))
17 //resistor voltage , VR
18 VR6 = V*(1 - %e^(-1*tvr*R/L))
19 //inductor voltage , VL

```

```

20 VL6 = V*(%e^(-1*tvl*R/L))
21 //time, t
22 ti = (-1*L/R)*log(1 - it*R/V)
23
24 printf("\n\n Result \n\n")
25 printf("\n steady state current i is %.0f A",i)
26 printf("\n when time t = 4ms current is is %.2f A",
    i4)
27 printf("\n value of resistor voltage at t = 6ms is
    %.2f V",VR6)
28 printf("\n value of inductor voltage at t = 6ms is
    %.2f V",VL6)
29 printf("\n the time after connection when the
    current is 15 A is %.5f sec",ti)

```

---

#### Scilab code Exa 45.04 Example 4

```

1 //Problem 45.04: In the circuit shown in Figure
    45.8, a current of 5 A flows from the supply
    source. Switch S is then opened. Determine (a)
    the time for the current in the 2 H inductor to
    fall to 200 mA, and (b) the maximum voltage
    appearing across the resistor.
2
3 //initializing the variables:
4 i = 5; // in Amperes
5 L = 2 // in Henry
6 i1 = 0.2; // in Amperes
7 R = 10; // in Ohm
8
9 //calculation:
10 //time t
11 ti = (-1*L/R)*log(i1/i)
12 //voltage across the resistor is a maximum
13 VRm = i*R

```

```

14
15 printf("\n\n Result \n\n")
16 printf("\n  time t for the current in the 2 H
      inductor to fall to 200 mA is %.3f sec",ti)
17 printf("\n  max voltage across the resistor is %.0f
      V",VRm)

```

---

### Scilab code Exa 45.05 Example 5

```

1 //Problem 45.05: A series L R C circuit has
      inductance , L = 2 mH, resistance , R = 1 kohm and
      capacitance , C = 5 F . (a) Determine whether the
      circuit is over, critical or underdamped. (b) If
      C = 5 nF, determine the state of damping.
2
3 //initializing the variables:
4 L = 0.002 // in Henry
5 R = 1000; // in Ohm
6 C1 = 5E-6; // in farad
7 C2 = 5E-9; // in farad
8
9 //calculation:
10 a = (R/(2*L))^2
11 b = 1/(L*C1)
12 if (a>b) then
13     s1 = "overdamped";
14 elseif (a<b) then
15     s1 = "underdamped";
16 else
17     s1 = "critically damped";
18 end
19 c = 1/(L*C2)
20 if (a>c) then
21     s2 = "overdamped";
22 elseif (a<c) then

```

```

23     s2 = "underdamped";
24 else
25     s2 = "critically damped";
26 end
27
28 printf("\n\n Result \n\n")
29 printf("\n  circuit is %s",s1)
30 printf("\n  if C = 5 nF, circuit is %s",s2)

```

---

#### Scilab code Exa 45.06 Example 6

```

1 //Problem 45.06: In the circuit of problem 45.05,
   what value of capacitance will give critical
   damping ?
2
3
4 //initializing the variables:
5 L = 0.002 // in Henry
6 R = 1000; // in Ohm
7
8 //calculation:
9 a = (R/(2*L))^2
10 //for critically damped
11 C = 4*L/R^2
12
13 printf("\n\n Result \n\n")
14 printf("\n  capacitance C is %.2E F",C)

```

---