

Scilab Textbook Companion for
Basic Electrical Engineering
by D. P. Kothari And I. J. Nagrath¹

Created by
Ashish Bora
B. Tech.
Electrical Engineering
IIT Bombay
College Teacher
Prof. Madhu Belur
Cross-Checked by
Lavitha Pereira

May 23, 2016

¹Funded by a grant from the National Mission on Education through ICT, <http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab codes written in it can be downloaded from the "Textbook Companion Project" section at the website <http://scilab.in>

Book Description

Title: Basic Electrical Engineering

Author: D. P. Kothari And I. J. Nagrath

Publisher: Tata McGraw - Hill Education, New Delhi

Edition: 3

Year: 2010

ISBN: 9780070146112

Scilab numbering policy used in this document and the relation to the above book.

Exa Example (Solved example)

Eqn Equation (Particular equation of the above book)

AP Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

Contents

List of Scilab Codes	4
1 Elementary Concepts and Definitions	5
2 Fundamentals of Resistive Circuits	16
3 Fundamentals of Reactive Circuits	35
4 Steady State Analysis For Sinusoidal Excitation	48
5 Frequency Response	80
6 Three Phase Circuits	93
7 Magnetic Circuits	107
8 Transformers	119
9 EMF and Torque in Electric Machines	143
10 DC Machines	152
11 Synchronous Machine	168
12 Induction Motor	180
14 Measurement Techniques and Electric and Electronic Instrumentation	191
15 Power Systems	199

List of Scilab Codes

Exa 1.A.1	Additional Solved Problem 1	5
Exa 1.A.2	Additional Solved Problem 2	5
Exa 1.A.3	Additional Solved Problem 3	6
Exa 1.A.4	Additional Solved Problem 4	7
Exa 1.A.5	Additional Solved Problem 5	7
Exa 1.A.6	Additional Solved Problem 6	8
Exa 1.A.7	Additional Solved Problem 7	8
Exa 1.A.9	Additional Solved Problem 9	9
Exa 1.1	Problem1	9
Exa 1.2	Problem2	10
Exa 1.3	Problem3	11
Exa 1.5	Problem5	11
Exa 1.7	Problem7	11
Exa 1.9	Problem9	12
Exa 1.10	Problem10	13
Exa 1.11	Problem11	13
Exa 1.12	Problem12	13
Exa 1.13	Problem13	14
Exa 1.15	Problem15	14
Exa 2.1	Problem1	16
Exa 2.2	Problem2	17
Exa 2.3	Problem3	17
Exa 2.4	Problem4	18
Exa 2.5	Problem5	18
Exa 2.6	Problem6	19
Exa 2.7	Problem7	19
Exa 2.8	Problem8	19
Exa 2.9	Problem9	20

Exa 2.10	Problem10	20
Exa 2.11	Problem11	21
Exa 2.13	Problem13	21
Exa 2.14	Problem14	22
Exa 2.15	Problem15	22
Exa 2.16	Problem16	22
Exa 2.17	Problem17	23
Exa 2.18	Problem18	23
Exa 2.19	Problem19	24
Exa 2.20	Problem20	24
Exa 2.21	Problem21	25
Exa 2.22	Problem22	25
Exa 2.23	Problem23	26
Exa 2.24	Problem24	26
Exa 2.25	Problem25	27
Exa 2.26	Problem26	27
Exa 2.27	Problem27	28
Exa 2.28	Problem28	28
Exa 2.29	Problem29	29
Exa 2.30	Problem30	29
Exa 2.31	Problem31	30
Exa 2.32	Problem32	30
Exa 2.33	Problem33	31
Exa 2.35	Problem35	31
Exa 2.36	Problem36	32
Exa 2.37	Problem37	32
Exa 2.38	Problem38	33
Exa 2.39	Problem39	33
Exa 2.40	Problem40	33
Exa 3.1	Problem1	35
Exa 3.2	Problem2	35
Exa 3.3	Problem3	36
Exa 3.4	Problem4	36
Exa 3.5	Problem5	37
Exa 3.6	Problem6	37
Exa 3.7	Problem7	37
Exa 3.8	Problem8	38
Exa 3.9	Problem9	38

Exa 3.11	Problem11	39
Exa 3.12	Problem12	39
Exa 3.13	Problem13	40
Exa 3.16	Problem16	40
Exa 3.18	Problem18	41
Exa 3.21	Problem21	41
Exa 3.22	Problem22	41
Exa 3.24	Problem24	42
Exa 3.26	Problem26	42
Exa 3.27	Problem27	43
Exa 3.29	Problem29	44
Exa 3.32	Problem32	44
Exa 3.33	Problem33	45
Exa 3.36	Problem36	46
Exa 3.37.38	Problem37 and 38	46
Exa 4.1	Problem1	48
Exa 4.2	Problem2	48
Exa 4.4	Problem4	49
Exa 4.5	Problem5	49
Exa 4.6	Problem6	50
Exa 4.7	Problem7	50
Exa 4.8	Problem8	51
Exa 4.9	Problem9	53
Exa 4.10	Problem10	53
Exa 4.11	Problem11	53
Exa 4.12	Problem12	54
Exa 4.13	Problem13	55
Exa 4.14	Problem14	55
Exa 4.15	Problem15	56
Exa 4.16	Problem16	57
Exa 4.17	Problem17	58
Exa 4.18	Problem18	58
Exa 4.21	Problem21	59
Exa 4.22	Problem22	60
Exa 4.23	Problem23	60
Exa 4.24	Problem24	61
Exa 4.25	Problem25	62
Exa 4.26	Problem26	62

Exa 4.27	Problem27	63
Exa 4.28	Problem28	64
Exa 4.29	Problem29	64
Exa 4.30	Problem30	65
Exa 4.31	Problem31	65
Exa 4.32	Problem32	66
Exa 4.33	Problem33	66
Exa 4.34	Problem34	67
Exa 4.35	Problem35	68
Exa 4.36	Problem36	69
Exa 4.37	Problem37	69
Exa 4.38	Problem38	70
Exa 4.39	Problem39	71
Exa 4.40	Problem40	71
Exa 4.41	Problem41	72
Exa 4.42	Problem42	72
Exa 4.43	Problem43	73
Exa 4.44	Problem44	73
Exa 4.45	Problem45	74
Exa 4.46	Problem46	75
Exa 4.47	Problem47	75
Exa 4.48	Problem48	76
Exa 4.49	Problem49	77
Exa 4.50	Problem50	77
Exa 4.51	Problem51	78
Exa 4.52	Problem52	79
Exa 5.1	Problem1	80
Exa 5.2	Problem2	80
Exa 5.3	Problem3	81
Exa 5.4	Problem4	81
Exa 5.5	Problem5	82
Exa 5.6	Problem6	82
Exa 5.7	Problem7	83
Exa 5.8	Problem8	83
Exa 5.9	Problem9	83
Exa 5.10	Problem10	84
Exa 5.11	Problem11	84
Exa 5.12	Problem12	85

Exa 5.13	Problem13	85
Exa 5.14	Problem14	86
Exa 5.15	Problem15	86
Exa 5.17	Problem17	87
Exa 5.18	Problem18	87
Exa 5.19	Problem19	88
Exa 5.20	Problem20	88
Exa 5.21	Problem21	89
Exa 5.22	Problem22	90
Exa 5.28	Problem28	90
Exa 5.29	Problem29	91
Exa 6.1	Problem1	93
Exa 6.2	Problem2	94
Exa 6.3	Problem3	94
Exa 6.4	Problem4	95
Exa 6.5	Problem5	95
Exa 6.6	Problem6	96
Exa 6.7	Problem7	96
Exa 6.9	Problem9	97
Exa 6.10	Problem10	98
Exa 6.11	Problem11	99
Exa 6.12	Problem12	99
Exa 6.13	Problem13	100
Exa 6.14	Problem14	101
Exa 6.15	Problem15	101
Exa 6.16	Problem16	102
Exa 6.17	Problem17	103
Exa 6.18	Problem18	103
Exa 6.19	Problem19	104
Exa 6.20	Problem20	104
Exa 6.21	Problem21	105
Exa 7.1	Problem1	107
Exa 7.2	Problem2	107
Exa 7.3	Problem3	108
Exa 7.4	Problem4	108
Exa 7.5	Problem5	109
Exa 7.6	Problem6	109
Exa 7.7	Problem7	110

Exa 7.8	Problem8	111
Exa 7.9	Problem9	112
Exa 7.10	Problem10	113
Exa 7.11	Problem11	114
Exa 7.12	Problem12	114
Exa 7.14	Problem14	114
Exa 7.15	Problem15	115
Exa 7.16	Problem16	116
Exa 7.17	Problem17	116
Exa 7.18	Problem18	117
Exa 7.19	Problem19	118
Exa 8.1	Problem1	119
Exa 8.2	Problem2	119
Exa 8.3	Problem3	120
Exa 8.4	Problem4	121
Exa 8.5	Problem5	122
Exa 8.6	Problem6	122
Exa 8.7	Problem7	123
Exa 8.8	Problem8	123
Exa 8.9	Problem9	124
Exa 8.10	Problem10	126
Exa 8.11	Problem11	126
Exa 8.12	Problem12	128
Exa 8.13	Problem13	129
Exa 8.14	Problem14	130
Exa 8.15	Problem15	131
Exa 8.16	Problem16	132
Exa 8.17	Problem17	133
Exa 8.18	Problem18	134
Exa 8.19	Problem19	134
Exa 8.20	Problem20	135
Exa 8.21	Problem21	136
Exa 8.22	Problem22	137
Exa 8.23	Problem23	137
Exa 8.24	Problem24	138
Exa 8.25	Problem25	138
Exa 8.26	Problem26	139
Exa 8.27	Problem27	140

Exa 8.28	Problem28	141
Exa 8.29	Problem29	141
Exa 9.1	Problem1	143
Exa 9.2	Problem2	144
Exa 9.3	Problem3	144
Exa 9.4	Problem4	145
Exa 9.5	Problem5	145
Exa 9.6	Problem6	146
Exa 9.7	Problem7	146
Exa 9.8	Problem8	147
Exa 9.9	Problem9	147
Exa 9.10	Problem10	148
Exa 9.11	Problem11	148
Exa 9.12	Problem12	149
Exa 9.13	Problem13	149
Exa 9.14	Problem14	149
Exa 9.15	Problem15	150
Exa 9.16	Problem16	150
Exa 10.1	Problem1	152
Exa 10.2	Problem2	153
Exa 10.3	Problem3	153
Exa 10.4	Problem4	154
Exa 10.5	Problem5	154
Exa 10.6	Problem6	155
Exa 10.7	Problem7	155
Exa 10.8	Problem8	156
Exa 10.9	Problem9	157
Exa 10.10	Problem10	157
Exa 10.11	Problem11	158
Exa 10.12	Problem12	159
Exa 10.13	Problem13	159
Exa 10.14	Problem14	160
Exa 10.15	Problem15	160
Exa 10.16	Problem16	161
Exa 10.17	Problem17	162
Exa 10.18	Problem18	162
Exa 10.19	Problem19	163
Exa 10.20	Problem20	163

Exa 10.21	Problem21	164
Exa 10.22	Problem22	164
Exa 10.23	Problem23	165
Exa 10.24	Problem24	165
Exa 10.25	Problem25	166
Exa 10.26	Problem26	166
Exa 11.1	Problem1	168
Exa 11.2	Problem2	168
Exa 11.3	Problem3	169
Exa 11.4	Problem4	170
Exa 11.5	Problem5	171
Exa 11.6	Problem6	171
Exa 11.7	Problem7	172
Exa 11.8	Problem8	172
Exa 11.9	Problem9	173
Exa 11.10	Problem10	174
Exa 11.11	Problem11	175
Exa 11.12	Problem12	176
Exa 11.13	Problem13	176
Exa 11.14	Problem14	177
Exa 11.15	Problem15	178
Exa 12.1	Problem1	180
Exa 12.2	Problem2	180
Exa 12.3	Problem3	181
Exa 12.5	Problem5	181
Exa 12.6	Problem6	182
Exa 12.7	Problem7	183
Exa 12.8	Problem8	184
Exa 12.9	Problem9	185
Exa 12.10	Problem10	185
Exa 12.11	Problem11	186
Exa 12.12	Problem12	186
Exa 12.13	Problem13	187
Exa 12.14	Problem14	187
Exa 12.15	Problem15	188
Exa 12.16	Problem16	189
Exa 12.17	Problem17	190
Exa 14.1	Problem1	191

Exa 14.2	Problem2	191
Exa 14.3	Problem3	192
Exa 14.4	Problem4	192
Exa 14.5	Problem5	192
Exa 14.6	Problem6	193
Exa 14.7	Problem7	194
Exa 14.8	Problem8	194
Exa 14.9	Problem9	195
Exa 14.10	Problem10	195
Exa 14.11	Problem11	195
Exa 14.12	Problem12	196
Exa 14.13	Problem13	196
Exa 14.14	Problem14	197
Exa 14.15	Problem15	197
Exa 14.17	Problem17	198
Exa 14.18	Problem18	198
Exa 15.1	Problem1	199
Exa 15.2	Problem2	199
Exa 15.3	Problem3	200
Exa 15.4	Problem4	200
Exa 15.5	Problem5	201
Exa 15.6	Problem6	201
Exa 15.7	Problem7	202

Chapter 1

Elementary Concepts and Definitions

Scilab code Exa 1.A.1 Additional Solved Problem 1

```
1 t=0.1
2 R=800
3 i=50*exp(-10*t)/1000
4 v=50*cos(25*t)
5 v_i=10*t^(2.5)
6
7 P1=i*i*R
8 P2=v*v/R
9 P3=v_i
10
11 disp(P3,P2,P1)
```

Scilab code Exa 1.A.2 Additional Solved Problem 2

```
1 v2=5
2 i2=v2/1000
```

```

3 v1=-i2/5
4 vs=v1
5
6 disp(vs)

```

Scilab code Exa 1.A.3 Additional Solved Problem 3

```

1 L=20/1000
2
3 //////////////////////////////////////
4 disp(" Part1")
5 function i = i(t)
6     i = 8*exp(-100*t);
7 endfunction
8
9 t=10/1000
10 v= L*(derivative(i,t))
11 disp(v,"V=")
12
13 //////////////////////////////////////Part2
14 disp(" Part2")
15 t=0.1
16
17 function v=v(t)
18     v=6*exp(-12*t)
19 endfunction
20
21 i0=8
22
23 i2=1/L*intg(0,t,v)+i0
24 disp(i2)
25
26 //////////////////////////////////////Part3
27 disp(" Part3")
28 function i3 = i3(t)

```

```

29     i3 = 10-10*exp(-50*t);
30 endfunction
31
32 t=40/1000
33 v3=L*(derivative(i3,t))
34 P40=v3*i3(t)
35 disp(P40)
36
37 t=50/1000
38 P50=1/2*L*(i3(50)^2)
39 disp(P50)

```

Scilab code Exa 1.A.4 Additional Solved Problem 4

```

1 function i = i(t)
2     i = 9*sin(%pi*t)/1000;
3 endfunction
4
5 t=200/1000
6 CV=intg(0,t,i)
7 Wc=300E-6
8 C=(CV^2)/(2*Wc)
9 disp(C)

```

Scilab code Exa 1.A.5 Additional Solved Problem 5

```

1 L=25E-3
2
3 T=5/1000
4 I=1/L*integrate('25*cos(500*t)', 't', 0, T)
5 P=25*cos(500*T)*I
6
7 t1=%pi/2/500          //power absorbed zero

```



```
8 t2=%pi/500          /////energy stored zero
9
10 disp(I,P,t1,t2)
```

Scilab code Exa 1.A.6 Additional Solved Problem 6

```
1 e0=8.85E-12
2 er=1
3 A=%pi*(1/200)^2
4 d=150/1000000
5 C=er*e0*A/d
6
7 E=1/1000
8 v=sqrt(2*E/C)
9 disp(v)
10
11 E=2/1000000
12 v=100
13 er=2*E/(v^2)/C
14 disp(er)
```

Scilab code Exa 1.A.7 Additional Solved Problem 7

```
1 t=10/1000
2 v3=8*exp(-50*t)
3 p3=v3*(-3.6)
4 P=[230/1000*4.8; (-3.2)*1.45;p3]
5
6 disp("Power absorbed are respectively")
7 disp(P)
```

Scilab code Exa 1.A.9 Additional Solved Problem 9

```
1 Im=250/1000
2 w=100
3 r=4
4 L=50/1000
5 t=25/1000
6
7 i=Im*sin(w*t)
8 Vr=i*r
9 Vl=Im*L*w*cos(w*t)
10
11 Pr=i*i*r
12 Pl=Vl*i
13 wl=1/2*L*i*i
14 wl_min=0 //min current =0
15 wl_max=1/2*L*Im*Im //Im is the max current
16
17 disp(" All values in Joules")
18 disp(wl_max, wl_min, wl, Pl, Pr)
```

Scilab code Exa 1.1 Problem1

```
1 disp(" v1=A cos(w t+p)")
2 disp(" i1=B cos(w1 t+p1)")
3 disp(" i2=C sin(w2 t+p2)")
4 disp(" All values in degrees")
5 w=input("w=")
6 p=input("p=")
7 w1=input("w1=")
8 p1=input("p1=")
9 w2=input("w2=")
10 p2=input("p2=")
11
12 if(w==w1)
```

```

13     lag1=p-p1;
14     disp(lag1, "i1 lags v1 by ")
15 else
16     disp("Lag undefined for i1")
17 end
18
19
20 if(w==w2)
21     lag2=p-p2+90;
22     disp(lag2, "i2 lags v1 by ")
23 else
24     disp("Lag undefined for i2")
25 end

```

Scilab code Exa 1.2 Problem2

```

1 // X cos(w t+p)+Y sin(w t+q)
2
3 X=50
4 Y=-30
5 w=120
6 p=-45
7 p=p/180*%pi;
8 q=160
9 q=q/180*%pi;
10
11 //Part1
12
13 A=X*cos(p)+ Y*sin(q);
14 B=-X*sin(p)+ Y*cos(q);
15
16 disp(B,"B=" ,A,"A=")

```

Scilab code Exa 1.3 Problem3

```
1 G1=input("G1=")
2 G2=input("G2=")
3 G3=input("G3=")
4 Is1=input("Is1=")
5 Is2=input("Is2=")
6
7 A=[G1+G3, -G3; -G3, G2+G3];
8 I=[Is1; Is2];
9 V=inv(A)*I;
10
11 disp(V)
```

Scilab code Exa 1.5 Problem5

```
1
2
3 R1=input("R1=")
4 R2=input("R2=")
5 R3=input("R3=")
6 Vs1=input("Vs1=")
7 Vs2=input("Vs2=")
8
9 R=[R1+R3, -R3; -R3, R2+R3];
10 V=[Vs1; -Vs2];
11 I=inv(R)*V;
12
13 disp(I)
```

Scilab code Exa 1.7 Problem7

```
1 R1=1
```

```

2 R2=6
3 R3=12
4 R4=4
5 I4=3/4
6 V6=6
7
8 V4=3/4*4
9 I12=3/12
10 IR=3/4+I12
11
12 R=-12*I12+V6 //KVL
13 disp(R,"R(Ohm)=")
14
15 I6=V6/6
16 I1=I6+IR
17
18 Vs=1*I1+V6 //KVL
19 disp(Vs,"Vs(V)=")
20
21 disp(Vs*I1,"Power(W)=")

```

Scilab code Exa 1.9 Problem9

```

1 i1=4
2 v3=3
3 v4=8
4
5 i3=v3/3
6 i4=v4/4
7
8 i2=(i1-i3-i4)/2 //KCL
9 v2=2*i2
10
11 disp(v2,"v2=")

```

Scilab code Exa 1.10 Problem10

```
1 v1=6
2 i2=2
3 i3=4
4
5 v2=2*i2
6 v3=2*i3
7
8 v4=-v1+4*i2+v3-v2 //KVL
9 i4=v4/3
10 disp(i4)
```

Scilab code Exa 1.11 Problem11

```
1 i1=4-1 // KCL at node 1
2 disp(i1,"i1=")
3
4 v1=i1*1
5 v12=1*1
6 v2=v1-v12
7 i2=v2/1
8
9 i3=1-i2 //KCL at node 2
10
11 Vs=v2-1*i3 //KVL
12 disp(Vs,"Vs=")
```

Scilab code Exa 1.12 Problem12

```

1 i34=10-8 //KCL at node 4
2 v34=5*i34
3 v23=40-10 //KVL
4 vx=v23
5 disp(vx,"vx=")
6 ix=4-8 //KCL at node 1
7 disp(ix,"ix=")
8 i23=ix+10 //KCL at node 2
9 R2=vx/i23
10 disp(R2,"R2=")
11 v14=40+6*ix //KVL
12 R1=v14/8
13 disp(R1,"R1=")

```

Scilab code Exa 1.13 Problem13

```

1 vs=0.01 // *cos(1000*t)
2
3 vpi=vs
4 i0=-vpi/1000
5 vo=i0*1000;
6 printf("v0 = %f *cos(1000*t)",vo)

```

Scilab code Exa 1.15 Problem15

```

1 t=0.1
2 R=800
3 i=50*exp(-10*t)/1000
4 v=50*cos(25*t)
5 v_i=10*t^(2.5)
6
7 P1=i*i*R
8 P2=v*v/R

```

```
9 P3=v_i
10
11 disp(P3,P2,P1)
```

Chapter 2

Fundamentals of Resistive Circuits

Scilab code Exa 2.1 Problem1

```
1 function s=series(r1,r2)
2     s=r1+r2
3 endfunction
4
5 function p=parallel(r1,r2)
6     p=r1*r2/(r1+r2)
7 endfunction
8
9 r1=series(12,8)
10 r2=parallel(20,r1)
11 r3=series(r2,50)
12 r4=parallel(30,r3)
13 r5=series(10,r4)
14 r6=series(r5,20)
15 Req_ab=parallel(r5,40)
16 disp(Req_ab)
17
18 r7=40+20+10 //series
19 Req_bc=parallel(r4,r7)
```

20 `disp(Req_bc)`

Scilab code Exa 2.2 Problem2

```
1 I=(14-4)/(8+5+5+7) //KVL
2 disp(I)
```

Scilab code Exa 2.3 Problem3

```
1 r1=100
2 v=3/4
3
4 r2=r1*v/(1-v)
5
6
7 function p=parallel(r1,r2)
8     p=r1*r2/(r1+r2)
9 endfunction
10
11 //Part1
12 R2_eq=parallel(r2,10000)
13 k=R2_eq/(R2_eq+r1)
14 change1=(3/4-k)/(3/4)*100
15 disp(change1)
16 //Part2
17
18 R2_eq=parallel(r2,1000)
19 k=R2_eq/(R2_eq+r1)
20 change2=(3/4-k)/(3/4)*100
21 disp(change2)
```

Scilab code Exa 2.4 Problem4

```
1 function p=parallel(r1,r2)
2     p=r1*r2/(r1+r2)
3 endfunction
4
5
6 v=150
7
8 Req=1000*parallel(parallel(10,5),4)
9 i1=v/(2000+0.2*1000+Req)
10 v1=i1*0.2*1000
11 VReq=Req*i1
12 i2=VReq/4000
13
14 disp(v1)
15 disp(i2)
```

Scilab code Exa 2.5 Problem5

```
1 function [Rab,Rbc,Rca]=star_to_delta(Ra,Rb,Rc)
2     X=Ra*Rb+Rb*Rc+Rc*Ra
3     Rab=X/Rc
4     Rbc=X/Ra
5     Rca=X/Rb
6 endfunction
7
8 function p=parallel(r1,r2)
9     p=r1*r2/(r1+r2)
10 endfunction
11
12 [Rx,Ry,Rz]=star_to_delta(8,4,2)
13
14 Req_ad=parallel(parallel(4,Rx)+parallel(12,Rz),
15     parallel(3,Ry))
```

```
15 disp(Req_ad)
```

Scilab code Exa 2.6 Problem6

```
1 //Converting Voltage source with series resistance
  to current source
2 I=1/(1/4)
3
4 //KCL at nodes 1,2,3 using conductances
5 A=[11, -3, -4; -3, 6, -2; -4, -2, 11]
6 V=inv(A)*[5; -7; 6]
7
8 disp(V)
```

Scilab code Exa 2.7 Problem7

```
1 function p=parallel(r1,r2)
2     p=r1*r2/(r1+r2)
3 endfunction
4
5 Req=parallel(15,30)
6
7 //KCL at nodes 1 and 2
8 A=[3, -1; -3, 5]
9 V=inv(A)*[80; -360]
10
11 disp(V(1))
```

Scilab code Exa 2.8 Problem8

```

1 //Converting practical voltage source to current
  source
2 I=12/6
3
4 //KCLs
5 A=[0.7, -0.5; -0.5, 0.767]
6 V=inv(A)*[7;2]
7 disp(V)
8
9 I12=(V(1)-V(2))/2
10 disp(I12)

```

Scilab code Exa 2.9 Problem9

```

1 //KCLs
2
3 A=[2, -1; -4, 19]
4 V=inv(A)*[10;25]
5
6 Pc=1*V(1)
7 Iv=(5-V(2))/2 + (5-V(1))/5
8 Pv=5*Iv
9
10 disp(V)
11 disp(Pv, Pc)

```

Scilab code Exa 2.10 Problem10

```

1 //converting 9v voltage source to current source
2 I=9/0.45
3 I=I-7
4
5 //KCLs

```

```
6 A=[1/0.45+1/10, -1/10 ; 0.2-1/10, 1/10-0.2]
7 V=inv(A)*[-18;5]
8
9 disp(V(2))
```

Scilab code Exa 2.11 Problem11

```
1 //converting voltage source to current source
2
3 I=240/3
4
5 //KCLs
6
7 A=[1/3+1/6, -1/6; -1/6, 1/6+1/12+1/30]
8 V=inv(A)*[70;5]
9 Vx=V(1)
10 Vy=V(2)-60
11
12 V6=V(2)-V(1)
13 P6=V6*V6/6
14
15 disp(P6)
```

Scilab code Exa 2.13 Problem13

```
1 // KVLs
2
3 A=[24, -6, -8; -6, 20, -5; -8, -5, 25]
4 I=inv(A)*[16;0;0]
5 I5=I(2)-I(3)
6 disp(I5)
```

Scilab code Exa 2.14 Problem14

```
1 //convert practical current source to voltage source
2 V=10*5
3
4 //KVLs
5 A=[35, -20; -20, 50]
6 I=inv(A)*[50; -100]
7
8 v=20*(I(1)-I(2))
9 disp(v)
```

Scilab code Exa 2.15 Problem15

```
1 i1=0.37
2
3 //KVL for loop 2
4 i2=(-100+20*i1)/50
5
6 //KVL for loop 1
7 R=(50+20*(i2-i1))/i1
8 disp(R)
```

Scilab code Exa 2.16 Problem16

```
1 //Converting current sources to voltage sources
2 // O=[i1; i2; vx]
3
4 A=[10, -3, 4; -3, 7, 0; 3, -3, -1]
```

```
5 0=inv(A)*[16;-6;0]
6
7 disp(0)
```

Scilab code Exa 2.17 Problem17

```
1 //convert current sources to voltage
2
3 A=[95,-15;-15,135]
4 I=inv(A)*[20;-70]
5
6 i3=I(1)-I(2)
7
8 I60=0.5-I(1)
9 V60=I60*60
10 P1= 0.5*V60           //0.5 A source
11
12 I80=1+I(2)
13 V80=I80*80
14 P2=1*V80
15
16 disp(P2,P1)
```

Scilab code Exa 2.18 Problem18

```
1 //Nodal Equations
2
3 A=[0.6,-0.5;2,-1.6]
4 V=inv(A)*[4;0]
5 V12=V(1)-V(2)
6 disp(V12)
```

Scilab code Exa 2.19 Problem19

```
1 //convert dependent current source to dependent
   voltage source
2
3 //Mesh Equations
4 A=[14,-2,0;-2,18,3;2,-2,-1]
5 O=inv(A)*[100;0;0]
6
7 disp(O(3))
```

Scilab code Exa 2.20 Problem20

```
1 //////////////////////////////////////////////////Part 1
2
3 //Nodal Method
4 v1=(8/5+16/10)/(1/5+1/2+1/10)
5 disp(v1)
6 i5=(8-v1)/5000
7 disp(i5)
8
9
10 //////////////////////////////////////////////////Part2
11
12 //Mesh Method
13
14 A=[7,-2;-2,12]
15 I=inv(A)*[8;-16]/1000
16 disp(I)
17
18 v1=2*1000*(I(1)-I(2))
19 disp(v1)
```

Scilab code Exa 2.21 Problem21

```
1 function p=parallel(r1,r2)
2     p=r1*r2/(r1+r2)
3 endfunction
4
5 //deactivate voltage source
6
7 i11=4*6/8
8 i21=4*2/8
9 v11=i11*2
10 v21=1*1
11
12 //deactivate current source
13 Req=parallel(2,7)
14
15 v22=8*Req/(2+Req)
16 v12=v22*(2/(2+5))
17
18 v1=v11+v12
19 v2=v21+v22
20
21 disp(v2,v1)
```

Scilab code Exa 2.22 Problem22

```
1 function p=parallel(r1,r2)
2     p=r1*r2/(r1+r2)
3 endfunction
4
5 //Thevenin Equivalent
```

```

6 I=(32-8)/30
7 Voc=32-20*I
8 Ro=parallel(20,10)
9 disp(Ro,Voc)
10
11 //Norton Equivalent
12 Isc=32/20+8/10
13 disp(Ro,Isc)

```

Scilab code Exa 2.23 Problem23

```

1 //convert current source to voltage source
2 V=3.5*20
3
4 //KVL
5 I=100/(10+20+V)
6 Voc=100-10*I
7
8 //Finding Isc
9 I=100/10
10 Isc=(1+3.5)*I
11
12 Ro=Voc/Isc
13
14 disp(Ro,Voc)

```

Scilab code Exa 2.24 Problem24

```

1 V=32
2 I=1
3 R1=20
4 R2=8
5 R3=2

```

```

6 Voc1=V/(R1+R2+R3)*(R2+R3)   ///a,b open
7 Isc1=V/R1                    ///a,b short
8
9 Voc2=I*R2/(R1+R2+R3)*R1
10 Isc2=I*R2/(R2+R3)
11
12 ////by superposition
13 Voc=Voc1+Voc2
14 Isc=Isc1+Isc2
15
16 disp(Voc)
17 disp(Isc)

```

Scilab code Exa 2.25 Problem25

```

1 function [Ra,Rb,Rc]=delta_to_star(Rab,Rbc,Rca)
2     X=Rab+Rbc+Rca
3     Ra=Rab*Rca/X
4     Rb=Rab*Rbc/X
5     Rc=Rca*Rbc/X
6 endfunction
7
8 function p=parallel(r1,r2)
9     p=r1*r2/(r1+r2)
10 endfunction
11
12 [R1,R2,R3]=delta_to_star(4,12,8)
13 Req=10+4+parallel(R1+15,R2+16)
14
15 I=12/Req
16 disp(I)

```

Scilab code Exa 2.26 Problem26

```

1 //convert current source to voltage source
2
3 V1=4*2
4 V2=2*2
5
6 //Mesh Analysis
7
8 A=[7, -3; -15, 19]
9 I=inv(A)*[6; -14]
10
11 Vx=3*(I(1)-I(2))
12 disp(Vx)

```

Scilab code Exa 2.27 Problem27

```

1 //Short Circuit AB and convert Curr Source to V
  source
2
3 V=9*5
4 Isc=(45-9)/6
5
6 function p=parallel(r1,r2)
7     p=r1*r2/(r1+r2)
8 endfunction
9
10 Ro=parallel(5+1,3)
11 disp(Ro,Isc)

```

Scilab code Exa 2.28 Problem28

```

1 //Mesh Analysis
2
3 A=[4, -2; 998, 24.5]

```

```
4 I=inv(A)*[1/1000;0]
5
6 disp(I)
7
8 P1=I(2)^2*2.5*1000
9 P2=1/1000*I(1)
10 P3=-10^6*I(1)*I(2)
11 P=[P1,P2,P3]
12 disp(P)
```

Scilab code Exa 2.29 Problem29

```
1 function p=parallel(r1,r2)
2     p=r1*r2/(r1+r2)
3 endfunction
4
5 //as seen from ab
6 Vth1=30*60/(30+60)
7 Rth1=parallel(30,60)
8
9 //as seen from cd
10 Vth2=80*40/(40+60)
11 Rth2=parallel(40,60)
12
13 Vnet=60+Vth1-Vth2
14 Rnet=Rth1+Rth2
15
16 disp(Rnet,Vnet)
```

Scilab code Exa 2.30 Problem30

```
1 function p=parallel(r1,r2)
2     p=r1*r2/(r1+r2)
```

```

3  endfunction
4
5  R=parallel(60,120)
6
7  //Mesh Analysis
8
9  A=[6,-4;-4,12]
10 I=inv(A)*[2.4;-3.6]
11 I3=I(1)-I(2)
12
13 I60=I3*120/(120+60)
14 disp(I60)

```

Scilab code Exa 2.31 Problem31

```

1  //Nodal Equation
2
3  Vn=198/10.5
4  I60=Vn/60
5  disp(I60)

```

Scilab code Exa 2.32 Problem32

```

1  V8=2*8
2
3  //KVL
4  I1=(30-16)/10
5
6  //KCL at left node
7  I2=2-I1
8
9  //KVL middle mesh
10 I4=(10*I1-2*I2)/4

```

```
11 Vx=4*I4
12
13 //right node
14 Ix=I4-I2
15
16 disp(Vx)
```

Scilab code Exa 2.33 Problem33

```
1 //investigate the if
  then else construct
2
3
4
5 I=5
6
7 //KVL
8 R=(-12.5+15)/I-0.02-0.035
9 disp(R)
10
11 P=poly([-25,12.5,0.035], "I", "coeff")
12 Z=roots(P)
13 Ib=Z(2)
14 disp(Ib)
15
16 I=(13-12.5)/0.035
17 R=(15-13)/I-0.02
18 disp(R)
```

Scilab code Exa 2.35 Problem35

```
1 R=12*12/4-25
2 disp(R)
```



```
3
4 I=sqrt(1.6/1000/10000)
5 R=12/I-10000-15000
6 disp(R)
7
8 I=0
9 V=12
10 disp(V)
```

Scilab code Exa 2.36 Problem36

```
1 function p=parallel(r1,r2)
2     p=r1*r2/(r1+r2)
3 endfunction
4
5 Req=1+parallel(parallel(1,1),1)
6
7 disp(Req)
```

Scilab code Exa 2.37 Problem37

```
1 function p=parallel(r1,r2)
2     p=r1*r2/(r1+r2)
3 endfunction
4
5 R1=parallel(parallel(40,60),80+40)
6
7 Req=20+parallel(10+R1,30)
8 disp(Req)
```

Scilab code Exa 2.38 Problem38

```
1 function p=parallel(r1,r2)
2     p=r1*r2/(r1+r2)
3 endfunction
4
5 R1=parallel(5,40)+15
6 Req=parallel(R1,15)+10
7 i=6/(1000*Req)
8
9 ix=i*R1/(R1+15)
10 disp(ix)
11
12 P=i*i*10000 //wrongly done in the book as ix*ix
13     *10000
14 disp(P)
```

Scilab code Exa 2.39 Problem39

```
1 function p=parallel(r1,r2)
2     p=r1*r2/(r1+r2)
3 endfunction
4
5 R1=parallel(1,3)
6
7 //convert current source to voltage
8 V=20/1000*2000
9 I=(40-8)/(2+0.75)
10
11 Pr=8*I
12 disp(Pr)
```

Scilab code Exa 2.40 Problem40

```

1 function p=parallel(r1,r2)
2     p=r1*r2/(r1+r2)
3 endfunction
4
5 I1=12/1000
6 Ix=I1*30/(30+60)
7 disp(Ix)
8
9 I2=20/1000
10 V2=I2*(10+5)
11 R1=10+parallel(30,60)
12 I1=V2/R1
13 Ix=I1*30/(30+60)
14 disp(Ix) //Wrongly printed in the book as 10
15
16 Ix=6/1000
17 I1=(30+60)/30*Ix
18 V2=I1*R1
19 I2=V2/15
20 disp(I2)
21
22 Is=45
23 I1=45*(10+5)/(10+5+R1)
24 Ix=I1*30/(30+60)
25 disp(Ix) ///Answer is wrong in the book

```

Chapter 3

Fundamentals of Reactive Circuits

Scilab code Exa 3.1 Problem1

```
1 function C=seriesC(C1,C2)
2     C=C1*C2/(C1+C2)
3 endfunction
4
5 Ceq1=10+seriesC(10,10)
6 Ceq2=Ceq1
7
8 Ceq=seriesC(seriesC(Ceq1,Ceq2),10)
9 disp(Ceq)
```

Scilab code Exa 3.2 Problem2

```
1 function p=parallel(r1,r2)
2     p=r1*r2/(r1+r2)
3 endfunction
4
```

```
5 Leq=1+parallel(2,2)+parallel(parallel(3,3),3)
6
7 disp(Leq)
```

Scilab code Exa 3.3 Problem3

```
1 function C=seriesC(C1,C2)
2     C=C1*C2/(C1+C2)
3 endfunction
4
5 V=100
6
7 Cp=1+2
8 Ceq=seriesC(Cp,6)
9 q=Ceq*V
10
11 q1=q*(1/(1+2))
12 q2=q-q1
13
14 disp(q2,q1,q)
15
16 E6=q*q/2/6/1000
17 E1=q1*q1/2/1/1000
18 E2=q2*q2/2/2/1000
19 Enet=E1+E2+E6
20
21 disp(Enet,E6,E2,E1)
```

Scilab code Exa 3.4 Problem4

```
1 L=poly([3,-4,1],"L","coeff")
2 disp(roots(L))
```

Scilab code Exa 3.5 Problem5

```
1 function C=seriesC(C1,C2)
2     C=C1*C2/(C1+C2)
3 endfunction
4
5 Ceq=1+seriesC(6,3)
6
7 disp(Ceq)
```

Scilab code Exa 3.6 Problem6

```
1 function p=parallel(r1,r2)
2     p=r1*r2/(r1+r2)
3 endfunction
4
5 Lbc=parallel(1/10,1/20)
6 Leq=1/50+Lbc
7 disp(Leq)
8
9 Vbc=Lbc*150
10 disp(Vbc)
```

Scilab code Exa 3.7 Problem7

```
1 function C=seriesC(C1,C2)
2     C=C1*C2/(C1+C2)
3 endfunction
4
```

```
5 Ceq=seriesC(seriesC(10,20),40)
6 disp(Ceq)
7
8 q=Ceq*280
9 disp(q)
10
11 V1=q/10
12 V2=q/20
13 V3=q/40
14
15 disp(V3,V2,V1)
```

Scilab code Exa 3.8 Problem8

```
1 Ceq=10+20+40
2 Q=200*[10,20,40]
3
4 disp(Q)
5 Qnet=Q(1)+Q(2)+Q(3)
6 disp(Qnet)
```

Scilab code Exa 3.9 Problem9

```
1 //deactivate all independent sources
2
3 function p=parallel(r1,r2)
4     p=r1*r2/(r1+r2)
5 endfunction
6
7 L=2
8 Req=parallel(6,12)+4
9 T1=L/Req
10 disp(T1)
```

```
11
12 C=1/2
13 Req=2+parallel(6,12)+2
14 T2=Req*C
15 disp(T2)
```

Scilab code Exa 3.11 Problem11

```
1 L=2
2
3 VL_0minus=0 //steady state
4 disp(VL_0minus)
5
6 i_0minus=1
7 i_0plus=i_0minus
8 VL_0plus=12-4*i_0plus
9 disp(VL_0plus)
10
11 di_by_dt_0plus=VL_0plus/L
12 disp(di_by_dt_0plus)
```

Scilab code Exa 3.12 Problem12

```
1 Vc_0m=100
2 Vc_0p=Vc_0m
3 T=(400+100)*2E-6
4 i_0p=100/500
5 P_0p=i_0p^2*400
6 disp(P_0p)
```

Scilab code Exa 3.13 Problem13

```
1 Vc_0m=10
2 Vc_0p=Vc_0m
3 disp(Vc_0p)
4
5 //KVL
6 i1_0p=(10-Vc_0p)/20
7 i2_0p=Vc_0p/20
8
9 //KCL
10 iC_0p=i1_0p-i2_0p
11 disp(iC_0p)
12 iC_inf=0 //capacitor is open circuit
13 disp(iC_inf)
14 VC_inf=10*20/(20+20)
15 disp(VC_inf)
```

Scilab code Exa 3.16 Problem16

```
1 L=0.25
2 R=250
3 V=10
4 T=L/R
5
6 t=0.5E-3
7 i=V/R*(1-exp(-t/T))
8 disp(i)
9
10 t=2E-3
11 i=V/R*((exp((1E-3-t)/T)-exp(-t/T)))
12 disp(i)
```

Scilab code Exa 3.18 Problem18

```
1 R=5000
2 C=1.0E-6
3 Ie=1/1000
4 Vcf=Ie*R
5 T=R*C
6
7 t=10/1000
8 Vc10=Vcf*(1-exp(-t/T))
9 disp(Vc10)
10
11 t=20/1000
12 Vc20=Vcf*(1-exp(-t/T))-Vc10
13 disp(Vc20)
```

Scilab code Exa 3.21 Problem21

```
1 //Replace curr source by voltage source
2 Ics=1/1000
3 R=100*1000
4 V=Ics*R
5
6 Vc_0m=25/(25+100)*V
7 disp(Vc_0m)
8
9 Vc_0p=Vc_0m
10 disp(Vc_0p)
11
12 Vc_inf=(V-10)*25/(100+25)
13 disp(Vc_inf)
```

Scilab code Exa 3.22 Problem22

```

1 L=20/1000
2 VR2_0p=10
3 VR2_inf=0
4 VR2_1=5
5
6 t=1/1000
7 T=-t/log((VR2_1-VR2_inf)/(VR2_0p-VR2_inf))
8
9 R2=L/T
10 R1=1/(2/VR2_0p-1/R2)
11
12 disp(R2,R1)

```

Scilab code Exa 3.24 Problem24

```

1 C=1/4
2 Vc_0m=12/(12+6)*12
3 Vc_0p=8
4 disp(Vc_0p)
5 t=0
6 V_0p=6*cos(t)
7
8 //at t=0+
9 Vth=12/(12+6)*6
10 Rth=6*12/(6+12)
11 ic_0p=(Vth-8)/Rth
12 disp(ic_0p)
13 d_by_dt_Vc_0p=ic_0p/C
14 disp(d_by_dt_Vc_0p)

```

Scilab code Exa 3.26 Problem26

```

1 //at t=0-

```

```
2 iL=4
3 v=0
4 disp(v,iL)
5
6 //at t=0+
7 iL=4
8 v=-4*20
9 disp(v,iL)
```

Scilab code Exa 3.27 Problem27

```
1 function p=parallel(r1,r2)
2     p=r1*r2/(r1+r2)
3 endfunction
4
5 L=25/1000
6
7 //at t=0-
8 R1=parallel(150,75)
9 iL_0m=30/2
10 disp(iL_0m)
11
12 R2=parallel(150,50)
13 ix_0m=R2/(R2+75)*30
14 disp(ix_0m)
15
16
17 //at t=0+
18 iL_0p=iL_0m
19
20 T=L/(75+50)
21 iL_inf=0
22
23 //at t=0.2ms
24 t=0.2E-3
```

```
25
26 iL=iL_inf+(iL_0p-iL_inf)*exp(-t/T)
27 ix=-iL
28 disp(ix,iL)
```

Scilab code Exa 3.29 Problem29

```
1 R=250
2 C=25E-3
3
4 //at t=0-
5 v_0m=200*0.2
6
7 //at t=0+
8 v_0p=v_0m
9
10 T=R*C
11 v_inf=0
12
13 //at t=0.2ms
14 t=0.2E-3
15
16 t=T*log((v_0p-v_inf)/(20-v_inf))
17 disp(t)
```

Scilab code Exa 3.32 Problem32

```
1 L=0.2
2 R=50+30
3
4 iL_0m=100/50
5 iL_0p=iL_0m
6 iL_inf=0
```

```

7 T=L/R
8
9 t=10/1000
10 iL_10=iL_0p*exp(-t/T)
11 disp(iL_10)
12
13 t1=-T*log(0.5*iL_0p/(iL_0p))
14 disp(t1)

```

Scilab code Exa 3.33 Problem33

```

1 R=5
2 L=2
3 V=10
4 T=L/R
5
6 iL_m=V/R
7 disp(iL_m)
8 iL_0p=iL_m
9 iL_inf=2+V/R
10
11 //function I=iL(t)
12 //      I=iL_inf+(iL_0p-iL_inf)*exp(-t/T)
13 //endfunction
14
15 //disp(iL(0.5))
16 //disp(iL(1.5))
17
18 t=0.5
19 I=iL_inf+(iL_0p-iL_inf)*exp(-t/T)
20 disp(I)
21
22 t=1.5
23 I=iL_inf+(iL_0p-iL_inf)*exp(-t/T)
24 disp(I)

```

Scilab code Exa 3.36 Problem36

```
1 L=4/1000
2 R=1000
3 V=9
4
5 iL_0m=V/(2*R)
6 iL_0p=iL_0m
7 iL_inf=0
8 isw_inf=V/R
9 T=L/R
10
11 t=5E-6
12
13 iL_5=iL_0p*exp(-t/T)
14 disp(iL_5)
15
16 isw_5=isw_inf*(1-exp(-t/T))
17 disp(isw_5)
```

Scilab code Exa 3.37.38 Problem37 and 38

```
1 R=20
2 L=2
3 C=1/25
4
5 //at t=0-
6 iR=-4
7 iL=4
8 iC=0
9 vR=-R*4
```

```

10 vC=-vR
11 vL=0
12
13 disp(iR,iL,iC,vR,vL,vC)
14
15 //at t=0+
16 iL=iL
17 vC=vC
18 iR=5-4 //KCL at node 1
19 vR=R*iR
20 iC=4+iR //KCL at node 2
21 vL=vC+vR //KVL inner mesh
22
23 disp(iR,iL,iC,vR,vL,vC)
24
25
26 //at t=0+ derivatives are
27 DiL=vL/L
28 DvC=iC/C
29 DiR=-DiL //Differentiating KCL at node 1
30 DiC=DiR //Differentiating KCL at node 2
31 DvR=R*DiR
32 DvL=DvR+DvC //Differentiating KVL inner mesh
33
34 disp(DiR,DiL,DiC,DvR,DvL,DvC)

```

Chapter 4

Steady State Analysis For Sinusoidal Excitation

Scilab code Exa 4.1 Problem1

```
1 Iav=1/(2*%pi)*integrate('20*sin(wt)', 'wt', %pi/3, %pi)
2 disp(Iav)
3
4 Irms=sqrt(1/(2*%pi)*integrate('(20*sin(wt))^2', 'wt',
   %pi/3, %pi))
5 disp(Irms)
```

Scilab code Exa 4.2 Problem2

```
1 Iav_by_Im=1/%pi*integrate('sin(wt)', 'wt', 0, %pi)
2 disp(Iav_by_Im)
3
4 //final answer is wrong in the book
```

Scilab code Exa 4.4 Problem4

```
1  ////////////////////////////////////part a
2  L=0.05
3  R=20
4  w=1.2E3
5  Xl=w*L
6  V=complex(100,200)
7  I=complex(5,0)
8
9  Xc=-imult(R+imult(Xl)-V/I)
10 C=1/w/Xc
11
12 disp(C)
13
14 ////////////////////////////////////part b
15 w=200
16 V=complex(100,0)
17 Xl=w*L
18 Xc=-imult(R+imult(Xl)-V/I)
19 C=1/w/Xc
20
21 disp(C)
```

Scilab code Exa 4.5 Problem5

```
1  L=0.0255
2  R1=6
3  V=240
4  f=50
5  w=2*%pi*f
6  Va=sqrt(V^2/10)
7  Vb=3*Va
8  Xl=w*L
9  Theta1=atan(Xl/R1)
```

```

10 Theta2=%pi/2-Theta1 //Va and Vb are in quadrature
11
12 I=Vb/sqrt(R1^2+X1^2)
13
14 R=(Va/I)/sqrt(1+tan(Theta2)^2)
15 disp(R)
16
17 Xc=R*tan(Theta2)
18 C=1/w/Xc
19 disp(C)

```

Scilab code Exa 4.6 Problem6

```

1 Z1=complex(10,15)
2 Z2=complex(6,-8)
3
4 I=complex(15,0)
5 I1=I*Z2/(Z1+Z2)
6 I2=I*Z1/(Z1+Z2)
7 phase=[atan(imag(I1)/real(I1));atan(imag(I2)/real(I2
    ))]
8 disp(phase*180/%pi)
9
10 V=I1*Z1
11 disp(180/%pi*atan(imag(V)/real(V)))

```

Scilab code Exa 4.7 Problem7

```

1 function [r,theta]=cart_to_polar(z)
2     x=real(z)
3     y=imag(z)
4     r=norm(z)
5     theta=atan(y/x)

```

```

6  endfunction
7
8  function Zeq=parallel(Z1,Z2)
9      Zeq=Z1*Z2/(Z1+Z2)
10 endfunction
11
12 w=400
13 R=10
14 L=25E-3
15 C=250E-6
16 Xl=w*L*%i
17 Xc=1/(w*C*%i)
18
19 ////////////////part a
20 Zin1=R+Xc
21 [r1,theta1]=cart_to_polar(Zin1)
22 disp(theta1*180/%pi,r1)
23
24 ////////////////part b
25 //Zin2=10+parallel(Xc,Xl)    ///impedence is infinite
    ...thus an error
26 //[r2,theta2]=cart_to_polar(Zin2)
27 disp(90,"    inf")
28
29
30 ////////////////part c
31 Zin3=R+parallel(Xc,Xl+10)
32 [r3,theta3]=cart_to_polar(Zin3)
33 disp(theta3*180/%pi,r3)

```

Scilab code Exa 4.8 Problem8

```

1  function [r,theta]=cart_to_polar(z)
2      x=real(z)
3      y=imag(z)

```

```

4     r=norm(z)
5     theta=atan(y/x)
6 endfunction
7
8 function [x,y]=polar_to_cart(zpolar)
9     r=real(zpolar)
10    theta=imag(zpolar)/180*%pi
11    x=r*cos(theta)
12    y=r*sin(theta)
13 endfunction
14
15 function Zeq=parallel(Z1,Z2)
16     Zeq=Z1*Z2/(Z1+Z2)
17 endfunction
18
19 R=200
20 L=0.5
21 C=50E-6
22 w=200
23
24 Xl=w*L*%i
25 Xc=1/(w*C*%i)
26
27 ////////////////////////////////////part a
28 Ir=complex(0.02*cos(30*%pi/180),0.02*sin(30*%pi/180)
29 )
29 V=Ir*R
30 Il=V/Xl
31 Ic=V/Xc
32 I=Ir+Il+Ic
33 disp(I)
34
35 ////////////////////////////////////part b
36 [Ix,Iy]=polar_to_cart(complex(2,-40))
37 I=complex(Ix,Iy)
38 Zin=parallel(parallel(R,Xc),Xl)
39 V=Zin*I
40 Ir=V/R

```

```
41 disp(V, Ir)
```

Scilab code Exa 4.9 Problem9

```
1 p=poly([0,2,0,-8], "w", "coeff")
2 w=roots(p)
3 disp(w(1))
```

Scilab code Exa 4.10 Problem10

```
1 function Zeq=parallel(Z1,Z2)
2     Zeq=Z1*Z2/(Z1+Z2)
3 endfunction
4
5 Zeq=parallel(5,3-imult(6))
6 I=complex(10,0)
7 V=Zeq*I
8 pf=cos(atan(imag(V)/real(V)))
9 P=norm(V)*norm(I)*pf
10 disp(pf,P)
```

Scilab code Exa 4.11 Problem11

```
1 P1=8000
2 pf1=0.8
3 V1=430
4
5 I1=P1/V1/pf1
6 Pr1=P1-I1^2*1
7 Q1=P1*tan(acos(pf1))
```

```

8  Qr1=Q1-I1^2*1.2
9  Sr1=sqrt(Pr1^2+Qr1^2)
10
11 V1=Sr1/I1
12 P1=15000
13 Q1=P1*tan(acos(0.8))
14 Pr2=P1-Pr1
15 Qr2=Q1-Qr1
16 Sr2=sqrt(Pr2^2+Qr2^2)
17
18 I2=Sr2/V1
19 P2=Pr2+I2^2*0.7
20 Q2=Qr2+I2^2*0.9
21
22 pf=cos(atan(Q2/P2))
23 S2=sqrt(P2^2+Q2^2)
24 V2=S2/I2
25
26 disp(V2, pf, P2, Q2, Q1, V1)

```

Scilab code Exa 4.12 Problem12

```

1  V=231
2  f=50
3  w=2*%pi*f
4  S1=10
5  pf=0.8
6  P1=S1*pf
7  Q1=S1*sin(acos(pf))
8  Qc=Q1-tan(acos(0.95))*P1
9
10 C=Qc*1000/V^2/w
11
12 Is1=10*1000/V
13 I1=Is1

```

```
14 Is2=norm(P1+%i*(Q1-Qc))*1000/V
15
16 disp(Is2,Is1,C,Qc)
```

Scilab code Exa 4.13 Problem13

```
1 function [x,y]=polar_to_cart(r,theta)
2     theta=theta/180*%pi
3     x=r*cos(theta)
4     y=r*sin(theta)
5 endfunction
6
7 //converting v source to curr source
8 V=15
9 R=5
10 I1=V/R
11
12
13 [Ix,Iy]=polar_to_cart(2,-30)
14 I2=complex(Ix,Iy)
15
16 //nodal analysis
17 A=[0.7-0.1*%i,-0.5;-0.5,0.5+0.5*%i]
18 V=inv(A)*[I1;I2]
19
20 [rv1,thetav1]=polar(V(1))
21 [rv2,thetav2]=polar(V(2))
22
23 disp(real(thetav2*180/%pi),rv2,real(thetav1*180/%pi)
    ,rv1)
```

Scilab code Exa 4.14 Problem14


```

1 w=600
2 R=10
3 L=10E-3
4 C=0.5E-3
5 Xl=w*L*%i
6 Xc=1/(w*C*%i) //Xc value in the book is wrong
7 V1=40
8 V2=complex(0,-30)
9
10 //mesh analysis
11 A=[R+Xl,-R;-R,R+Xc]
12 I=inv(A)*[V1;V2]
13
14 Ir=I(1)-I(2)
15 Vr=R*Ir
16
17 disp(Vr) //Final answer is different

```

Scilab code Exa 4.15 Problem15

```

1 Z1=complex(2,-1)
2 Z2=complex(0,-5)
3 Z3=complex(2,1)
4 I1=1
5 I2=complex(0,-2)
6
7 //deactivate curr source 2
8 V11=I1*(Z2+Z3)/(Z1+Z2+Z3)*Z1
9 V21=I1*Z1/(Z1+Z2+Z3)*Z3
10
11 //deactivate curr source 1
12 V12=I2*Z3*Z1/(Z1+Z2+Z3)
13 V22=I2*(Z1+Z2)/(Z1+Z2+Z3)*Z3
14
15 V1=V11+V12

```

```
16 V2=V21+V22
17
18 disp(V2,V1)
```

Scilab code Exa 4.16 Problem16

```
1 function [Ra,Rb,Rc]=delta_to_star(Rab,Rbc,Rca)
2     X=Rab+Rbc+Rca
3     Ra=Rab*Rca/X
4     Rb=Rab*Rbc/X
5     Rc=Rca*Rbc/X
6 endfunction
7
8 function Zeq=parallel(Z1,Z2)
9     Zeq=Z1*Z2/(Z1+Z2)
10 endfunction
11
12 V=20
13 w=2
14 R=1
15 C=1/2
16 Xc=1/(w*C*%i)
17 Zab=-%i
18 Zbc=2
19 Zca=2
20
21 [Za,Zb,Zc]=delta_to_star(Zab,Zbc,Zca)
22 Zth=Za+parallel(R+Zb,Xc+Zc)
23
24 Vdc=V*(Zc+Xc)/(R+Zb+Zc+Xc)
25 disp(Zth,Vdc)
26
27 Isc=Vdc/Zth
28 disp(Zth,Isc)
```

Scilab code Exa 4.17 Problem17

```
1 function Zeq=parallel(Z1,Z2)
2     Zeq=Z1*Z2/(Z1+Z2)
3 endfunction
4
5 V=20
6 Z1=complex(5,10)
7 Z2=complex(3,-4)
8
9 Vth=V*Z2/(Z1+Z2)
10 Zth=parallel(Z1,Z2)
11
12 //by maximum power transfer theorem
13 Zl=conj(Zth)
14 P=norm(Vth/(Zth+Zl))^2*real(Zl)
15 disp(P,Zl)
16
17 Rl=sqrt(real(Zth)^2+(4+imag(Zth))^2)
18 disp(Rl)
```

Scilab code Exa 4.18 Problem18

```
1 function [x,y]=polar_to_cart(r,theta)
2     theta=theta/180*%pi
3     x=r*cos(theta)
4     y=r*sin(theta)
5 endfunction
6
7 R1=1
8 R2=6
9 L=2
```

```

10 C=1/3
11
12 [Vx,Vy]=polar_to_cart(4,30)
13 [Ix,Iy]=polar_to_cart(0.8,-10)
14
15 //deactivate current source
16 V=complex(Vx,Vy)
17 w=3
18 Xl=w*L*i
19 Xc=1/(w*C*i)
20
21 I11=V/(R1+R2+Xl+Xc)
22 Pav1=norm(I11)^2*R1
23
24 //deactivate voltage source
25 I=complex(Ix,Iy)
26 w=5
27 Xl=w*L*i
28 Xc=1/(w*C*i)
29
30 I12=I*(R2+Xl)/(R2+Xl+R1+Xc)
31 Pav2=norm(I12)^2*R1
32
33 Pav=Pav1+Pav2
34 disp(Pav)

```

Scilab code Exa 4.21 Problem21

```

1 I=35
2 VR=25
3 Vr1=40
4 VRr1=50
5 Vc=45
6 C=50E-6
7 Xc=Vc/I

```

```

8 w=1/(Xc*C)
9
10 theta=acos((VR^2+VRr1^2-Vr1^2)/(2*VR*VRr1))
11 x=VRr1*cos(theta)-25
12 y=VRr1*sin(theta)
13
14 r=x/I
15 L=y/(I*w)
16 Vappl=sqrt((VR+x)^2+y^2)
17 R=VR/I
18
19 disp(L,r,R)

```

Scilab code Exa 4.22 Problem22

```

1 V=12
2 w=1000
3 R=4
4 L=5E-3
5 C=400E-6
6 Xl=w*L*%i
7 Xc=1/(w*C*%i)
8
9 //mesh analysis
10 A=[R+Xl,-Xl;2-Xl,Xl+Xc]
11 I=inv(A)*[12;0]
12
13 disp(I(1)) //answer is wrong in the book

```

Scilab code Exa 4.23 Problem23

```

1 function [x,y]=polar_to_cart(r,theta)
2     theta=theta/180*%pi

```

```

3     x=r*cos(theta)
4     y=r*sin(theta)
5 endfunction
6
7 [I1x,I1y]=polar_to_cart(2,10)
8 [I2x,I2y]=polar_to_cart(3,120)
9
10 I1=complex(I1x,I1y)
11 I2=complex(I2x,I2y)
12 w=4
13 R=2
14 L=3
15 C=1/4
16 Xl=w*L*%i
17 Xc=1/(w*C*%i)
18
19 //deactivate source 2
20 i1=(R+Xl)/(R+Xl+Xc)*I1
21 i2=1/(R+Xl+Xc)*I2
22 i=i1+i2
23 disp(i) //answer is wrong in the book

```

Scilab code Exa 4.24 Problem24

```

1 V=230
2 w=2*%pi*50
3 R=8
4 L=0.1
5 C=160E-6
6
7 Xl=w*L*%i
8 disp(Xl)
9
10 Xc=1/(w*C*%i)
11 disp(Xc)

```

```

12
13 Z=norm(R+Xl+Xc)
14 disp(Z)
15 I=V/Z
16 disp(I)
17 pf=cos(atan(norm(Xl+Xc)/R))
18 disp(pf)
19
20 Vcoil=I*norm(R+Xl)
21 Vc=norm(I*Xc)
22 disp(Vc,Vcoil)

```

Scilab code Exa 4.25 Problem25

```

1 function Zeq=parallel(Z1,Z2)
2     Zeq=Z1*Z2/(Z1+Z2)
3 endfunction
4
5 V=100
6 Z1=complex(0,-5)
7 Z2=complex(5,0)
8 Z3=complex(0,5)
9 I=[0,0,0]
10
11 Z=Z1+parallel(Z2,Z3)
12 I(1)=V/Z
13
14 I(2)=Z3/(Z2+Z3)*I(1)
15 I(3)=Z2/(Z2+Z3)*I(1)
16
17 disp(I)

```

Scilab code Exa 4.26 Problem26

```

1 function Zeq=parallel(Z1,Z2)
2     Zeq=Z1*Z2/(Z1+Z2)
3 endfunction
4
5 //converting curr source to v source
6 I=0.4
7 R1=15
8 V=I*R1
9 w=400
10
11 R2=5
12 R3=80
13 L=25E-3
14 Xl=w*L*%i
15
16 Zeq=R1+R2+parallel(R3,Xl)
17 I=V/Zeq
18 I1=I*R3/(R3+Xl)
19 Ix=I*Xl/(R3+Xl)
20
21 disp(I1,Ix)

```

Scilab code Exa 4.27 Problem27

```

1 V=4
2 w=2
3
4 R=4
5 L=2
6 Xl=w*L*%i
7
8 I1=V/(Xl+R)
9 Xc=-V/imag(I1)
10 C=1/(w*Xc)
11 disp(C)

```

Scilab code Exa 4.28 Problem28

```
1 function [x,y]=polar_to_cart(r,theta)
2     theta=theta/180*%pi
3     x=r*cos(theta)
4     y=r*sin(theta)
5 endfunction
6
7 I=4
8 w=500
9 [Ir,Ic]=polar_to_cart(3,40)
10 Ix=complex(Ir,Ic)
11 C=1E-3
12 L=10E-3
13 Xl=w*L*%i
14 Xc=1/(w*C*%i)
15
16 Il=I-Ix
17 Ic=Ix
18 Vc=Ic*Xc
19 Vl=Il*Xl
20 Vx=Vl-Vc
21 disp(Vx) //answer wrong in the book
```

Scilab code Exa 4.29 Problem29

```
1 w=10
2 R=2
3 L=0.3
4 Ir=10*(cos(%pi/4)+%i*sin(%pi/4))
5 Vr=Ir*R
```

```

6 Vc=20*(cos(%pi/4)-%i*sin(%pi/4))
7 V=Vr+Vc
8 Ic=Ir
9 C=Ic/(w*Vc*%i)
10 disp(real(C))          //////////Wrong in book

```

Scilab code Exa 4.30 Problem30

```

1 R=2000
2 C=5E-6
3 w=1000
4
5 Xc=1/(w*C*%i)
6 Y=1/R+1/Xc
7 Z=1/Y
8 Req=real(Z)
9 Ceq=-1/(imag(Z)*w)
10
11 disp(Ceq*1E6,Req)     //////////Answer wrong in the book

```

Scilab code Exa 4.31 Problem31

```

1 I=10*(cos(%pi/180*37)-%i*sin(%pi/180*37))
2 V=6
3 C=250E-6
4 w=1000
5 Xc=1/(w*C*%i)
6
7 Ic=V/Xc
8 disp(Ic)
9
10 Ix=imag(I-Ic)
11 X=abs(V/Ix)

```

```
12 Ir=real(I-Ic)
13 R=V/Ir
14
15 disp(R,X)
```

Scilab code Exa 4.32 Problem32

```
1 V1=30+10*%i
2 V2=30
3 w=1000
4 L=1
5 C1=1E-6
6 C2=1E-6
7 R1=1000
8 R2=1000
9
10 Xl=%i*w*L
11 Xc1=%i/(w*C1)
12 Xc2=%i/(w*C2)
13
14 ///////////mesh equations
15
16 A=[1,%i; %i,1-2*%i]
17 I=inv(A)*[10*%i;30]
18
19 Ic1=I(1)-I(2)
20
21 disp(Ic1)
```

Scilab code Exa 4.33 Problem33

```
1 function [x,y]=polar_to_cart(r,theta)
2     theta=theta/180*%pi
```

```

3     x=r*cos(theta)
4     y=r*sin(theta)
5 endfunction
6
7 [Ir,Ic]=polar_to_cart(3,30)
8 I=complex(Ir,Ic)
9 Zc=-5*i
10 Zr1=10+5*i
11
12 Ic=Zr1/(Zc+Zr1)*I
13 Vth=Ic*Zc
14 Zth=parallel(Zc,Zr1)
15 In=Vth/Zth
16
17 disp(Rth,In,Vth)

```

Scilab code Exa 4.34 Problem34

```

1 function [x,y]=polar_to_cart(r,theta)
2     theta=theta/180*pi
3     x=r*cos(theta)
4     y=r*sin(theta)
5 endfunction
6
7 [Ir,Ic]=polar_to_cart(2,10)
8 I1=complex(Ir,Ic)
9 [Ir,Ic]=polar_to_cart(3,90+30)
10 I2=complex(Ir,Ic)
11
12 w=4
13 R=2
14 L=0.5
15 C=1/4
16 Xl=w*L*i
17 Xc=1/(w*C*i)

```

```

18
19 //deactivate voltage source
20 i1=I1*(R+Xl)/(R+Xl+Xc)
21
22 //deactivate curr source
23 i2=I2/(R+Xl+Xc)
24
25 i=i1+i2
26 disp(i)

```

Scilab code Exa 4.35 Problem35

```

1 function Zeq=parallel(Z1,Z2)
2     Zeq=Z1*Z2/(Z1+Z2)
3 endfunction
4
5 I=10
6 w=2000
7 R=200
8 L=0.125
9
10 Xl=w*L*%i
11
12 Zeq=parallel(R,Xl)
13 V=I*Zeq
14 I1=V/Xl
15 Ir=V/R
16
17 t=1/1000
18 I1=sqrt(2)*real(I*exp(%i*w*t))
19 I11=sqrt(2)*real(I1*exp(%i*w*t))
20 Ir1=sqrt(2)*real(Ir*exp(%i*w*t))
21 V1=sqrt(2)*real(V*exp(%i*w*t))
22
23 Ps=-V1*I1

```

```
24 Pr=-V1*Ir1
25 Pl=-V1*I11
26
27 disp(Pl,Pr,Ps)
```

Scilab code Exa 4.36 Problem36

```
1 function [x,y]=polar_to_cart(r,theta)
2     theta=theta/180*%pi
3     x=r*cos(theta)
4     y=r*sin(theta)
5 endfunction
6
7 [Vr,Vc]=polar_to_cart(120,45)
8 V=complex(Vr,Vc)
9
10 [Zr,Zc]=polar_to_cart(16.3,24.5)
11 Z=complex(Zr,Zc)
12
13 w=50
14
15 I=V/Z
16 P=V*conj(I)
17 Pavg=real(P)
18 pf=real((V/I)/norm(V/I))
19
20 disp(pf,Pavg)
```

Scilab code Exa 4.37 Problem37

```
1 function Zeq=parallel(Z1,Z2)
2     Zeq=Z1*Z2/(Z1+Z2)
3 endfunction
```

```

4
5 function [x,y]=polar_to_cart(r,theta)
6     theta=theta/180*%pi
7     x=r*cos(theta)
8     y=r*sin(theta)
9 endfunction
10
11 [Ir,Ic]=polar_to_cart(20,60)
12 I=complex(Ir,Ic)
13
14 w=5000
15 R=3000
16 L=1
17 C=0.25E-6
18 Xl=w*L*%i
19 Xc=1/(w*C*%i)
20
21 Z=parallel(R+Xl,Xc)
22 V=I*Z
23 disp(V)

```

Scilab code Exa 4.38 Problem38

```

1 function Zeq=parallel(Z1,Z2)
2     Zeq=Z1*Z2/(Z1+Z2)
3 endfunction
4
5 V=5
6 w=5
7 R=2
8 L1=0.8
9 L2=1
10 C=1/5
11 Xl1=w*L1*%i
12 Xl2=w*L2*%i

```

```

13 Xc=1/(w*C*%i)
14
15 Vth=R/(R+Xl2)*V
16 Zth=Xc+parallel(Xl2,R)
17 disp(Zth,Vth)
18
19 I=Vth/(Zth+Xl1)
20 Vl=I*Xl1
21 S=Vl*conj(I)/2
22 disp(S)

```

Scilab code Exa 4.39 Problem39

```

1 Pm=600
2 Vm=sqrt(3*Pm)
3 f=15.36E6
4 w=2*%pi*f
5 t=20.3E-3
6 theta=%pi/2-modulo(w*t,2*%pi)
7
8 disp(theta*180/%pi)

```

Scilab code Exa 4.40 Problem40

```

1 V=240
2 w=100*%pi
3 R=6
4
5 Vr=120
6 I=Vr/R
7
8 t=(205/I)^2          //t=r^2+Xl^2

```



```

9 r=((240/I)^2-t-R*R)/2/R           ///this part solved
   wrong in the book
10 Xl=sqrt(t-r*r)
11 Z=sqrt(t)
12 disp(r)
13 disp(Xl)
14 disp(Z)
15
16 Pl_choke=I*I*r
17 disp(Pl_choke)
18 pf=Pl_choke/205/20
19 disp(pf)

```

Scilab code Exa 4.41 Problem41

```

1 w=2
2 L=1
3 C=0.5
4 Xl=w*L*%i
5 Xc=1/(w*C*%i)
6
7 V=1
8 I=V/(1+%i)
9 Y=I/V
10 R=1/real(Y)
11
12 disp(R, Y)

```

Scilab code Exa 4.42 Problem42

```

1 w=400
2 R=5
3 L=25E-3

```

```

4 C=1.25E-3
5 Xl=w*L*%i
6 Xc=1/(w*C*%i)
7
8 Z=R+Xl+Xc
9 Y=1/Z
10 C=-imag(Y)/w
11 Yn=real(Y)
12 Rn=1/Y
13
14 disp(C)

```

Scilab code Exa 4.43 Problem43

```

1 function Zeq=parallel(Z1,Z2)
2     Zeq=Z1*Z2/(Z1+Z2)
3 endfunction
4
5 w=800
6 R1=10
7 R2=20
8 L=0.05
9 C=0.25E-3
10 Xl=w*L*%i
11 Xc=1/(w*C*%i)
12
13 Zeq1=R2+parallel(Xc,R1+Xl)
14 Zeq2=parallel(parallel(R1,R2)+Xc,Xl)
15
16 disp(Zeq2,Zeq1)

```

Scilab code Exa 4.44 Problem44

```

1 pf=0.707
2 theta=acos(pf)
3 P=200
4 Q=tan(theta)*P
5 pf2=0.85
6 theta_n=acos(pf2)
7 Qn=Q*tan(theta_n)
8 Qc=Q-Qn
9
10 w=314
11 V=2000
12 C=Qc/(V*V*w)
13
14 disp(C)

```

Scilab code Exa 4.45 Problem45

```

1 I=20
2 w=2000
3 R=200
4 L=0.25
5 Xl=w*L*%i
6
7 Ir=I*Xl/(Xl+R)
8 Il=I-Ir
9 Vl=Xl*Il
10
11 t=1E-3
12 ir=sqrt(2)*real(Ir*exp(%i*w*t))
13 il=sqrt(2)*real(Il*exp(%i*w*t))
14 vl=sqrt(2)*real(Vl*exp(%i*w*t))
15 is=sqrt(2)*real(I*exp(%i*w*t))
16 vs=vl
17
18 Pr=ir*ir*R

```

```
19 P1=v1*il
20 Ps=is*ir*R
21 Pr=ir*v1
22
23 disp(Ps ,P1 ,Pr)
```

Scilab code Exa 4.46 Problem46

```
1 V1=1
2 w=2
3 R=1
4 r=1/2
5 L=0.5
6 C=1
7 Xl=w*L*%i
8 Xc=1/(w*C*%i)
9
10 I1=V1/X1
11 VR=I1*R
12 Vs=V1+VR
13
14 Vr=Vs
15 Ir=Vr/r
16 Ic=Vs/Xc
17 Is=Ir+Ic+I1
18
19 PR=-VR*VR/R
20 Pr=-Vr*Vr/r
21 Ps=Vs*conj(Is)
22
23 disp(real(Ps) ,Pr ,PR)
```

Scilab code Exa 4.47 Problem47

```

1 V=10*%i
2 w=1000
3 R=2
4 L=2E-3
5 C=500E-6
6 Xl=w*L*%i
7 Xc=1/(w*C*%i)
8
9 Zeq=Xl+Xc+parallel(R,Xl)
10 disp(Zeq)
11
12 I=V/Z
13 Ir=I*Xl/(R+Xl)
14 Il2=I-Ir
15 Vl=I*Xl
16 Vc=I*Xc
17
18 disp(I,Ir,Il2,Vl,Vc)

```

Scilab code Exa 4.48 Problem48

```

1 function [x,y]=polar_to_cart(r,theta)
2     theta=theta/180*%pi
3     x=r*cos(theta)
4     y=r*sin(theta)
5 endfunction
6
7 [Vr,Vc]=polar_to_cart(100,120)
8 V1=complex(Vr,Vc)
9
10 I=10
11 w=5000
12 R=10000
13 L=2.4E-3
14 C=0.05E-3

```

```

15
16
17 [Vr,Vc]=polar_to_cart(96,60)
18 V1=complex(Vr,Vc)
19
20 Xl=w*L*%i
21 Xc=1/(w*C*%i)
22
23 I1=V1/Xl
24 Ic=I-I1
25 V2=(R+Xc)*Ic+V1
26 V3=V2-V1
27 V1=Ic*Xc
28
29 disp(V1,V2,V3)

```

Scilab code Exa 4.49 Problem49

```

1 function Zeq=parallel(Z1,Z2)
2     Zeq=Z1*Z2/(Z1+Z2)
3 endfunction
4
5 ////////////////short AB
6 Vab=0
7 Isc=50/4
8
9 ////////////////for Zn
10 Zn=parallel(4,8*%i)
11
12 disp(Isc,Zn)

```

Scilab code Exa 4.50 Problem50

```

1 function Zeq=parallel(Z1,Z2)
2     Zeq=Z1*Z2/(Z1+Z2)
3 endfunction
4
5 V=12*i
6
7 Vth=4-12*i/(4-12*i+6+9*i)*V
8 Zth=parallel(4-12*i,6+9*i)
9
10 I=Vth/(Zth+6+12*i)
11 S=V*conj(I)
12 disp(S)
13
14 Z1=conj(Zth)
15 I=Vth/(Zth+Z1)
16 S=V*conj(I)
17 disp(Zth,S)

```

Scilab code Exa 4.51 Problem51

```

1 function Zeq=parallel(Z1,Z2)
2     Zeq=Z1*Z2/(Z1+Z2)
3 endfunction
4
5 I=5
6
7 Zth=parallel(40,30*i)
8 Z1=conj(Zth)
9 Vth=Zth*I
10 Z=Zth+Z1
11 I1=Vth/Z
12 Pmax=abs(I1*I1*real(Z1))
13
14 disp(Zth,Pmax)

```

Scilab code Exa 4.52 Problem52

```
1 V=4*sqrt(2)
2 w=2
3 R=4
4 L=2
5 Xl=w*L*%i
6
7 I1=V/(R+Xl)
8 Ic=-imag(I1)*%i
9 C=Ic/(V*%i*w)
10
11 disp(C)
```

Chapter 5

Frequency Response

Scilab code Exa 5.1 Problem1

```
1 Q0=200
2
3 //a
4 R=1
5 C=2E-6
6 L=C/(Q0/R)^2
7 disp(L)
8
9 L=2E-15
10 C=1.2E-9
11 R=Q0*sqrt(L/C)
12 disp(R)
13
14 R=118500
15 L=120E-12
16 C=L*(Q0/R)^2
17 disp(C)
```

Scilab code Exa 5.2 Problem2

```
1 R=1000
2 C=49E-6
3 L=13E-3
4
5 w0=1/sqrt(L*C)
6 Q0=w0*R*C
7
8 disp(Q0,w0)
```

Scilab code Exa 5.3 Problem3

```
1 R=5
2 C=0.08E-6
3 L=5E-3
4
5 w0=1/sqrt(L*C)
6 f0=w0/2/%pi
7 Q0=w0*L/R
8 bandwidth=w0/Q0
9 wb=bandwidth
10 w=[w0-1/2*wb,w0+1/2*wb]
11
12 disp(w(2),w(1))
```

Scilab code Exa 5.4 Problem4

```
1 L=40E-6
2 R=4.02
3 f0=800E3
4
5 w0=2*%pi*f0
6 C=1/(w0*w0*L)
7 Q0=w0*L/R
```

```
8 fb=f0/Q0
9
10 Xl=w0*L*%i
11 Xc=1/(w0*C*%i)
12 Zin=R+Xl+Xc
13
14 disp(Zin,fb,C)
```

Scilab code Exa 5.5 Problem5

```
1 G=5E-6
2 L=2E-3
3 I=2E-3
4 w=5000
5
6 C=1/(w*w*L)
7 Vmax=I/G
8 Il=1
9 I=Il*w*L*G
10
11 disp(I,Vmax,C)
```

Scilab code Exa 5.6 Problem6

```
1 w0=1000
2 w2=1050
3 wb=2*(w2-w0)
4
5 Q0=w0/wb
6 disp(Q0)
```

Scilab code Exa 5.7 Problem7

```
1 w0=200E3
2 wb=5E3
3 L=2.5E-3
4 Q=65
5
6 Q0=w0/wb
7 r=w0*L/Q
8
9 disp(r)
```

Scilab code Exa 5.8 Problem8

```
1 C=12E-9
2 L=4E-3
3 R=5
4
5 w0=1/sqrt(L*C)
6
7 Vc=1.5
8 I=w0*C*Vc
9 Zi=R
10 Vi=R*I
11
12 disp(Vi , w0)
```

Scilab code Exa 5.9 Problem9

```
1 w0=2.5E6
2 Zin=60E3
3 Q0=80
4
```

```
5 R=60E3
6 C=Q0/(w0*R)
7 L=1/(C*w0*w0)
8
9 disp(C,L,R)
```

Scilab code Exa 5.10 Problem10

```
1 C=2.5E-6
2 R=8
3 wb=400
4
5 L=R/wb
6 w0=1/sqrt(L*C)
7 Q0=w0*L/R
8 w1=w0-wb/2
9 w2=w0+wb/2
10
11 disp(w2,w1,Q0,w0,L)
```

Scilab code Exa 5.11 Problem11

```
1 w=1E6
2 wb=1000
3 V=0.05
4 I=5E-3
5
6 R=V/I
7 Q0=w0/wb
8 L=R*Q0/w0
9 C=1/(w0*w0*L)
10 V1=w0*L*I
11 Vc=V1
```

```
12 w1=w0-wb/2
13 w2=w0+wb/2
14
15 disp(w2,w1,Vc,Vl,C,L,Q0,R)
```

Scilab code Exa 5.12 Problem12

```
1 R=1E6
2 L=1
3 C=1E-6
4 I=10E-6
5
6 w0=1/sqrt(L*C)
7 V=I*R
8
9 wb=1/(R*C)
10 Q0=w0/wb
11 w1=w0-wb/2
12 w2=w0+wb/2
13
14 disp(w2,w1,V,Q0,w0)
```

Scilab code Exa 5.13 Problem13

```
1 f0=1E6
2 Cmax=500E-12
3 C=450E-12
4 w0=2*%pi*f
5
6 L=1/(w0*w0*Cmax)
7
8 w=1/sqrt(L*C)
9 f=w/(2*%pi)
```

```
10 wb=2*2*%pi*(f-f0)
11 r=wb*L
12 Q0=2*%pi*f*L/r
13
14 disp(Q0,L,r)
15
16 //////////////calculation mistakes in book
```

Scilab code Exa 5.14 Problem14

```
1 R=10E3
2 L=50E-3
3 C=100E-6
4
5 w0=1/sqrt(L*C)
6 Q0=w0*R*C
7 alpha=w0/2/Q0
8 zeta=alpha/w0
9 wd=w0*sqrt(1-zeta^2)
10
11 disp(wd,zeta,alpha,Q0,w0)
12
13 //////////////calculation mistakes in the book
```

Scilab code Exa 5.15 Problem15

```
1 w0=1000
2 wd=997
3 Yin=1.2E-3
4
5 zeta=sqrt(1-(wd/w0)^2)
6 alpha=zeta*w0
7 R=1/Yin
```

```
8 C=1/(2*alpha*R)
9 L=1/(w0*w0*C)
10
11 disp(C,L,R)
```

Scilab code Exa 5.17 Problem17

```
1 I=1
2 w=400
3 R=500
4 L=1/40
5 C=250E-6
6 Xl=w*L*%i
7 Xc=1/(w*C*%i)
8
9 w0=1/sqrt(L*C)
10 //////////////at resonance
11 Ir=I
12 V=R*I
13 Il=V/Xl
14 Ic=V/Xc
15 Icir=abs(Il)
16 Ic+Il=0
17 Icl=Ic+Il
18
19 disp(Icl,Ic,Il,Ir)
```

Scilab code Exa 5.18 Problem18

```
1 V=100
2 R=10
3 L=2E-3
4 C=200E-6
```



```
5
6 w0=1/sqrt(L*C)
7 Xl=w0*L*i
8 Xc=1/(w0*C*i)
9 I=V/R
10
11 Vl=I*Xl
12 Vc=I*Xc
13 Vlc=Vl+Vc
14
15 disp(Vlc, Vc, Vl, I, w0)
```

Scilab code Exa 5.19 Problem19

```
1 R=1
2 L=10E-6
3 C=10E-12
4 V=10
5
6
7 w0=1/sqrt(L*C)
8 Xl=w0*L*i
9 Xc=1/(w0*C*i)
10
11 Q0=w0*L/R
12 Z=R*Q0*Q0
13 Iin=V/Z
14
15 Ic=V/Xc
16
17 disp(Ic, Iin, Z, Q0, w0)
```

Scilab code Exa 5.20 Problem20

```

1 V=200
2 R=2
3 L=0.02
4
5 f=25
6 w0=2*%pi*f
7 C=1/(w0*w0*L)
8 I=V/2
9 Vc=1/(C*w0)
10 disp(I,Vc)
11
12 f=50
13 w0=2*%pi*f
14 C=1/(w0*w0*L)
15 I=V/2
16 Vc=1/(C*w0)
17 disp(I,Vc)
18
19 f=100
20 w0=2*%pi*f
21 C=1/(w0*w0*L)
22 I=V/2
23 Vc=1/(C*w0)
24 disp(I,Vc)

```

Scilab code Exa 5.21 Problem21

```

1 R=10
2 L=0.1
3 C=150E-6
4
5 w=sqrt((1+R*R*C/L)/(L*C))
6 f=w/(2*%pi)
7
8 disp(f)

```

```
9 Req=R/(1-w*w*L*C+(w*R*C)^2)
10 disp(Req)
```

Scilab code Exa 5.22 Problem22

```
1 R=35
2 Q0=50
3 f1=540E3
4 f2=1610E3
5 w1=2*%pi*f1
6 w2=2*%pi*f2
7
8
9 L=1/(w1*(Q0/R))
10 Cmax=(Q0/R)^2*L
11 Cmin=1/(L*w2^2)
12
13 disp(Cmin*1000000,Cmax*1000000,L*1000000)
```

Scilab code Exa 5.28 Problem28

```
1 function [x,y]=polar_to_cart(r,theta)
2     theta=theta/180*%pi
3     x=r*cos(theta)
4     y=r*sin(theta)
5 endfunction
6
7 [Vr,Vc]=polar_to_cart(4,30)
8 V=complex(Vr,Vc)
9
10 [Ir,Ic]=polar_to_cart(0.8,-10)
11 I=complex(Ir,Ic)
12
```

```

13 wv=3
14 wi=5
15 R1=1
16 L=2
17 R6=6
18 C=1/3
19
20 //deactivating curr source
21 Xl=wv*L*%i
22 Xc=1/(wv*C*%i)
23 I11=V/(R1+R6+Xl+Xc)
24 Pav1=norm(I11)^2*R1
25
26 //deactivating voltage source
27 Xl=wi*L*%i
28 Xc=1/(wi*C*%i)
29 I12=I*(R6+Xl)/(R6+Xl+R1+Xc)
30 Pav2=norm(I12)^2*R1
31
32 Pav=Pav1+Pav2
33
34 disp(Pav)

```

Scilab code Exa 5.29 Problem29

```

1 L=10E-6
2 R=1
3 C=10E-9
4 V=10
5
6 Zmax=L/R/C
7 I=V/Zmax
8 w0=1/sqrt(L*C)
9 w=0.9*w0
10

```

```
11 Y=R*C/L+%i*(w*C-1/w/L)
12 I=norm(Y)*V
13
14 disp(I)
```

Chapter 6

Three Phase Circuits

Scilab code Exa 6.1 Problem1

```
1 function [x,y]=polar_to_cart(r,theta)
2     theta=theta/180*%pi
3     x=r*cos(theta)
4     y=r*sin(theta)
5 endfunction
6
7 omega=exp(%i*120/180*%pi)
8 Va=200
9 Vb=200/omega
10 Vc=200*omega
11
12 [Zr,Zc]=polar_to_cart(100,60)
13 Z=complex(Zr,Zc)
14
15 Ia=Va/Z
16 Ib=Vb/Z
17 Ic=Vc/Z
18
19 disp(Va,Vb,Vc,Ia,Ib,Ic)
```

Scilab code Exa 6.2 Problem2

```
1 V1=400
2 Vph=V1
3 pf=0.8
4
5 Pph=1500/3
6 Iph=Pph/Vph/pf
7 I1=sqrt(3)*Iph
8 theta=acos(0.8)
9 Iph=Iph*exp(%i*theta)
10 Zph=Vph/Iph
11
12 disp(Iph, I1, Zph)
```

Scilab code Exa 6.3 Problem3

```
1 V1=400
2 pf=0.8
3
4 Pph=1200/3
5 Vph=V1/sqrt(3)
6 Iph=Pph/Vph/pf
7 I1=Iph
8 theta=acos(0.8)
9 Zph=Vph/Iph*exp(%i*theta)
10
11 disp(I1, Iph, Zph)
```

Scilab code Exa 6.4 Problem4

```
1 function [x,y]=polar_to_cart(r,theta)
2     theta=theta/180*%pi
3     x=r*cos(theta)
4     y=r*sin(theta)
5 endfunction
6
7 V1=400
8 Vp=V1/sqrt(3)
9 disp(Vp)
10
11 [Ir,Ic]=polar_to_cart(50,-30)
12 I1=complex(Ir,Ic)
13 Ip=I1
14 Zy=Vp/I1
15 disp(Zy)
16
17 P=sqrt(3)*V1*I1*cos(30/180*%pi)
18 Q=sqrt(3)*V1*I1*sin(30/180*%pi)
19 disp(P,Q)
```

Scilab code Exa 6.5 Problem5

```
1 V1=400
2 Z=16+%i*12
3
4 Vp=V1
5 Ip=Vp/Z
6 pf=cos(atan(imag(Z)/real(Z)))
7 I1=Ip*sqrt(3)
8
9 P=sqrt(3)*V1*I1*pf
10 Q=sqrt(3)*V1*I1*sin(acos(pf))
11
```



```
12 S=P+%i*Q
13
14 disp(Ip,I1, pf,P,Q,S)
```

Scilab code Exa 6.6 Problem6

```
1 V1=400
2 Zload=60+%i*15
3
4 Vs=V1/sqrt(3)
5 Z=0.3+%i*1+Zload
6
7 I1=Vs/Z
8 Vload=I1*Zload*sqrt(3)
9 Pload=3*I1*I1*real(Zload)
10 Qload=3*I1*I1*imag(Zload)
11 Sload=Pload+%i*Qload
12
13 ////////////////////////////////////ll=lineloss
14 P11=3*I1*I1*real(Z-Zload)
15 Q11=3*I1*I1*imag(Z-Zload)
16 S11=P11+%i*Q11
17
18 Ssource=Sload+S11
19
20 disp(I1,Vload,Sload,S11,Ssource)
```

Scilab code Exa 6.7 Problem7

```
1 Ig1=200000/sqrt(3)/11000/0.75
2 PG1=200000
3 QG1=200000*tan(acos(0.75))
4 SG1=PG1+%i*QG1
```

```

5
6 P11=3*Ig1*Ig1*1
7 Q11=3*Ig1*Ig1*2.2
8 S11=P11+%i*Q11
9 S1G1=SG1-S11
10 V1=S1G1/sqrt(3)/Ig1
11
12
13 P1=400000
14 Q1=400000*tan(acos(0.8))
15 P1G2=P1-real(S1G1)
16 Q1G2=Q1-imag(S1G1)
17 S1G2=P1G2+%i*Q1G2
18
19 IG2=S1G2/sqrt(3)/V1
20
21 P112=3*IG2*IG2*0.6
22 Q112=3*IG2*IG2*1.2
23
24 PG2=P1G2+P112
25 QG2=Q1G2+Q112
26 SG2=PG2+%i*QG2
27 VG2=SG2/sqrt(3)/IG2
28
29 disp(norm(SG2),norm(VG2))

```

Scilab code Exa 6.9 Problem9

```

1 function [x,y]=polar_to_cart(r,theta)
2     theta=theta/180*%pi
3     x=r*cos(theta)
4     y=r*sin(theta)
5 endfunction
6
7 V1=400

```

```

8 [Ir,Ic]=polar_to_cart(20,-30)
9 Iab=complex(Ir,Ic)
10
11 omega=exp(%i*120/180*%pi)
12 Ibc=Iab/omega
13 Ica=Iab*omega
14
15 IAa=Iab-Ica
16 Pab=Vl*norm(Iab)*cos(30/180*%pi)
17 Ptotal=3*Pab
18
19 Zp=Vl/Iab
20 Rp=real(Zp)
21
22 disp(IAa)
23 disp(Ptotal)
24 disp(Rp)

```

Scilab code Exa 6.10 Problem10

```

1 omega=exp(%i*120/180*%pi)
2
3 Zp=17.32+%i*10
4 Vab=400
5 Iab=Vab/Zp
6 Ica=Iab/omega
7 IAa=Iab-Ica
8 IBb=IAa/omega
9 ICc=IAa*omega
10 disp(ICc,IBb,IAa)
11
12 Pab=(norm(Iab)^2)*real(Zp)
13 Ptotal=3*Pab
14 disp(Ptotal)
15

```

```
16 Itotal=IAa+IBb+ICc
17 disp(Itotal)
```

Scilab code Exa 6.11 Problem11

```
1 omega=exp(%i*120/180*%pi)
2
3 function [x,y]=polar_to_cart(r,theta)
4     theta=theta/180*%pi
5     x=r*cos(theta)
6     y=r*sin(theta)
7 endfunction
8
9 [Zr,Zc]=polar_to_cart(5,60)
10 Z=complex(Zr,Zc)
11
12 [Vr,Vc]=polar_to_cart(25,30)
13 Van=complex(Vr,Vc)
14
15 Ian=Van/Z
16 Ibn=Ian/omega
17 Icn=Ian*omega
18
19 Vcn=Van*omega
20 Vac=Van-Vcn
21
22 disp(Ibn,Icn,Vac)
```

Scilab code Exa 6.12 Problem12

```
1 V=400
2 w=2*50*%pi
3 P=25000
```

```

4 pf1=0.7
5 theta1=acos(pf1)
6 I11=P/(sqrt(3)*V*pf1)*exp(-%i*theta1)
7 Ip1=I11/sqrt(3)
8
9
10 pf2=0.85
11 theta2=acos(pf2)
12 I12=P/(sqrt(3)*V*pf2)*exp(-%i*theta2)
13 Ip2=I12/sqrt(3)
14
15 Ic=Ip2-Ip1          //// calculation
    mistake in the book at this step
16 C=real(Ic/(V*w*%i))
17 disp(C)

```

Scilab code Exa 6.13 Problem13

```

1 omega=exp(%i*120/180*%pi)
2 Vrn=400/sqrt(3)
3 Vyn=Vrn/omega
4 Vbn=Vrn*omega
5
6 P1=4000
7 P2=8000
8 P3=12000
9
10 Ir=conj(P1/Vrn)
11 Iy=conj(P2/Vyn)
12 Ib=conj(P3/Vbn)
13
14 In=Ir+Iy+Ib
15
16 disp(norm(Ir),norm(Iy),norm(Ib),norm(In))

```

Scilab code Exa 6.14 Problem14

```
1 function [x,y]=polar_to_cart(r,theta)
2     theta=theta/180*%pi
3     x=r*cos(theta)
4     y=r*sin(theta)
5 endfunction
6
7
8 Vbc=-400*i
9 Rl=1
10
11 [Sr,Sc]=polar_to_cart(10000,acos(0.8))
12 S=complex(Sr,Sc)
13
14
15 V1=Vbc
16 I1=norm(S/(sqrt(3)*V1))           // calculation
17     mistake in book here
18 P=3*I1*I1*Rl
19 disp(P)
20 Van=norm(Vbc/sqrt(3))
21
22 Ia=I1*exp(-i*acos(0.8))
23 omega=exp(i*120/180*%pi)
24 Ib=Ia/omega
25
26 disp(Van, Ia, Ib)
```

Scilab code Exa 6.15 Problem15

```

1 function [x,y]=polar_to_cart(r,theta)
2     theta=theta/180*%pi
3     x=r*cos(theta)
4     y=r*sin(theta)
5 endfunction
6
7 [Vr,Vc]=polar_to_cart(231,60)
8 Van=complex(Vr,Vc)
9
10 Sp=(2.5-%i*1.2)*1000
11
12 omega=exp(%i*120/180*%pi)
13 Vbn=Van/omega
14 Vcn=Van*omega
15
16 Vbc=Vbn-Vcn
17
18 Ibc=conj(Sp/Vbc)
19 Ica=Ibc*omega
20 Iab=Ibc/omega
21
22 IaA=Ica-Iab
23
24 disp(IaA)

```

Scilab code Exa 6.16 Problem16

```

1 omega=exp(%i*120/180*%pi)
2 Vab=400
3 Vca=400*omega
4 Vbc=400/omega
5
6 //Mesh Method
7 A=[80+100*%i,100*%i;100*%i,50*%i]
8 I=inv(A)*[-Vca;Vbc]

```

```

9 Ia=I(1)
10 Ib=I(2)
11
12 Ic=-(Ia+Ib)
13 Van=80*Ia
14 Vbn=-50*%i*Ib
15 Vcn=100*%i*Ic
16
17 disp(Ia , Ib , Ic , Van , Vbn , Vcn)

```

Scilab code Exa 6.17 Problem17

```

1 omega=exp(%i*120/180*%pi)
2 Vab=400
3 Vca=400*omega
4 Vbc=400/omega
5
6 Iab=Vab/(100*%i)
7 Ibc=Vbc/(-50*%i)
8 Ica=Vca/80
9
10 Ia=Iab-Ica      ///calaculation mistake in the book
    here
11 Ib=Ibc-Iab
12 Ic=Ica-Ibc
13
14 disp(Ia , Ib , Ic)

```

Scilab code Exa 6.18 Problem18

```

1 V=400
2 P=900
3 pf=0.8

```



```

4
5 Pph=P/3
6 Vph=V/sqrt(3)
7 Iph=Pph/Vph/pf
8 Zph=Vph/Iph
9 theta=acos(pf)
10 Zph=Zph*exp(-%i*theta)
11 disp(Zph)

```

Scilab code Exa 6.19 Problem19

```

1 V=400
2 Z=complex(40,30)
3
4 Iph=V/Z
5 I1=sqrt(3)*norm(Iph)
6 Ptotal=sqrt(3)*I1*V*cos(atan(imag(Z)/real(Z)))
7
8 disp(Iph,I1,Ptotal)

```

Scilab code Exa 6.20 Problem20

```

1 Ig1=15000/sqrt(3)/800/0.8
2 PG1=15000
3 QG1=15000*tan(acos(0.8))
4 SG1=PG1+%i*QG1
5
6 P11=3*Ig1*Ig1*1.2
7 Q11=3*Ig1*Ig1*1.8
8 S11=P11+%i*Q11
9 S1G1=SG1-S11
10 V1=S1G1/sqrt(3)/Ig1
11

```

```

12
13 P1=30000
14 Q1=30000*tan(acos(0.8))
15 P1G2=P1-real(S1G1)
16 Q1G2=Q1-imag(S1G1)
17 S1G2=P1G2+%i*Q1G2
18
19 IG2=S1G2/sqrt(3)/V1
20
21 P112=3*IG2*IG2*0.8
22 Q112=3*IG2*IG2*1.2
23
24 PG2=P1G2+P112
25 QG2=Q1G2+Q112
26 SG2=PG2+%i*QG2
27 VG2=SG2/sqrt(3)/IG2
28
29 disp(norm(SG2),norm(VG2))

```

Scilab code Exa 6.21 Problem21

```

1 omega=exp(%i*120/180*%pi)
2 w=2*50*%pi
3 Vry=415
4 Vyb=Vry/omega
5 Vbr=Vry*omega
6
7 C=40E-6
8 Zry=100
9 Zyb=complex(20,60)
10 Zbr=1/(%i*w*C)
11
12 I1=Vry/Zry
13 I2=Vyb/Zyb
14 I3=Vbr/Zbr

```

```
15
16 Ir=I1-I3
17 Iy=I2-I1
18 Ib=I3-I2
19
20 disp(norm(Ir),norm(Iy),norm(Ib))
```

Chapter 7

Magnetic Circuits

Scilab code Exa 7.1 Problem1

```
1 uo=(4*%pi)*1E-7
2
3 i1=5
4 i2=2.5
5 r=0.4
6 H=i1/(2*%pi*r)
7
8 F=uo*H*i2          ////////////// attractive
9 ur=8000
10 Firon=ur*F
11
12 disp(H,F,Firon)
```

Scilab code Exa 7.2 Problem2

```
1 l=0.15
2 i1=50
3
```

```
4 H1=i1/(2*%pi*(0.1+1))
5 i2=-H1*(2*%pi*0.1)
6
7
8 disp(i2)
```

Scilab code Exa 7.3 Problem3

```
1 Ha=4/(2*%pi*0.2)
2 Hb=Ha
3 H=sqrt(Ha^2+Hb^2)
4 theta=(%pi+atan(-Hb/Ha))*180/%pi
5
6 disp(H,theta)
```

Scilab code Exa 7.4 Problem4

```
1 uo=(4*%pi)*1E-7
2
3 Bg=1.2
4 N=400
5 ur=4000
6
7 lc=(2*(20-4+16-4)-0.2)/100
8 Ac=4/100*4/100
9 Rc=lc/(ur*uo*Ac)
10
11 lg=0.2/100
12 Rg=lg/(uo*Ac)
13
14 R=Rc+Rg
15
16 flux=Bg*Ac
```

```
17 i=flux*R/N
18
19 disp(i)
```

Scilab code Exa 7.5 Problem5

```
1 function Zeq=parallel(Z1,Z2)
2     Zeq=Z1*Z2/(Z1+Z2)
3 endfunction
4
5 uo=(4*%pi)*1E-7
6 fluxg1=0.8E-3
7
8 lg1=0.02/100
9 lg2=0.02/100
10 lg3=0.025/100
11 Ag1=2/100*1/100
12 Ag2=1/100*1/100
13 Ag3=1/100*1/100
14
15 Rg1=lg1/(uo*Ag1)
16 Rg2=lg2/(uo*Ag2)
17 Rg3=lg3/(uo*Ag3)
18 Req=Rg1+parallel(Rg2,Rg3)
19
20 MMF=fluxg1*Req
21
22 disp(MMF)
```

Scilab code Exa 7.6 Problem6

```
1 uo=(4*%pi)*1E-7
2 ur=4000
```

```

3 fluxc=0.01
4 N=500
5
6 L1=(2*(20+4)+25+4)/100
7 Lc=(25+4)/100
8 Lr=L1-0.02/100
9 Lg=0.02/100
10 A=4/100*4/100
11
12 Rl=L1/(ur*uo*A)
13 Rc=Lc/(ur*uo*A)
14 Rr=Lr/(ur*uo*A)
15 Rg=Lg/(uo*A)
16
17 Fab=fluxc*Rc
18 fluxr=Fab/(Rr+Rg)
19 fluxl=fluxc+fluxr
20
21 F=fluxl*Rl+Fab
22 I=F/N
23
24 disp(I)

```

Scilab code Exa 7.7 Problem7

```

1 uo=(4*%pi)*1E-7
2
3 l1=50/100
4 l2=20/100
5 l3=50/100
6 lbc=0.025/100
7
8 A1=25E-4
9 A2=12.5E-4
10 A3=25E-4

```

```

11
12 fluxg=0.75E-3
13
14 B=fluxg/A1
15 Fbc=B/uo*lbc
16
17 Hcd=200
18 Hab=Hcd
19 Fabcd=Hab*l1
20 Fad=Fbc+Fabcd
21 Had=Fab/l2
22 Bad=1.04
23 fluxad=Bad*A2
24
25 fluxdea=fluxad+fluxg
26 Bdea=fluxdea/A3
27 Hdea=500
28 Fdea=Hdea*l3
29
30 F=Fdea+Fad
31
32 disp(F)

```

Scilab code Exa 7.8 Problem8

```

1 uo=(4*%pi)*1E-7
2 ur=3000
3 Ac=10/100*10/1000
4 Bc=1.4
5 Hc=Bc/(uo*ur)
6 lc=150/100
7 Ftotal=Hc*lc
8
9 N2=800
10 I2=2

```



```

11 F2=N2*I2
12 F1=Ftotal-F2
13
14 N1=400
15 I1=F1/N1  ////out of terminal a
16 disp(I1)
17
18
19 Bc=1.4
20 fluxc=Bc*Ac
21 Rc=lc/(Ac*uo*ur)
22 Wf=1/2*Rc*fluxc*fluxc
23 disp(Wf)
24
25
26
27 L1=N1*N1/Rc
28 L2=N2*N2/Rc
29 M=sqrt(L1*L2)
30 disp(M)

```

Scilab code Exa 7.9 Problem9

```

1 uo=(4*%pi)*1E-7
2 ur=6000
3 A=5/2*2/10000
4 Lr=(%pi*(20+25)/2-0.1)/100
5 Lg=0.1/100
6 Rr=Lr/(uo*ur*A)
7 Rg=Lg/(uo*A)
8 Rtotal=Rr+Rg
9
10 F=2*500
11 flux=F/Rtotal
12 Bg=flux/A

```

```

13 disp(Bg)
14
15 L=flux*500/2
16 disp(L)
17
18 Wfr=1/2*Rr*flux*flux
19 Wfg=1/2*Rg*flux*flux
20 disp(Wfg,Wfr)
21
22 imax=2
23 flux_max=flux
24 E=4.44*314/(2*pi)*500*flux_max
25 flux_max2=100/(sqrt(2)*4.44*314/(2*pi)*500)
26 Fmax2=flux_max2*Rtotal
27 imax2=Fmax2/500
28 disp(imax2)

```

Scilab code Exa 7.10 Problem10

```

1 Ac=12/10000
2 Fmin=160*9.81
3 B=sqrt(Fmin*2*uo/Ac)
4
5 H=2800
6 L=75/100
7 F=H*L
8 Lg=0.1/1000
9 A=24/10000
10 Rg=Lg/(uo*A)
11 fluxg=B*A
12 Fg=fluxg*Rg
13
14 Ftotal=F+Fg
15 imin=Ftotal/1000
16 disp(imin)

```

Scilab code Exa 7.11 Problem11

```
1 Wm1=1/2*(1200-750)*0.012
2 disp(Wm1)
3
4 flux_g=0.012/750*1200
5 Wm2=1/2*(flux_g-0.012)*1200
6 disp(Wm2)
7
8 Ra=1200/0.012
9 Rb=1200/flux_g
10 Fo=-1/2*(0.012^2)*0.75*10^6
11 Fc=-1/2*(flux_g^2)*0.75*10^6
12 disp(Fc,Fo)
```

Scilab code Exa 7.12 Problem12

```
1 V1=10
2
3 //Mesh Method
4 A=[1+10*i,-80*i;80*i,-500-800*i]
5 I=inv(A)*[V1;0]
6
7 V2=500*I(2)
8
9 disp(V1,V2,I)
```

Scilab code Exa 7.14 Problem14

```
1 uo=(4*%pi)*1E-7
2 ur=1600
3
4 lc=160/100
5 lg=0.8/1000
6 A=5/10000
7 N=1200
8
9 Rc=lc/(uo*ur*A)
10 Rg=lg/(uo*A)
11 R=Rc+Rg
12
13 L=N*N/R
14 disp(L)
```

Scilab code Exa 7.15 Problem15

```
1 N=100
2 l1=0.15
3 l2=0.3
4 l3=0.45
5 A=0.001
6
7 ur1=1447
8 ur2=5969
9 ur3=47750
10
11 flux=0.6E-3
12
13 B=flux/A
14
15 H1=B/(uo*ur1)
16 H2=B/(uo*ur2)
17 H3=B/(uo*ur3)
18 disp(H1 , H2 , H3)
```

```
19
20 F=H1*11+H2*12+H3*13
21 disp(F)
22
23 I=F/N
24 disp(I)
```

Scilab code Exa 7.16 Problem16

```
1 P11=1500
2 f1=50
3 P12=3000
4 f2=75
5
6 Y=[1, f1; 1, f2]
7 X=inv(Y)*[P11/f1; P12/f2]
8
9 Ph1=X(1)*f1
10 Pe1=X(2)*f1*f1
11 Ph2=X(1)*f2
12 Pe2=X(2)*f2*f2
13
14 disp(Ph1, Pe1, Ph2, Pe2)
```

Scilab code Exa 7.17 Problem17

```
1 uo=(4*%pi)*1E-7
2 F=750*1
3 disp(F)
4
5 dm=(16+20)/200
6 lc=dm*%pi
7 Hc=F/lc
```

```
8 disp(Hc)
9
10 flux=1.25/1000
11 Ac=(20-16)*2.5/10000
12 Bc=flux/Ac
13 disp(Bc)
14
15 R=F/flux
16 disp(R)
17
18 u=Bc/Hc
19 disp(u)
20
21 ur=u/uo
22 disp(ur) //calculation mistake in the book
    here
```

Scilab code Exa 7.18 Problem18

```
1 fluxc=1.5E-3
2 Ac=12/10000
3 Bc=fluxc/Ac
4 Hc=1250
5 lc=0.3
6 F=Hc*lc
7
8 Fa=200*1
9 Fb=600*0.75
10
11 Fc=F-Fb+Fa
12 Nc=Fc/0.5
13 disp(Nc) ////clockwise5
```

Scilab code Exa 7.19 Problem19

```
1 uo=(4*%pi)*1E-7
2 ur=2000
3 V=200
4 f=50
5 N=1600
6 Ac=5/10000
7
8 flux_max=V/(4.44*f*N)
9 Bmax=flux_max/Ac
10 disp(Bmax)
11
12 Rc=20/100/(uo*ur*Ac)
13 Rg=0.5/1000/(uo*Ac)
14 R=Rc+Rg
15
16 imax=flux_max*R/N
17 disp(imax)
18
19 Wfmax=1/2*R*(flux_max^2)
20 disp(Wfmax)
21
22 percent=Rg/R*100
23 disp(percent)
```

Chapter 8

Transformers

Scilab code Exa 8.1 Problem1

```
1 V1=3300
2 f=50
3 N1=100
4 N2=300
5 Z=100+35*%i
6 flux_max=V1/(sqrt(2)*%pi*f*N1)
7 V2=V1*N2/N1
8 I2=V2/Z
9 I1=N2/N1*I2
10 S=V1*conj(I1)
11 Z1=Z*(N1/N2)^2
12
13 disp(flux_max)
14 disp(I1,I2)
15 disp(real(S),imag(S))
16 disp(Z1)
```

Scilab code Exa 8.2 Problem2


```

1 a=2400/240
2
3 R=0.2+a*a*2/1000
4 X=0.6+a*a*6/1000
5 disp(R,X)
6
7 Rlv=1/a/a*R
8 Xlv=1/a/a*X
9 disp(Rlv,Xlv)
10
11 I2=150*1000/2400
12 Z=R+%i*X
13 V=I2*Z
14 pcnt=norm(V)/2400*100
15 disp(V,pcnt)
16
17 Im=2400/1600
18 Ii=2400/10000
19 Io=Ii-%i*Im
20 pf=cos(atan(imag(Io)/real(Io)))
21 disp(Io,pf)

```

Scilab code Exa 8.3 Problem3

```

1 P=200E3
2 V1=11000
3 V2=415
4 f=50
5 N2=80
6
7 N1=V1/V2*N2
8 a=N1/N2
9 disp(a)
10
11 I2=P/V2

```

```
12 disp(I2)
13 I1=I2/a
14 disp(I1)
15
16 Z2=V2*V2/P
17 disp(Z2)
18 Z21=Z2*a*a
19 disp(Z21)
```

Scilab code Exa 8.4 Problem4

```
1 V1=200
2 f=50
3 N1=150
4 Ac=10*5/10000
5
6
7 Flux_max=V1/(sqrt(2)*%pi*f*N1)
8 Bmax=Flux_max/Ac
9 Hmax=250
10 l=2*(25+10)+2*(20+10)
11 l=l/100
12 AT_max=Hmax*l
13 Im_max=AT_max/150
14 Im_rms=Im_max/sqrt(2)
15 disp(Im_rms)
16
17 Fe_loss=23000
18
19 Cv = 2*(25+2*10)*10*5 + 2*20*10*5
20 Cv=Cv/1000000
21 Cl=Fe_loss*Cv
22 disp(Cl)
23
24 Ii=150/V1
```

25 `disp(Ii)`

Scilab code Exa 8.5 Problem5

```
1 function [x,y]=polar_to_cart(r,theta)
2     theta=theta/180*%pi
3     x=r*cos(theta)
4     y=r*sin(theta)
5 endfunction
6
7 [Zr,Zc]=polar_to_cart(5,30)
8 Z2=complex(Zr,Zc)
9
10 V=200
11 N2=75
12 N1=100
13
14 I2=V/Z2
15 I1=N2/N1*I2
16
17 disp(norm(I1))
18 disp(" lagging" , real(I1)/norm(I1))
```

Scilab code Exa 8.6 Problem6

```
1 R=60
2 V=6
3 Rs=2400
4
5 a=sqrt(Rs/R)
6 disp(a)
7
8 Pl_max=1/2*(R*R)/(Rs+Rs)
```

```
9 I1=V/2/Rs
10
11 I1=I1*a
12 disp(I1)
13 V1=V/2/a
14 disp(V1)
```

Scilab code Exa 8.7 Problem7

```
1 f=50
2 a=1100/220
3 Rhv=0.125
4 Xhv=0.625
5 Rlv=0.005
6 Xlv=0.025
7
8 Zhv=Rhv+%i*Xhv
9 Zlv=Rlv+%i*Xlv
10
11 Z1=Zhv+a*a*Zlv
12 disp(Z1)
13 Z2=Z1/a/a
14 disp(Z2)
15
16 Zpu1=Z1*0.05/1.1/1.1
17 disp(Zpu1)
18 Zpu2=Z2*0.05/0.22/0.22
19 disp(Zpu2)
```

Scilab code Exa 8.8 Problem8

```
1 P=600E3
2 a=2400/600
```

```

3 r1=0.05
4 r2=0.004
5 x1=0.025
6 x2=0.016
7 R1=1667
8 Xm=417
9
10 /////As seen from the LV side
11
12 Zlv=r2+%i*x2+1/a/a*(r1+%i*x1)
13 disp(Zlv)
14
15 RiLV=R1/a/a
16 disp(RiLV)
17 XmLV=Xm/a/a
18 disp(XmLV)
19
20
21 Zpu=Zlv*0.6/0.6/0.6
22 disp(Zpu)
23 Ri=RiLV*0.6/0.6/0.6
24 disp(Ri)
25 Xm=XmLV*0.6/0.6/0.6
26 disp(Xm)

```

Scilab code Exa 8.9 Problem9

```

1 P=50E3
2 a=2200/220
3
4 /////OC Parameters
5 Poc=405
6 Ioc=5
7 Voc=220
8

```

```

9  /////SC Parameters
10 Psc=805
11 Isc=20.2
12 Vsc=95
13
14
15 Y0=Ioc/Voc
16 Gi=Poc/Voc/Voc
17 Bm=sqrt(Y0*Y0-Gi*Gi)
18
19 Z=Vsc/Isc
20 R=Psc/Isc/Isc
21 X=sqrt(Z*Z-R*R)
22
23 ///////////////Referred to HV side
24 GiHV=Gi/a/a
25 disp(GiHV)
26 BmHV=Bm/a/a
27 disp(BmHV)
28 disp(R)
29 disp(X)
30
31 ///////////////Referred to LV side
32 disp(Gi)
33 disp(Bm)
34 RLV=R/a/a
35 disp(RLV)
36 XLV=X/a/a
37 disp(XLV)
38
39
40 ///////////////Per unit
41 GiPU=GiHV/0.0103
42 BmPU=BmHV/0.0103
43 RPU=R/96.8
44 XPU=X/96.8
45 disp(GiPU)
46 disp(BmPU)

```

```
47 disp(RPU)
48 disp(XPU)
```

Scilab code Exa 8.10 Problem10

```
1 P=50E3
2 a=2200/110
3
4 //OC Parameters
5 Poc=400
6 Ioc=10
7 Voc=110
8
9 Y0=Ioc/Voc
10 Gi=Poc/Voc/Voc
11 disp(Gi)
12 Bm=sqrt(Y0*Y0-Gi*Gi)
13 disp(Bm)
14
15 //Referred to HV side
16 GiHV=Gi/a/a
17 disp(GiHV)
18 BmHV=Bm/a/a
19 disp(BmHV)
20
21 //Per unit
22 GiPU=Gi*P/Voc/Voc
23 BmPU=Bm*P/Voc/Voc
24 disp(GiPU)
25 disp(BmPU)
```

Scilab code Exa 8.11 Problem11

```

1 P=25000
2 V1=2200
3 V2=220
4 a=V1/V2
5 f=50
6 r1=2
7 r2=0.025
8 x1=7
9 x2=0.07
10 Xm=16000
11
12 Im=V2/Xm
13 disp(" pf=0, 90 degree lag Po=0", Im)
14
15 R=r1+a*a*r2
16 X=x1+a*a*x2
17 Z=sqrt(R*R+X*X)
18 Ifl=P/V1
19 Vsc=Z*Ifl
20 Vsc_percent=Vsc/V1*100
21 disp(Vsc,Vsc_percent)
22 Im=Vsc/Xm
23 Im_percent=Im/Ifl*100
24 disp(Im,Im_percent)
25
26 Sc_pf=cos(atan(X/R))
27 disp(Sc_pf)
28
29 ////////////////Per unit
30 ZBpu=1000*2.2*2.2/25
31 r1pu=r1/193.6
32 r2pu=a*a*r2/193.6
33 x1pu=x1/193.6
34 x2pu=a*a*x2/193.6
35
36 Rpu=r1pu+r2pu
37 Xpu=x1pu+x2pu
38

```



```
39 Xmpu=Xm/193.6
40 disp(Rpu , Xpu , Xmpu)
```

Scilab code Exa 8.12 Problem12

```
1 P=10000
2 v1=2300
3 v2=230
4 a=v1/v2
5 f=50
6 r1=3.96
7 r2=0.0396
8 x1=15.8
9 x2=0.158
10
11 R=r1+a*a*r2
12 X=x1+a*a*x2
13 V2=v2*a
14 I=P/V2
15 theta=acos(0.80)
16 V1=V2+I*(R*cos(theta)+X*sin(theta))
17 disp(V1)
18 VR=(V1-V2)/V2
19 disp(VR)
20
21 pf=X/sqrt(R*R+X*X)
22 theta2=acos(pf)
23 I1=I*(cos(theta)-%i*sin(theta))
24 Ic=real(I1*tan(theta2))-imag(I1)
25 Rating_Cap=V2*Ic
26 disp(Rating_Cap)
27 V1=V2
28 disp(V1)
```

Scilab code Exa 8.13 Problem13

```
1 P=100000
2 N1=400
3 N2=100
4 a=N1/N2
5 r1=0.3
6 r2=0.015
7 x1=1.1
8 x2=0.055
9 V1=2400
10
11 R=r1+a*a*r2
12 disp(R)
13 X=x1+a*a*x2
14 disp(X)
15
16 I1=P/V1
17 pf=0.8
18 theta=acos(pf)
19 Vd=I1*(R*cos(theta)+X*sin(theta))
20 VR=Vd/V1*100
21 V2=(V1-Vd)/a
22 disp(VR,V2)
23 Vd=I1*(R*cos(theta)-X*sin(theta))
24 VR=Vd/V1*100
25 V2=(V1-Vd)/a
26 disp(VR,V2)
27
28 pf=cos(atan(R/X))          //wrong in the book
29 disp("leading",pf)
```

Scilab code Exa 8.14 Problem14

```
1 P=10000
2 v1=2300
3 v2=230
4 a=v1/v2
5 f=50
6 r1=3.96
7 r2=0.0396
8 x1=15.8
9 x2=0.158
10
11 R=r1+a*a*r2
12 X=x1+a*a*x2
13 V2=v2*a
14 I=P/V2
15 pf=0.8
16 theta=acos(pf)
17 V1=V2+I*(R*cos(theta)+X*sin(theta))
18 Pi=75*V1*V1/V2/V2
19 Pc=I*I*R
20 P1=Pi+Pc
21 P0=P*pf
22 effi=P0/(P0+P1)*100
23 disp(effi)
24
25 V1=V2
26 Pi=75
27 pf2=X/sqrt(R*R+X*X)
28 I=P0/V1/pf2
29 Pc=I*I*R
30 P1=Pi+Pc
31 P0=P*pf
32 effi=P0/(P0+P1)*100
33 disp(effi)
34
35 I=sqrt(Pi/R)
36 Load=V2*I
```

```
37 P0=Load*pf
38 P1=2*Pi
39 effi_max=P0/(P0+P1)*100
40 disp(effi_max)
```

Scilab code Exa 8.15 Problem15

```
1 P=15E3
2 a=3000/250
3
4 //OC Parameters
5 Poc=105
6 Ioc=0.62
7 Voc=250
8
9 //SC Parameters
10 Psc=360
11 Isc=5.2
12 Vsc=157
13
14
15 Y0=Ioc/Voc
16 Gi=Poc/Voc/Voc
17 Bm=sqrt(Y0*Y0-Gi*Gi)
18
19 Z=Vsc/Isc
20 R=Psc/Isc/Isc
21 X=sqrt(Z*Z-R*R)
22
23 //Referred to HV side
24 GiHV=Gi/a/a
25 disp(GiHV)
26 BmHV=Bm/a/a
27 disp(BmHV)
28 disp(R)
```

```

29 disp(X)
30
31 //////////////Per unit
32 ZB=3.12/5.2
33 GiPU=Gi*ZB
34 BmPU=Y0*ZB
35 RPU=R/ZB/1000
36 XPU=X/ZB/1000
37 disp(GiPU)
38 disp(BmPU)
39 disp(RPU)
40 disp(XPU)
41
42
43 pf=0.8
44 theta=acos(pf)
45 V2=250*a
46 I=P/V2
47 Vd=I*(R*cos(theta)-X*sin(theta))
48 VR=-Vd/V2*100
49 disp(VR)
50 Pi=105
51 Pc=I*I*R
52 Pl=Pi+Pc
53 P0=P*pf
54 effi=P0/(Pl+P0)*100
55
56 pf2=cos(atan(R/X))
57 disp("leading", pf2)
58
59
60 IPU=sqrt(Pi/P/RPU)
61 effi_max=IPU
62 disp(effi_max)

```

Scilab code Exa 8.16 Problem16

```
1 v1=2500
2 v2=250
3 P=25000
4 Pc=130
5 Pcfl=320
6 pf=0.8
7
8 V2=2750
9
10 P0=P*pf
11 P1=Pcfl+Pc
12 effi=P0/(P0+P1)*100
13 disp(effi)
14
15 I2=P/v2
16 I1=I2+P/v1
17 kVA=I1*v1/1000
18 P0=kVA*pf*1000
19 effi=P0/(P0+P1)*100
20 disp(effi)
```

Scilab code Exa 8.17 Problem17

```
1 a=10
2 Load=120000
3 V=400
4
5 I=Load/V/sqrt(3)
6 Vll=a*V/sqrt(3)
7 I11=sqrt(3)*I/a
8 all=Vll/V
9 disp(Vll, I11, all)
10
```

```
11 V11=a*V*sqrt(3)
12 I11=I/a/sqrt(3)
13 all=V11/V
14 disp(V11,I11,all)
```

Scilab code Exa 8.18 Problem18

```
1 f=50
2 N1=500
3
4 Pin=60
5 Io=0.4
6 Vin=220
7 r=0.8
8
9 Pci=Io*Io*r
10 Pi=Pin-Pci
11 disp(Pi)
12 theta=acos(Pin/Vin/Io)
13 Im=Io*sin(theta)
14 Xm=Vin/Im
15 disp(Xm)
16 Iio=Io*cos(theta)
17 Ri=Vin/Iio
18 disp(Ri)
```

Scilab code Exa 8.19 Problem19

```
1 P=15E3
2 v1=2200
3 v2=220
4 a=v1/v2
5
```

```

6  /////OC Parameters
7  Poc=185
8  Ioc=2.72
9  Voc=220
10
11  /////SC Parameters
12  Psc=197
13  Isc=6.3
14  Vsc=112
15
16  Pi=Poc
17  disp(Pi)
18
19  IHVf1=P/v1
20  Pcfl=IHVf1*IHVf1/Isc/Isc*Psc
21  disp(Pcfl)
22
23  pf=0.85
24  Po=P*pf
25  Pl=Pi+Pcfl
26  effi=Po/(Po+Pl)*100
27  disp(effi)
28
29  Z=Vsc/Isc
30  R=Psc/Isc/Isc
31  X=sqrt(Z*Z-R*R)
32  pf=0.8
33  theta=acos(pf)
34  Vd1=IHVf1*(R*cos(theta)+X*sin(theta))
35  Vd2=IHVf1*(R*cos(theta)-X*sin(theta))
36  VR1=Vd1/v1*100
37  VR2=Vd2/v1*100
38  disp(VR1, VR2)

```

Scilab code Exa 8.20 Problem20


```

1 P=50000
2 lr=0.9
3
4 P0=P*1*0.9
5 effi=0.974
6 P1=(1-effi)/effi*P0
7 Pi=P1/2
8 Pcfl=Pi/lr/lr
9
10 pf=0.8
11 P0=P*pf
12 P1=Pi+Pcfl
13 effi=P0/(P0+P1)*100
14 disp(effi)
15
16 P0=P/2*lr
17 P1=Pi+Pcfl/2/2
18 effi=P0/(P0+P1)*100
19 disp(effi)
20
21 // calculation mistakes in the book

```

Scilab code Exa 8.21 Problem21

```

1 P=500E3
2 effi=0.95
3
4 A=[1,1;1,0.6*0.6]
5 Pa=inv(A)*[P*(1-effi)/effi;P*0.6*(1-effi)/effi]
6 Pi=Pa(1)
7 disp(Pi)
8 Pc=Pa(2)
9 disp(Pc)
10
11 P1=Pi+0.75*0.75*Pc

```

```
12 effi=P*0.75/(P*0.75+P1)
13 disp(effi)
```

Scilab code Exa 8.22 Problem22

```
1 v1=2200
2 v2=220
3 f=50
4 emfperturn=12
5
6 N1=floor(v1/emfperturn)
7 N2=floor(v2/emfperturn)
8 disp(N1)
9 disp(N2)
10
11 fluxmax=emfperturn/4.44/f
12 Bmax=1.5
13 Ac=fluxmax/Bmax
14 disp(Ac)
```

Scilab code Exa 8.23 Problem23

```
1 v1=3300
2 v2=600
3 f=50
4 Ac=25/10000
5 l=1.2
6
7 Bmax=1.2
8 fluxmax1=Bmax*Ac
9 N1=v1/4.44/f/fluxmax1
10 N2=v2/4.44/f/fluxmax1
11 disp(N1,N2)
```

```

12
13 I2=20
14 pf=0.8
15 I1=N2/N1*I2
16 I1=I1*(pf-%i*sin(acos(0.8)))
17 disp(I1)
18
19 Hmax=250
20 ATmax=Hmax*1
21 immax=ATmax/N1/sqrt(2)
22 Ii=0
23 I1=-%i*immax+I1
24 disp("lagging", real(I1)/norm(I1), norm(I1))

```

Scilab code Exa 8.24 Problem24

```

1 P=50000
2 v1=2400
3 v2=240
4 f=50
5 a=v1/v2
6 Pd=375
7 pf=0.4
8
9 I0=Pd/v1/pf
10 I0_prime=I0*a
11 disp(I0_prime, pf)

```

Scilab code Exa 8.25 Problem25

```

1 v1=220
2 v2=110
3 z1=0.32+%i*0.85

```

```

4 z2=0.11+%i*0.27
5 a=v1/v2
6
7 z=z1+a*a*z2
8 IHV=v1/norm(z)
9 ILV=IHV*a
10 disp(IHV,ILV)

```

Scilab code Exa 8.26 Problem26

```

1 P=1000000
2 v1=11000
3 v2=230
4 f=50
5 Vsc=310
6 Psc=5210
7
8 Isc=P/v1
9 Z=Vsc/Isc
10 R=Psc/Isc/Isc
11 X=sqrt(Z*Z-R*R)
12
13 pf=1
14 theta=acos(pf)
15 Vd=Isc*(R*cos(theta)+X*sin(theta))
16 VR=Vd/v1*100
17 V1=v1+Vd
18 disp(VR,V1)
19
20 pf=0.8
21 theta=acos(pf)
22 Vd=Isc*(R*cos(theta)+X*sin(theta))
23 VR=Vd/v1*100
24 V1=v1+Vd
25 disp(VR,V1)

```

```

26
27 pf=0.8
28 theta=acos(pf)
29 Vd=Isc*(R*cos(theta)-X*sin(theta)) // calculation
    mistake in the book at this point
30 VR=Vd/v1*100
31 V1=v1+Vd
32 disp(VR,V1)

```

Scilab code Exa 8.27 Problem27

```

1 P=10000
2 v1=2200
3 v2=220
4 r1=4
5 r2=0.04
6 x1=5
7 x2=0.05
8 a=v1/v2
9 R=r1+a*a*r2
10 X=x1+a*a*x2
11 I1=P/v1
12 pf=0.8
13 V2=v2*a
14 theta=acos(pf)
15 Vd=I1*(R*cos(theta)+X*sin(theta))
16 VR=Vd/v1*100
17 V1=v1+Vd
18 disp(VR,V1)
19
20 pf=cos(atan(X/R))
21 disp("leading",pf)
22
23 Pr=P*pf
24 Q=-P*sin(acos(pf))

```

25 `disp(Q,Pr)`

Scilab code Exa 8.28 Problem28

```
1 P=20000
2 v1=200
3 v2=400
4 f=50
5 V1=600
6 V2=200
7
8 a=V1/V2
9 disp(a)
10
11 I1=P/v2
12 VA=V1*I1
13 disp(VA)
14
15 disp(I1)
16 I2=30000/V2
17 Is=I2-I1
18 disp(I2)
19 disp(Is)
20
21 VAtrans=v2*I1
22 VAcond=30000-VAtrans
23 disp(VAtrans)
24 disp(VAcond)
```

Scilab code Exa 8.29 Problem29

```
1 P=100000
2 v1=11000
```

```
3 v2=400
4
5 V1=400
6 Vp=V1/sqrt(3)
7
8 a=ceil(v1/Vp)
9 disp(a)
10
11 I1=P/sqrt(3)/V1
12 Ip=I1
13 disp(I1,Ip)
14
15 I1=P/sqrt(3)/v1
16 Ip=I1/sqrt(3)
17 disp(I1,Ip)
```

Chapter 9

EMF and Torque in Electric Machines

Scilab code Exa 9.1 Problem1

```
1 f=50
2 flux=0.016
3 S=36
4 P=6
5 N=10
6
7
8 m=S/P
9 gammaa=%pi/m
10 Kb=sin(m*gammaa/2)/m/sin(gammaa/2)
11 Nph=S*N*2/2
12 Ep=4.44*Kb*f*Nph*flux
13 kVA=Ep*N/1000
14 disp(kVA)
15
16 m=S/2/P
17 gammaa=%pi/2/m
18 Kb=sin(m*gammaa/2)/m/sin(gammaa/2)
19 Nph=S*N*2/2/2
```



```

20 Ep=4.44*Kb*f*Nph*flux
21 Eline=Ep*sqrt(2)
22 kVA=Ep*N*2/1000
23 disp(kVA)
24
25 m=S/3/P
26 gammaa=%pi/3/m
27 Kb=sin(m*gammaa/2)/m/sin(gammaa/2)
28 Nph=S*N*2/2/3
29 Ep=4.44*Kb*f*Nph*flux
30 Eline=Ep*sqrt(3)
31 kVA=Ep*N*3/1000
32 disp(kVA)

```

Scilab code Exa 9.2 Problem2

```

1 S=54
2 P=6
3 m=S/3/P
4 gammaa=%pi/3/m
5
6 Kb1=sin(m*gammaa/2)/m/sin(gammaa/2)
7 Kb3=sin(m*gammaa/2*3)/m/sin(gammaa/2*3)
8 Kb5=sin(m*gammaa/2*5)/m/sin(gammaa/2*5)
9
10 disp(Kb1)
11 disp(Kb3)
12 disp(Kb5)

```

Scilab code Exa 9.3 Problem3

```

1 f=50
2 n=500

```

```

3 m=5
4 N=12
5 flux=0.025
6
7 P=120*f/n
8 S=m*3*P
9 Nph=S*N*2/2/3
10 gammaa=%pi/3/m
11 Kb=sin(m*gammaa/2)/m/sin(gammaa/2)
12 polepitch=S/N
13 coilpitch=13
14 spa=(polepitch-coilpitch)*gammaa
15 Kp=cos(spa/2)
16
17 Ep=4.44*Kb*Kp*f*Nph*flux
18 disp(Ep)
19 Eline=sqrt(3)*Ep
20 disp(Eline)

```

Scilab code Exa 9.4 Problem4

```

1 f=50
2 P=6
3 ns=120*f/P
4 disp(ns)
5 wm=2*%pi/60*ns
6 disp(wm)

```

Scilab code Exa 9.5 Problem5

```

1 F2=850
2 F1=400
3 lambda=123.6/180*%pi

```

```
4 ppp=1.408/1000
5
6 theta=%pi-lambda
7 Fr=sqrt(F1*F1+F2*F2-2*F1*F2*cos(theta))
8
9 fluxr=2/%pi*ppp*Fr
10 disp(fluxr)
```

Scilab code Exa 9.6 Problem6

```
1
2 P=6
3 N=1000
4
5 f=P*N/120
6 ns=120*f/4
7 s=0.04
8 n=(1-s)*ns
9 disp(n)
```

Scilab code Exa 9.7 Problem7

```
1
2 P=4
3 f=50
4
5
6 ns=120*f/P
7 n1=-1500
8 s1=(ns-n1)/ns
9 f2=s1*f
10 SRV=s1*80
11 disp(f2,SRV)
```

```
12
13 n2=1000
14 s2=(ns-n2)/ns
15 f2=s2*f
16 SRV=s2*80
17 disp(f2,SRV)
```

Scilab code Exa 9.8 Problem8

```
1
2 betaa=acos(0)*2/5
3 coilpitch=%pi-betaa
4 disp(coilpitch/%pi*180)
5
6 P=6
7 S=72
8 m=S/P
9 gammaa=%pi/m
10 cpis=150/180*%pi
11 betaa=%pi-cpis
12 Kp1=cos(betaa/2)
13 Kp3=cos(5*betaa/2)
14 Kp13=cos(13*betaa/2)
15 disp(Kp1)
16 disp(Kp3)
17 disp(Kp13)
```

Scilab code Exa 9.9 Problem9

```
1
2 P=2
3 f=50
4 S=42
```

```

5 m=S/3/P
6 gammaa=%pi/3/m
7 Kb=sin(m*gammaa/2)/m/sin(gammaa/2)
8 coilpitch=17
9 polepitch=S/2
10 spa=(polepitch-coilpitch)*gammaa
11 Kp=cos(spa/2)
12
13 N=S*2
14 Nc=N/2
15 Coilsperphase=Nc/3
16 Nph=Coilsperphase/2
17 Eline=2300
18 flux=Eline/sqrt(3)/4.44/Kb/Kp/f/Nph
19 disp(flux)

```

Scilab code Exa 9.10 Problem10

```

1 f=50
2 ns=1000
3 P=120*f/ns
4 disp(P)
5 s=(ns-940)/ns
6 disp(s*100)
7 nrr=ns-940
8 disp(nrr)
9 nrs=1000
10 disp(nrs)
11 s=2*s
12 n=1000*(1-s)
13 disp(n)

```

Scilab code Exa 9.11 Problem11

```
1 ns=1000
2 s=(ns-940)/ns
3 news=2*s
4 n=1000*(1-news)
5 disp(n)
```

Scilab code Exa 9.12 Problem12

```
1 P=8
2 f1=60
3 f2=50
4 If1=5
5 If2=f1/f2*If1
6 disp(If2)
7 nA2=120*f2/P
8 disp(nA2)
```

Scilab code Exa 9.13 Problem13

```
1 f1=60
2 f2=50
3 P1=12
4 P2=f2/f1*P1
5 disp(P2)
6 nset=120*f1/P1
7 disp(nset)
```

Scilab code Exa 9.14 Problem14

```
1 m=6
```

```
2 gammaa=%pi/m
3 Kb=sin(m*gammaa/2)/m/sin(gammaa/2)
4
5 m=4
6 Kb=sin(m*gammaa/2)/m/sin(gammaa/2)
```

Scilab code Exa 9.15 Problem15

```
1
2 f=50
3 n=965
4 P=floor(120*f/n)
5 disp(P)
6
7 s=(1000-965)/1000
8 disp(s)
9 f2=s*f
10 disp(f2)
11
12 nsr=1000-965
13 disp(nsr)
14 nrr=120*f2/P
15 nsrf=1000-965-nrr
16 disp(nsrf)
```

Scilab code Exa 9.16 Problem16

```
1 f=50
2 P=4
3 a=2
4
5 ns=120*f/P
6 n=1440
```

```
7 s=1-n/ns
8 disp(s)
9 f2=s*f
10 disp(f2)
11 E1p=400
12 E2f=400/a
13 E2f2=E2f*f2/f
14 E21=sqrt(3)*E2f2
15 disp(E21)
```

Chapter 10

DC Machines

Scilab code Exa 10.1 Problem1

```
1 P=6
2 S=36
3 coilside=2
4 N=8
5 A=2
6 d=0.25
7 l=0.18
8 Ia=10
9 avgflux=0.8
10 n=1200
11
12 Z=S*coilside*N
13 flux=%pi*d/P*l*avgflux
14 Ea=flux*n*Z/60*P/A
15 Pm=Ea*Ia
16 disp(Pm)
17 T=Pm/2/%pi/n*60
18 disp(T)
```

Scilab code Exa 10.2 Problem2

```
1 P=4
2 A=4
3 ra=0.145
4 l=0.21
5 Z=2*33*11
6 K=Z*P/2/%pi/A
7 disp(K)
8
9 Ap=2*%pi*ra/P*0.7*l
10 Barc=0.8
11 flux=Ap*Barc
12 n=1200
13 Ea=K*flux*2*%pi*n/60
14 disp(Ea)
15
16 Ia=240
17 Ic=Ia/A
18 disp(Ic)
19
20 T=K*flux*Ia
21 disp(T)
22 Pg=Ea*Ia
23 disp(Pg)
```

Scilab code Exa 10.3 Problem3

```
1 P=5000
2 Vt=215
3 n=1000
4 Ra=0.4
5 Ia=P/Vt
6 Eag=Vt+Ra*Ia
7 Eam=Vt-Ra*Ia
```

```
8 newn=Eam/Eag*n/1.1
9 disp(newn)
```

Scilab code Exa 10.4 Problem4

```
1 P=200000
2 V=400
3 n=600
4 Z=864
5 P1=8000
6
7 Ia=P/V
8 Ra=P1/Ia/Ia
9 Ea=V-Ia*Ra
10 flux=Ea*60/n/Z
11 disp(flux)
```

Scilab code Exa 10.5 Problem5

```
1 N=1800
2 //from figure
3 Voc=250
4 If=4.1
5 Rf=Voc/If
6 disp(If)
7 disp(Rf)
8
9 Rfcrit=150/2
10 disp(Rfcrit)
11
12 V3=120
13 Ncrit=N*V3/150
14 disp(Ncrit)
```

```
15
16 Rf220=220/3.2
17 Rext=Rf220-Rf
18 disp(Rext)
```

Scilab code Exa 10.6 Problem6

```
1 P=4
2 V=230
3 Z=888
4 Ra=0.8
5 flux=5.4E-3
6 A=2
7
8 I1=2
9 If=0.6
10 Ia=I1-If
11 Ea=V-Ia*Ra
12 n0=Ea*60/flux/Z/P*A
13 disp(n0)
14
15 T=29.6
16 Ia=T*2*%pi/flux/Z/P*A
17 I1=Ia+If
18 disp(I1)
19 Ea=V-Ra*Ia
20 n=Ea*60/flux/Z/P*A
21 disp(n)
22 sr=(1-n/n0)*100
23 disp(sr)
```

Scilab code Exa 10.7 Problem7

```

1 n1=1000
2 V=230
3 Ia=75
4 Ra=0.1
5 Ea1=V-Ia*Ra
6 Rf=275
7 If=V/Rf
8 Ke=Ea1/If/n1
9
10 n2=1200
11 Ia=125
12 Ea2=V-Ia*Ra
13 If2=Ea2/Ke/n2
14 Rf2=V/If2
15 Rfext=Rf2-Rf
16 disp(Rfext)

```

Scilab code Exa 10.8 Problem8

```

1 V=115
2 Ia1=25
3 Ra=0.3
4
5 n1=1450
6 Ea1=V-Ia1*Ra
7 Ke=Ea1/n1
8
9 n2=1200
10 Ea2=Ke*n2
11 Ia2=3/4*Ia1
12 Raext=(V-Ea2)/Ia2-Ra
13 disp(Raext)
14 effia=Ea2/V*100    ///calculation mistake in the
    book at this point
15 disp(effia)

```

```
16 V=Ea2+Ia2*Ra
17 effia=Ea2/V*100
18 disp(effia)
```

Scilab code Exa 10.9 Problem9

```
1  /////solving quadratic
2  Ra=0.5
3  P=8000
4  V=230
5  Ea=V
6  n=1200
7  Ke=V/n
8
9  p=poly([P*Ra,-V,1],"w","coeff")
10 w=roots(p)
11
12 Ea=w(1)      ///rejecting small value
13 n=Ea/Ke
14 disp(n)
15 T=P/2/%pi/n*60
16 disp(T)
17 Ia=(V-Ea)/Ra
18 disp(Ia)
19 Kt=T/Ia
20
21
22 p=poly([-Kt*V/Ra,Kt*Ke/Ra,0.6E-4],"w","coeff")
23 w=roots(p)
24 n=w(2)
25 disp(n)
```

Scilab code Exa 10.10 Problem10

```

1 V=300
2 Ea=V
3 n1=1200
4 n2=1100
5 Kaphi=Ea/2/%pi/n1*60
6
7 T=350
8 Ia=T/Kaphi
9 disp(Ia)
10 Ea=V*n2/n1
11 Pm=Ea*Ia
12 disp(Pm)
13
14 Ra=(V-Ea)/Ia
15 disp(Ra)
16
17 disp(T)
18 Ea=600-Ia*Ra
19 n=Ea*60/Kaphi/2/%pi
20 Pm=Ea*Ia
21 disp(Pm)
22 disp(n)

```

Scilab code Exa 10.11 Problem11

```

1 V=300
2 Ea=V
3 n1=1200
4 n2=1100
5 Kaphi=Ea/2/%pi/n1*60
6
7 T=350
8 Ia=T/Kaphi
9 Ea=V*n2/n1
10

```

```

11 Ra=(V-Ea)/Ia
12
13
14 Kaphi=Kaphi/2
15 n=Ea/Kaphi*60/2/%pi
16 Pm=Ea*Ia
17 T=Kaphi*Ia
18 disp(T)
19 disp(Pm)
20 disp(n)

```

Scilab code Exa 10.12 Problem12

```

1 V=600
2 Ia=40
3 R=0.5
4 Ea=V-Ia*R
5 n=500
6 Ka=Ea/Ia/2/%pi/n*60
7 T=Ka*Ia*Ia
8
9 n2=450
10 T=T*n2*n2/n/n
11 Ia=sqrt(T/Ka)
12 Ea=Ka*Ia*2*%pi*n2/60
13 Rtotal=(V-Ea)/Ia
14 Rext=Rtotal-R
15 disp(Rext)

```

Scilab code Exa 10.13 Problem13

```

1 V=220
2 Ra=1

```



```

3 Rse=0.4
4 Ia1=20
5 Ia2=sqrt(Ia1*Ia1*0.7*0.7*0.7)
6 Ea1=V-Ia1*(Ra+Rse)
7 Ea2=Ia2*0.7*Ea1/Ia1
8 Rext=(V-Ea2)/Ia2-Ra-Rse
9 disp(Rext)

```

Scilab code Exa 10.14 Problem14

```

1 V=250
2 Ia=25
3 n=1000
4 KaNfNse=V/Ia*60/2/%pi/n
5 T=KaNfNse*Ia*Ia
6 Ia=sqrt(V*2/KaNfNse/sqrt(KaNfNse*2*%pi*n/60*2*%pi*n
   /60/T/2))
7 w=sqrt(KaNfNse*2*%pi*n/60*2*%pi*n/60/T/2)*Ia
8 n=w*60/2/%pi
9
10 disp(n)
11 disp(Ia)

```

Scilab code Exa 10.15 Problem15

```

1 V=230
2 Rf=120
3 Ra=0.15
4 If=V/Rf
5 Psh=V*V/Rf
6
7 I=14.5
8 Pin=I*V

```

```

9 Ia=I-If
10 Pk=Pin-Ia*Ia*Ra
11
12 I=215
13 Ia=I-If
14 Pl=Ia*Ia*Ra+Pk
15 Pin=V*I
16 effi=(Pin-Pl)/Pin
17 disp(effi)
18
19 Ia=sqrt(Pk/Ra)
20 Il=Ia+If
21 Pl=2*Pk
22 Pin=V*Il
23 effi=(Pin-Pl)/Pin
24 disp(effi)

```

Scilab code Exa 10.16 Problem16

```

1 V=250
2 Rf=125
3 Ra=0.2
4 If=V/Rf
5 I=16
6 Ia0=I-If
7 Pk=V*Ia0-Ia0*Ia0*Ra+V*If
8
9 I=152
10 Ia=I-If
11 Pl=Ia*Ia*Ra+Pk
12 Pin=V*I
13 effi=(Pin-Pl)/Pin
14 disp(effi)
15
16 Il=152

```

```
17 Ia=I1+If
18 P1=Ia*Ia*Ra+Pk
19 Pout=V*I1
20 effi=Pout/(Pout+P1)
21 disp(effi)
```

Scilab code Exa 10.17 Problem17

```
1 V=250
2 n=800
3 Ra=0.15
4 Rse=0.1
5 R=Ra+Rse
6
7 Ia1=120
8 Ea1=V-Ia1*R
9
10 Ia2=60
11 Ea2=V-Ia2*R
12 n2=Ea2/Ea1*n/0.7
13 disp(n2)
```

Scilab code Exa 10.18 Problem18

```
1 R=1.2
2 V=220
3 Ea35=V-35*R
4 n35=(475+400)/2
5
6 V=200
7 E0=V-35*(R+2)
8 n=n35*E0/Ea35
9 disp(n)
```

Scilab code Exa 10.19 Problem19

```
1 V=250
2 Ia=200
3 Ra=0.22
4
5 Ea=V-Ia*Ra
6 Pm=Ea*Ia
7 Prl=600
8 Pmout=Pm-Prl
9 n=1250
10 wm=2*%pi*n/60
11 Tl=Pmout/wm
12 disp(Tl)
13
14 Rf=125
15 Psh=V*V/Rf
16 Pein=V*Ia+Psh
17 effi=Pmout/Pein
18 disp(effi)
```

Scilab code Exa 10.20 Problem20

```
1 P=25000
2 n=1600
3 V=250
4 If=1.5
5 Rf=V/If
6 disp(Rf)
7
8 Ra=0.1
```

```
9 V=220
10 Ia=P/V
11 Ea=V-Ia*Ra
12 If=0.875
13 disp(If)
14 Rf=V/If
15 disp(Rf)
16
17 Pdev=Ea*Ia
18 disp(Pdev)
19 Tdev=Pdev/2/%pi/n*60
20 disp(Tdev)
```

Scilab code Exa 10.21 Problem21

```
1
2 V=230
3 Ea=210
4 Ia=40
5 Ra=(V-Ea)/Ia
6 disp(Ra)
7
8 Pdev=Ea*Ia
9 n=1200
10 wm=2*%pi*n/60
11 Tdev=Pdev/wm
12 disp(Pdev)
13 disp(Tdev)
14
15 n=n*V/Ea
16 disp(n)
```

Scilab code Exa 10.22 Problem22

```
1 V=400
2 Ia=50
3 n=500
4 Ra=0.5
5 Ea=V-Ia*Ra
6 Tdev=Ea*Ia/2/%pi/n*60
7
8 Iastart=75
9 Rs=V/Iastart-Ra
10 disp(Rs)
11 Tstart=Tdev*(Iastart/Ia)^2
12 disp(Tstart)
13
14 n2=200
15 Ea200=Ea*n2/n
16 Rs=(V-Ea200)/Iastart-Ra
17 disp(Rs)
```

Scilab code Exa 10.23 Problem23

```
1 n1=1200
2 Rfcrit=260/4
3 n2=1600
4 Vfactor=n2/n2
5 Vn1=395
6 disp(Vn1)
```

Scilab code Exa 10.24 Problem24

```
1
2 Ia=500
3 Ra=0.05
4 Vb=2
```

```
5 Va=Ia*Ra+Vb
6 Vt=330
7 disp(Vt)
```

Scilab code Exa 10.25 Problem25

```
1 V=240
2 Ea=V
3 n=800
4 I=16
5 Ke=V/n/I
6 K=I/n
7
8 n=sqrt(V*2/Ke/K/sqrt(2))
9 disp(n)
10 Ia=sqrt(2)*K*n
11 disp(Ia)
```

Scilab code Exa 10.26 Problem26

```
1 V=600
2 Pout=60000
3 effi=0.85
4 Pin=Pout/effi
5 Il=Pin/V
6 Rf=100
7 If=V/Rf
8 Ia=Il-If
9 Ra=0.16
10 Ea=V-Ia*Ra
11
12 n=900
13 n0=n*V/Ea
```

```
14 sr=n0/n-1
15 disp(n0)
16 disp(sr)
17
18 TL=Pin-Pout
19 Pcu=Ia*Ia*Ra
20 Psh=If*If*Rf
21 Prl=TL-Pcu-Psh
22 disp(Prl)
```

Chapter 11

Synchronous Machine

Scilab code Exa 11.1 Problem1

```
1 P=1000000
2 Vrated=6600
3 If=60
4 Xs_unsat=4700/sqrt(3)/98
5 disp(Xs_unsat)
6 Xs_adj=Vrated/sqrt(3)/143
7 disp(Xs_adj)
8
9 Ia=P/sqrt(3)/Vrated
10 pf=0.8
11 theta=-acos(pf)
12 Ia=Ia*(exp(%i*theta))
13 Ef=norm(Vrated+%i*Xs_adj*Ia*sqrt(3))
14 disp(Ef)
15 VR=Ef/Vrated-1
16 disp(VR)
```

Scilab code Exa 11.2 Problem2

```

1 P=45000
2 V=440
3 pf=0.8
4 Ia=P/sqrt(3)/V*exp(%i*acos(pf))
5 Vt=V/sqrt(3)
6 Rs=0.2
7 Xs=1.8
8 Ef=norm(Vt-Ia*(Rs+%i*Xs))
9 If=Ef/85
10 Pein=pf*P
11 Rf=35
12 Fl=If*If*Rf
13 Pin=Pein+Fl
14 Pcu=norm(3*Ia*Ia*Rs)
15 Pshaft=Pein-Pcu
16 Prl=1500
17 Pshaft_net=Pshaft-Prl
18 effi=Pshaft_net/Pin
19
20 disp(Pshaft_net)
21 disp(If)
22 disp(effi)

```

Scilab code Exa 11.3 Problem3

```

1 V=12500
2 Xs=8
3
4 Vt=V/sqrt(3)
5 Ef=Vt
6
7 Ef=Vt*1.2
8 Ia=(Ef-Vt)/Xs
9 theta=%pi/2
10 pf=0

```

```

11 Pe=0
12 Qe=-sqrt(3)*V*Ia
13 disp(Ia)
14 disp(Pe)
15 disp(Qe)
16 disp(pf)
17
18 Ef=Vt*0.8
19 Ia=(Vt-Ef)/Xs
20 theta=-%pi/2
21 pf=0
22 Pe=0
23 Qe=sqrt(3)*V*Ia
24 disp(Ia)
25 disp(Pe)
26 disp(Qe)
27 disp(pf)

```

Scilab code Exa 11.4 Problem4

```

1 Pe=10000000
2 V=12500
3 Xs=8
4 Vt=V/sqrt(3)
5 Ef=Vt*1.2
6
7 delta=asin(Pe/3/Vt/Ef*Xs)
8 Ia=(Ef*exp(%i*delta)-Vt)/%i/Xs
9 pf=real(Ia)/norm(Ia)
10 Qe=-sqrt(3)*V*imag(Ia)
11
12 disp(norm(Ia))
13 disp(pf)
14 disp(Qe)

```

Scilab code Exa 11.5 Problem5

```
1
2 Pein=1000000
3 pf=0.9
4 Xs=3.24
5 theta=acos(pf)
6 V=3300
7 Ia=Pein/sqrt(3)/pf/V*exp(%i*theta)
8 Vt=V/sqrt(3)
9 Ef=norm(Vt-%i*Ia*Xs)
10 Pemax=3*Vt*Ef/Xs
11 Ia=(Vt+Ef*%i)/%i/Xs
12 Qe=-sqrt(3)*V*imag(Ia)
13
14 disp(Pemax)
15 disp(norm(Ia))
16 disp(real(Ia)/norm(Ia))
17 disp(Qe)
```

Scilab code Exa 11.6 Problem6

```
1 Pe=20000
2 Pm=20000
3 V=400
4 pf=0.8
5 Xs=4.5
6 Ia=Pm/sqrt(3)/V/pf*exp(%i*acos(pf))
7 Vt=V/sqrt(3)
8 Ef=Vt-%i*Ia*Xs      ///calculation mistake in the
                       ///book at this step
9 Eflin=norm(Ef)*sqrt(3)
```

```

10 disp(Efline)
11 disp(atan(imag(Ef)/real(Ef)))
12
13 delta=-%pi/2
14 Efmin=Pe/3*Xs/Vt*sin(-delta)
15 Efminline=Efmin*sqrt(3)
16 disp(Efminline)
17 disp(delta/%pi*180)
18 Ia=(Vt+%i*Efmin)/%i/Xs
19 disp(norm(Ia))
20 disp(real(Ia)/norm(Ia))

```

Scilab code Exa 11.7 Problem7

```

1 f=50
2 ns=100
3 P=110000
4 pf=0.8
5
6 p=120*f/ns
7 disp(p)
8 kVA=P/pf/1000
9 disp(kVA)
10 kW=P/0.971/1000
11 disp(kW)
12 Tpm=kW*1000*60/2/%pi/ns
13 disp(Tpm)

```

Scilab code Exa 11.8 Problem8

```

1 P=12E6
2 Q=6E6
3 V=22000

```

```

4 Xs=8
5 S=P+%i*Q
6 theta=atan(Q/P)
7 disp(theta/%pi*180)
8
9 Ia=norm(S)/sqrt(3)/V
10 Ef=V/sqrt(3)+%i*Xs*Ia*exp(-%i*theta)
11 delta=atan(imag(Ef)/real(Ef))
12 disp(delta/%pi*180)
13
14 emf=norm(Ef)*sqrt(3)
15 disp(emf)

```

Scilab code Exa 11.9 Problem9

```

1 Isc=60
2 If=50
3
4 Voc=15300
5 Isc=60
6 Xs_unsat=Voc/sqrt(3)/Isc
7 disp(Xs_unsat)
8
9 V=11000
10 Isc=67.5
11 Xs_sat=V/sqrt(3)/Isc
12 disp(Xs_sat)
13
14 pf=0.85
15 theta=acos(pf)
16 Ia=50*exp(-%i*theta)
17 Vt=11000
18 Vl=Vt/sqrt(3)
19 Ef=Vl+%i*Xs_sat*Ia
20 Efline=norm(Ef)*sqrt(3)

```

```

21 disp(Efline)
22
23 Voc=Efline
24 VR=Voc/Vt-1
25 disp(VR)
26 If=57.5
27 disp(If)

```

Scilab code Exa 11.10 Problem10

```

1 P=10000
2 V=400
3 pf=0.8
4 Xs=16
5 theta=acos(pf)
6 Ia=P/sqrt(3)/V*exp(-%i*theta)
7 Vt=V/sqrt(3)
8 Ef=Vt+%i*Xs*Ia
9 disp(norm(Ef))
10 disp(atan(imag(Ef)/real(Ef))*180/%pi)
11
12 Ef2=1.2*norm(Ef)
13 Pe=P*pf
14 delta=asin(norm(Pe/3*Xs/Ef2/Vt))
15 Ef2=Ef2*exp(%i*delta)
16 Ia=(Ef2-Vt)/%i/Xs //calculation mistake in the
    book at this point
17 disp(norm(Ia))
18 pf=real(Ia)/norm(Ia)
19 disp(pf)
20 disp(acos(pf)*180/%pi)
21
22 delta=%pi/2
23 Pemax=norm(3*Ef*Vt/Xs*sin(delta))
24 disp(Pemax)

```

```

25 Ef=norm(Ef)*%i
26 Ia=(Ef-Vt)/%i/Xs
27 disp(norm(Ia))
28 disp(real(Ia)/norm(Ia))

```

Scilab code Exa 11.11 Problem11

```

1 f=50
2 MechLoad=(8+0.5)*1000
3 Pein=MechLoad
4 Vt=231
5 Ef=750/sqrt(3)
6 Xs=16
7 delta=asin(Pein/3*Xs/Ef/Vt)
8 Ef=Ef*exp(-%i*delta)
9 Ia=(Vt-Ef)/%i/Xs
10 ns=120*50/4
11 ws=ns/60*2*%pi
12 Tdev=Pein/ws
13 Tshaft=8000/ws
14 disp(norm(Ia))
15 disp(real(Ia)/norm(Ia))
16 disp(acos(real(Ia)/norm(Ia))*180/%pi)
17 disp(Tdev)
18 disp(Tshaft)
19
20 Ef=600/sqrt(3)
21 delta=0
22 Ia=(Vt-Ef)/%i/Xs
23 kVAR=sqrt(3)*400*norm(Ia)
24 disp(norm(Ia))
25 disp(real(Ia)/norm(Ia))
26 disp(kVAR)
27 C=norm(Ia)/Vt/2/%pi/f
28

```



```

29 Ef=300/sqrt(3)
30 Ia=(Vt-Ef)/%i/Xs
31 kVAR=sqrt(3)*400*norm(Ia)
32 disp(norm(Ia))
33 disp(real(Ia)/norm(Ia))
34 disp(kVAR)
35 L=Vt/norm(Ia)/2/%pi/f
36
37 kVAR=6000
38 Ia=kVAR/sqrt(3)/400*%i
39 Ef=Vt-%i*Xs*Ia
40 disp(Ef*sqrt(3))

```

Scilab code Exa 11.12 Problem12

```

1 P=1000000
2 V=6600
3 Xs=25
4 pf=0.8
5 theta=acos(pf)
6 Ia=P/sqrt(3)/V*exp(-%i*theta)
7 Vt=V/sqrt(3)
8 Ef=Vt+%i*Xs*Ia
9 delta=asin(norm(Xs*Ia*cos(theta)/Ef))
10 Vt=norm(Ia)*Xs*sin(%pi-asin(pf)-delta)/sin(delta)
11 V1=Vt*sqrt(3)
12 disp(V1)

```

Scilab code Exa 11.13 Problem13

```

1
2
3 Xs=8

```

```

4 Ia=40
5 V=600
6 Vt=V/sqrt(3)
7 Ef=V
8
9 delta=acos((1-(Xs*Ia/V)^2+(Vt/V)^2)/2/Vt*V)
10 theta=-atan((cos(delta)-Vt/V)/sin(delta))
11 pf=cos(theta)
12 Pout=sqrt(3)*V*pf*Ia
13 disp(Pout)
14
15 theta=-theta
16 Pin=Pout
17 disp(Pout)

```

Scilab code Exa 11.14 Problem14

```

1
2 V=400
3 Vt=V/sqrt(3)
4 Ia=50
5 pf=1
6 theta=0
7 Xs=1.3
8
9 Ef=Vt-%i*Xs*Ia
10 delta=atan(imag(Ef)/real(Ef))
11 disp(delta*180/%pi)
12
13 Pelec=sqrt(3)*V*pf*Ia
14 Pmech=Pelec
15 pf=0.8
16 theta=acos(0.8)
17 Ia=Pelec/sqrt(3)/V/pf*exp(%i*theta)
18 Ef2=Vt-%i*Xs*Ia

```

```
19 If=0.9*norm(Ef2)/norm(Ef)
20 disp(If)
```

Scilab code Exa 11.15 Problem15

```
1 Xspu=0.8
2 P=1000000
3 V=3000
4 Xs=Xspu*V*V/P
5
6 Vt=V/sqrt(3)
7 Pm=750000
8 Pe=Pm
9 pf=0.85
10 theta=acos(pf)
11 Ia=Pm/0.8/sqrt(3)/V*exp(-%i*theta)
12
13 Ef=Vt-%i*Xs*Ia
14 Efline=sqrt(3)*norm(Ef)
15 disp(Efline)
16
17 delta=%pi/2
18 Pmax=3*Vt*norm(Ef)/Xs
19 disp(Pmax)
20 ns=120*50/12
21 ws=ns*2*%pi/60
22 Tmax=Pmax/ws          // calculation mistake in the
    book at this point
23 disp(Tmax)
24
25 delta=90
26 Efmin=Pm/3*Xs/Vt
27 Efmin_line=sqrt(3)*Efmin
28 disp(Efmin_line)
29
```

```
30 Ia=(Vt+%i*Efmin)/%i/Xs
31 disp(norm(Ia))
32 pf=real(Ia)/norm(Ia)
33 disp(pf)
```

Chapter 12

Induction Motor

Scilab code Exa 12.1 Problem1

```
1 V=400
2 I=80
3 pf=0.75
4 Pin=sqrt(3)*V*I*pf
5 Pshaft=Pin*0.85
6 disp(Pshaft)
7 ns=1000
8 s=0.04
9 n=(1-s)*ns
10 w=2*%pi*n/60
11 Tshaft=Pshaft/w
12 disp(Tshaft)
```

Scilab code Exa 12.2 Problem2

```
1 f=50
2 f2=120/60
3 s=f2/f
```

```

4 ns=1500
5 n=(1-s)*ns
6 w=2*%pi*n/60
7
8 T=100
9 Pshaft=T*w
10 disp(Pshaft)
11 Pm=(T+7)*w
12 Pcur=Pm*s/(1-s)
13 disp(Pcur)
14 Pin=Pm+Pcur+700
15 disp(Pin)
16 effi=Pshaft/Pin
17 disp(effi)

```

Scilab code Exa 12.3 Problem3

```

1
2 ns=120*50/20
3 sf1=1-292.5/ns
4
5 R2=0.12
6 X2=1.12
7 smaxT=R2/X2
8 disp(smaxT)
9
10 Tmax_by_Tf1=0.5/X2/(R2/sf1/((R2/sf1)^2+X2^2))
11 disp(Tmax_by_Tf1)

```

Scilab code Exa 12.5 Problem5

```

1
2 ns=750

```

```

3 R2=0.5
4 X2=5
5 smaxT=R2/X2
6 n=(1-smaxT)*ns
7 disp(n)
8
9 k=R2/X2
10 Tmax_by_Tstart=(1+k*k)/2/k
11 disp(Tmax_by_Tstart)
12
13 p=poly([1,-4,1],"k","coeff")
14 w=roots(p)
15 R2=w*5
16 R2ext=R2-0.5
17
18 R2total=18.66
19 smaxT=R2total/X2
20 R2ext=R2ext(2)
21 disp(R2ext)

```

Scilab code Exa 12.6 Problem6

```

1
2 Tmax=200
3 Tstart=80
4
5 p=poly([1,-2*Tmax/Tstart,1],"smaxT","coeff")
6 smaxT=roots(p)
7 smaxT=smaxT(2)
8 disp(smaxT)
9
10
11 p=poly([1,-4,1],"w","coeff")
12 w=roots(p)
13 sfl=smaxT/w(1)

```

```

14 disp(sf1)
15
16 ratio=sqrt(((smaxT/sf1)^2+1)/(smaxT^2+1))
17 disp(ratio)
18
19 p=poly([1,-((smaxT/sf1)^2+1)*sf1,smaxT^2],"k","coeff
      ")
20 k=roots(p)
21 k=k(2)
22 disp(k)

```

Scilab code Exa 12.7 Problem7

```

1 V=440
2 ns=1000
3 ws=2*%pi*ns/60
4 n=975
5 s=1-n/ns
6 Z=1.06+0.576/s+%i*(1.68+0.75)
7 I2=V/sqrt(3)/Z
8 Im=-%i*V/sqrt(3)/44.2
9 I1=Im+I2
10 pf=real(I1)/norm(I1)
11 Pin=sqrt(3)*V*norm(I1)*pf
12 Pout=norm(3*I2*I2*0.576*(1/s-1))-415
13 effi=Pout/Pin
14 Tnet=Pout/ws/(1-s)
15
16 disp(Tnet)
17 disp(Pin)
18 disp(norm(I1))
19 disp(pf)
20 disp(effi)

```

Scilab code Exa 12.8 Problem8

```
1 V=400
2 P0=1210
3 I0=8.7
4 Ri=(V/sqrt(3))^2/P0*3
5 disp(Ri)
6 pf=P0/sqrt(3)/V/I0
7 theta0=acos(pf)
8 Xm=Ri/tan(theta0)
9 disp(Xm)
10
11 P1=6050
12 V1=200
13 I1=47.8
14 R=P1/3/I1/I1
15 R1=0.42
16 disp(R1)
17 R2=R-R1
18 disp(R2)
19 Z=V1/sqrt(3)/I1
20 X=sqrt(Z*Z-R*R)
21 disp(X)
22
23 ns=750
24 n=710
25 ws=ns*2*%pi/60
26 s=1-n/ns
27 Z=R1+R2/s+%i*X
28 I2=V/sqrt(3)/Z
29 I0=I0*exp(-%i*theta0)
30 I1=I0+I2
31 disp(norm(I1))
32 pf=real(I1)/norm(I1)
```

```

33 disp(pf)
34 T=norm(3*I2*I2*R2/s/ws)
35 disp(T)
36 Pout=T*ws*(1-s)
37 Pin=sqrt(3)*V*norm(I1)*pf
38 effi=Pout/Pin
39 disp(effi)
40
41 s=1
42 Z=R+%i*X
43 I2=V/sqrt(3)/Z
44 I1=I0+I2
45 disp(norm(I1))
46 Tstart=norm(3*I2*I2*R2/s/ws)
47 disp(Tstart)
48
49 smaxT=R2/sqrt(R1^2+X^2)
50 Z=R1+R2/smaxT+%i*X
51 I2=V/sqrt(3)/norm(Z)
52 Tmax=3*I2*I2*R2/smaxT/ws
53 disp(Tmax)
54 disp(smaxT)

```

Scilab code Exa 12.9 Problem9

```

1 Is_by_Ifl=5
2 sfl=0.04
3 Ts_by_Tfl=Is_by_Ifl^2*sfl
4 disp(" pu" ,Ts_by_Tfl)

```

Scilab code Exa 12.10 Problem10

1

```

2 R2=0.5
3 X2=5
4 Tm_by_Tf1=3.5
5
6 Ts_by_Tf1=R2*Tm_by_Tf1*2*X2/(R2^2+X2^2)
7 disp(Ts_by_Tf1)
8
9 Ts_by_Tf12=Ts_by_Tf1/3
10 disp(Ts_by_Tf12)
11
12 Ts_by_Tf13=0.7*0.7*Ts_by_Tf1 //calculation
    mistake in the book at this point
13 disp(Ts_by_Tf13)

```

Scilab code Exa 12.11 Problem11

```

1
2 s1=1-960/1000
3 s2=1-800/1000
4 R2ext=4/3*s2*0.25/s1-0.25
5 disp(R2ext)

```

Scilab code Exa 12.12 Problem12

```

1
2 smaxT=1-860/1000
3 R2=0.25
4 X2=R2/smaxT
5 Tmax=180
6 k=Tmax*X2
7
8 s=0.045

```

```

9 T=2*100.6/((R2/s)^2+X2^2)*R2/s //some mistake in
   the book at this point. (What is V1/a)
10 T=105
11 disp(T)
12
13 R2ext=X2-R2
14 disp(R2ext)

```

Scilab code Exa 12.13 Problem13

```

1 V=400
2 Poutmech=5000
3 Pr1=285
4 Pm=Poutmech+Pr1
5 s=1-1445/1500
6 s2=1-900/1500
7
8
9
10 p=poly([0,-(1-s)*V*V/Pm/s,1/s/s+1/s2/s2], "R2", "coeff
   ")
11 r=roots(p)
12 R2=r(1)
13 X2=R2/s2
14
15 ws=2*%pi*1500/60
16 Tmax=3/ws*V*V/3*0.5/X2
17 disp(Tmax)

```

Scilab code Exa 12.14 Problem14

```

1 Pmout=20000
2 Pwfl=1500

```

```

3 Pm=Pmout+Pwfl
4 disp(Pm)
5 ns=1500
6 n=1440
7 s=1-n/ns
8 Pg=Pm/(1-s)
9 disp(Pg)
10 Pcu=s*Pg
11 disp(Pcu)

```

Scilab code Exa 12.15 Problem15

```

1 V1=400
2 R1=2.28*3/2
3 R1ac=1.1*3.42
4
5 Y0=3.5/sqrt(3)/V1
6 Gi=(445/3)/V1/V1
7 Bm=sqrt(Y0^2-Gi^2)
8 Ri=1/Gi
9 Xm=1/Bm
10
11 V2=200
12 Z=V2/16.7*sqrt(3)
13 R=2220/16.7/16.7
14 X=sqrt(Z*Z-R*R)
15 R2=R-R1ac
16
17 n=935
18 ns=1000
19 s=1-n/ns
20 Z=R1ac+R2/s+%i*X
21 I2=V1/Z
22 Ii=V1/Ri-%i*V1/Xm
23 I1=I2+Ii

```

```

24 Iline=norm(I1)*sqrt(3)
25 pf=real(I1)/norm(I1)
26 ws=2*%pi*ns/60
27 T=norm(3*I2*I2*R2/s/ws)
28 disp(T)
29 disp(Iline)
30
31 Pm=norm(3*I2*I2*R2*(1-s)/s)
32 Pin=sqrt(3)*V1*Iline*pf
33 effi=Pm/Pin
34 disp(effi)
35
36 V=400
37 s=1
38 Z=R1ac+R2/s+%i*X
39 I2=V/sqrt(3)/Z      ////calculation mistake in the
      book at this step
40 Ts=norm(3*I2*I2*R2/ws)
41 disp(Ts)

```

Scilab code Exa 12.16 Problem16

```

1 V=400
2 Pmout=5000
3 Pr1=285
4 Pm=Pmout+Pr1
5
6 s=1-1445/1500
7 smaxT=1-900/1500
8 R2=(1/s-1)*V*V/Pm/(1/s^2+1/smaxT^2)
9 X2=R2/smaxT
10 ws=2*%pi*1500/60
11 Tmax=V*V/ws/2/X2
12 disp(Tmax)

```

Scilab code Exa 12.17 Problem17

```
1 V=440
2 I=25
3 pf=0.85
4 Pin=sqrt(3)*V*I*pf
5 ns=1500
6 Pcore=750
7 Pcus=950
8 Pcur=450
9 Pwfl=250
10
11 Pg=Pin-Pcore-Pcus
12 disp(Pg)
13
14 Pm=Pg-Pcur
15 disp(Pm)
16
17 Pmout=Pm-Pwfl
18 disp(Pmout)
19
20 effi=Pmout/Pin
21 disp(effi)
22
23 s=Pcur/Pg
24 n=(1-s)*ns
25 disp(n)
26
27 w=2*%pi*n/60
28 Tdev=Pm/w
29 disp(Tdev)
30 Tnet=Pmout/w
31 disp(Tnet)
```

Chapter 14

Measurement Techniques and Electric and Electronic Instrumentation

Scilab code Exa 14.1 Problem1

```
1 Rv1=60/1000*10000
2 Rv2=120/1000*10000
3 Rx=(Rv2-Rv1)*(1/(27.5/30*2-1)-1)
4 I=27.5/1000/600*(Rx+600)/Rx
5 Vact=Rx*I
6 disp(Vact)
```

Scilab code Exa 14.2 Problem2

```
1
2 Ifsd=25/1000
3 Ix=4.975
4 Rx=Ifsd*5/Ix
5 disp(Rx)
```



```
6
7 Rx=20/Ifsd-5
8 disp(Rx)
```

Scilab code Exa 14.3 Problem3

```
1
2 R1=40/0.025-5
3 R2=60/0.025-5-R1
4 disp(R1)
5 disp(R2)
```

Scilab code Exa 14.4 Problem4

```
1
2 W1=500
3 W2=-200
4 P=W1+W2
5 phi=atan((W1-W2)/(W1+W2))
6 pf=cos(phi)
7 disp(pf)
8 disp(P)
```

Scilab code Exa 14.5 Problem5

```
1
2 E=4
3 R1=800
4 R2=80
5 R3=1605
```

```

6 R4=160
7 Rg=80
8 s=8
9
10 Eth=E*(R2/(R2+R4)-R1/(R1+R3))
11 Rth=R1*R3/(R1+R3)+R2*R4/(R2+R4)
12 Ig=Eth/(Rth+Rg)
13 D=s*Ig*1000000
14 disp(D)

```

Scilab code Exa 14.6 Problem6

```

1 function Zeq=parallel(Z1,Z2)
2     Zeq=Z1*Z2/(Z1+Z2)
3 endfunction
4
5 f=1000
6 w=2*%pi*f
7
8 ///AB
9 R=2000
10 C=0.045E-6
11 Xc=1/%i/w/C
12 Z1=parallel(R,Xc)
13
14 ///BC
15 R=1000
16 C=0.45E-6
17 Xc=1/%i/w/C
18 Z2=R+Xc
19
20 ///AD
21 C=0.4E-6
22 Z3=1/%i/w/C
23

```

```
24 Z4=Z2*Z3/Z1
25 disp(Z4)
```

Scilab code Exa 14.7 Problem7

```
1
2 ksine=1.11
3 ksqr=1
4
5 err=(ksine-ksqr)/ksqr*100
6 disp(" percent",err)
```

Scilab code Exa 14.8 Problem8

```
1
2 f=50E6
3 w=2*%pi*f
4 theta=5*%pi/180
5
6
7 C=1E-12
8 R=1/theta/w/C
9 disp(R)
10
11 C=10E-12
12 R=1/theta/w/C
13 disp(R)
14
15 C=100E-12
16 R=1/theta/w/C
17 disp(R)
```

Scilab code Exa 14.9 Problem9

```
1
2 f=8E6
3 w=2*%pi*f
4 C=150E-12
5 R=5
6
7 Q1=1/w/C/R
8
9 Rins=0.1
10 Q2=1/w/C/(R+Rins)
11 err=(Q1-Q2)/Q1*100
12 disp(err)
```

Scilab code Exa 14.10 Problem10

```
1 f=100E3
2 w=2*%pi*f
3 C=400E-12
4
5 L=1/C/w/w
6 disp(L)
```

Scilab code Exa 14.11 Problem11

```
1
2 Resolution=1/10^4
3 disp(Resolution)
```

```
4
5 disp(" 14.760")
6
7 R_1V=1*Resolution
8 disp(" 0.5434") ///since any digits upto 4th decimal
   can be shown
9
10 R_10V=10*Resolution
11 disp(" 00.543") ///since only three decimal digits
   can be shown
```

Scilab code Exa 14.12 Problem12

```
1
2 Vp=10
3 Vref=5
4 R=100000
5 C=0.22E-6
6 T=Vp*R*C/Vref
7 disp(T)
```

Scilab code Exa 14.13 Problem13

```
1
2 V=3.217
3 bits=4
4 base=5
5 a=0
6
7 for i=1:bits
8     a=floor(V/base*(2^i))
9     disp(a);
10    V=V-a*base/(2^i)
```

11 end

Scilab code Exa 14.14 Problem14

```
1
2 reading=5
3 x=0.005/100*reading //0.005% of reading
4 err=x+1E-6 //final digit
5 disp("seconds",err)
6
7 reading=500
8 x=0.005/100*reading //0.005% of reading
9 err=x+1 //final digit
10 disp("seconds",err)
```

Scilab code Exa 14.15 Problem15

```
1 V=5.9
2 Rx=0
3 Rm=2000
4 R1=49000
5 Ifsd=100E-6
6 Vam=Rm*Ifsd
7 I=(V-Vam)/R1
8 Ish=I-Ifsd
9 R2=Vam/Ish
10 disp(R2)
11
12 I=0.6*I
13 Req=V/I
14 Rx=Req-R1-Rm*R2/(R2+Rm)
15 disp(Rx)
```

Scilab code Exa 14.17 Problem17

```
1 f=50
2 w=2*%pi*f
3
4 Z2=1000
5 Z3=16800
6
7 C=0.38E-6
8 Xc=1/%i/w/C
9 Z4=833+Xc
10
11 Z1=Z2*Z3/Z4
12 Rx=real(Z1)
13 Lx=imag(Z1)/w
14
15 disp(Rx)
16 disp(Lx)
```

Scilab code Exa 14.18 Problem18

```
1 f=50
2 w=2*%pi*f
3 T=1/f
4
5 Iav=1/(T/2)*integrate('sin(w*t)', 't', 0, T/2)
6 disp(Iav)
```

Chapter 15

Power Systems

Scilab code Exa 15.1 Problem1

```
1 V1=250
2 V2=480
3 Vol2_by_Vol1=V1/V2
4
5 sav=(1-Vol2_by_Vol1)*100
6 disp(sav)
```

Scilab code Exa 15.2 Problem2

```
1 P=5E6
2 pf=0.85
3 V=33000
4 l=50000
5 rho=3E-8
6 Pt=P*pf
7 Pl=Pt*0.1
8 I=P/V
9 A1=2*I*I*rho*l/Pl
```



```
10 Vol1=2*1*A1
11 disp(Vol1)
12
13 I1=P/sqrt(3)/V
14 A2=3*I1*I1*rho*l/P1
15 Vol2=3*1*A2
16 disp(Vol2)
```

Scilab code Exa 15.3 Problem3

```
1 f=50
2 w=2*%pi*f
3 I=0.8
4 V=220
5 P=75
6 phi=acos(P/V/I)
7
8 phi_new=acos(0.9)
9 Ic=I*cos(phi)*(tan(phi)-tan(phi_new))
10 C=Ic/V/w
11 disp(C)
12
13 phi_new=acos(1)
14 Ic=I*cos(phi)*(tan(phi)-tan(phi_new))
15 C=Ic/V/w
16 disp(C)
```

Scilab code Exa 15.4 Problem4

```
1 Cond_cost=100
2 charge=60
3 phi2=asin(0.1*Cond_cost/charge)
4 pf=cos(phi2)
```

5 `disp(pf)`

Scilab code Exa 15.5 Problem5

```
1
2 Oc=400000
3 pf1=0.8
4 phi1=acos(pf1)
5 ab=Oc/cos(phi1)*sin(phi1)
6 pf2=0.25
7 phi3=acos(pf2)
8 pf2=0.484
9
10 gammaa=(ab-pf2*Oc)/(pf2*cos(phi3)+sin(phi3))
11 disp(gammaa)
```

Scilab code Exa 15.6 Problem6

```
1 f=50
2 w=2*%pi*f
3 P=2E6
4 V=11000
5 pf=0.8
6 phi=acos(pf)
7 Xl=10
8 IR=P/sqrt(3)/V/pf
9 Vr=V/sqrt(3)
10 Vs=Vr+IR*Xl*sin(phi)
11 Vs11=Vs*sqrt(3)
12 disp(Vs11)
13 VR=Vs11/V-1
14 disp(VR)
15
```

```

16 pf=1
17 disp(pf)
18 Qc=P*tan(phi)
19 C=Qc/V/V/w
20 disp(C)

```

Scilab code Exa 15.7 Problem7

```

1 f=50
2 w=2*%pi*f
3 V=33000
4 Vr=V/sqrt(3)
5 P=24E6/3
6 pf=0.8
7 phi=acos(pf)
8 Ia=P/Vr/pf
9 Rl=4
10 Xl=20
11 Vs=Vr+Ia*(Xl*sin(phi)+Rl*cos(phi))
12 Vsll=sqrt(3)*Vs
13 VR=Vsll/V-1
14 disp(Vsll)
15 Ia=Ia*exp(-%i*phi)
16 disp(norm(Ia))
17
18 phi1=atan(-Rl/Xl)
19 pf=cos(phi1)
20 Ia1=P/Vr/pf
21 Ia1=Ia1*exp(-%i*phi1)      ////calculation mistake
    in the book at this step
22
23 Ic=Ia1-Ia
24 C=norm(Ic/w/Vr)
25 disp(C)
26

```

```
27 LL1=norm(Ia*Ia*R1)
28 effi1=P/(P+LL1)
29 LL2=norm(Ia1*Ia1*R1)
30 effi2=P/(P+LL2)
31 disp(effi1)
32 disp(effi2)
```
