

Scilab Textbook Companion for  
Basic Electrical Engineering  
by D. P. Kothari And I. J. Nagrath<sup>1</sup>

Created by  
Ashish Bora  
B. Tech.  
Electrical Engineering  
IIT Bombay  
College Teacher  
Prof. Madhu Belur  
Cross-Checked by  
Lavitha Pereira

August 21, 2013

<sup>1</sup>Funded by a grant from the National Mission on Education through ICT,  
<http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab  
codes written in it can be downloaded from the "Textbook Companion Project"  
section at the website <http://scilab.in>

# **Book Description**

**Title:** Basic Electrical Engineering

**Author:** D. P. Kothari And I. J. Nagrath

**Publisher:** Tata McGraw - Hill Education, New Delhi

**Edition:** 3

**Year:** 2010

**ISBN:** 9780070146112

Scilab numbering policy used in this document and the relation to the above book.

**Exa** Example (Solved example)

**Eqn** Equation (Particular equation of the above book)

**AP** Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

# Contents

<b>List of Scilab Codes</b>	<b>4</b>
<b>1 Elementary Concepts and Definitions</b>	<b>13</b>
<b>2 Fundamentals of Resistive Circuits</b>	<b>24</b>
<b>3 Fundamentals of Reactive Circuits</b>	<b>43</b>
<b>4 Steady State Analysis For Sinusoidal Excitation</b>	<b>56</b>
<b>5 Frequency Response</b>	<b>88</b>
<b>6 Three Phase Circuits</b>	<b>101</b>
<b>7 Magnetic Circuits</b>	<b>115</b>
<b>8 Transformers</b>	<b>127</b>
<b>9 EMF and Torque in Electric Machines</b>	<b>151</b>
<b>10 DC Machines</b>	<b>160</b>
<b>11 Synchronous Machine</b>	<b>176</b>
<b>12 Induction Motor</b>	<b>188</b>
<b>14 Measurement Techniques and Electric and Electronic Instrumentation</b>	<b>199</b>
<b>15 Power Systems</b>	<b>207</b>

# List of Scilab Codes

Exa 1.A.1	Additional Solved Problem 1	13
Exa 1.A.2	Additional Solved Problem 2	13
Exa 1.A.3	Additional Solved Problem 3	14
Exa 1.A.4	Additional Solved Problem 4	15
Exa 1.A.5	Additional Solved Problem 5	15
Exa 1.A.6	Additional Solved Problem 6	16
Exa 1.A.7	Additional Solved Problem 7	16
Exa 1.A.9	Additional Solved Problem 9	17
Exa 1.1	Problem1	17
Exa 1.2	Problem2	18
Exa 1.3	Problem3	19
Exa 1.5	Problem5	19
Exa 1.7	Problem7	19
Exa 1.9	Problem9	20
Exa 1.10	Problem10	21
Exa 1.11	Problem11	21
Exa 1.12	Problem12	21
Exa 1.13	Problem13	22
Exa 1.15	Problem15	22
Exa 2.1	Problem1	24
Exa 2.2	Problem2	25
Exa 2.3	Problem3	25
Exa 2.4	Problem4	26
Exa 2.5	Problem5	26
Exa 2.6	Problem6	27
Exa 2.7	Problem7	27
Exa 2.8	Problem8	27
Exa 2.9	Problem9	28

Exa 2.10	Problem10	28
Exa 2.11	Problem11	29
Exa 2.13	Problem13	29
Exa 2.14	Problem14	30
Exa 2.15	Problem15	30
Exa 2.16	Problem16	30
Exa 2.17	Problem17	31
Exa 2.18	Problem18	31
Exa 2.19	Problem19	32
Exa 2.20	Problem20	32
Exa 2.21	Problem21	33
Exa 2.22	Problem22	33
Exa 2.23	Problem23	34
Exa 2.24	Problem24	34
Exa 2.25	Problem25	35
Exa 2.26	Problem26	35
Exa 2.27	Problem27	36
Exa 2.28	Problem28	36
Exa 2.29	Problem29	37
Exa 2.30	Problem30	37
Exa 2.31	Problem31	38
Exa 2.32	Problem32	38
Exa 2.33	Problem33	39
Exa 2.35	Problem35	39
Exa 2.36	Problem36	40
Exa 2.37	Problem37	40
Exa 2.38	Problem38	41
Exa 2.39	Problem39	41
Exa 2.40	Problem40	41
Exa 3.1	Problem1	43
Exa 3.2	Problem2	43
Exa 3.3	Problem3	44
Exa 3.4	Problem4	44
Exa 3.5	Problem5	45
Exa 3.6	Problem6	45
Exa 3.7	Problem7	45
Exa 3.8	Problem8	46
Exa 3.9	Problem9	46

Exa 3.11	Problem11	47
Exa 3.12	Problem12	47
Exa 3.13	Problem13	48
Exa 3.16	Problem16	48
Exa 3.18	Problem18	49
Exa 3.21	Problem21	49
Exa 3.22	Problem22	49
Exa 3.24	Problem24	50
Exa 3.26	Problem26	50
Exa 3.27	Problem27	51
Exa 3.29	Problem29	52
Exa 3.32	Problem32	52
Exa 3.33	Problem33	53
Exa 3.36	Problem36	54
Exa 3.37.38	Problem37 and 38	54
Exa 4.1	Problem1	56
Exa 4.2	Problem2	56
Exa 4.4	Problem4	57
Exa 4.5	Problem5	57
Exa 4.6	Problem6	58
Exa 4.7	Problem7	58
Exa 4.8	Problem8	59
Exa 4.9	Problem9	61
Exa 4.10	Problem10	61
Exa 4.11	Problem11	61
Exa 4.12	Problem12	62
Exa 4.13	Problem13	63
Exa 4.14	Problem14	63
Exa 4.15	Problem15	64
Exa 4.16	Problem16	65
Exa 4.17	Problem17	66
Exa 4.18	Problem18	66
Exa 4.21	Problem21	67
Exa 4.22	Problem22	68
Exa 4.23	Problem23	68
Exa 4.24	Problem24	69
Exa 4.25	Problem25	70
Exa 4.26	Problem26	70

Exa 4.27	Problem27	71
Exa 4.28	Problem28	72
Exa 4.29	Problem29	72
Exa 4.30	Problem30	73
Exa 4.31	Problem31	73
Exa 4.32	Problem32	74
Exa 4.33	Problem33	74
Exa 4.34	Problem34	75
Exa 4.35	Problem35	76
Exa 4.36	Problem36	77
Exa 4.37	Problem37	77
Exa 4.38	Problem38	78
Exa 4.39	Problem39	79
Exa 4.40	Problem40	79
Exa 4.41	Problem41	80
Exa 4.42	Problem42	80
Exa 4.43	Problem43	81
Exa 4.44	Problem44	81
Exa 4.45	Problem45	82
Exa 4.46	Problem46	83
Exa 4.47	Problem47	83
Exa 4.48	Problem48	84
Exa 4.49	Problem49	85
Exa 4.50	Problem50	85
Exa 4.51	Problem51	86
Exa 4.52	Problem52	87
Exa 5.1	Problem1	88
Exa 5.2	Problem2	88
Exa 5.3	Problem3	89
Exa 5.4	Problem4	89
Exa 5.5	Problem5	90
Exa 5.6	Problem6	90
Exa 5.7	Problem7	91
Exa 5.8	Problem8	91
Exa 5.9	Problem9	91
Exa 5.10	Problem10	92
Exa 5.11	Problem11	92
Exa 5.12	Problem12	93

Exa 5.13	Problem13	93
Exa 5.14	Problem14	94
Exa 5.15	Problem15	94
Exa 5.17	Problem17	95
Exa 5.18	Problem18	95
Exa 5.19	Problem19	96
Exa 5.20	Problem20	96
Exa 5.21	Problem21	97
Exa 5.22	Problem22	98
Exa 5.28	Problem28	98
Exa 5.29	Problem29	99
Exa 6.1	Problem1	101
Exa 6.2	Problem2	102
Exa 6.3	Problem3	102
Exa 6.4	Problem4	103
Exa 6.5	Problem5	103
Exa 6.6	Problem6	104
Exa 6.7	Problem7	104
Exa 6.9	Problem9	105
Exa 6.10	Problem10	106
Exa 6.11	Problem11	107
Exa 6.12	Problem12	107
Exa 6.13	Problem13	108
Exa 6.14	Problem14	109
Exa 6.15	Problem15	109
Exa 6.16	Problem16	110
Exa 6.17	Problem17	111
Exa 6.18	Problem18	111
Exa 6.19	Problem19	112
Exa 6.20	Problem20	112
Exa 6.21	Problem21	113
Exa 7.1	Problem1	115
Exa 7.2	Problem2	115
Exa 7.3	Problem3	116
Exa 7.4	Problem4	116
Exa 7.5	Problem5	117
Exa 7.6	Problem6	117
Exa 7.7	Problem7	118

Exa 7.8	Problem8	119
Exa 7.9	Problem9	120
Exa 7.10	Problem10	121
Exa 7.11	Problem11	122
Exa 7.12	Problem12	122
Exa 7.14	Problem14	122
Exa 7.15	Problem15	123
Exa 7.16	Problem16	124
Exa 7.17	Problem17	124
Exa 7.18	Problem18	125
Exa 7.19	Problem19	126
Exa 8.1	Problem1	127
Exa 8.2	Problem2	127
Exa 8.3	Problem3	128
Exa 8.4	Problem4	129
Exa 8.5	Problem5	130
Exa 8.6	Problem6	130
Exa 8.7	Problem7	131
Exa 8.8	Problem8	131
Exa 8.9	Problem9	132
Exa 8.10	Problem10	134
Exa 8.11	Problem11	134
Exa 8.12	Problem12	136
Exa 8.13	Problem13	137
Exa 8.14	Problem14	138
Exa 8.15	Problem15	139
Exa 8.16	Problem16	140
Exa 8.17	Problem17	141
Exa 8.18	Problem18	142
Exa 8.19	Problem19	142
Exa 8.20	Problem20	143
Exa 8.21	Problem21	144
Exa 8.22	Problem22	145
Exa 8.23	Problem23	145
Exa 8.24	Problem24	146
Exa 8.25	Problem25	146
Exa 8.26	Problem26	147
Exa 8.27	Problem27	148

Exa 8.28	Problem28	149
Exa 8.29	Problem29	149
Exa 9.1	Problem1	151
Exa 9.2	Problem2	152
Exa 9.3	Problem3	152
Exa 9.4	Problem4	153
Exa 9.5	Problem5	153
Exa 9.6	Problem6	154
Exa 9.7	Problem7	154
Exa 9.8	Problem8	155
Exa 9.9	Problem9	155
Exa 9.10	Problem10	156
Exa 9.11	Problem11	156
Exa 9.12	Problem12	157
Exa 9.13	Problem13	157
Exa 9.14	Problem14	157
Exa 9.15	Problem15	158
Exa 9.16	Problem16	158
Exa 10.1	Problem1	160
Exa 10.2	Problem2	161
Exa 10.3	Problem3	161
Exa 10.4	Problem4	162
Exa 10.5	Problem5	162
Exa 10.6	Problem6	163
Exa 10.7	Problem7	163
Exa 10.8	Problem8	164
Exa 10.9	Problem9	165
Exa 10.10	Problem10	165
Exa 10.11	Problem11	166
Exa 10.12	Problem12	167
Exa 10.13	Problem13	167
Exa 10.14	Problem14	168
Exa 10.15	Problem15	168
Exa 10.16	Problem16	169
Exa 10.17	Problem17	170
Exa 10.18	Problem18	170
Exa 10.19	Problem19	171
Exa 10.20	Problem20	171

Exa 10.21	Problem21	172
Exa 10.22	Problem22	172
Exa 10.23	Problem23	173
Exa 10.24	Problem24	173
Exa 10.25	Problem25	174
Exa 10.26	Problem26	174
Exa 11.1	Problem1	176
Exa 11.2	Problem2	176
Exa 11.3	Problem3	177
Exa 11.4	Problem4	178
Exa 11.5	Problem5	179
Exa 11.6	Problem6	179
Exa 11.7	Problem7	180
Exa 11.8	Problem8	180
Exa 11.9	Problem9	181
Exa 11.10	Problem10	182
Exa 11.11	Problem11	183
Exa 11.12	Problem12	184
Exa 11.13	Problem13	184
Exa 11.14	Problem14	185
Exa 11.15	Problem15	186
Exa 12.1	Problem1	188
Exa 12.2	Problem2	188
Exa 12.3	Problem3	189
Exa 12.5	Problem5	189
Exa 12.6	Problem6	190
Exa 12.7	Problem7	191
Exa 12.8	Problem8	192
Exa 12.9	Problem9	193
Exa 12.10	Problem10	193
Exa 12.11	Problem11	194
Exa 12.12	Problem12	194
Exa 12.13	Problem13	195
Exa 12.14	Problem14	195
Exa 12.15	Problem15	196
Exa 12.16	Problem16	197
Exa 12.17	Problem17	198
Exa 14.1	Problem1	199

Exa 14.2	Problem2	199
Exa 14.3	Problem3	200
Exa 14.4	Problem4	200
Exa 14.5	Problem5	200
Exa 14.6	Problem6	201
Exa 14.7	Problem7	202
Exa 14.8	Problem8	202
Exa 14.9	Problem9	203
Exa 14.10	Problem10	203
Exa 14.11	Problem11	203
Exa 14.12	Problem12	204
Exa 14.13	Problem13	204
Exa 14.14	Problem14	205
Exa 14.15	Problem15	205
Exa 14.17	Problem17	206
Exa 14.18	Problem18	206
Exa 15.1	Problem1	207
Exa 15.2	Problem2	207
Exa 15.3	Problem3	208
Exa 15.4	Problem4	208
Exa 15.5	Problem5	209
Exa 15.6	Problem6	209
Exa 15.7	Problem7	210

# Chapter 1

## Elementary Concepts and Definitions

**Scilab code Exa 1.A.1** Additional Solved Problem 1

```
1 t=0.1
2 R=800
3 i=50*exp(-10*t)/1000
4 v=50*cos(25*t)
5 v_i=10*t^(2.5)
6
7 P1=i*i*R
8 P2=v*v/R
9 P3=v_i
10
11 disp(P3,P2,P1)
```

---

**Scilab code Exa 1.A.2** Additional Solved Problem 2

```
1 v2=5
2 i2=v2/1000
```

```
3 v1=-i2/5
4 vs=v1
5
6 disp(vs)
```

---

### Scilab code Exa 1.A.3 Additional Solved Problem 3

```
1 L=20/1000
2
3 ///////////////////////////////////////////////////////////////////
4 disp("Part1")
5 function i = i(t)
6     i = 8*exp(-100*t);
7 endfunction
8
9 t=10/1000
10 v= L*(derivative(i,t))
11 disp(v,"V=")
12
13 /////////////////////////////////////////////////////////////////// Part2
14 disp("Part2")
15 t=0.1
16
17 function v=v(t)
18     v=6*exp(-12*t)
19 endfunction
20
21 i0=8
22
23 i2=1/L*intg(0,t,v)+i0
24 disp(i2)
25
26 /////////////////////////////////////////////////////////////////// Part3
27 disp("Part3")
28 function i3 = i3(t)
```

```
29     i3 = 10-10*exp(-50*t);
30 endfunction
31
32 t=40/1000
33 v3=L*(derivative(i3,t))
34 P40=v3*i3(t)
35 disp(P40)
36
37 t=50/1000
38 P50=1/2*L*(i3(50)^2)
39 disp(P50)
```

---

#### Scilab code Exa 1.A.4 Additional Solved Problem 4

```
1 function i = i(t)
2     i = 9*sin(%pi*t)/1000;
3 endfunction
4
5 t=200/1000
6 CV=intg(0,t,i)
7 Wc=300E-6
8 C=(CV^2)/(2*Wc)
9 disp(C)
```

---

#### Scilab code Exa 1.A.5 Additional Solved Problem 5

```
1 L=25E-3
2
3 T=5/1000
4 I=1/L*integrate('25*cos(500*t)', 't', 0, T)
5 P=25*cos(500*T)*I
6
7 t1=%pi/2/500      //// power absorbed zero
```

```
8 t2=%pi/500           /////////////////////////////////////////////////////////////////// energy stored zero  
9  
10 disp(I,P,t1,t2)
```

---

### Scilab code Exa 1.A.6 Additional Solved Problem 6

```
1 e0=8.85E-12  
2 er=1  
3 A=%pi*(1/200)^2  
4 d=150/1000000  
5 C=er*e0*A/d  
6  
7 E=1/1000  
8 v=sqrt(2*E/C)  
9 disp(v)  
10  
11 E=2/1000000  
12 v=100  
13 er=2*E/(v^2)/C  
14 disp(er)
```

---

### Scilab code Exa 1.A.7 Additional Solved Problem 7

```
1 t=10/1000  
2 v3=8*exp(-50*t)  
3 p3=v3*(-3.6)  
4 P=[230/1000*4.8; (-3.2)*1.45; p3]  
5  
6 disp("Power absorbed are respectively")  
7 disp(P)
```

---

### Scilab code Exa 1.A.9 Additional Solved Problem 9

```
1 Im=250/1000
2 w=100
3 r=4
4 L=50/1000
5 t=25/1000
6
7 i=Im*sin(w*t)
8 Vr=i*r
9 Vl=Im*L*w*cos(w*t)
10
11 Pr=i*i*r
12 P1=Vl*i
13 wl=1/2*L*i*i
14 wl_min=0 //min current =0
15 wl_max=1/2*L*Im*Im //Im is the max current
16
17 disp(" All values in Joules")
18 disp(wl_max, wl_min, wl, P1, Pr)
```

---

### Scilab code Exa 1.1 Problem1

```
1 disp(" v1=A cos(w t+p)" )
2 disp(" i1=B cos(w1 t+p1)" )
3 disp(" i2=C sin(w2 t+p2)" )
4 disp(" All values in degrees" )
5 w=input("w=")
6 p=input("p=")
7 w1=input("w1=")
8 p1=input("p1=")
9 w2=input("w2=")
10 p2=input("p2=")
11
12 if (w==w1)
```

```
13      lag1=p-p1;
14      disp(lag1, "i1 lags v1 by ")
15 else
16     disp("Lag undefined for i1")
17 end
18
19
20 if (w==w2)
21     lag2=p-p2+90;
22     disp(lag2, "i2 lags v1 by ")
23 else
24     disp("Lag undefined for i2")
25 end
```

---

### Scilab code Exa 1.2 Problem2

```
1 // X cos(w t+p)+Y sin(w t+q)
2
3 X=50
4 Y=-30
5 w=120
6 p=-45
7 p=p/180*pi;
8 q=160
9 q=q/180*pi;
10
11 //Part1
12
13 A=X*cos(p)+ Y*sin(q);
14 B=-X*sin(p)+ Y*cos(q);
15
16 disp(B,"B=",A,"A=")
```

---

### Scilab code Exa 1.3 Problem3

```
1 G1=input("G1=")
2 G2=input("G2=")
3 G3=input("G3=")
4 Is1=input("Is1=")
5 Is2=input("Is2=")
6
7 A=[G1+G3,-G3;-G3,G2+G3];
8 I=[Is1;Is2];
9 V=inv(A)*I;
10
11 disp(V)
```

---

### Scilab code Exa 1.5 Problem5

```
1
2
3 R1=input("R1=")
4 R2=input("R2=")
5 R3=input("R3=")
6 Vs1=input("Vs1=")
7 Vs2=input("Vs2=")
8
9 R=[R1+R3,-R3;-R3,R2+R3];
10 V=[Vs1;-Vs2];
11 I=inv(R)*V;
12
13 disp(I)
```

---

### Scilab code Exa 1.7 Problem7

```
1 R1=1
```

```

2 R2=6
3 R3=12
4 R4=4
5 I4=3/4
6 V6=6
7
8 V4=3/4*4
9 I12=3/12
10 IR=3/4+I12
11
12 R=-12*I12+V6 //KVL
13 disp(R,"R(Ohm)="" )
14
15 I6=V6/6
16 I1=I6+IR
17
18 Vs=1*I1+V6 //KVL
19 disp(Vs, "Vs(V)="" )
20
21 disp(Vs*I1, " Power(W)="" )

```

---

### Scilab code Exa 1.9 Problem9

```

1 i1=4
2 v3=3
3 v4=8
4
5 i3=v3/3
6 i4=v4/4
7
8 i2=(i1-i3-i4)/2 //KCL
9 v2=2*i2
10
11 disp(v2, " v2="" )

```

---

**Scilab code Exa 1.10** Problem10

```
1 v1=6
2 i2=2
3 i3=4
4
5 v2=2*i2
6 v3=2*i3
7
8 v4=-v1+4*i2+v3-v2 //KVL
9 i4=v4/3
10 disp(i4)
```

---

**Scilab code Exa 1.11** Problem11

```
1 i1=4-1 // KCL at node 1
2 disp(i1,"i1=")
3
4 v1=i1*1
5 v12=1*1
6 v2=v1-v12
7 i2=v2/1
8
9 i3=1-i2 //KCL at node 2
10
11 Vs=v2-1*i3 //KVL
12 disp(Vs,"Vs=")
```

---

**Scilab code Exa 1.12** Problem12

```
1 i34=10-8 //KCL at node 4
2 v34=5*i34
3 v23=40-10 //KVL
4 vx=v23
5 disp(vx,"vx=")
6 ix=4-8 //KCL at node 1
7 disp(ix,"ix=")
8 i23=ix+10 //KCL at node 2
9 R2=vx/i23
10 disp(R2,"R2=")
11 v14=40+6*ix //KVL
12 R1=v14/8
13 disp(R1,"R1=")
```

---

### Scilab code Exa 1.13 Problem13

```
1 vs=0.01 // *cos(1000*t)
2
3 vpi=vs
4 i0=-vpi/1000
5 vo=i0*1000;
6 printf("vo = %f *cos(1000*t)",vo)
```

---

### Scilab code Exa 1.15 Problem15

```
1 t=0.1
2 R=800
3 i=50*exp(-10*t)/1000
4 v=50*cos(25*t)
5 v_i=10*t^(2.5)
6
7 P1=i*i*R
8 P2=v*v/R
```

```
9 P3=v_i  
10  
11 disp(P3,P2,P1)
```

---

# Chapter 2

## Fundamentals of Resistive Circuits

Scilab code Exa 2.1 Problem1

```
1 function s=series(r1,r2)
2     s=r1+r2
3 endfunction
4
5 function p=parallel(r1,r2)
6     p=r1*r2/(r1+r2)
7 endfunction
8
9 r1=series(12,8)
10 r2=parallel(20,r1)
11 r3=series(r2,50)
12 r4=parallel(30,r3)
13 r5=series(10,r4)
14 r6=series(r5,20)
15 Req_ab=parallel(r5,40)
16 disp(Req_ab)
17
18 r7=40+20+10 // series
19 Req_bc=parallel(r4,r7)
```

20 `disp(Req_bc)`

---

### Scilab code Exa 2.2 Problem2

```
1 I=(14-4)/(8+5+5+7) //KVL  
2 disp(I)
```

---

### Scilab code Exa 2.3 Problem3

```
1 r1=100  
2 v=3/4  
3  
4 r2=r1*v/(1-v)  
5  
6  
7 function p=parallel(r1,r2)  
8     p=r1*r2/(r1+r2)  
9 endfunction  
10  
11 /////Part1  
12 R2_eq=parallel(r2,10000)  
13 k=R2_eq/(R2_eq+r1)  
14 change1=(3/4-k)/(3/4)*100  
15 disp(change1)  
16 /////Part2  
17  
18 R2_eq=parallel(r2,1000)  
19 k=R2_eq/(R2_eq+r1)  
20 change2=(3/4-k)/(3/4)*100  
21 disp(change2)
```

---

### Scilab code Exa 2.4 Problem4

```
1 function p=parallel(r1,r2)
2     p=r1*r2/(r1+r2)
3 endfunction
4
5
6 v=150
7
8 Req=1000*parallel(parallel(10,5),4)
9 i1=v/(2000+0.2*1000+Req)
10 v1=i1*0.2*1000
11 VReq=Req*i1
12 i2=VReq/4000
13
14 disp(v1)
15 disp(i2)
```

---

### Scilab code Exa 2.5 Problem5

```
1 function [Rab,Rbc,Rca]=star_to_delta(Ra,Rb,Rc)
2     X=Ra*Rb+Rb*Rc+Rc*Ra
3     Rab=X/Rc
4     Rbc=X/Ra
5     Rca=X/Rb
6 endfunction
7
8 function p=parallel(r1,r2)
9     p=r1*r2/(r1+r2)
10 endfunction
11
12 [Rx,Ry,Rz]=star_to_delta(8,4,2)
13
14 Req_ad=parallel(parallel(4,Rx)+parallel(12,Rz),
    parallel(3,Ry))
```

```
15 disp(Req_ad)
```

---

### Scilab code Exa 2.6 Problem6

```
1 //Converting Voltage source with series resistance  
  to current source  
2 I=1/(1/4)  
3  
4 //KCL at nodes 1,2,3 using conductances  
5 A=[11,-3,-4;-3,6,-2;-4,-2,11]  
6 V=inv(A)*[5;-7;6]  
7  
8 disp(V)
```

---

### Scilab code Exa 2.7 Problem7

```
1 function p=parallel(r1,r2)  
2     p=r1*r2/(r1+r2)  
3 endfunction  
4  
5 Req=parallel(15,30)  
6  
7 //KCL at nodes 1 and 2  
8 A=[3,-1;-3,5]  
9 V=inv(A)*[80;-360]  
10  
11 disp(V(1))
```

---

### Scilab code Exa 2.8 Problem8

```
1 //Converting practical voltage source to current
   source
2 I=12/6
3
4 //KCLs
5 A=[0.7,-0.5;-0.5,0.767]
6 V=inv(A)*[7;2]
7 disp(V)
8
9 I12=(V(1)-V(2))/2
10 disp(I12)
```

---

### Scilab code Exa 2.9 Problem9

```
1 //KCLs
2
3 A=[2,-1;-4,19]
4 V=inv(A)*[10;25]
5
6 Pc=1*V(1)
7 Iv=(5-V(2))/2 + (5-V(1))/5
8 Pv=5*Iv
9
10 disp(V)
11 disp(Pv,Pc)
```

---

### Scilab code Exa 2.10 Problem10

```
1 //converting 9v voltage source to current source
2 I=9/0.45
3 I=I-7
4
5 //KCLs
```

```
6 A=[1/0.45+1/10 , -1/10 ; 0.2-1/10 , 1/10-0.2]
7 V=inv(A)*[-18;5]
8
9 disp(V(2))
```

---

### Scilab code Exa 2.11 Problem11

```
1 // converting voltage source to current source
2
3 I=240/3
4
5 //KCLs
6
7 A=[1/3+1/6 , -1/6 ; -1/6 , 1/6+1/12+1/30]
8 V=inv(A)*[70;5]
9 Vx=V(1)
10 Vy=V(2)-60
11
12 V6=V(2)-V(1)
13 P6=V6*V6/6
14
15 disp(P6)
```

---

### Scilab code Exa 2.13 Problem13

```
1 // KVLs
2
3 A=[24 , -6 , -8 ; -6 , 20 , -5 ; -8 , -5 , 25]
4 I=inv(A)*[16;0;0]
5 I5=I(2)-I(3)
6 disp(I5)
```

---

**Scilab code Exa 2.14** Problem14

```
1 //convert practical current source to voltage source
2 V=10*5
3
4 //KVLs
5 A=[35 , -20 ; -20 , 50]
6 I=inv(A)*[50 ; -100]
7
8 v=20*(I(1)-I(2))
9 disp(v)
```

---

**Scilab code Exa 2.15** Problem15

```
1 i1=0.37
2
3 //KVL for loop 2
4 i2=(-100+20*i1)/50
5
6 //KVL for loop 1
7 R=(50+20*(i2-i1))/i1
8 disp(R)
```

---

**Scilab code Exa 2.16** Problem16

```
1 //Converting current sources to voltage sources
2 // O=[i1 ; i2 ; vx]
3
4 A=[10 , -3 , 4 ; -3 , 7 , 0 ; 3 , -3 , -1]
```

```
5 O=inv(A)*[16 ; -6 ; 0]
6
7 disp(O)
```

---

### Scilab code Exa 2.17 Problem17

```
1 // convert current sources to voltage
2
3 A=[95 , -15 ; -15 , 135]
4 I=inv(A)*[20 ; -70]
5
6 i3=I(1)-I(2)
7
8 I60=0.5-I(1)
9 V60=I60*60
10 P1= 0.5*V60           //0.5 A source
11
12 I80=1+I(2)
13 V80=I80*80
14 P2=1*V80
15
16 disp(P2,P1)
```

---

### Scilab code Exa 2.18 Problem18

```
1 //Nodal Equations
2
3 A=[0.6 , -0.5 ; 2 , -1.6]
4 V=inv(A)*[4 ; 0]
5 V12=V(1)-V(2)
6 disp(V12)
```

---

### Scilab code Exa 2.19 Problem19

```
1 // convert dependent current source to dependent  
    voltage source  
2  
3 //Mesh Equations  
4 A=[14,-2,0;-2,18,3;2,-2,-1]  
5 O=inv(A)*[100;0;0]  
6  
7 disp(O(3))
```

---

### Scilab code Exa 2.20 Problem20

```
1 ////////////////////Part 1  
2  
3 //Nodal Method  
4 v1=(8/5+16/10)/(1/5+1/2+1/10)  
5 disp(v1)  
6 i5=(8-v1)/5000  
7 disp(i5)  
8  
9  
10 ////////////////////Part2  
11  
12 //Mesh Method  
13  
14 A=[7,-2;-2,12]  
15 I=inv(A)*[8;-16]/1000  
16 disp(I)  
17  
18 v1=2*1000*(I(1)-I(2))  
19 disp(v1)
```

---

### Scilab code Exa 2.21 Problem21

```
1 function p=parallel(r1,r2)
2     p=r1*r2/(r1+r2)
3 endfunction
4
5 // deactivate voltage source
6
7 i11=4*6/8
8 i21=4*2/8
9 v11=i11*2
10 v21=1*1
11
12 // deactivate current source
13 Req=parallel(2,7)
14
15 v22=8*Req/(2+Req)
16 v12=v22*(2/(2+5))
17
18 v1=v11+v12
19 v2=v21+v22
20
21 disp(v2,v1)
```

---

### Scilab code Exa 2.22 Problem22

```
1 function p=parallel(r1,r2)
2     p=r1*r2/(r1+r2)
3 endfunction
4
5 // Thevenin Equivalent
```

```
6 I=(32-8)/30
7 Voc=32-20*I
8 Ro=parallel(20,10)
9 disp(Ro,Voc)
10
11 //Norton Equivalent
12 Isc=32/20+8/10
13 disp(Ro,Isc)
```

---

### Scilab code Exa 2.23 Problem23

```
1 //convert current source to voltage source
2 V=3.5*20
3
4 //KVL
5 I=100/(10+20+V)
6 Voc=100-10*I
7
8 //Finding Isc
9 I=100/10
10 Isc=(1+3.5)*I
11
12 Ro=Voc/Isc
13
14 disp(Ro,Voc)
```

---

### Scilab code Exa 2.24 Problem24

```
1 V=32
2 I=1
3 R1=20
4 R2=8
5 R3=2
```

```
6 Voc1=V/(R1+R2+R3)*(R2+R3) //a,b open
7 Isc1=V/R1 //a,b short
8
9 Voc2=I*R2/(R1+R2+R3)*R1
10 Isc2=I*R2/(R2+R3)
11
12 ////by superposition
13 Voc=Voc1+Voc2
14 Isc=Isc1+Isc2
15
16 disp(Voc)
17 disp(Isc)
```

---

### Scilab code Exa 2.25 Problem25

```
1 function [Ra,Rb,Rc]=delta_to_star(Rab,Rbc,Rca)
2     X=Rab+Rbc+Rca
3     Ra=Rab*Rca/X
4     Rb=Rab*Rbc/X
5     Rc=Rca*Rbc/X
6 endfunction
7
8 function p=parallel(r1,r2)
9     p=r1*r2/(r1+r2)
10 endfunction
11
12 [R1,R2,R3]=delta_to_star(4,12,8)
13 Req=10+4+parallel(R1+15,R2+16)
14
15 I=12/Req
16 disp(I)
```

---

### Scilab code Exa 2.26 Problem26

```
1 // convert current source to voltage source
2
3 V1=4*2
4 V2=2*2
5
6 //Mesh Analysis
7
8 A=[7 , -3 ; -15 , 19]
9 I=inv(A)*[6 ; -14]
10
11 Vx=3*(I(1)-I(2))
12 disp(Vx)
```

---

### Scilab code Exa 2.27 Problem27

```
1 // Short Circuit AB and convert Curr Source to V
   source
2
3 V=9*5
4 Isc=(45-9)/6
5
6 function p=parallel(r1,r2)
7     p=r1*r2/(r1+r2)
8 endfunction
9
10 Ro=parallel(5+1,3)
11 disp(Ro,Isc)
```

---

### Scilab code Exa 2.28 Problem28

```
1 //Mesh Analysis
2
3 A=[4 , -2 ; 998 , 24.5]
```

```
4 I=inv(A)*[1/1000;0]
5
6 disp(I)
7
8 P1=I(2)^2*2.5*1000
9 P2=1/1000*I(1)
10 P3=-10^6*I(1)*I(2)
11 P=[P1,P2,P3]
12 disp(P)
```

---

### Scilab code Exa 2.29 Problem29

```
1 function p=parallel(r1,r2)
2     p=r1*r2/(r1+r2)
3 endfunction
4
5 // as seen from ab
6 Vth1=30*60/(30+60)
7 Rth1=parallel(30,60)
8
9 // as seen from cd
10 Vth2=80*40/(40+60)
11 Rth2=parallel(40,60)
12
13 Vnet=60+Vth1-Vth2
14 Rnet=Rth1+Rth2
15
16 disp(Rnet,Vnet)
```

---

### Scilab code Exa 2.30 Problem30

```
1 function p=parallel(r1,r2)
2     p=r1*r2/(r1+r2)
```

```
3 endfunction
4
5 R=parallel(60,120)
6
7 //Mesh Analysis
8
9 A=[6,-4;-4,12]
10 I=inv(A)*[2.4;-3.6]
11 I3=I(1)-I(2)
12
13 I60=I3*120/(120+60)
14 disp(I60)
```

---

### Scilab code Exa 2.31 Problem31

```
1 //Nodal Equation
2
3 Vn=198/10.5
4 I60=Vn/60
5 disp(I60)
```

---

### Scilab code Exa 2.32 Problem32

```
1 V8=2*8
2
3 //KVL
4 I1=(30-16)/10
5
6 //KCL at left node
7 I2=2-I1
8
9 //KVL middle mesh
10 I4=(10*I1-2*I2)/4
```

```
11 Vx=4*I4
12
13 // right node
14 Ix=I4-I2
15
16 disp(Vx)
```

---

### Scilab code Exa 2.33 Problem33

```
1 /////////////////////////////////////////////////////////////////// investigate the if
  then else construct
2
3
4
5 I=5
6
7 //KVL
8 R=(-12.5+15)/I-0.02-0.035
9 disp(R)
10
11 P=poly([-25,12.5,0.035],"I","coeff")
12 Z=roots(P)
13 Ib=Z(2)
14 disp(Ib)
15
16 I=(13-12.5)/0.035
17 R=(15-13)/I-0.02
18 disp(R)
```

---

### Scilab code Exa 2.35 Problem35

```
1 R=12*12/4-25
2 disp(R)
```

```
3
4 I=sqrt(1.6/1000/10000)
5 R=12/I-10000-15000
6 disp(R)
7
8 I=0
9 V=12
10 disp(V)
```

---

### Scilab code Exa 2.36 Problem36

```
1 function p=parallel(r1,r2)
2     p=r1*r2/(r1+r2)
3 endfunction
4
5 Req=1+parallel(parallel(1,1),1)
6
7 disp(Req)
```

---

### Scilab code Exa 2.37 Problem37

```
1 function p=parallel(r1,r2)
2     p=r1*r2/(r1+r2)
3 endfunction
4
5 R1=parallel(parallel(40,60),80+40)
6
7 Req=20+parallel(10+R1,30)
8 disp(Req)
```

---

### Scilab code Exa 2.38 Problem38

```
1 function p=parallel(r1,r2)
2     p=r1*r2/(r1+r2)
3 endfunction
4
5 R1=parallel(5,40)+15
6 Req=parallel(R1,15)+10
7 i=6/(1000*Req)
8
9 ix=i*R1/(R1+15)
10 disp(ix)
11
12 P=i*i*10000 // ////wrongly done in the book as ix*ix
13 *10000
14 disp(P)
```

---

### Scilab code Exa 2.39 Problem39

```
1 function p=parallel(r1,r2)
2     p=r1*r2/(r1+r2)
3 endfunction
4
5 R1=parallel(1,3)
6
7 //convert current source to voltage
8 V=20/1000*2000
9 I=(40-8)/(2+0.75)
10
11 Pr=8*I
12 disp(Pr)
```

---

### Scilab code Exa 2.40 Problem40

```

1 function p=parallel(r1,r2)
2     p=r1*r2/(r1+r2)
3 endfunction
4
5 I1=12/1000
6 Ix=I1*30/(30+60)
7 disp(Ix)
8
9 I2=20/1000
10 V2=I2*(10+5)
11 R1=10+parallel(30,60)
12 I1=V2/R1
13 Ix=I1*30/(30+60)
14 disp(Ix) //Wrongly printed in the book as 10
15
16 Ix=6/1000
17 I1=(30+60)/30*Ix
18 V2=I1*R1
19 I2=V2/15
20 disp(I2)
21
22 Is=45
23 I1=45*(10+5)/(10+5+R1)
24 Ix=I1*30/(30+60)
25 disp(Ix) ///Answer is wrong in the book

```

---

# Chapter 3

## Fundamentals of Reactive Circuits

Scilab code Exa 3.1 Problem1

```
1 function C=seriesC(C1,C2)
2     C=C1*C2/(C1+C2)
3 endfunction
4
5 Ceq1=10+seriesC(10,10)
6 Ceq2=Ceq1
7
8 Ceq=seriesC(seriesC(Ceq1,Ceq2),10)
9 disp(Ceq)
```

---

Scilab code Exa 3.2 Problem2

```
1 function p=parallel(r1,r2)
2     p=r1*r2/(r1+r2)
3 endfunction
4
```

```
5 Leq=1+parallel(2,2)+parallel(parallel(3,3),3)
6
7 disp(Leq)
```

---

### Scilab code Exa 3.3 Problem3

```
1 function C=seriesC(C1,C2)
2     C=C1*C2/(C1+C2)
3 endfunction
4
5 V=100
6
7 Cp=1+2
8 Ceq=seriesC(Cp,6)
9 q=Ceq*V
10
11 q1=q*(1/(1+2))
12 q2=q-q1
13
14 disp(q2,q1,q)
15
16 E6=q*q/2/6/1000
17 E1=q1*q1/2/1/1000
18 E2=q2*q2/2/2/1000
19 Enet=E1+E2+E6
20
21 disp(Enet,E6,E2,E1)
```

---

### Scilab code Exa 3.4 Problem4

```
1 L=poly([3,-4,1],"L","coeff")
2 disp(roots(L))
```

---

### Scilab code Exa 3.5 Problem5

```
1 function C=seriesC(C1,C2)
2     C=C1*C2/(C1+C2)
3 endfunction
4
5 Ceq=1+seriesC(6,3)
6
7 disp(Ceq)
```

---

### Scilab code Exa 3.6 Problem6

```
1 function p=parallel(r1,r2)
2     p=r1*r2/(r1+r2)
3 endfunction
4
5 Lbc=parallel(1/10,1/20)
6 Leq=1/50+Lbc
7 disp(Leq)
8
9 Vbc=Lbc*150
10 disp(Vbc)
```

---

### Scilab code Exa 3.7 Problem7

```
1 function C=seriesC(C1,C2)
2     C=C1*C2/(C1+C2)
3 endfunction
4
```

```
5 Ceq=seriesC(seriesC(10,20),40)
6 disp(Ceq)
7
8 q=Ceq*280
9 disp(q)
10
11 V1=q/10
12 V2=q/20
13 V3=q/40
14
15 disp(V3,V2,V1)
```

---

### Scilab code Exa 3.8 Problem8

```
1 Ceq=10+20+40
2 Q=200*[10,20,40]
3
4 disp(Q)
5 Qnet=Q(1)+Q(2)+Q(3)
6 disp(Qnet)
```

---

### Scilab code Exa 3.9 Problem9

```
1 // deactivate all independent sources
2
3 function p=parallel(r1,r2)
4     p=r1*r2/(r1+r2)
5 endfunction
6
7 L=2
8 Req=parallel(6,12)+4
9 T1=L/Req
10 disp(T1)
```

```
11
12 C=1/2
13 Req=2+parallel(6,12)+2
14 T2=Req*C
15 disp(T2)
```

---

### Scilab code Exa 3.11 Problem11

```
1 L=2
2
3 VL_0minus=0 //steady state
4 disp(VL_0minus)
5
6 i_0minus=1
7 i_0plus=i_0minus
8 VL_0plus=12-4*i_0plus
9 disp(VL_0plus)
10
11 di_by_dt_0plus=VL_0plus/L
12 disp(di_by_dt_0plus)
```

---

### Scilab code Exa 3.12 Problem12

```
1 Vc_0m=100
2 Vc_0p=Vc_0m
3 T=(400+100)*2E-6
4 i_0p=100/500
5 P_0p=i_0p^2*400
6 disp(P_0p)
```

---

### Scilab code Exa 3.13 Problem13

```
1 Vc_0m=10
2 Vc_0p=Vc_0m
3 disp(Vc_0p)
4
5 //KVL
6 i1_0p=(10-Vc_0p)/20
7 i2_0p=Vc_0p/20
8
9 //KCL
10 iC_0p=i1_0p-i2_0p
11 disp(iC_0p)
12 iC_inf=0 //capacitor is open circuit
13 disp(iC_inf)
14 VC_inf=10*20/(20+20)
15 disp(VC_inf)
```

---

### Scilab code Exa 3.16 Problem16

```
1 L=0.25
2 R=250
3 V=10
4 T=L/R
5
6 t=0.5E-3
7 i=V/R*(1-exp(-t/T))
8 disp(i)
9
10 t=2E-3
11 i=V/R*((exp((1E-3-t)/T)-exp(-t/T)))
12 disp(i)
```

---

### Scilab code Exa 3.18 Problem18

```
1 R=5000
2 C=1.0E-6
3 Ie=1/1000
4 Vcf=Ie*R
5 T=R*C
6
7 t=10/1000
8 Vc10=Vcf*(1-exp(-t/T))
9 disp(Vc10)
10
11 t=20/1000
12 Vc20=Vcf*(1-exp(-t/T))-Vc10
13 disp(Vc20)
```

---

### Scilab code Exa 3.21 Problem21

```
1 //Replace curr source by voltage source
2 Ics=1/1000
3 R=100*1000
4 V=Ics*R
5
6 Vc_0m=25/(25+100)*V
7 disp(Vc_0m)
8
9 Vc_0p=Vc_0m
10 disp(Vc_0p)
11
12 Vc_inf=(V-10)*25/(100+25)
13 disp(Vc_inf)
```

---

### Scilab code Exa 3.22 Problem22

```
1 L=20/1000
2 VR2_0p=10
3 VR2_inf=0
4 VR2_1=5
5
6 t=1/1000
7 T=-t/log((VR2_1-VR2_inf)/(VR2_0p-VR2_inf))
8
9 R2=L/T
10 R1=1/(2/VR2_0p-1/R2)
11
12 disp(R2,R1)
```

---

### Scilab code Exa 3.24 Problem24

```
1 C=1/4
2 Vc_0m=12/(12+6)*12
3 Vc_0p=8
4 disp(Vc_0p)
5 t=0
6 V_0p=6*cos(t)
7
8 // at t=0+
9 Vth=12/(12+6)*6
10 Rth=6*12/(6+12)
11 ic_0p=(Vth-8)/Rth
12 disp(ic_0p)
13 d_by_dt_Vc_0p=ic_0p/C
14 disp(d_by_dt_Vc_0p)
```

---

### Scilab code Exa 3.26 Problem26

```
1 // at t=0-
```

```
2 iL=4
3 v=0
4 disp(v,iL)
5
6 // at t=0+
7 iL=4
8 v=-4*20
9 disp(v,iL)
```

---

### Scilab code Exa 3.27 Problem27

```
1 function p=parallel(r1,r2)
2     p=r1*r2/(r1+r2)
3 endfunction
4
5 L=25/1000
6
7 // at t=0-
8 R1=parallel(150,75)
9 iL_0m=30/2
10 disp(iL_0m)
11
12 R2=parallel(150,50)
13 ix_0m=R2/(R2+75)*30
14 disp(ix_0m)
15
16
17 // at t=0+
18 iL_0p=iL_0m
19
20 T=L/(75+50)
21 iL_inf=0
22
23 // at t=0.2ms
24 t=0.2E-3
```

```
25
26 iL=iL_inf+(iL_0p-iL_inf)*exp(-t/T)
27 ix=-iL
28 disp(ix,iL)
```

---

### Scilab code Exa 3.29 Problem29

```
1 R=250
2 C=25E-3
3
4 // at t=0-
5 v_0m=200*0.2
6
7 // at t=0+
8 v_0p=v_0m
9
10 T=R*C
11 v_inf=0
12
13 // at t=0.2ms
14 t=0.2E-3
15
16 t=T*log((v_0p-v_inf)/(20-v_inf))
17 disp(t)
```

---

### Scilab code Exa 3.32 Problem32

```
1 L=0.2
2 R=50+30
3
4 iL_0m=100/50
5 iL_0p=iL_0m
6 iL_inf=0
```

```

7 T=L/R
8
9 t=10/1000
10 iL_10=iL_0p*exp(-t/T)
11 disp(iL_10)
12
13 t1=-T*log(0.5*iL_0p/(iL_0p))
14 disp(t1)

```

---

### Scilab code Exa 3.33 Problem33

```

1 R=5
2 L=2
3 V=10
4 T=L/R
5
6 iL_m=V/R
7 disp(iL_m)
8 iL_0p=iL_m
9 iL_inf=2+V/R
10
11 //function I=iL(t)
12 //    I=iL_inf+(iL_0p-iL_inf)*exp(-t/T)
13 //endfunction
14
15 //disp(iL(0.5))
16 //disp(iL(1.5))
17
18 t=0.5
19 I=iL_inf+(iL_0p-iL_inf)*exp(-t/T)
20 disp(I)
21
22 t=1.5
23 I=iL_inf+(iL_0p-iL_inf)*exp(-t/T)
24 disp(I)

```

---

### Scilab code Exa 3.36 Problem36

```
1 L=4/1000
2 R=1000
3 V=9
4
5 iL_0m=V/(2*R)
6 iL_0p=iL_0m
7 iL_inf=0
8 isw_inf=V/R
9 T=L/R
10
11 t=5E-6
12
13 iL_5=iL_0p*exp(-t/T)
14 disp(iL_5)
15
16 isw_5=isw_inf*(1-exp(-t/T))
17 disp(isw_5)
```

---

### Scilab code Exa 3.37.38 Problem37 and 38

```
1 R=20
2 L=2
3 C=1/25
4
5 // at t=0-
6 iR=-4
7 iL=4
8 iC=0
9 vR=-R*4
```

```

10 vC=-vR
11 vL=0
12
13 disp(iR,iL,iC,vR,vL,vC)
14
15 // at t=0+
16 iL=iL
17 vC=vC
18 iR=5-4 //KCL at node 1
19 vR=R*iR
20 iC=4+iR //KCL at node 2
21 vL=vC+vR //KVL inner mesh
22
23 disp(iR,iL,iC,vR,vL,vC)
24
25
26 //at t=0+ derivatives are
27 DiL=vL/L
28 DvC=iC/C
29 DiR=-DiL // Differentiating KCL at node 1
30 DiC=DiR // Differentiating KCL at node 2
31 DvR=R*DiR
32 DvL=DvR+DvC // Differentiating KVL inner mesh
33
34 disp(DiR,DiL,DiC,DvR,DvL,DvC)

```

---

# Chapter 4

## Steady State Analysis For Sinusoidal Excitation

Scilab code Exa 4.1 Problem1

```
1 Iav=1/(2*%pi)*integrate('20*sin(wt)', 'wt', %pi/3, %pi)
2 disp(Iav)
3
4 Irms=sqrt(1/(2*%pi)*integrate('(20*sin(wt))^2', 'wt',
    %pi/3, %pi))
5 disp(Irms)
```

---

Scilab code Exa 4.2 Problem2

```
1 Iav_by_Im=1/%pi*integrate('sin(wt)', 'wt', 0, %pi)
2 disp(Iav_by_Im)
3
4 // final answer is wrong in the book
```

---

### Scilab code Exa 4.4 Problem4

```
1 ////////////////////////////////////////////////////////////////// part a
2 L=0.05
3 R=20
4 w=1.2E3
5 Xl=w*L
6 V=complex(100,200)
7 I=complex(5,0)
8
9 Xc=-imult(R+imult(Xl)-V/I)
10 C=1/w/Xc
11
12 disp(C)
13
14 ////////////////////////////////////////////////////////////////// part b
15 w=200
16 V=complex(100,0)
17 Xl=w*L
18 Xc=-imult(R+imult(Xl)-V/I)
19 C=1/w/Xc
20
21 disp(C)
```

---

### Scilab code Exa 4.5 Problem5

```
1 L=0.0255
2 R1=6
3 V=240
4 f=50
5 w=2*pi*f
6 Va=sqrt(V^2/10)
7 Vb=3*Va
8 Xl=w*L
9 Theta1=atan(Xl/R1)
```

```
10 Theta2=%pi/2-Theta1 //Va and Vb are in quadrature
11
12 I=Vb/sqrt(R1^2+X1^2)
13
14 R=(Va/I)/sqrt(1+tan(Theta2)^2)
15 disp(R)
16
17 Xc=R*tan(Theta2)
18 C=1/w/Xc
19 disp(C)
```

---

### Scilab code Exa 4.6 Problem6

```
1 Z1=complex(10,15)
2 Z2=complex(6,-8)
3
4 I=complex(15,0)
5 I1=I*Z2/(Z1+Z2)
6 I2=I*Z1/(Z1+Z2)
7 phase=[atan(imag(I1)/real(I1)); atan(imag(I2)/real(I2))]
8 disp(phase*180/%pi)
9
10 V=I1*Z1
11 disp(180/%pi*atan(imag(V)/real(V)))
```

---

### Scilab code Exa 4.7 Problem7

```
1 function [r,theta]=cart_to_polar(z)
2     x=real(z)
3     y=imag(z)
4     r=norm(z)
5     theta=atan(y/x)
```

```

6  endfunction
7
8  function Zeq=parallel(Z1,Z2)
9      Zeq=Z1*Z2/(Z1+Z2)
10 endfunction
11
12 w=400
13 R=10
14 L=25E-3
15 C=250E-6
16 Xl=w*L*%i
17 Xc=1/(w*C*%i)
18
19 /////////// part a
20 Zin1=R+Xc
21 [r1,theta1]=cart_to_polar(Zin1)
22 disp(theta1*180/%pi,r1)
23
24 /////////// part b
25 //Zin2=10+parallel(Xc,Xl)    /// impedance is infinite
26 //... thus an error
27 // [r2,theta2]=cart_to_polar(Zin2)
28 disp(90," inf")
29
30 /////////// part c
31 Zin3=R+parallel(Xc,Xl+10)
32 [r3,theta3]=cart_to_polar(Zin3)
33 disp(theta3*180/%pi,r3)

```

---

### Scilab code Exa 4.8 Problem8

```

1  function [r,theta]=cart_to_polar(z)
2      x=real(z)
3      y=imag(z)

```

```

4     r=norm(z)
5     theta=atan(y/x)
6 endfunction
7
8 function [x,y]=polar_to_cart(zpolar)
9     r=real(zpolar)
10    theta=imag(zpolar)/180*%pi
11    x=r*cos(theta)
12    y=r*sin(theta)
13 endfunction
14
15 function Zeq=parallel(Z1,Z2)
16     Zeq=Z1*Z2/(Z1+Z2)
17 endfunction
18
19 R=200
20 L=0.5
21 C=50E-6
22 w=200
23
24 Xl=w*L*%i
25 Xc=1/(w*C*%i)
26
27 //////////// part a
28 Ir=complex(0.02*cos(30*%pi/180),0.02*sin(30*%pi/180)
   )
29 V=Ir*R
30 I1=V/Xl
31 Ic=V/Xc
32 I=Ir+I1+Ic
33 disp(I)
34
35 //////////// part b
36 [Ix,Iy]=polar_to_cart(complex(2,-40))
37 I=complex(Ix,Iy)
38 Zin=parallel(parallel(R,Xc),Xl)
39 V=Zin*I
40 Ir=V/R

```

```
41 disp(V,Ir)
```

---

### Scilab code Exa 4.9 Problem9

```
1 p=poly([0,2,0,-8],"w","coeff")
2 w=roots(p)
3 disp(w(1))
```

---

### Scilab code Exa 4.10 Problem10

```
1 function Zeq=parallel(Z1,Z2)
2     Zeq=Z1*Z2/(Z1+Z2)
3 endfunction
4
5 Zeq=parallel(5,3-imult(6))
6 I=complex(10,0)
7 V=Zeq*I
8 pf=cos(atan(imag(V)/real(V)))
9 P=norm(V)*norm(I)*pf
10 disp(pf,P)
```

---

### Scilab code Exa 4.11 Problem11

```
1 P1=8000
2 pf1=0.8
3 V1=430
4
5 I1=P1/V1/pf1
6 Pr1=P1-I1^2*1
7 Q1=P1*tan(acos(pf1))
```

```

8  Qr1=Q1-I1^2*1.2
9  Sr1=sqrt(Pr1^2+Qr1^2)
10
11 V1=Sr1/I1
12 P1=15000
13 Q1=P1*tanacos(0.8))
14 Pr2=P1-Pr1
15 Qr2=Q1-Qr1
16 Sr2=sqrt(Pr2^2+Qr2^2)
17
18 I2=Sr2/V1
19 P2=Pr2+I2^2*0.7
20 Q2=Qr2+I2^2*0.9
21
22 pf=cosatan(Q2/P2))
23 S2=sqrt(P2^2+Q2^2)
24 V2=S2/I2
25
26 disp(V2, pf, P2, Q2, Q1, V1)

```

---

### Scilab code Exa 4.12 Problem12

```

1  V=231
2  f=50
3  w=2*pi*f
4  S1=10
5  pf=0.8
6  P1=S1*pf
7  Q1=S1*sinacos(pf))
8  Qc=Q1-tanacos(0.95))*P1
9
10 C=Qc*1000/V^2/w
11
12 Is1=10*1000/V
13 I1=Is1

```

```
14 Is2=norm(Pl+%i*(Ql-Qc))*1000/V  
15  
16 disp(Is2,Is1,C,Qc)
```

---

### Scilab code Exa 4.13 Problem13

```
1 function [x,y]=polar_to_cart(r,theta)  
2 theta=theta/180*pi  
3 x=r*cos(theta)  
4 y=r*sin(theta)  
5 endfunction  
6  
7 //converting v source to curr source  
8 V=15  
9 R=5  
10 I1=V/R  
11  
12  
13 [Ix,Iy]=polar_to_cart(2,-30)  
14 I2=complex(Ix,Iy)  
15  
16 //nodal analysis  
17 A=[0.7-0.1*i,-0.5;-0.5,0.5+0.5*i]  
18 V=inv(A)*[I1;I2]  
19  
20 [rv1,thetav1]=polar(V(1))  
21 [rv2,thetav2]=polar(V(2))  
22  
23 disp(real(thetav2*180/%pi),rv2,real(thetav1*180/%pi)  
,rv1)
```

---

### Scilab code Exa 4.14 Problem14

```

1 w=600
2 R=10
3 L=10E-3
4 C=0.5E-3
5 Xl=w*L*%i
6 Xc=1/(w*C*%i) //Xc value in the book is wrong
7 V1=40
8 V2=complex(0,-30)
9
10 //mesh analysis
11 A=[R+Xl,-R;-R,R+Xc]
12 I=inv(A)*[V1;V2]
13
14 Ir=I(1)-I(2)
15 Vr=R*Ir
16
17 disp(Vr) //Final answer is different

```

---

### Scilab code Exa 4.15 Problem15

```

1 Z1=complex(2,-1)
2 Z2=complex(0,-5)
3 Z3=complex(2,1)
4 I1=1
5 I2=complex(0,-2)
6
7 // deactivate curr source 2
8 V11=I1*(Z2+Z3)/(Z1+Z2+Z3)*Z1
9 V21=I1*Z1/(Z1+Z2+Z3)*Z3
10
11 // deactivate curr source 1
12 V12=I2*Z3*Z1/(Z1+Z2+Z3)
13 V22=I2*(Z1+Z2)/(Z1+Z2+Z3)*Z3
14
15 V1=V11+V12

```

```
16 V2=V21+V22  
17  
18 disp(V2,V1)
```

---

### Scilab code Exa 4.16 Problem16

```
1 function [Ra,Rb,Rc]=delta_to_star(Rab,Rbc,Rca)  
2 X=Rab+Rbc+Rca  
3 Ra=Rab*Rca/X  
4 Rb=Rab*Rbc/X  
5 Rc=Rca*Rbc/X  
6 endfunction  
7  
8 function Zeq=parallel(Z1,Z2)  
9 Zeq=Z1*Z2/(Z1+Z2)  
10 endfunction  
11  
12 V=20  
13 w=2  
14 R=1  
15 C=1/2  
16 Xc=1/(w*C*%i)  
17 Zab=-%i  
18 Zbc=2  
19 Zca=2  
20  
21 [Za,Zb,Zc]=delta_to_star(Zab,Zbc,Zca)  
22 Zth=Za+parallel(R+Zb,Xc+Zc)  
23  
24 Vdc=V*(Zc+Xc)/(R+Zb+Zc+Xc)  
25 disp(Zth,Vdc)  
26  
27 Isc=Vdc/Zth  
28 disp(Zth,Isc)
```

---

### Scilab code Exa 4.17 Problem17

```
1 function Zeq=parallel(Z1,Z2)
2     Zeq=Z1*Z2/(Z1+Z2)
3 endfunction
4
5 V=20
6 Z1=complex(5,10)
7 Z2=complex(3,-4)
8
9 Vth=V*Z2/(Z1+Z2)
10 Zth=parallel(Z1,Z2)
11
12 //by maximum power transfer theorem
13 Zl=conj(Zth)
14 P=norm(Vth/(Zth+Zl))^2*real(Z1)
15 disp(P,Z1)
16
17 Rl=sqrt(real(Zth)^2+(4+imag(Zth))^2)
18 disp(Rl)
```

---

### Scilab code Exa 4.18 Problem18

```
1 function [x,y]=polar_to_cart(r,theta)
2     theta=theta/180*%pi
3     x=r*cos(theta)
4     y=r*sin(theta)
5 endfunction
6
7 R1=1
8 R2=6
9 L=2
```

```

10 C=1/3
11
12 [Vx,Vy]=polar_to_cart(4,30)
13 [Ix,Iy]=polar_to_cart(0.8,-10)
14
15 // deactivate current source
16 V=complex(Vx,Vy)
17 w=3
18 Xl=w*L*%i
19 Xc=1/(w*C*%i)
20
21 I11=V/(R1+R2+Xl+Xc)
22 Pav1=norm(I11)^2*R1
23
24 // deactivate voltage source
25 I=complex(Ix,Iy)
26 w=5
27 Xl=w*L*%i
28 Xc=1/(w*C*%i)
29
30 I12=I*(R2+Xl)/(R2+Xl+R1+Xc)
31 Pav2=norm(I12)^2*R1
32
33 Pav=Pav1+Pav2
34 disp(Pav)

```

---

### Scilab code Exa 4.21 Problem21

```

1 I=35
2 VR=25
3 Vrl=40
4 VRrl=50
5 Vc=45
6 C=50E-6
7 Xc=Vc/I

```

```

8 w=1/(Xc*C)
9
10 theta=acos((VR^2+VRrl^2-Vrl^2)/(2*VR*VRrl))
11 x=VRrl*cos(theta)-25
12 y=VRrl*sin(theta)
13
14 r=x/I
15 L=y/(I*w)
16 Vappl=sqrt((VR+x)^2+y^2)
17 R=VR/I
18
19 disp(L,r,R)

```

---

### Scilab code Exa 4.22 Problem22

```

1 V=12
2 w=1000
3 R=4
4 L=5E-3
5 C=400E-6
6 Xl=w*L*%i
7 Xc=1/(w*C*%i)
8
9 //mesh analysis
10 A=[R+Xl,-Xl;2-Xl,Xl+Xc]
11 I=inv(A)*[12;0]
12
13 disp(I(1)) //answer is wrong in the book

```

---

### Scilab code Exa 4.23 Problem23

```

1 function [x,y]=polar_to_cart(r,theta)
2     theta=theta/180*pi

```

```

3      x=r*cos(theta)
4      y=r*sin(theta)
5 endfunction
6
7 [I1x,I1y]=polar_to_cart(2,10)
8 [I2x,I2y]=polar_to_cart(3,120)
9
10 I1=complex(I1x,I1y)
11 I2=complex(I2x,I2y)
12 w=4
13 R=2
14 L=3
15 C=1/4
16 Xl=w*L*%i
17 Xc=1/(w*C*%i)
18
19 // deactivate source 2
20 i1=(R+Xl)/(R+Xl+Xc)*I1
21 i2=1/(R+Xl+Xc)*I2
22 i=i1+i2
23 disp(i) // answer is wrong in the book

```

---

### Scilab code Exa 4.24 Problem24

```

1 V=230
2 w=2*%pi*50
3 R=8
4 L=0.1
5 C=160E-6
6
7 Xl=w*L*%i
8 disp(Xl)
9
10 Xc=1/(w*C*%i)
11 disp(Xc)

```

```
12
13 Z=norm(R+Xl+Xc)
14 disp(Z)
15 I=V/Z
16 disp(I)
17 pf=cos(atan(norm(Xl+Xc)/R))
18 disp(pf)
19
20 Vcoil=I*norm(R+Xl)
21 Vc=norm(I*Xc)
22 disp(Vc ,Vcoil)
```

---

### Scilab code Exa 4.25 Problem25

```
1 function Zeq=parallel(Z1,Z2)
2     Zeq=Z1*Z2/(Z1+Z2)
3 endfunction
4
5 V=100
6 Z1=complex(0,-5)
7 Z2=complex(5,0)
8 Z3=complex(0,5)
9 I=[0,0,0]
10
11 Z=Z1+parallel(Z2,Z3)
12 I(1)=V/Z
13
14 I(2)=Z3/(Z2+Z3)*I(1)
15 I(3)=Z2/(Z2+Z3)*I(1)
16
17 disp(I)
```

---

### Scilab code Exa 4.26 Problem26

```

1 function Zeq=parallel(Z1,Z2)
2     Zeq=Z1*Z2/(Z1+Z2)
3 endfunction
4
5 // converting curr source to v source
6 I=0.4
7 R1=15
8 V=I*R1
9 w=400
10
11 R2=5
12 R3=80
13 L=25E-3
14 Xl=w*L*%i
15
16 Zeq=R1+R2+parallel(R3,Xl)
17 I=V/Zeq
18 Il=I*R3/(R3+Xl)
19 Ix=I*Xl/(R3+Xl)
20
21 disp(Il,Ix)

```

---

### Scilab code Exa 4.27 Problem27

```

1 V=4
2 w=2
3
4 R=4
5 L=2
6 Xl=w*L*%i
7
8 Il=V/(Xl+R)
9 Xc=-V/ imag(Il)
10 C=1/(w*Xc)
11 disp(C)

```

---

### Scilab code Exa 4.28 Problem28

```
1 function [x,y]=polar_to_cart(r,theta)
2     theta=theta/180*pi
3     x=r*cos(theta)
4     y=r*sin(theta)
5 endfunction
6
7 I=4
8 w=500
9 [Ir,Ic]=polar_to_cart(3,40)
10 Ix=complex(Ir,Ic)
11 C=1E-3
12 L=10E-3
13 Xl=w*L*%i
14 Xc=1/(w*C*%i)
15
16 I1=I-Ix
17 Ic=Ix
18 Vc=Ic*Xc
19 Vl=I1*Xl
20 Vx=Vl-Vc
21 disp(Vx) // answer wrong in the book
```

---

### Scilab code Exa 4.29 Problem29

```
1 w=10
2 R=2
3 L=0.3
4 Ir=10*(cos(%pi/4)+%i*sin(%pi/4))
5 Vr=Ir*R
```

```
6 Vc=20*(cos(%pi/4)-%i*sin(%pi/4))  
7 V=Vr+Vc  
8 Ic=Ir  
9 C=Ic/(w*Vc*%i)  
10 disp(real(C))      /////////////////////////////////////////////////////////////////// Wrong in book
```

---

### Scilab code Exa 4.30 Problem30

```
1 R=2000  
2 C=5E-6  
3 w=1000  
4  
5 Xc=1/(w*C*%i)  
6 Y=1/R+1/Xc  
7 Z=1/Y  
8 Req=real(Z)  
9 Ceq=-1/(imag(Z)*w)  
10  
11 disp(Ceq*1E6,Req) /////////////////////////////////////////////////////////////////// Answer wrong in the book
```

---

### Scilab code Exa 4.31 Problem31

```
1 I=10*(cos(%pi/180*37)-%i*sin(%pi/180*37))  
2 V=6  
3 C=250E-6  
4 w=1000  
5 Xc=1/(w*C*%i)  
6  
7 Ic=V/Xc  
8 disp(Ic)  
9  
10 Ix=imag(I-Ic)  
11 X=abs(V/Ix)
```

```
12 Ir=real(I-Ic)
13 R=V/Ir
14
15 disp(R,X)
```

---

### Scilab code Exa 4.32 Problem32

```
1 V1=30+10*%i
2 V2=30
3 w=1000
4 L=1
5 C1=1E-6
6 C2=1E-6
7 R1=1000
8 R2=1000
9
10 Xl=%i*w*L
11 Xc1=%i/(w*C1)
12 Xc2=%i/(w*C2)
13
14 ////////// mesh equations
15
16 A=[1,%i; %i,1-2*%i]
17 I=inv(A)*[10*%i;30]
18
19 Ic1=I(1)-I(2)
20
21 disp(Ic1)
```

---

### Scilab code Exa 4.33 Problem33

```
1 function [x,y]=polar_to_cart(r,theta)
2 theta=theta/180*pi
```

```

3      x=r*cos(theta)
4      y=r*sin(theta)
5  endfunction
6
7 [Ir,Ic]=polar_to_cart(3,30)
8 I=complex(Ir,Ic)
9 Zc=-5*i
10 Zrl=10+5*i
11
12 Ic=Zrl/(Zc+Zrl)*I
13 Vth=Ic*Zc
14 Zth=parallel(Zc,Zrl)
15 In=Vth/Zth
16
17 disp(Rth,In,Vth)

```

---

### Scilab code Exa 4.34 Problem34

```

1 function [x,y]=polar_to_cart(r,theta)
2     theta=theta/180*pi
3     x=r*cos(theta)
4     y=r*sin(theta)
5 endfunction
6
7 [Ir,Ic]=polar_to_cart(2,10)
8 I1=complex(Ir,Ic)
9 [Ir,Ic]=polar_to_cart(3,90+30)
10 I2=complex(Ir,Ic)
11
12 w=4
13 R=2
14 L=0.5
15 C=1/4
16 Xl=w*L*%i
17 Xc=1/(w*C*%i)

```

```

18
19 // deactivate voltage source
20 i1=I1*(R+Xl)/(R+Xl+Xc)
21
22 // deactivate curr source
23 i2=I2/(R+Xl+Xc)
24
25 i=i1+i2
26 disp(i)

```

---

### Scilab code Exa 4.35 Problem35

```

1 function Zeq=parallel(Z1,Z2)
2     Zeq=Z1*Z2/(Z1+Z2)
3 endfunction
4
5 I=10
6 w=2000
7 R=200
8 L=0.125
9
10 Xl=w*L*%i
11
12 Zeq=parallel(R,Xl)
13 V=I*Zeq
14 I1=V/Xl
15 Ir=V/R
16
17 t=1/1000
18 I1=sqrt(2)*real(I*exp(%i*w*t))
19 I11=sqrt(2)*real(I1*exp(%i*w*t))
20 Ir1=sqrt(2)*real(Ir*exp(%i*w*t))
21 V1=sqrt(2)*real(V*exp(%i*w*t))
22
23 Ps=-V1*I1

```

```
24 Pr=-V1*Ir1
25 P1=-V1*I11
26
27 disp(P1,Pr,Ps)
```

---

### Scilab code Exa 4.36 Problem36

```
1 function [x,y]=polar_to_cart(r,theta)
2     theta=theta/180*pi
3     x=r*cos(theta)
4     y=r*sin(theta)
5 endfunction
6
7 [Vr,Vc]=polar_to_cart(120,45)
8 V=complex(Vr,Vc)
9
10 [Zr,Zc]=polar_to_cart(16.3,24.5)
11 Z=complex(Zr,Zc)
12
13 w=50
14
15 I=V/Z
16 P=V*conj(I)
17 Pavg=real(P)
18 pf=real((V/I)/norm(V/I))
19
20 disp(pf,Pavg)
```

---

### Scilab code Exa 4.37 Problem37

```
1 function Zeq=parallel(Z1,Z2)
2     Zeq=Z1*Z2/(Z1+Z2)
3 endfunction
```

```

4
5 function [x,y]=polar_to_cart(r,theta)
6     theta=theta/180*%pi
7     x=r*cos(theta)
8     y=r*sin(theta)
9 endfunction
10
11 [Ir,Ic]=polar_to_cart(20,60)
12 I=complex(Ir,Ic)
13
14 w=5000
15 R=3000
16 L=1
17 C=0.25E-6
18 Xl=w*L*%i
19 Xc=1/(w*C*%i)
20
21 Z=parallel(R+Xl,Xc)
22 V=I*Z
23 disp(V)

```

---

### Scilab code Exa 4.38 Problem38

```

1 function Zeq=parallel(Z1,Z2)
2     Zeq=Z1*Z2/(Z1+Z2)
3 endfunction
4
5 V=5
6 w=5
7 R=2
8 L1=0.8
9 L2=1
10 C=1/5
11 Xl1=w*L1*%i
12 Xl2=w*L2*%i

```

```
13 Xc=1/(w*C*%i)
14
15 Vth=R/(R+Xl2)*V
16 Zth=Xc+parallel(Xl2,R)
17 disp(Zth,Vth)
18
19 I=Vth/(Zth+Xl1)
20 Vl=I*Xl1
21 S=Vl*conj(I)/2
22 disp(S)
```

---

### Scilab code Exa 4.39 Problem39

```
1 Pm=600
2Vm=sqrt(3*Pm)
3 f=15.36E6
4 w=2*pi*f
5 t=20.3E-3
6 theta=%pi/2-modulo(w*t,2*pi)
7
8 disp(theta*180/pi)
```

---

### Scilab code Exa 4.40 Problem40

```
1 V=240
2 w=100*pi
3 R=6
4
5 Vr=120
6 I=Vr/R
7
8 t=(205/I)^2           // // t=r^2+Xl^2
```

```
9 r=((240/I)^2-t-R*R)/2/R           //this part solved  
      wrong in the book  
10 X1=sqrt(t-r*r)  
11 Z=sqrt(t)  
12 disp(r)  
13 disp(X1)  
14 disp(Z)  
15  
16 P1_choke=I*I*r  
17 disp(P1_choke)  
18 pf=P1_choke/205/20  
19 disp(pf)
```

---

### Scilab code Exa 4.41 Problem41

```
1 w=2  
2 L=1  
3 C=0.5  
4 X1=w*L*%i  
5 Xc=1/(w*C*%i)  
6  
7 V=1  
8 I=V/(1+%i)  
9 Y=I/V  
10 R=1/real(Y)  
11  
12 disp(R,Y)
```

---

### Scilab code Exa 4.42 Problem42

```
1 w=400  
2 R=5  
3 L=25E-3
```

```
4 C=1.25E-3
5 Xl=w*L*%i
6 Xc=1/(w*C*%i)
7
8 Z=R+Xl+Xc
9 Y=1/Z
10 C=-imag(Y)/w
11 Yn=real(Y)
12 Rn=1/Y
13
14 disp(C)
```

---

### Scilab code Exa 4.43 Problem43

```
1 function Zeq=parallel(Z1,Z2)
2     Zeq=Z1*Z2/(Z1+Z2)
3 endfunction
4
5 w=800
6 R1=10
7 R2=20
8 L=0.05
9 C=0.25E-3
10 Xl=w*L*%i
11 Xc=1/(w*C*%i)
12
13 Zeq1=R2+parallel(Xc,R1+Xl)
14 Zeq2=parallel(parallel(R1,R2)+Xc,Xl)
15
16 disp(Zeq2,Zeq1)
```

---

### Scilab code Exa 4.44 Problem44

```

1 pf=0.707
2 theta=acos(pf)
3 P=200
4 Q=tan(theta)*P
5 pf2=0.85
6 theta_n=acos(pf2)
7 Qn=Q*tan(theta_n)
8 Qc=Q-Qn
9
10 w=314
11 V=2000
12 C=Qc/(V*V*w)
13
14 disp(C)

```

---

### Scilab code Exa 4.45 Problem45

```

1 I=20
2 w=2000
3 R=200
4 L=0.25
5 Xl=w*L*%i
6
7 Ir=I*Xl/(Xl+R)
8 Il=I-Ir
9 Vl=Xl*Il
10
11 t=1E-3
12 ir=sqrt(2)*real(Ir*exp(%i*w*t))
13 il=sqrt(2)*real(Il*exp(%i*w*t))
14 vl=sqrt(2)*real(Vl*exp(%i*w*t))
15 is=sqrt(2)*real(I*exp(%i*w*t))
16 vs=vl
17
18 Pr=ir*ir*R

```

```
19 P1=vl*il  
20 Ps=is*ir*R  
21 Pr=ir*vl  
22  
23 disp(Ps,P1,Pr)
```

---

### Scilab code Exa 4.46 Problem46

```
1 Vl=1  
2 w=2  
3 R=1  
4 r=1/2  
5 L=0.5  
6 C=1  
7 Xl=w*L*%i  
8 Xc=1/(w*C*%i)  
9  
10 Il=Vl/Xl  
11 VR=Il*R  
12 Vs=Vl+VR  
13  
14 Vr=Vs  
15 Ir=Vr/r  
16 Ic=Vs/Xc  
17 Is=Ir+Ic+Il  
18  
19 PR=-VR*VR/R  
20 Pr=-Vr*Vr/r  
21 Ps=Vs*conj(Is)  
22  
23 disp(real(Ps),Pr,PR)
```

---

### Scilab code Exa 4.47 Problem47

```

1 V=10*i
2 w=1000
3 R=2
4 L=2E-3
5 C=500E-6
6 Xl=w*L*i
7 Xc=1/(w*C*i)
8
9 Zeq=Xl+Xc+parallel(R,Xl)
10 disp(Zeq)
11
12 I=V/Z
13 Ir=I*Xl/(R+Xl)
14 Il2=I-Ir
15 Vl=I*Xl
16 Vc=I*Xc
17
18 disp(I,Ir,Il2,Vl,Vc)

```

---

### Scilab code Exa 4.48 Problem48

```

1 function [x,y]=polar_to_cart(r,theta)
2     theta=theta/180*pi
3     x=r*cos(theta)
4     y=r*sin(theta)
5 endfunction
6
7 [Vr,Vc]=polar_to_cart(100,120)
8 V1=complex(Vr,Vc)
9
10 I=10
11 w=5000
12 R=10000
13 L=2.4E-3
14 C=0.05E-3

```

```
15
16
17 [Vr ,Vc ]=polar_to_cart(96 ,60)
18 Vl=complex(Vr ,Vc )
19
20 Xl=w*L*%i
21 Xc=1/(w*C*%i)
22
23 I1=Vl/Xl
24 Ic=I-I1
25 V2=(R+Xc)*Ic+V1
26 V3=V2-Vl
27 V1=Ic*Xc
28
29 disp(V1 ,V2 ,V3)
```

---

### Scilab code Exa 4.49 Problem49

```
1 function Zeq=parallel(Z1 ,Z2)
2     Zeq=Z1*Z2/(Z1+Z2)
3 endfunction
4
5 /////////// short AB
6 Vab=0
7 Isc=50/4
8
9 /////////// for Zn
10 Zn=parallel(4 ,8*%i)
11
12 disp(Isc ,Zn)
```

---

### Scilab code Exa 4.50 Problem50

```
1 function Zeq=parallel(Z1,Z2)
2     Zeq=Z1*Z2/(Z1+Z2)
3 endfunction
4
5 V=12*%i
6
7 Vth=4-12*%i/(4-12*%i+6+9*%i)*V
8 Zth=parallel(4-12*%i,6+9*%i)
9
10 I=Vth/(Zth+6+12*%i)
11 S=V*conj(I)
12 disp(S)
13
14 Zl=conj(Zth)
15 I=Vth/(Zth+Zl)
16 S=V*conj(I)
17 disp(Zth,S)
```

---

### Scilab code Exa 4.51 Problem51

```
1 function Zeq=parallel(Z1,Z2)
2     Zeq=Z1*Z2/(Z1+Z2)
3 endfunction
4
5 I=5
6
7 Zth=parallel(40,30*%i)
8 Zl=conj(Zth)
9 Vth=Zth*I
10 Z=Zth+Zl
11 Il=Vth/Z
12 Pmax=abs(Il*Il*real(Z1))
13
14 disp(Zth,Pmax)
```

---

### Scilab code Exa 4.52 Problem52

```
1 V=4*sqrt(2)
2 w=2
3 R=4
4 L=2
5 Xl=w*L%i
6
7 I1=V/(R+Xl)
8 Ic=-imag(I1)*%i
9 C=Ic/(V*%i*w)
10
11 disp(C)
```

---

# Chapter 5

## Frequency Response

**Scilab code Exa 5.1** Problem1

```
1 Q0=200
2
3 //a
4 R=1
5 C=2E-6
6 L=C/(Q0/R)^2
7 disp(L)
8
9 L=2E-15
10 C=1.2E-9
11 R=Q0*sqrt(L/C)
12 disp(R)
13
14 R=118500
15 L=120E-12
16 C=L*(Q0/R)^2
17 disp(C)
```

---

**Scilab code Exa 5.2** Problem2

```
1 R=1000
2 C=49E-6
3 L=13E-3
4
5 w0=1/sqrt(L*C)
6 Q0=w0*R*C
7
8 disp(Q0,w0)
```

---

### Scilab code Exa 5.3 Problem3

```
1 R=5
2 C=0.08E-6
3 L=5E-3
4
5 w0=1/sqrt(L*C)
6 f0=w0/2/%pi
7 Q0=w0*L/R
8 bandwidth=w0/Q0
9 wb=bandwidth
10 w=[w0-1/2*wb , w0+1/2*wb]
11
12 disp(w(2),w(1))
```

---

### Scilab code Exa 5.4 Problem4

```
1 L=40E-6
2 R=4.02
3 f0=800E3
4
5 w0=2*pi*f0
6 C=1/(w0*w0*L)
7 Q0=w0*L/R
```

```
8 fb=f0/Q0
9
10 Xl=w0*L%i
11 Xc=1/(w0*C%i)
12 Zin=R+Xl+Xc
13
14 disp(Zin,fb,C)
```

---

### Scilab code Exa 5.5 Problem5

```
1 G=5E-6
2 L=2E-3
3 I=2E-3
4 w=5000
5
6 C=1/(w*w*L)
7 Vmax=I/G
8 I1=1
9 I=I1*w*L*G
10
11 disp(I,Vmax,C)
```

---

### Scilab code Exa 5.6 Problem6

```
1 w0=1000
2 w2=1050
3 wb=2*(w2-w0)
4
5 Q0=w0/wb
6 disp(Q0)
```

---

### Scilab code Exa 5.7 Problem7

```
1 w0=200E3
2 wb=5E3
3 L=2.5E-3
4 Q=65
5
6 Q0=w0/wb
7 r=w0*L/Q
8
9 disp(r)
```

---

### Scilab code Exa 5.8 Problem8

```
1 C=12E-9
2 L=4E-3
3 R=5
4
5 w0=1/sqrt(L*C)
6
7 Vc=1.5
8 I=w0*C*Vc
9 Zi=R
10 Vi=R*I
11
12 disp(Vi,w0)
```

---

### Scilab code Exa 5.9 Problem9

```
1 w0=2.5E6
2 Zin=60E3
3 Q0=80
4
```

```
5 R=60E3
6 C=Q0/(w0*R)
7 L=1/(C*w0*w0)
8
9 disp(C,L,R)
```

---

### Scilab code Exa 5.10 Problem10

```
1 C=2.5E-6
2 R=8
3 wb=400
4
5 L=R/wb
6 w0=1/sqrt(L*C)
7 Q0=w0*L/R
8 w1=w0-wb/2
9 w2=w0+wb/2
10
11 disp(w2,w1,Q0,w0,L)
```

---

### Scilab code Exa 5.11 Problem11

```
1 w=1E6
2 wb=1000
3 V=0.05
4 I=5E-3
5
6 R=V/I
7 Q0=w0/wb
8 L=R*Q0/w0
9 C=1/(w0*w0*L)
10 V1=w0*L*I
11 Vc=V1
```

```
12 w1=w0-wb/2
13 w2=w0+wb/2
14
15 disp(w2,w1,Vc,Vl,C,L,Q0,R)
```

---

### Scilab code Exa 5.12 Problem12

```
1 R=1E6
2 L=1
3 C=1E-6
4 I=10E-6
5
6 w0=1/sqrt(L*C)
7 V=I*R
8
9 wb=1/(R*C)
10 Q0=w0/wb
11 w1=w0-wb/2
12 w2=w0+wb/2
13
14 disp(w2,w1,V,Q0,w0)
```

---

### Scilab code Exa 5.13 Problem13

```
1 f0=1E6
2 Cmax=500E-12
3 C=450E-12
4 w0=2*pi*f
5
6 L=1/(w0*w0*Cmax)
7
8 w=1/sqrt(L*C)
9 f=w/(2*pi)
```

```
10 wb=2*2*%pi*(f-f0)
11 r=wb*L
12 Q0=2*%pi*f*L/r
13
14 disp(Q0,L,r)
15
16 /////////////// calculation mistakes in book
```

---

### Scilab code Exa 5.14 Problem14

```
1 R=10E3
2 L=50E-3
3 C=100E-6
4
5 w0=1/sqrt(L*C)
6 Q0=w0*R*C
7 alpha=w0/2/Q0
8 zeta=alpha/w0
9 wd=w0*sqrt(1-zeta^2)
10
11 disp(wd,zeta,alpha,Q0,w0)
12
13 /////////////// calculation mistakes in the book
```

---

### Scilab code Exa 5.15 Problem15

```
1 w0=1000
2 wd=997
3 Yin=1.2E-3
4
5 zeta=sqrt(1-(wd/w0)^2)
6 alpha=zeta*w0
7 R=1/Yin
```

```
8 C=1/(2*alpha*R)
9 L=1/(w0*w0*C)
10
11 disp(C,L,R)
```

---

### Scilab code Exa 5.17 Problem17

```
1 I=1
2 w=400
3 R=500
4 L=1/40
5 C=250E-6
6 Xl=w*L*%i
7 Xc=1/(w*C*%i)
8
9 w0=1/sqrt(L*C)
10 ////////// at resonance
11 Ir=I
12 V=R*I
13 Il=V/Xl
14 Ic=V/Xc
15 Icir=abs(Il)
16 Ic+Il=0
17 Icl=Ic+Il
18
19 disp(Icl,Ic,Il,Ir)
```

---

### Scilab code Exa 5.18 Problem18

```
1 V=100
2 R=10
3 L=2E-3
4 C=200E-6
```

```
5
6 w0=1/sqrt(L*C)
7 Xl=w0*L%i
8 Xc=1/(w0*C%i)
9 I=V/R
10
11 Vl=I*Xl
12 Vc=I*Xc
13 Vlc=Vl+Vc
14
15 disp(Vlc,Vc,Vl,I,w0)
```

---

### Scilab code Exa 5.19 Problem19

```
1 R=1
2 L=10E-6
3 C=10E-12
4 V=10
5
6
7 w0=1/sqrt(L*C)
8 Xl=w0*L%i
9 Xc=1/(w0*C%i)
10
11 Q0=w0*L/R
12 Z=R*Q0*Q0
13 Iin=V/Z
14
15 Ic=V/Xc
16
17 disp(Ic,Iin,Z,Q0,w0)
```

---

### Scilab code Exa 5.20 Problem20

```

1 V=200
2 R=2
3 L=0.02
4
5 f=25
6 w0=2*pi*f
7 C=1/(w0*w0*L)
8 I=V/2
9 Vc=1/(C*w0)
10 disp(I,Vc)
11
12 f=50
13 w0=2*pi*f
14 C=1/(w0*w0*L)
15 I=V/2
16 Vc=1/(C*w0)
17 disp(I,Vc)
18
19 f=100
20 w0=2*pi*f
21 C=1/(w0*w0*L)
22 I=V/2
23 Vc=1/(C*w0)
24 disp(I,Vc)

```

---

### Scilab code Exa 5.21 Problem21

```

1 R=10
2 L=0.1
3 C=150E-6
4
5 w=sqrt((1+R*R*C/L)/(L*C))
6 f=w/(2*pi)
7
8 disp(f)

```

```
9 Req=R/(1-w*w*L*C+(w*R*C)^2)
10 disp(Req)
```

---

### Scilab code Exa 5.22 Problem22

```
1 R=35
2 Q0=50
3 f1=540E3
4 f2=1610E3
5 w1=2*pi*f1
6 w2=2*pi*f2
7
8
9 L=1/(w1*(Q0/R))
10 Cmax=(Q0/R)^2*L
11 Cmin=1/(L*w2^2)
12
13 disp(Cmin*1000000,Cmax*1000000,L*1000000)
```

---

### Scilab code Exa 5.28 Problem28

```
1 function [x,y]=polar_to_cart(r,theta)
2     theta=theta/180*pi
3     x=r*cos(theta)
4     y=r*sin(theta)
5 endfunction
6
7 [Vr,Vc]=polar_to_cart(4,30)
8 V=complex(Vr,Vc)
9
10 [Ir,Ic]=polar_to_cart(0.8,-10)
11 I=complex(Ir,Ic)
12
```

```

13 wv=3
14 wi=5
15 R1=1
16 L=2
17 R6=6
18 C=1/3
19
20 //////////////deactivating curr source
21 Xl=wv*L*%i
22 Xc=1/(wv*C*%i)
23 I11=V/(R1+R6+Xl+Xc)
24 Pav1=norm(I11)^2*R1
25
26 //////////////deactivating voltage source
27 Xl=wi*L*%i
28 Xc=1/(wi*C*%i)
29 I12=I*(R6+Xl)/(R6+Xl+R1+Xc)
30 Pav2=norm(I12)^2*R1
31
32 Pav=Pav1+Pav2
33
34 disp(Pav)

```

---

### Scilab code Exa 5.29 Problem29

```

1 L=10E-6
2 R=1
3 C=10E-9
4 V=10
5
6 Zmax=L/R/C
7 I=V/Zmax
8 w0=1/sqrt(L*C)
9 w=0.9*w0
10

```

```
11 Y=R*C/L+%i*(w*C-1/w/L)
12 I=norm(Y)*V
13
14 disp(I)
```

---

# Chapter 6

## Three Phase Circuits

Scilab code Exa 6.1 Problem1

```
1 function [x,y]=polar_to_cart(r,theta)
2     theta=theta/180*pi
3     x=r*cos(theta)
4     y=r*sin(theta)
5 endfunction
6
7 omega=exp(%i*120/180*pi)
8 Va=200
9 Vb=200/omega
10 Vc=200*omega
11
12 [Zr,Zc]=polar_to_cart(100,60)
13 Z=complex(Zr,Zc)
14
15 Ia=Va/Z
16 Ib=Vb/Z
17 Ic=Vc/Z
18
19 disp(Va,Vb,Vc,Ia,Ib,Ic)
```

---

### Scilab code Exa 6.2 Problem2

```
1 Vl=400
2 Vph=Vl
3 pf=0.8
4
5 Pph=1500/3
6 Iph=Pph/Vph/pf
7 Il=sqrt(3)*Iph
8 theta=acos(0.8)
9 Iph=Iph*exp(%i*theta)
10 Zph=Vph/Iph
11
12 disp(Iph,Il,Zph)
```

---

### Scilab code Exa 6.3 Problem3

```
1 Vl=400
2 pf=0.8
3
4 Pph=1200/3
5 Vph=Vl/sqrt(3)
6 Iph=Pph/Vph/pf
7 Il=Iph
8 theta=acos(0.8)
9 Zph=Vph/Iph*exp(%i*theta)
10
11 disp(Il,Iph,Zph)
```

---

### Scilab code Exa 6.4 Problem4

```
1 function [x,y]=polar_to_cart(r,theta)
2     theta=theta/180*%pi
3     x=r*cos(theta)
4     y=r*sin(theta)
5 endfunction
6
7 Vl=400
8 Vp=Vl/sqrt(3)
9 disp(Vp)
10
11 [Ir,Ic]=polar_to_cart(50,-30)
12 Il=complex(Ir,Ic)
13 Ip=Il
14 Zy=Vp/Il
15 disp(Zy)
16
17 P=sqrt(3)*Vl*Il*cos(30/180*%pi)
18 Q=sqrt(3)*Vl*Il*sin(30/180*%pi)
19 disp(P,Q)
```

---

### Scilab code Exa 6.5 Problem5

```
1 Vl=400
2 Z=16+%i*12
3
4 Vp=Vl
5 Ip=Vp/Z
6 pf=cos(atan(imag(Z)/real(Z)))
7 Il=Ip*sqrt(3)
8
9 P=sqrt(3)*Vl*Il*pf
10 Q=sqrt(3)*Vl*Il*sin(acos(pf))
11
```

```
12 S=P+%i*Q
13
14 disp(Ip,I1,PF,P,Q,S)
```

---

### Scilab code Exa 6.6 Problem6

```
1 V1=400
2 Zload=60+%i*15
3
4 Vs=V1/sqrt(3)
5 Z=0.3+%i*1+Zload
6
7 I1=Vs/Z
8 Vload=I1*Zload*sqrt(3)
9 Pload=3*I1*I1*real(Zload)
10 Qload=3*I1*I1*imag(Zload)
11 Sload=Pload+%i*Qload
12
13 //////////// l1=lineloss
14 P11=3*I1*I1*real(Z-Zload)
15 Q11=3*I1*I1*imag(Z-Zload)
16 S11=P11+%i*Q11
17
18 Ssource=Sload+S11
19
20 disp(I1,Vload,Sload,S11,Ssource)
```

---

### Scilab code Exa 6.7 Problem7

```
1 Ig1=200000/sqrt(3)/11000/0.75
2 PG1=200000
3 QG1=200000*tan(acos(0.75))
4 SG1=PG1+%i*QG1
```

```

5
6 P11=3*Ig1*Ig1*1
7 Q11=3*Ig1*Ig1*2.2
8 S11=P11+%i*Q11
9 S1G1=SG1-S11
10 V1=S1G1/sqrt(3)/Ig1
11
12
13 P1=400000
14 Q1=400000*tan(acos(0.8))
15 P1G2=P1-real(S1G1)
16 Q1G2=Q1-imag(S1G1)
17 S1G2=P1G2+%i*Q1G2
18
19 IG2=S1G2/sqrt(3)/V1
20
21 P112=3*IG2*IG2*0.6
22 Q112=3*IG2*IG2*1.2
23
24 PG2=P1G2+P112
25 QG2=Q1G2+Q112
26 SG2=PG2+%i*QG2
27 VG2=SG2/sqrt(3)/IG2
28
29 disp(norm(SG2),norm(VG2))

```

---

### Scilab code Exa 6.9 Problem9

```

1 function [x,y]=polar_to_cart(r,theta)
2     theta=theta/180*pi
3     x=r*cos(theta)
4     y=r*sin(theta)
5 endfunction
6
7 V1=400

```

```

8 [Ir,Ic]=polar_to_cart(20,-30)
9 Iab=complex(Ir,Ic)
10
11 omega=exp(%i*120/180*pi)
12 Ib=Iab/omega
13 Ica=Iab*omega
14
15 IAa=Iab-Ica
16 Pab=Vl*norm(Iab)*cos(30/180*pi)
17 Ptotal=3*Pab
18
19 Zp=Vl/Iab
20 Rp=real(Zp)
21
22 disp(IAa)
23 disp(Ptotal)
24 disp(Rp)

```

---

### Scilab code Exa 6.10 Problem10

```

1 omega=exp(%i*120/180*pi)
2
3 Zp=17.32+%i*10
4 Vab=400
5 Iab=Vab/Zp
6 Ica=Iab/omega
7 IAa=Iab-Ica
8 IBb=IAa/omega
9 ICc=IAa*omega
10 disp(ICc,IBb,IAa)
11
12 Pab=(norm(Iab)^2)*real(Zp)
13 Ptotal=3*Pab
14 disp(Ptotal)
15

```

```
16 Itotal=IAa+IBb+ICc  
17 disp(Itotal)
```

---

### Scilab code Exa 6.11 Problem11

```
1 omega=exp(%i*120/180*pi)  
2  
3 function [x,y]=polar_to_cart(r,theta)  
4     theta=theta/180*pi  
5     x=r*cos(theta)  
6     y=r*sin(theta)  
7 endfunction  
8  
9 [Zr,Zc]=polar_to_cart(5,60)  
10 Z=complex(Zr,Zc)  
11  
12 [Vr,Vc]=polar_to_cart(25,30)  
13 Van=complex(Vr,Vc)  
14  
15 Ian=Van/Z  
16 Ibn=Ian/omega  
17 Icn=Ian*omega  
18  
19 Vcn=Van*omega  
20 Vac=Van-Vcn  
21  
22 disp(Ibn,Icn,Vac)
```

---

### Scilab code Exa 6.12 Problem12

```
1 V=400  
2 w=2*50*pi  
3 P=25000
```

```

4 pf1=0.7
5 theta1=acos(pf1)
6 I11=P/(sqrt(3)*V*pf1)*exp(-%i*theta1)
7 Ip1=I11/sqrt(3)
8
9
10 pf2=0.85
11 theta2=acos(pf2)
12 I12=P/(sqrt(3)*V*pf2)*exp(-%i*theta2)
13 Ip2=I12/sqrt(3)
14
15 Ic=Ip2-Ip1 /////////////////////////////////////////////////////////////////// calculation
               mistake in the book at this step
16 C=real(Ic/(V*w*%i))
17 disp(C)

```

---

### Scilab code Exa 6.13 Problem13

```

1 omega=exp(%i*120/180*%pi)
2 Vrn=400/sqrt(3)
3 Vyn=Vrn/omega
4 Vbn=Vrn*omega
5
6 P1=4000
7 P2=8000
8 P3=12000
9
10 Ir=conj(P1/Vrn)
11 Iy=conj(P2/Vyn)
12 Ib=conj(P3/Vbn)
13
14 In=Ir+Iy+Ib
15
16 disp(norm(Ir),norm(Iy),norm(Ib),norm(In))

```

---

### Scilab code Exa 6.14 Problem14

```
1 function [x,y]=polar_to_cart(r,theta)
2     theta=theta/180*%pi
3     x=r*cos(theta)
4     y=r*sin(theta)
5 endfunction
6
7
8 Vbc=-400*%i
9 Rl=1
10
11 [Sr,Sc]=polar_to_cart(10000,acos(0.8))
12 S=complex(Sr,Sc)
13
14
15 Vl=Vbc
16 I1=norm(S/(sqrt(3)*Vl))           ////////////// calculation
    mistake in book here
17 P=3*I1*I1*Rl
18 disp(P)
19
20 Van=norm(Vbc/sqrt(3))
21
22 Ia=I1*exp(-%i*acos(0.8))
23 omega=exp(%i*120/180*%pi)
24 Ib=Ia/omega
25
26 disp(Van,Ia,Ib)
```

---

### Scilab code Exa 6.15 Problem15

```

1 function [x,y]=polar_to_cart(r,theta)
2     theta=theta/180*pi
3     x=r*cos(theta)
4     y=r*sin(theta)
5 endfunction
6
7 [Vr,Vc]=polar_to_cart(231,60)
8 Van=complex(Vr,Vc)
9
10 Sp=(2.5-%i*1.2)*1000
11
12 omega=exp(%i*120/180*pi)
13 Vbn=Van/omega
14 Vcn=Van*omega
15
16 Vbc=Vbn-Vcn
17
18 Ibc=conj(Sp/Vbc)
19 Ica=Ibc*omega
20 Iab=Ibc/omega
21
22 IaA=Ica-Iab
23
24 disp(IaA)

```

---

### Scilab code Exa 6.16 Problem16

```

1 omega=exp(%i*120/180*pi)
2 Vab=400
3 Vca=400*omega
4 Vbc=400/omega
5
6 //Mesh Method
7 A=[80+100*%i ,100*%i ;100*%i ,50*%i]
8 I=inv(A)*[-Vca;Vbc]

```

```
9 Ia=I(1)
10 Ib=I(2)
11
12 Ic=-(Ia+Ib)
13 Van=80*Ia
14 Vbn=-50*%i*Ib
15 Vcn=100*%i*Ic
16
17 disp(Ia,Ib,Ic, Van ,Vbn ,Vcn)
```

---

### Scilab code Exa 6.17 Problem17

```
1 omega=exp(%i*120/180*pi)
2 Vab=400
3 Vca=400*omega
4 Vbc=400/omega
5
6 Iab=Vab/(100*%i)
7 Ibc=Vbc/(-50*%i)
8 Ica=Vca/80
9
10 Ia=Iab-Ica           //calaculation mistake in the book
    here
11 Ib=Ibc-Iab
12 Ic=Ica-Ibc
13
14 disp(Ia,Ib,Ic)
```

---

### Scilab code Exa 6.18 Problem18

```
1 V=400
2 P=900
3 pf=0.8
```

```
4
5 Pph=P/3
6 Vph=V/sqrt(3)
7 Iph=Pph/Vph/pf
8 Zph=Vph/Iph
9 theta=acos(pf)
10 Zph=Zph*exp(-%i*theta)
11 disp(Zph)
```

---

### Scilab code Exa 6.19 Problem19

```
1 V=400
2 Z=complex(40,30)
3
4 Iph=V/Z
5 Il=sqrt(3)*norm(Iph)
6 Ptotal=sqrt(3)*Il*V*cos(atan(imag(Z)/real(Z)))
7
8 disp(Iph,Il,Ptotal)
```

---

### Scilab code Exa 6.20 Problem20

```
1 Ig1=15000/sqrt(3)/800/0.8
2 PG1=15000
3 QG1=15000*tan(acos(0.8))
4 SG1=PG1+%i*QG1
5
6 P11=3*Ig1*Ig1*1.2
7 Q11=3*Ig1*Ig1*1.8
8 S11=P11+%i*Q11
9 S1G1=SG1-S11
10 V1=S1G1/sqrt(3)/Ig1
11
```

```

12
13 P1=30000
14 Q1=30000*tan(acos(0.8))
15 P1G2=P1-real(S1G1)
16 Q1G2=Q1-imag(S1G1)
17 S1G2=P1G2+%i*Q1G2
18
19 IG2=S1G2/sqrt(3)/V1
20
21 P112=3*IG2*IG2*0.8
22 Q112=3*IG2*IG2*1.2
23
24 PG2=P1G2+P112
25 QG2=Q1G2+Q112
26 SG2=PG2+%i*QG2
27 VG2=SG2/sqrt(3)/IG2
28
29 disp(norm(SG2),norm(VG2))

```

---

### Scilab code Exa 6.21 Problem21

```

1 omega=exp(%i*120/180*pi)
2 w=2*50*pi
3 Vry=415
4 Vyb=Vry/omega
5 Vbr=Vry*omega
6
7 C=40E-6
8 Zry=100
9 Zyb=complex(20,60)
10 Zbr=1/(%i*w*C)
11
12 I1=Vry/Zry
13 I2=Vyb/Zyb
14 I3=Vbr/Zbr

```

```
15  
16 Ir=I1-I3  
17 Iy=I2-I1  
18 Ib=I3-I2  
19  
20 disp(norm(Ir),norm(Iy),norm(Ib))
```

---

# Chapter 7

## Magnetic Circuits

Scilab code Exa 7.1 Problem1

```
1 uo=(4*%pi)*1E-7
2
3 i1=5
4 i2=2.5
5 r=0.4
6 H=i1/(2*pi*r)
7
8 F=uo*H*i2      /////////////// attractive
9 ur=8000
10 Firon=ur*F
11
12 disp(H,F,Firon)
```

---

Scilab code Exa 7.2 Problem2

```
1 l=0.15
2 i1=50
3
```

```
4 H1=i1/(2*%pi*(0.1+1))
5 i2=-H1*(2*%pi*0.1)
6
7
8 disp(i2)
```

---

### Scilab code Exa 7.3 Problem3

```
1 Ha=4/(2*%pi*0.2)
2 Hb=Ha
3 H=sqrt(Ha^2+Hb^2)
4 theta=(%pi+atan(-Hb/Ha))*180/%pi
5
6 disp(H,theta)
```

---

### Scilab code Exa 7.4 Problem4

```
1 uo=(4*%pi)*1E-7
2
3 Bg=1.2
4 N=400
5 ur=4000
6
7 lc=(2*(20-4+16-4)-0.2)/100
8 Ac=4/100*4/100
9 Rc=lc/(ur*uo*Ac)
10
11 lg=0.2/100
12 Rg=lg/(uo*Ac)
13
14 R=Rc+Rg
15
16 flux=Bg*Ac
```

```
17 i=flux*N  
18  
19 disp(i)
```

---

### Scilab code Exa 7.5 Problem5

```
1 function Zeq=parallel(Z1,Z2)  
2     Zeq=Z1*Z2/(Z1+Z2)  
3 endfunction  
4  
5 uo=(4*%pi)*1E-7  
6 fluxg1=0.8E-3  
7  
8 lg1=0.02/100  
9 lg2=0.02/100  
10 lg3=0.025/100  
11 Ag1=2/100*1/100  
12 Ag2=1/100*1/100  
13 Ag3=1/100*1/100  
14  
15 Rg1=lg1/(uo*Ag1)  
16 Rg2=lg2/(uo*Ag2)  
17 Rg3=lg3/(uo*Ag3)  
18 Req=Rg1+parallel(Rg2,Rg3)  
19  
20 MMF=fluxg1*Req  
21  
22 disp(MMF)
```

---

### Scilab code Exa 7.6 Problem6

```
1 uo=(4*%pi)*1E-7  
2 ur=4000
```

```

3 fluxc=0.01
4 N=500
5
6 Ll=(2*(20+4)+25+4)/100
7 Lc=(25+4)/100
8 Lr=Ll-0.02/100
9 Lg=0.02/100
10 A=4/100*4/100
11
12 Rl=Ll/(ur*u0*A)
13 Rc=Lc/(ur*u0*A)
14 Rr=Lr/(ur*u0*A)
15 Rg=Lg/(u0*A)
16
17 Fab=fluxc*Rc
18 fluxr=Fab/(Rr+Rg)
19 fluxl=fluxc+fluxr
20
21 F=fluxl*Rl+Fab
22 I=F/N
23
24 disp(I)

```

---

### Scilab code Exa 7.7 Problem7

```

1 u0=(4*%pi)*1E-7
2
3 l1=50/100
4 l2=20/100
5 l3=50/100
6 lbc=0.025/100
7
8 A1=25E-4
9 A2=12.5E-4
10 A3=25E-4

```

```

11
12 fluxg=0.75E-3
13
14 B=fluxg/A1
15 Fbc=B/u0*lbc
16
17 Hcd=200
18 Hab=Hcd
19 Fabcd=Hab*l1
20 Fad=Fbc+Fabcd
21 Had=Fab/12
22 Bad=1.04
23 fluxad=Bad*A2
24
25 fluxdea=fluxad+fluxg
26 Bdea=fluxdea/A3
27 Hdea=500
28 Fdea=Hdea*l3
29
30 F=Fdea+Fad
31
32 disp(F)

```

---

### Scilab code Exa 7.8 Problem8

```

1 uo=(4*%pi)*1E-7
2 ur=3000
3 Ac=10/100*10/1000
4 Bc=1.4
5 Hc=Bc/(uo*ur)
6 lc=150/100
7 Ftotal=Hc*lc
8
9 N2=800
10 I2=2

```

```

11 F2=N2*I2
12 F1=Ftotal-F2
13
14 N1=400
15 I1=F1/N1 //out of terminal a
16 disp(I1)
17
18
19 Bc=1.4
20 fluxc=Bc*Ac
21 Rc=lc/(Ac*uo*ur)
22 Wf=1/2*Rc*fluxc*fluxc
23 disp(Wf)
24
25
26
27 L1=N1*N1/Rc
28 L2=N2*N2/Rc
29 M=sqrt(L1*L2)
30 disp(M)

```

---

### Scilab code Exa 7.9 Problem9

```

1 uo=(4*%pi)*1E-7
2 ur=6000
3 A=5/2*2/10000
4 Lr=(%pi*(20+25)/2-0.1)/100
5 Lg=0.1/100
6 Rr=Lr/(uo*ur*A)
7 Rg=Lg/(uo*A)
8 Rtotal=Rr+Rg
9
10 F=2*500
11 flux=F/Rtotal
12 Bg=flux/A

```

```

13 disp(Bg)
14
15 L=flux*500/2
16 disp(L)
17
18 Wfr=1/2*Rr*flux*flux
19 Wfg=1/2*Rg*flux*flux
20 disp(Wfg,Wfr)
21
22 imax=2
23 flux_max=flux
24 E=4.44*314/(2*pi)*500*flux_max
25 flux_max2=100/(sqrt(2)*4.44*314/(2*pi)*500)
26 Fmax2=flux_max2*Rtotal
27 imax2=Fmax2/500
28 disp(imax2)

```

---

### Scilab code Exa 7.10 Problem10

```

1 Ac=12/10000
2 Fmin=160*9.81
3 B=sqrt(Fmin*2*u0/Ac)
4
5 H=2800
6 L=75/100
7 F=H*L
8 Lg=0.1/1000
9 A=24/10000
10 Rg=Lg/(u0*A)
11 fluxg=B*A
12 Fg=fluxg*Rg
13
14 Ftotal=F+Fg
15 imin=Ftotal/1000
16 disp(imin)

```

---

### Scilab code Exa 7.11 Problem11

```
1 Wm1=1/2*(1200-750)*0.012
2 disp(Wm1)
3
4 flux_g=0.012/750*1200
5 Wm2=1/2*(flux_g-0.012)*1200
6 disp(Wm2)
7
8 Ra=1200/0.012
9 Rb=1200/flux_g
10 Fo=-1/2*(0.012^2)*0.75*10^6
11 Fc=-1/2*(flux_g^2)*0.75*10^6
12 disp(Fc ,Fo)
```

---

### Scilab code Exa 7.12 Problem12

```
1 V1=10
2
3 //Mesh Method
4 A=[1+10*%i ,-80*%i ;80*%i ,-500-800*%i]
5 I=inv(A)*[V1;0]
6
7 V2=500*I(2)
8
9 disp(V1,V2,I)
```

---

### Scilab code Exa 7.14 Problem14

```
1 uo=(4*%pi)*1E-7
2 ur=1600
3
4 lc=160/100
5 lg=0.8/1000
6 A=5/10000
7 N=1200
8
9 Rc=lc/(uo*ur*A)
10 Rg=lg/(uo*A)
11 R=Rc+Rg
12
13 L=N*N/R
14 disp(L)
```

---

### Scilab code Exa 7.15 Problem15

```
1 N=100
2 l1=0.15
3 l2=0.3
4 l3=0.45
5 A=0.001
6
7 ur1=1447
8 ur2=5969
9 ur3=47750
10
11 flux=0.6E-3
12
13 B=flux/A
14
15 H1=B/(uo*ur1)
16 H2=B/(uo*ur2)
17 H3=B/(uo*ur3)
18 disp(H1,H2,H3)
```

```
19
20 F=H1*l1+H2*l2+H3*l3
21 disp(F)
22
23 I=F/N
24 disp(I)
```

---

### Scilab code Exa 7.16 Problem16

```
1 P11=1500
2 f1=50
3 P12=3000
4 f2=75
5
6 Y=[1 ,f1 ;1 ,f2]
7 X=inv(Y)*[P11/f1;P12/f2]
8
9 Ph1=X(1)*f1
10 Pe1=X(2)*f1*f1
11 Ph2=X(1)*f2
12 Pe2=X(2)*f2*f2
13
14 disp(Ph1,Pe1,Ph2,Pe2)
```

---

### Scilab code Exa 7.17 Problem17

```
1 uo=(4*%pi)*1E-7
2 F=750*1
3 disp(F)
4
5 dm=(16+20)/200
6 lc=dm*%pi
7 Hc=F/lc
```

```

8 disp(Hc)
9
10 flux=1.25/1000
11 Ac=(20-16)*2.5/10000
12 Bc=flux/Ac
13 disp(Bc)
14
15 R=F/flux
16 disp(R)
17
18 u=Bc/Hc
19 disp(u)
20
21 ur=u/u0
22 disp(ur)           // calculation mistake in the book
                     here

```

---

### Scilab code Exa 7.18 Problem18

```

1 fluxc=1.5E-3
2 Ac=12/10000
3 Bc=fluxc/Ac
4 Hc=1250
5 lc=0.3
6 F=Hc*lc
7
8 Fa=200*1
9 Fb=600*0.75
10
11 Fc=F-Fb+Fa
12 Nc=Fc/0.5
13 disp(Nc)      ////clockwise5

```

---

### Scilab code Exa 7.19 Problem19

```
1 uo=(4*%pi)*1E-7
2 ur=2000
3 V=200
4 f=50
5 N=1600
6 Ac=5/10000
7
8 flux_max=V/(4.44*f*N)
9 Bmax=flux_max/Ac
10 disp(Bmax)
11
12 Rc=20/100/(uo*ur*Ac)
13 Rg=0.5/1000/(uo*Ac)
14 R=Rc+Rg
15
16 imax=flux_max*R/N
17 disp(imax)
18
19 Wfmax=1/2*R*(flux_max^2)
20 disp(Wfmax)
21
22 percent=Rg/R*100
23 disp(percent)
```

---

# Chapter 8

## Transformers

**Scilab code Exa 8.1** Problem1

```
1 V1=3300
2 f=50
3 N1=100
4 N2=300
5 Z=100+35*%i
6 flux_max=V1/(sqrt(2)*%pi*f*N1)
7 V2=V1*N2/N1
8 I2=V2/Z
9 I1=N2/N1*I2
10 S=V1*conj(I1)
11 Z1=Z*(N1/N2)^2
12
13 disp(flux_max)
14 disp(I1,I2)
15 disp(real(S),imag(S))
16 disp(Z1)
```

---

**Scilab code Exa 8.2** Problem2

```

1 a=2400/240
2
3 R=0.2+a*a*2/1000
4 X=0.6+a*a*6/1000
5 disp(R,X)
6
7 Rlv=1/a/a*R
8 Xlv=1/a/a*X
9 disp(Rlv,Xlv)
10
11 I2=150*1000/2400
12 Z=R+%i*X
13 V=I2*Z
14 pcnt=norm(V)/2400*100
15 disp(V,pcnt)
16
17 Im=2400/1600
18 Ii=2400/10000
19 Io=Ii-%i*Im
20 pf=cos(atan(imag(Io)/real(Io)))
21 disp(Io,pf)

```

---

### Scilab code Exa 8.3 Problem3

```

1 P=200E3
2 V1=11000
3 V2=415
4 f=50
5 N2=80
6
7 N1=V1/V2*N2
8 a=N1/N2
9 disp(a)
10
11 I2=P/V2

```

```
12 disp(I2)
13 I1=I2/a
14 disp(I1)
15
16 Z2=V2*V2/P
17 disp(Z2)
18 Z21=Z2*a*a
19 disp(Z21)
```

---

### Scilab code Exa 8.4 Problem4

```
1 V1=200
2 f=50
3 N1=150
4 Ac=10*5/10000
5
6
7 Flux_max=V1/(sqrt(2)*%pi*f*N1)
8 Bmax=Flux_max/Ac
9 Hmax=250
10 l=2*(25+10)+2*(20+10)
11 l=l/100
12 AT_max=Hmax*l
13 Im_max=AT_max/150
14 Im_rms=Im_max/sqrt(2)
15 disp(Im_rms)
16
17 Fe_loss=23000
18
19 Cv = 2*(25+2*10)*10*5 + 2*20*10*5
20 Cv=Cv/1000000
21 C1=Fe_loss*Cv
22 disp(C1)
23
24 Ii=150/V1
```

25 **disp**(Ii)

---

### Scilab code Exa 8.5 Problem5

```
1 function [x,y]=polar_to_cart(r,theta)
2     theta=theta/180*%pi
3     x=r*cos(theta)
4     y=r*sin(theta)
5 endfunction
6
7 [Zr,Zc]=polar_to_cart(5,30)
8 Z2=complex(Zr,Zc)
9
10 V=200
11 N2=75
12 N1=100
13
14 I2=V/Z2
15 I1=N2/N1*I2
16
17 disp(norm(I1))
18 disp(" lagging" , real(I1)/norm(I1))
```

---

### Scilab code Exa 8.6 Problem6

```
1 R=60
2 V=6
3 Rs=2400
4
5 a=sqrt(Rs/R)
6 disp(a)
7
8 P1_max=1/2*(R*R)/(Rs+Rs)
```

```
9 I1=V/2/Rs
10
11 I1=I1*a
12 disp(I1)
13 V1=V/2/a
14 disp(V1)
```

---

### Scilab code Exa 8.7 Problem7

```
1 f=50
2 a=1100/220
3 Rhv=0.125
4 Xhv=0.625
5 Rlv=0.005
6 Xlv=0.025
7
8 Zhv=Rhv+%i*Xhv
9 Zlv=Rlv+%i*Xlv
10
11 Z1=Zhv+a*a*Zlv
12 disp(Z1)
13 Z2=Z1/a/a
14 disp(Z2)
15
16 Zpu1=Z1*0.05/1.1/1.1
17 disp(Zpu1)
18 Zpu2=Z2*0.05/0.22/0.22
19 disp(Zpu2)
```

---

### Scilab code Exa 8.8 Problem8

```
1 P=600E3
2 a=2400/600
```

```

3 r1=0.05
4 r2=0.004
5 x1=0.025
6 x2=0.016
7 R1=1667
8 Xm=417
9
10 ///////////////////////////////////////////////////////////////////As seen from the LV side
11
12 Zlv=r2+%i*x2+1/a/a*(r1+%i*x1)
13 disp(Zlv)
14
15 RiLV=R1/a/a
16 disp(RiLV)
17 XmLV=Xm/a/a
18 disp(XmLV)
19
20
21 Zpu=Zlv*0.6/0.6/0.6
22 disp(Zpu)
23 Ri=RiLV*0.6/0.6/0.6
24 disp(Ri)
25 Xm=XmLV*0.6/0.6/0.6
26 disp(Xm)

```

---

### Scilab code Exa 8.9 Problem9

```

1 P=50E3
2 a=2200/220
3
4 ///////////////////////////////////////////////////////////////////OC Parameters
5 Poc=405
6 Ioc=5
7 Voc=220
8

```

```

9 ///////////////////////////////////////////////////////////////////SC Parameters
10 Psc=805
11 Isc=20.2
12 Vsc=95
13
14
15 Y0=Ioc/Voc
16 Gi=Poc/Voc/Voc
17 Bm=sqrt(Y0*Y0-Gi*Gi)
18
19 Z=Vsc/Isc
20 R=Psc/Isc/Isc
21 X=sqrt(Z*Z-R*R)
22
23 ////////////////////Referred to HV side
24 GiHV=Gi/a/a
25 disp(GiHV)
26 BmHV=Bm/a/a
27 disp(BmHV)
28 disp(R)
29 disp(X)
30
31 ////////////////////Referred to LV side
32 disp(Gi)
33 disp(Bm)
34 RLV=R/a/a
35 disp(RLV)
36 XLV=X/a/a
37 disp(XLV)
38
39
40 //////////////////Per unit
41 GiPU=GiHV/0.0103
42 BmPU=BmHV/0.0103
43 RPU=R/96.8
44 XPU=X/96.8
45 disp(GiPU)
46 disp(BmPU)

```

```
47 disp(RPU)
48 disp(XPU)
```

---

### Scilab code Exa 8.10 Problem10

```
1 P=50E3
2 a=2200/110
3
4 /////OC Parameters
5 Poc=400
6 Ioc=10
7 Voc=110
8
9 Y0=Ioc/Voc
10 Gi=Poc/Voc/Voc
11 disp(Gi)
12 Bm=sqrt(Y0*Y0-Gi*Gi)
13 disp(Bm)
14
15 ///////////Referred to HV side
16 GiHV=Gi/a/a
17 disp(GiHV)
18 BmHV=Bm/a/a
19 disp(BmHV)
20
21 ///////////Per unit
22 GiPU=Gi*P/Voc/Voc
23 BmPU=Bm*P/Voc/Voc
24 disp(GiPU)
25 disp(BmPU)
```

---

### Scilab code Exa 8.11 Problem11

```

1 P=25000
2 V1=2200
3 V2=220
4 a=V1/V2
5 f=50
6 r1=2
7 r2=0.025
8 x1=7
9 x2=0.07
10 Xm=16000
11
12 Im=V2/Xm
13 disp(" pf=0, 90 degree lag Po=0", Im)
14
15 R=r1+a*a*r2
16 X=x1+a*a*x2
17 Z=sqrt(R*R+X*X)
18 Ifl=P/V1
19 Vsc=Z*Ifl
20 Vsc_percent=Vsc/V1*100
21 disp(Vsc,Vsc_percent)
22 Im=Vsc/Xm
23 Im_percent=Im/Ifl*100
24 disp(Im,Im_percent)
25
26 Sc_pf=cos(atan(X/R))
27 disp(Sc_pf)
28
29 //////////// Per unit
30 ZBpu=1000*2.2*2.2/25
31 r1pu=r1/193.6
32 r2pu=a*a*r2/193.6
33 x1pu=x1/193.6
34 x2pu=a*a*x2/193.6
35
36 Rpu=r1pu+r2pu
37 Xpu=x1pu+x2pu
38

```

```
39 Xmpu=Xm/193.6
40 disp(Rpu,Xpu,Xmpu)
```

---

### Scilab code Exa 8.12 Problem12

```
1 P=10000
2 v1=2300
3 v2=230
4 a=v1/v2
5 f=50
6 r1=3.96
7 r2=0.0396
8 x1=15.8
9 x2=0.158
10
11 R=r1+a*a*r2
12 X=x1+a*a*x2
13 V2=v2*a
14 I=P/V2
15 theta=acos(0.80)
16 V1=V2+I*(R*cos(theta)+X*sin(theta))
17 disp(V1)
18 VR=(V1-V2)/V2
19 disp(VR)
20
21 pf=X/sqrt(R*R+X*X)
22 theta2=acos(pf)
23 I1=I*(cos(theta)-%i*sin(theta))
24 Ic=real(I1*tan(theta2))-imag(I1)
25 Rating_Cap=V2*Ic
26 disp(Rating_Cap)
27 V1=V2
28 disp(V1)
```

---

### Scilab code Exa 8.13 Problem13

```
1 P=100000
2 N1=400
3 N2=100
4 a=N1/N2
5 r1=0.3
6 r2=0.015
7 x1=1.1
8 x2=0.055
9 V1=2400
10
11 R=r1+a*a*r2
12 disp(R)
13 X=x1+a*a*x2
14 disp(X)
15
16 I1=P/V1
17 pf=0.8
18 theta=acos(pf)
19 Vd=I1*(R*cos(theta)+X*sin(theta))
20 VR=Vd/V1*100
21 V2=(V1-Vd)/a
22 disp(VR ,V2)
23 Vd=I1*(R*cos(theta)-X*sin(theta))
24 VR=Vd/V1*100
25 V2=(V1-Vd)/a
26 disp(VR ,V2)
27
28 pf=cos(atan(R/X))           //// wrong in the book
29 disp("leading" ,pf)
```

---

### Scilab code Exa 8.14 Problem14

```
1 P=10000
2 v1=2300
3 v2=230
4 a=v1/v2
5 f=50
6 r1=3.96
7 r2=0.0396
8 x1=15.8
9 x2=0.158
10
11 R=r1+a*a*r2
12 X=x1+a*a*x2
13 V2=v2*a
14 I=P/V2
15 pf=0.8
16 theta=acos(pf)
17 V1=V2+I*(R*cos(theta)+X*sin(theta))
18 Pi=75*V1*V1/V2/V2
19 Pc=I*I*R
20 P1=Pi+Pc
21 P0=P*pf
22 effi=P0/(P0+P1)*100
23 disp(effi)
24
25 V1=V2
26 Pi=75
27 pf2=X/sqrt(R*R+X*X)
28 I=P0/V1/pf2
29 Pc=I*I*R
30 P1=Pi+Pc
31 P0=P*pf
32 effi=P0/(P0+P1)*100
33 disp(effi)
34
35 I=sqrt(Pi/R)
36 Load=V2*I
```

```
37 P0=Load*pf
38 P1=2*Pi
39 effi_max=P0/(P0+P1)*100
40 disp(effi_max)
```

---

### Scilab code Exa 8.15 Problem15

```
1 P=15E3
2 a=3000/250
3
4 ///////////////////////////////////////////////////////////////////OC Parameters
5 Poc=105
6 Ioc=0.62
7 Voc=250
8
9 ///////////////////////////////////////////////////////////////////SC Parameters
10 Psc=360
11 Isc=5.2
12 Vsc=157
13
14
15 Y0=Ioc/Voc
16 Gi=Poc/Voc/Voc
17 Bm=sqrt(Y0*Y0-Gi*Gi)
18
19 Z=Vsc/Isc
20 R=Psc/Isc/Isc
21 X=sqrt(Z*Z-R*R)
22
23 /////////////////////////////////////////////////////////////////// Referred to HV side
24 GiHV=Gi/a/a
25 disp(GiHV)
26 BmHV=Bm/a/a
27 disp(BmHV)
28 disp(R)
```

```

29 disp(X)
30
31 ////////////// Per unit
32 ZB=3.12/5.2
33 GiPU=Gi*ZB
34 BmPU=Y0*ZB
35 RPU=R/ZB/1000
36 XPU=X/ZB/1000
37 disp(GiPU)
38 disp(BmPU)
39 disp(RPU)
40 disp(XPU)
41
42
43 pf=0.8
44 theta=acos(pf)
45 V2=250*a
46 I=P/V2
47 Vd=I*(R*cos(theta)-X*sin(theta))
48 VR=-Vd/V2*100
49 disp(VR)
50 Pi=105
51 Pc=I*I*R
52 Pl=Pi+Pc
53 P0=P*pf
54 effi=P0/(Pl+P0)*100
55
56 pf2=cos(atan(R/X))
57 disp(" leading", pf2)
58
59
60 IPU=sqrt(Pi/P/RPU)
61 effi_max=IPU
62 disp(effi_max)

```

---

### Scilab code Exa 8.16 Problem16

```
1 v1=2500
2 v2=250
3 P=25000
4 Pc=130
5 Pcfl=320
6 pf=0.8
7
8 V2=2750
9
10 P0=P*pf
11 P1=Pcfl+Pc
12 effi=P0/(P0+P1)*100
13 disp(effi)
14
15 I2=P/v2
16 I1=I2+P/v1
17 kVA=I1*v1/1000
18 P0=kVA*pf*1000
19 effi=P0/(P0+P1)*100
20 disp(effi)
```

---

### Scilab code Exa 8.17 Problem17

```
1 a=10
2 Load=120000
3 V=400
4
5 I=Load/V/sqrt(3)
6 Vll=a*V/sqrt(3)
7 Ill=sqrt(3)*I/a
8 all=Vll/V
9 disp(Vll,Ill,all)
10
```

```
11 Vll=a*V*sqrt(3)
12 Ill=I/a/sqrt(3)
13 all=Vll/V
14 disp(Vll,Ill,all)
```

---

### Scilab code Exa 8.18 Problem18

```
1 f=50
2 N1=500
3
4 Pin=60
5 Io=0.4
6 Vin=220
7 r=0.8
8
9 Pci=Io*Io*r
10 Pi=Pin-Pci
11 disp(Pi)
12 theta=acos(Pin/Vin/Io)
13 Im=Io*sin(theta)
14 Xm=Vin/Im
15 disp(Xm)
16 Iio=Io*cos(theta)
17 Ri=Vin/Iio
18 disp(Ri)
```

---

### Scilab code Exa 8.19 Problem19

```
1 P=15E3
2 v1=2200
3 v2=220
4 a=v1/v2
5
```

```

6 //OC Parameters
7 Poc=185
8 Ioc=2.72
9 Voc=220
10
11 //SC Parameters
12 Psc=197
13 Isc=6.3
14 Vsc=112
15
16 Pi=Poc
17 disp(Pi)
18
19 IHVfl=P/v1
20 Pcf1=IHVfl*IHVfl/Isc/Isc*Psc
21 disp(Pcf1)
22
23 pf=0.85
24 Po=P*pf
25 Pl=Pi+Pcf1
26 effi=Po/(Po+Pl)*100
27 disp(effi)
28
29 Z=Vsc/Isc
30 R=Psc/Isc/Isc
31 X=sqrt(Z*Z-R*R)
32 pf=0.8
33 theta=acos(pf)
34 Vd1=IHVfl*(R*cos(theta)+X*sin(theta))
35 Vd2=IHVfl*(R*cos(theta)-X*sin(theta))
36 VR1=Vd1/v1*100
37 VR2=Vd2/v1*100
38 disp(VR1, VR2)

```

---

**Scilab code Exa 8.20 Problem20**

```

1 P=50000
2 lr=0.9
3
4 P0=P*1*0.9
5 effi=0.974
6 P1=(1-effi)/effi*P0
7 Pi=P1/2
8 Pcf1=Pi/lr/lr
9
10 pf=0.8
11 P0=P*pf
12 P1=Pi+Pcf1
13 effi=P0/(P0+P1)*100
14 disp(effi)
15
16 P0=P/2*lr
17 P1=Pi+Pcf1/2/2
18 effi=P0/(P0+P1)*100
19 disp(effi)
20
21 /////////////// calculation mistakes in the book

```

---

### Scilab code Exa 8.21 Problem21

```

1 P=500E3
2 effi=0.95
3
4 A=[1 ,1 ,1 ,0 .6*0 .6]
5 Pa=inv(A)*[P*(1-effi)/effi;P*0.6*(1-effi)/effi]
6 Pi=Pa(1)
7 disp(Pi)
8 Pc=Pa(2)
9 disp(Pc)
10
11 P1=Pi+0.75*0.75*Pc

```

```
12 effi=P*0.75/(P*0.75+P1)
13 disp(effi)
```

---

### Scilab code Exa 8.22 Problem22

```
1 v1=2200
2 v2=220
3 f=50
4 emfperturn=12
5
6 N1=floor(v1/emfperturn)
7 N2=floor(v2/emfperturn)
8 disp(N1)
9 disp(N2)
10
11 fluxmax=emfperturn/4.44/f
12 Bmax=1.5
13 Ac=fluxmax/Bmax
14 disp(Ac)
```

---

### Scilab code Exa 8.23 Problem23

```
1 v1=3300
2 v2=600
3 f=50
4 Ac=25/10000
5 l=1.2
6
7 Bmax=1.2
8 fluxmax1=Bmax*Ac
9 N1=v1/4.44/f/fluxmax1
10 N2=v2/4.44/f/fluxmax1
11 disp(N1 ,N2)
```

```
12
13 I2=20
14 pf=0.8
15 I1=N2/N1*I2
16 I1=I1*(pf-%i*sinacos(0.8)))
17 disp(I1)
18
19 Hmax=250
20 ATmax=Hmax*l
21 immax=ATmax/N1/sqrt(2)
22 i=0
23 I1=-%i*immax+I1
24 disp("lagging", real(I1)/norm(I1), norm(I1))
```

---

### Scilab code Exa 8.24 Problem24

```
1 P=50000
2 v1=2400
3 v2=240
4 f=50
5 a=v1/v2
6 Pd=375
7 pf=0.4
8
9 I0=Pd/v1/pf
10 I0_prime=I0*a
11 disp(I0_prime,pf)
```

---

### Scilab code Exa 8.25 Problem25

```
1 v1=220
2 v2=110
3 z1=0.32+%i*0.85
```

```

4 z2=0.11+%i*0.27
5 a=v1/v2
6
7 z=z1+a*a*z2
8 IHV=v1/norm(z)
9 ILV=IHV*a
10 disp(IHV,ILV)

```

---

### Scilab code Exa 8.26 Problem26

```

1 P=1000000
2 v1=11000
3 v2=230
4 f=50
5 Vsc=310
6 Psc=5210
7
8 Isc=P/v1
9 Z=Vsc/Isc
10 R=Psc/Isc/Isc
11 X=sqrt(Z*Z-R*R)
12
13 pf=1
14 theta=acos(pf)
15 Vd=Isc*(R*cos(theta)+X*sin(theta))
16 VR=Vd/v1*100
17 V1=v1+Vd
18 disp(VR,V1)
19
20 pf=0.8
21 theta=acos(pf)
22 Vd=Isc*(R*cos(theta)+X*sin(theta))
23 VR=Vd/v1*100
24 V1=v1+Vd
25 disp(VR,V1)

```

```

26
27 pf=0.8
28 theta=acos(pf)
29 Vd=Isc*(R*cos(theta)-X*sin(theta)) // calculation
   mistake in the book at this point
30 VR=Vd/v1*100
31 V1=v1+Vd
32 disp(VR,V1)

```

---

### Scilab code Exa 8.27 Problem27

```

1 P=10000
2 v1=2200
3 v2=220
4 r1=4
5 r2=0.04
6 x1=5
7 x2=0.05
8 a=v1/v2
9 R=r1+a*a*r2
10 X=x1+a*a*x2
11 I1=P/v1
12 pf=0.8
13 V2=v2*a
14 theta=acos(pf)
15 Vd=I1*(R*cos(theta)+X*sin(theta))
16 VR=Vd/v1*100
17 V1=v1+Vd
18 disp(VR,V1)
19
20 pf=cos(atan(X/R))
21 disp("leading",pf)
22
23 Pr=P*pf
24 Q=-P*sin(acos(pf))

```

25 **disp**(Q,Pr)

---

**Scilab code Exa 8.28** Problem28

```
1 P=20000
2 v1=200
3 v2=400
4 f=50
5 V1=600
6 V2=200
7
8 a=V1/V2
9 disp(a)
10
11 I1=P/v2
12 VA=V1*I1
13 disp(VA)
14
15 disp(I1)
16 I2=30000/V2
17 Is=I2-I1
18 disp(I2)
19 disp(Is)
20
21 VATrans=v2*I1
22 VAcond=30000-VATrans
23 disp(VATrans)
24 disp(VAcond)
```

---

**Scilab code Exa 8.29** Problem29

```
1 P=100000
2 v1=11000
```

```
3 v2=400
4
5 V1=400
6 Vp=V1/sqrt(3)
7
8 a=ceil(v1/Vp)
9 disp(a)
10
11 I1=P/sqrt(3)/V1
12 Ip=I1
13 disp(I1,Ip)
14
15 I1=P/sqrt(3)/v1
16 Ip=I1/sqrt(3)
17 disp(I1,Ip)
```

---

# Chapter 9

## EMF and Torque in Electric Machines

Scilab code Exa 9.1 Problem1

```
1 f=50
2 flux=0.016
3 S=36
4 P=6
5 N=10
6
7
8 m=S/P
9 gammaa=%pi/m
10 Kb=sin(m*gammaa/2)/m/sin(gammaa/2)
11 Nph=S*N*2/2
12 Ep=4.44*Kb*f*Nph*flux
13 kVA=Ep*N/1000
14 disp(kVA)
15
16 m=S/2/P
17 gammaa=%pi/2/m
18 Kb=sin(m*gammaa/2)/m/sin(gammaa/2)
19 Nph=S*N*2/2/2
```

```
20 Ep=4.44*Kb*f*Nph*flux
21 Eline=Ep*sqrt(2)
22 kVA=Ep*N*2/1000
23 disp(kVA)
24
25 m=S/3/P
26 gammaa=%pi/3/m
27 Kb=sin(m*gammaa/2)/m/sin(gammaa/2)
28 Nph=S*N*2/2/3
29 Ep=4.44*Kb*f*Nph*flux
30 Eline=Ep*sqrt(3)
31 kVA=Ep*N*3/1000
32 disp(kVA)
```

---

### Scilab code Exa 9.2 Problem2

```
1 S=54
2 P=6
3 m=S/3/P
4 gammaa=%pi/3/m
5
6 Kb1=sin(m*gammaa/2)/m/sin(gammaa/2)
7 Kb3=sin(m*gammaa/2*3)/m/sin(gammaa/2*3)
8 Kb5=sin(m*gammaa/2*5)/m/sin(gammaa/2*5)
9
10 disp(Kb1)
11 disp(Kb3)
12 disp(Kb5)
```

---

### Scilab code Exa 9.3 Problem3

```
1 f=50
2 n=500
```

```
3 m=5
4 N=12
5 flux=0.025
6
7 P=120*f/n
8 S=m*3*P
9 Nph=S*N*2/2/3
10 gammaa=%pi/3/m
11 Kb=sin(m*gammaa/2)/m/sin(gammaa/2)
12 polepitch=S/N
13 coilpitch=13
14 spa=(polepitch-coilpitch)*gammaa
15 Kp=cos(spa/2)
16
17 Ep=4.44*Kb*Kp*f*Nph*flux
18 disp(Ep)
19 Eline=sqrt(3)*Ep
20 disp(Eline)
```

---

#### Scilab code Exa 9.4 Problem4

```
1 f=50
2 P=6
3 ns=120*f/P
4 disp(ns)
5 wm=2*%pi/60*ns
6 disp(wm)
```

---

#### Scilab code Exa 9.5 Problem5

```
1 F2=850
2 F1=400
3 lambda=123.6/180*%pi
```

```
4 ppp=1.408/1000
5
6 theta=%pi-lambda
7 Fr=sqrt(F1*F1+F2*F2-2*F1*F2*cos(theta))
8
9 fluxr=2/%pi*ppp*Fr
10 disp(fluxr)
```

---

### Scilab code Exa 9.6 Problem6

```
1
2 P=6
3 N=1000
4
5 f=P*N/120
6 ns=120*f/4
7 s=0.04
8 n=(1-s)*ns
9 disp(n)
```

---

### Scilab code Exa 9.7 Problem7

```
1
2 P=4
3 f=50
4
5
6 ns=120*f/P
7 n1=-1500
8 s1=(ns-n1)/ns
9 f2=s1*f
10 SRV=s1*80
11 disp(f2,SRV)
```

```
12
13 n2=1000
14 s2=(ns-n2)/ns
15 f2=s2*f
16 SRV=s2*80
17 disp(f2,SRV)
```

---

### Scilab code Exa 9.8 Problem8

```
1
2 betaa=acos(0)*2/5
3 coilpitch=%pi-betaa
4 disp(coilpitch/%pi*180)
5
6 P=6
7 S=72
8 m=S/P
9 gammaa=%pi/m
10 cpis=150/180*%pi
11 beta= %pi-cpis
12 Kp1=cos(betaa/2)
13 Kp3=cos(5*betaa/2)
14 Kp13=cos(13*betaa/2)
15 disp(Kp1)
16 disp(Kp3)
17 disp(Kp13)
```

---

### Scilab code Exa 9.9 Problem9

```
1
2 P=2
3 f=50
4 S=42
```

```
5 m=S/3/P
6 gammaa=%pi/3/m
7 Kb=sin(m*gammaa/2)/m/sin(gammaa/2)
8 coilpitch=17
9 polepitch=S/2
10 spa=(polepitch-coilpitch)*gammaa
11 Kp=cos(spa/2)
12
13 N=S*2
14 Nc=N/2
15 Coilsperphase=Nc/3
16 Nph=Coilsperphase/2
17 Eline=2300
18 flux=Eline/sqrt(3)/4.44/Kb/Kp/f/Nph
19 disp(flux)
```

---

### Scilab code Exa 9.10 Problem10

```
1 f=50
2 ns=1000
3 P=120*f/ns
4 disp(P)
5 s=(ns-940)/ns
6 disp(s*100)
7 nrr=ns-940
8 disp(nrr)
9 nrs=1000
10 disp(nrs)
11 s=2*s
12 n=1000*(1-s)
13 disp(n)
```

---

### Scilab code Exa 9.11 Problem11

```
1 ns=1000
2 s=(ns-940)/ns
3 news=2*s
4 n=1000*(1-news)
5 disp(n)
```

---

### Scilab code Exa 9.12 Problem12

```
1 P=8
2 f1=60
3 f2=50
4 If1=5
5 If2=f1/f2*If1
6 disp(If2)
7 nA2=120*f2/P
8 disp(nA2)
```

---

### Scilab code Exa 9.13 Problem13

```
1 f1=60
2 f2=50
3 P1=12
4 P2=f2/f1*P1
5 disp(P2)
6 nset=120*f1/P1
7 disp(nset)
```

---

### Scilab code Exa 9.14 Problem14

```
1 m=6
```

```
2 gammaa=%pi/m
3 Kb=sin(m*gammaa/2)/m/sin(gammaa/2)
4
5 m=4
6 Kb=sin(m*gammaa/2)/m/sin(gammaa/2)
```

---

### Scilab code Exa 9.15 Problem15

```
1
2 f=50
3 n=965
4 P=floor(120*f/n)
5 disp(P)
6
7 s=(1000-965)/1000
8 disp(s)
9 f2=s*f
10 disp(f2)
11
12 nsr=1000-965
13 disp(nsr)
14 nrr=120*f2/P
15 nsrf=1000-965-nrr
16 disp(nsrf)
```

---

### Scilab code Exa 9.16 Problem16

```
1 f=50
2 P=4
3 a=2
4
5 ns=120*f/P
6 n=1440
```

```
7 s=1-n/ns
8 disp(s)
9 f2=s*f
10 disp(f2)
11 E1p=400
12 E2f=400/a
13 E2f2=E2f*f2/f
14 E2l=sqrt(3)*E2f2
15 disp(E2l)
```

---

# Chapter 10

## DC Machines

Scilab code Exa 10.1 Problem1

```
1 P=6
2 S=36
3 coilside=2
4 N=8
5 A=2
6 d=0.25
7 l=0.18
8 Ia=10
9 avgflux=0.8
10 n=1200
11
12 Z=S*coilside*N
13 flux=%pi*d/P*l*avgflux
14 Ea=flux*n*Z/60*P/A
15 Pm=Ea*Ia
16 disp(Pm)
17 T=Pm/2/%pi/n*60
18 disp(T)
```

---

### Scilab code Exa 10.2 Problem2

```
1 P=4
2 A=4
3 ra=0.145
4 l=0.21
5 Z=2*33*11
6 K=Z*P/2/%pi/A
7 disp(K)
8
9 Ap=2*%pi*ra/P*0.7*l
10 Barc=0.8
11 flux=Ap*Barc
12 n=1200
13 Ea=K*flux*2*%pi*n/60
14 disp(Ea)
15
16 Ia=240
17 Ic=Ia/A
18 disp(Ic)
19
20 T=K*flux*Ia
21 disp(T)
22 Pg=Ea*Ia
23 disp(Pg)
```

---

### Scilab code Exa 10.3 Problem3

```
1 P=5000
2 Vt=215
3 n=1000
4 Ra=0.4
5 Ia=P/Vt
6 Eag=Vt+Ra*Ia
7 Eam=Vt-Ra*Ia
```

```
8 newn=Eam/Eag*n/1.1
9 disp(newn)
```

---

### Scilab code Exa 10.4 Problem4

```
1 P=200000
2 V=400
3 n=600
4 Z=864
5 P1=8000
6
7 Ia=P/V
8 Ra=P1/Ia/Ia
9 Ea=V-Ia*Ra
10 flux=Ea*60/n/Z
11 disp(flux)
```

---

### Scilab code Exa 10.5 Problem5

```
1 N=1800
2 //////////////from figure
3 Voc=250
4 If=4.1
5 Rf=Voc/If
6 disp(If)
7 disp(Rf)
8
9 Rfcrit=150/2
10 disp(Rfcrit)
11
12 V3=120
13 Ncrit=N*V3/150
14 disp(Ncrit)
```

```
15  
16 Rf220=220/3.2  
17 Rext=Rf220-Rf  
18 disp(Rext)
```

---

### Scilab code Exa 10.6 Problem6

```
1 P=4  
2 V=230  
3 Z=888  
4 Ra=0.8  
5 flux=5.4E-3  
6 A=2  
7  
8 I1=2  
9 If=0.6  
10 Ia=I1-If  
11 Ea=V-Ia*Ra  
12 n0=Ea*60/flux/Z/P*A  
13 disp(n0)  
14  
15 T=29.6  
16 Ia=T*2*pi/flux/Z/P*A  
17 I1=Ia+If  
18 disp(I1)  
19 Ea=V-Ra*Ia  
20 n=Ea*60/flux/Z/P*A  
21 disp(n)  
22 sr=(1-n/n0)*100  
23 disp(sr)
```

---

### Scilab code Exa 10.7 Problem7

```

1 n1=1000
2 V=230
3 Ia=75
4 Ra=0.1
5 Ea1=V-Ia*Ra
6 Rf=275
7 If=V/Rf
8 Ke=Ea1/If/n1
9
10 n2=1200
11 Ia=125
12 Ea2=V-Ia*Ra
13 If2=Ea2/Ke/n2
14 Rf2=V/If2
15 Rfext=Rf2-Rf
16 disp(Rfext)

```

---

### Scilab code Exa 10.8 Problem8

```

1 V=115
2 Ia1=25
3 Ra=0.3
4
5 n1=1450
6 Ea1=V-Ia1*Ra
7 Ke=Ea1/n1
8
9 n2=1200
10 Ea2=Ke*n2
11 Ia2=3/4*Ia1
12 Raext=(V-Ea2)/Ia2-Ra
13 disp(Raext)
14 effia=Ea2/V*100      // calculation mistake in the
                           book at this point
15 disp(effia)

```

```
16 V=Ea2+Ia2*Ra  
17 effia=Ea2/V*100  
18 disp(effia)
```

---

### Scilab code Exa 10.9 Problem9

```
1 //////////////////////////////////////////////////////////////////  
2 Ra=0.5  
3 P=8000  
4 V=230  
5 Ea=V  
6 n=1200  
7 Ke=V/n  
8  
9 p=poly([P*Ra,-V,1],"w","coeff")  
10 w=roots(p)  
11  
12 Ea=w(1) //rejecting small value  
13 n=Ea/Ke  
14 disp(n)  
15 T=P/2/%pi/n*60  
16 disp(T)  
17 Ia=(V-Ea)/Ra  
18 disp(Ia)  
19 Kt=T/Ia  
20  
21  
22 p=poly([-Kt*V/Ra,Kt*Ke/Ra,0.6E-4],"w","coeff")  
23 w=roots(p)  
24 n=w(2)  
25 disp(n)
```

---

### Scilab code Exa 10.10 Problem10

```

1 V=300
2 Ea=V
3 n1=1200
4 n2=1100
5 Kaphi=Ea/2/%pi/n1*60
6
7 T=350
8 Ia=T/Kaphi
9 disp(Ia)
10 Ea=V*n2/n1
11 Pm=Ea*Ia
12 disp(Pm)
13
14 Ra=(V-Ea)/Ia
15 disp(Ra)
16
17 disp(T)
18 Ea=600-Ia*Ra
19 n=Ea*60/Kaphi/2/%pi
20 Pm=Ea*Ia
21 disp(Pm)
22 disp(n)

```

---

### Scilab code Exa 10.11 Problem11

```

1 V=300
2 Ea=V
3 n1=1200
4 n2=1100
5 Kaphi=Ea/2/%pi/n1*60
6
7 T=350
8 Ia=T/Kaphi
9 Ea=V*n2/n1
10

```

```
11 Ra=(V-Ea)/Ia
12
13
14 Kaphi=Kaphi/2
15 n=Ea/Kaphi*60/2/%pi
16 Pm=Ea*Ia
17 T=Kaphi*Ia
18 disp(T)
19 disp(Pm)
20 disp(n)
```

---

### Scilab code Exa 10.12 Problem12

```
1 V=600
2 Ia=40
3 R=0.5
4 Ea=V-Ia*R
5 n=500
6 Ka=Ea/Ia/2/%pi/n*60
7 T=Ka*Ia*Ia
8
9 n2=450
10 T=T*n2*n2/n/n
11 Ia=sqrt(T/Ka)
12 Ea=Ka*Ia*2*pi*n2/60
13 Rtotal=(V-Ea)/Ia
14 Rext=Rtotal-R
15 disp(Rext)
```

---

### Scilab code Exa 10.13 Problem13

```
1 V=220
2 Ra=1
```

```
3 Rse=0.4
4 Ia1=20
5 Ia2=sqrt(Ia1*Ia1*0.7*0.7*0.7)
6 Ea1=V-Ia1*(Ra+Rse)
7 Ea2=Ia2*0.7*Ea1/Ia1
8 Rext=(V-Ea2)/Ia2-Ra-Rse
9 disp(Rext)
```

---

### Scilab code Exa 10.14 Problem14

```
1 V=250
2 Ia=25
3 n=1000
4 KaNfNse=V/Ia*60/2/%pi/n
5 T=KaNfNse*Ia*Ia
6 Ia=sqrt(V*2/KaNfNse/sqrt(KaNfNse*2*pi*n/60*2*pi*n
/60/T/2))
7 w=sqrt(KaNfNse*2*pi*n/60*2*pi*n/60/T/2)*Ia
8 n=w*60/2/%pi
9
10 disp(n)
11 disp(Ia)
```

---

### Scilab code Exa 10.15 Problem15

```
1 V=230
2 Rf=120
3 Ra=0.15
4 If=V/Rf
5 Psh=V*V/Rf
6
7 I=14.5
8 Pin=I*V
```

```

9 Ia=I-If
10 Pk=Pin-Ia*Ia*Ra
11
12 I=215
13 Ia=I-If
14 P1=Ia*Ia*Ra+Pk
15 Pin=V*I
16 effi=(Pin-P1)/Pin
17 disp(effi)
18
19 Ia=sqrt(Pk/Ra)
20 Il=Ia+If
21 P1=2*Pk
22 Pin=V*Il
23 effi=(Pin-P1)/Pin
24 disp(effi)

```

---

### Scilab code Exa 10.16 Problem16

```

1 V=250
2 Rf=125
3 Ra=0.2
4 If=V/Rf
5 I=16
6 Ia0=I-If
7 Pk=V*Ia0-Ia0*Ia0*Ra+V*If
8
9 I=152
10 Ia=I-If
11 P1=Ia*Ia*Ra+Pk
12 Pin=V*I
13 effi=(Pin-P1)/Pin
14 disp(effi)
15
16 Il=152

```

```
17 Ia=Il+If  
18 P1=Ia*Ia*Ra+Pk  
19 Pout=V*Il  
20 effi=Pout/(Pout+P1)  
21 disp(effi)
```

---

### Scilab code Exa 10.17 Problem17

```
1 V=250  
2 n=800  
3 Ra=0.15  
4 Rse=0.1  
5 R=Ra+Rse  
6  
7 Ia1=120  
8 Ea1=V-Ia1*R  
9  
10 Ia2=60  
11 Ea2=V-Ia2*R  
12 n2=Ea2/Ea1*n/0.7  
13 disp(n2)
```

---

### Scilab code Exa 10.18 Problem18

```
1 R=1.2  
2 V=220  
3 Ea35=V-35*R  
4 n35=(475+400)/2  
5  
6 V=200  
7 E0=V-35*(R+2)  
8 n=n35*E0/Ea35  
9 disp(n)
```

---

### Scilab code Exa 10.19 Problem19

```
1 V=250
2 Ia=200
3 Ra=0.22
4
5 Ea=V-Ia*Ra
6 Pm=Ea*Ia
7 Prl=600
8 Pmout=Pm-Prl
9 n=1250
10 wm=2*pi*n/60
11 Tl=Pmout/wm
12 disp(Tl)
13
14 Rf=125
15 Psh=V*V/Rf
16 Pein=V*Ia+Psh
17 effi=Pmout/Pein
18 disp(effi)
```

---

### Scilab code Exa 10.20 Problem20

```
1 P=25000
2 n=1600
3 V=250
4 If=1.5
5 Rf=V/If
6 disp(Rf)
7
8 Ra=0.1
```

```
9 V=220
10 Ia=P/V
11 Ea=V-Ia*Ra
12 If=0.875
13 disp(If)
14 Rf=V/If
15 disp(Rf)
16
17 Pdev=Ea*Ia
18 disp(Pdev)
19 Tdev=Pdev/2/%pi/n*60
20 disp(Tdev)
```

---

### Scilab code Exa 10.21 Problem21

```
1
2 V=230
3 Ea=210
4 Ia=40
5 Ra=(V-Ea)/Ia
6 disp(Ra)
7
8 Pdev=Ea*Ia
9 n=1200
10 wm=2*%pi*n/60
11 Tdev=Pdev/wm
12 disp(Pdev)
13 disp(Tdev)
14
15 n=n*V/Ea
16 disp(n)
```

---

### Scilab code Exa 10.22 Problem22

```
1 V=400
2 Ia=50
3 n=500
4 Ra=0.5
5 Ea=V-Ia*Ra
6 Tdev=Ea*Ia/2/%pi/n*60
7
8 Iastart=75
9 Rs=V/Iastart-Ra
10 disp(Rs)
11 Tstart=Tdev*(Iastart/Ia)^2
12 disp(Tstart)
13
14 n2=200
15 Ea200=Ea*n2/n
16 Rs=(V-Ea200)/Iastart-Ra
17 disp(Rs)
```

---

### Scilab code Exa 10.23 Problem23

```
1 n1=1200
2 Rfcrit=260/4
3 n2=1600
4 Vfactor=n2/n2
5 Vn1=395
6 disp(Vn1)
```

---

### Scilab code Exa 10.24 Problem24

```
1
2 Ia=500
3 Ra=0.05
4 Vb=2
```

```
5 Va=Ia*Ra+Vb  
6 Vt=330  
7 disp(Vt)
```

---

### Scilab code Exa 10.25 Problem25

```
1 V=240  
2 Ea=V  
3 n=800  
4 I=16  
5 Ke=V/n/I  
6 K=I/n  
7  
8 n=sqrt(V*2/Ke/K/sqrt(2))  
9 disp(n)  
10 Ia=sqrt(2)*K*n  
11 disp(Ia)
```

---

### Scilab code Exa 10.26 Problem26

```
1 V=600  
2 Pout=60000  
3 effi=0.85  
4 Pin=Pout/effi  
5 Il=Pin/V  
6 Rf=100  
7 If=V/Rf  
8 Ia=Il-If  
9 Ra=0.16  
10 Ea=V-Ia*Ra  
11  
12 n=900  
13 n0=n*V/Ea
```

```
14 sr=n0/n-1
15 disp(n0)
16 disp(sr)
17
18 TL=Pin-Pout
19 Pcu=Ia*Ia*Ra
20 Psh=If*If*Rf
21 Prl=TL-Pcu-Psh
22 disp(Prl)
```

---

# Chapter 11

## Synchronous Machine

Scilab code Exa 11.1 Problem1

```
1 P=1000000
2 Vrated=6600
3 If=60
4 Xs_unsat=4700/sqrt(3)/98
5 disp(Xs_unsat)
6 Xs_adj=Vrated/sqrt(3)/143
7 disp(Xs_adj)
8
9 Ia=P/sqrt(3)/Vrated
10 pf=0.8
11 theta=-acos(pf)
12 Ia=Ia*(exp(%i*theta))
13 Ef=norm(Vrated+%i*Xs_adj*Ia*sqrt(3))
14 disp(Ef)
15 VR=Ef/Vrated-1
16 disp(VR)
```

---

Scilab code Exa 11.2 Problem2

```

1 P=45000
2 V=440
3 pf=0.8
4 Ia=P/sqrt(3)/V*exp(%i*cos(pf))
5 Vt=V/sqrt(3)
6 Rs=0.2
7 Xs=1.8
8 Ef=norm(Vt-Ia*(Rs+%i*Xs))
9 If=Ef/85
10 Pein=pf*P
11 Rf=35
12 Fl=If*If*Rf
13 Pin=Pein+Fl
14 Pcu=norm(3*Ia*Ia*Rs)
15 Pshaft=Pein-Pcu
16 Prl=1500
17 Pshaft_net=Pshaft-Prl
18 effi=Pshaft_net/Pin
19
20 disp(Pshaft_net)
21 disp(If)
22 disp(effi)

```

---

### Scilab code Exa 11.3 Problem3

```

1 V=12500
2 Xs=8
3
4 Vt=V/sqrt(3)
5 Ef=Vt
6
7 Ef=Vt*1.2
8 Ia=(Ef-Vt)/Xs
9 theta=%pi/2
10 pf=0

```

```
11 Pe=0
12 Qe=-sqrt(3)*V*Ia
13 disp(Ia)
14 disp(Pe)
15 disp(Qe)
16 disp(pf)
17
18 Ef=Vt*0.8
19 Ia=(Vt-Ef)/Xs
20 theta=-pi/2
21 pf=0
22 Pe=0
23 Qe=sqrt(3)*V*Ia
24 disp(Ia)
25 disp(Pe)
26 disp(Qe)
27 disp(pf)
```

---

### Scilab code Exa 11.4 Problem4

```
1 Pe=10000000
2 V=12500
3 Xs=8
4 Vt=V/sqrt(3)
5 Ef=Vt*1.2
6
7 delta=asin(Pe/3/Vt/Ef*Xs)
8 Ia=(Ef*exp(%i*delta)-Vt)/%i/Xs
9 pf=real(Ia)/norm(Ia)
10 Qe=-sqrt(3)*V*imag(Ia)
11
12 disp(norm(Ia))
13 disp(pf)
14 disp(Qe)
```

---

### Scilab code Exa 11.5 Problem5

```
1
2 Pein=1000000
3 pf=0.9
4 Xs=3.24
5 theta=acos(pf)
6 V=3300
7 Ia=Pein/sqrt(3)/pf/V*exp(%i*theta)
8 Vt=V/sqrt(3)
9 Ef=norm(Vt-%i*Ia*Xs)
10 Pemax=3*Vt*Ef/Xs
11 Ia=(Vt+Ef*%i)/%i/Xs
12 Qe=-sqrt(3)*V*imag(Ia)
13
14 disp(Pemax)
15 disp(norm(Ia))
16 disp(real(Ia)/norm(Ia))
17 disp(Qe)
```

---

### Scilab code Exa 11.6 Problem6

```
1 Pe=20000
2 Pm=20000
3 V=400
4 pf=0.8
5 Xs=4.5
6 Ia=Pm/sqrt(3)/V/pf*exp(%i*acos(pf))
7 Vt=V/sqrt(3)
8 Ef=Vt-%i*Ia*Xs      //calculation mistake in the
book at this step
9 Efline=norm(Ef)*sqrt(3)
```

```
10 disp(Efline)
11 disp(atan(imag(Ef)/real(Ef)))
12
13 delta=-%pi/2
14 Efmin=Pe/3*Xs/Vt*sin(-delta)
15 Efminline=Efmin*sqrt(3)
16 disp(Efminline)
17 disp(delta/%pi*180)
18 Ia=(Vt+%i*Efmin)/%i/Xs
19 disp(norm(Ia))
20 disp(real(Ia)/norm(Ia))
```

---

### Scilab code Exa 11.7 Problem7

```
1 f=50
2 ns=100
3 P=110000
4 pf=0.8
5
6 p=120*f/ns
7 disp(p)
8 kVA=P/pf/1000
9 disp(kVA)
10 kW=P/0.971/1000
11 disp(kW)
12 Tpm=kW*1000*60/2/%pi/ns
13 disp(Tpm)
```

---

### Scilab code Exa 11.8 Problem8

```
1 P=12E6
2 Q=6E6
3 V=22000
```

```

4 Xs=8
5 S=P+%i*Q
6 theta=atan(Q/P)
7 disp(theta/%pi*180)
8
9 Ia=norm(S)/sqrt(3)/V
10 Ef=V/sqrt(3)+%i*Xs*Ia*exp(-%i*theta)
11 delta=atan(imag(Ef)/real(Ef))
12 disp(delta/%pi*180)
13
14 emf=norm(Ef)*sqrt(3)
15 disp(emf)

```

---

### Scilab code Exa 11.9 Problem9

```

1 Isc=60
2 If=50
3
4 Voc=15300
5 Isc=60
6 Xs_unsat=Voc/sqrt(3)/Isc
7 disp(Xs_unsat)
8
9 V=11000
10 Isc=67.5
11 Xs_sat=V/sqrt(3)/Isc
12 disp(Xs_sat)
13
14 pf=0.85
15 theta=acos(pf)
16 Ia=50*exp(-%i*theta)
17 Vt=11000
18 Vl=Vt/sqrt(3)
19 Ef=Vl+%i*Xs_sat*Ia
20 Efligne=norm(Ef)*sqrt(3)

```

```
21 disp(Efline)
22
23 Voc=Efline
24 VR=Voc/Vt-1
25 disp(VR)
26 If=57.5
27 disp(If)
```

---

### Scilab code Exa 11.10 Problem10

```
1 P=10000
2 V=400
3 pf=0.8
4 Xs=16
5 theta=acos(pf)
6 Ia=P/sqrt(3)/V*exp(-%i*theta)
7 Vt=V/sqrt(3)
8 Ef=Vt+%i*Xs*Ia
9 disp(norm(Ef))
10 disp(atan(imag(Ef)/real(Ef))*180/%pi)
11
12 Ef2=1.2*norm(Ef)
13 Pe=P*pf
14 delta=asin(norm(Pe/3*Xs/Ef2/Vt))
15 Ef2=Ef2*exp(%i*delta)
16 Ia=(Ef2-Vt)/%i/Xs           // calculation mistake in the
                                book at this point
17 disp(norm(Ia))
18 pf=real(Ia)/norm(Ia)
19 disp(pf)
20 disp(acos(pf)*180/%pi)
21
22 delta=%pi/2
23 Pemax=norm(3*Ef*Vt/Xs*sin(delta))
24 disp(Pemax)
```

```
25 Ef=norm(Ef)*%i
26 Ia=(Ef-Vt)/%i/Xs
27 disp(norm(Ia))
28 disp(real(Ia)/norm(Ia))
```

---

### Scilab code Exa 11.11 Problem11

```
1 f=50
2 MechLoad=(8+0.5)*1000
3 Pein=MechLoad
4 Vt=231
5 Ef=750/sqrt(3)
6 Xs=16
7 delta=asin(Pein/3*Xs/Ef/Vt)
8 Ef=Ef*exp(-%i*delta)
9 Ia=(Vt-Ef)/%i/Xs
10 ns=120*50/4
11 ws=ns/60*2*pi
12 Tdev=Pein/ws
13 Tshaft=8000/ws
14 disp(norm(Ia))
15 disp(real(Ia)/norm(Ia))
16 disp(acos(real(Ia)/norm(Ia))*180/pi)
17 disp(Tdev)
18 disp(Tshaft)
19
20 Ef=600/sqrt(3)
21 delta=0
22 Ia=(Vt-Ef)/%i/Xs
23 kVAR=sqrt(3)*400*norm(Ia)
24 disp(norm(Ia))
25 disp(real(Ia)/norm(Ia))
26 disp(kVAR)
27 C=norm(Ia)/Vt/2/pi/f
28
```

```
29 Ef=300/sqrt(3)
30 Ia=(Vt-Ef)/%i/Xs
31 kVAR=sqrt(3)*400*norm(Ia)
32 disp(norm(Ia))
33 disp(real(Ia)/norm(Ia))
34 disp(kVAR)
35 L=Vt/norm(Ia)/2/%pi/f
36
37 kVAR=6000
38 Ia=kVAR/sqrt(3)/400*%i
39 Ef=Vt-%i*Xs*Ia
40 disp(Ef*sqrt(3))
```

---

### Scilab code Exa 11.12 Problem12

```
1 P=1000000
2 V=6600
3 Xs=25
4 pf=0.8
5 theta=acos(pf)
6 Ia=P/sqrt(3)/V*exp(-%i*theta)
7 Vt=V/sqrt(3)
8 Ef=Vt+%i*Xs*Ia
9 delta=asin(norm(Xs*Ia*cos(theta)/Ef))
10 Vt=norm(Ia)*Xs*sin(%pi-asin(pf)-delta)/sin(delta)
11 Vl=Vt*sqrt(3)
12 disp(Vl)
```

---

### Scilab code Exa 11.13 Problem13

```
1
2
3 Xs=8
```

```

4 Ia=40
5 V=600
6 Vt=V/sqrt(3)
7 Ef=V
8
9 delta=acos((1-(Xs*Ia/V)^2+(Vt/V)^2)/2/Vt*V)
10 theta=-atan((cos(delta)-Vt/V)/sin(delta))
11 pf=cos(theta)
12 Pout=sqrt(3)*V*pf*Ia
13 disp(Pout)
14
15 theta=-theta
16 Pin=Pout
17 disp(Pout)

```

---

### Scilab code Exa 11.14 Problem14

```

1
2 V=400
3 Vt=V/sqrt(3)
4 Ia=50
5 pf=1
6 theta=0
7 Xs=1.3
8
9 Ef=Vt-%i*Xs*Ia
10 delta=atan(imag(Ef)/real(Ef))
11 disp(delta*180/%pi)
12
13 Pelec=sqrt(3)*V*pf*Ia
14 Pmech=Pelec
15 pf=0.8
16 theta=acos(0.8)
17 Ia=Pelec/sqrt(3)/V/pf*exp(%i*theta)
18 Ef2=Vt-%i*Xs*Ia

```

```
19 If=0.9*norm(Ef2)/norm(Ef)
20 disp(If)
```

---

### Scilab code Exa 11.15 Problem15

```
1 Xspu=0.8
2 P=1000000
3 V=3000
4 Xs=Xspu*V*V/P
5
6 Vt=V/sqrt(3)
7 Pm=750000
8 Pe=Pm
9 pf=0.85
10 theta=acos(pf)
11 Ia=Pm/0.8/sqrt(3)/V*exp(-%i*theta)
12
13 Ef=Vt-%i*Xs*Ia
14 Efligne=sqrt(3)*norm(Ef)
15 disp(Efligne)
16
17 delta=%pi/2
18 Pmax=3*Vt*norm(Ef)/Xs
19 disp(Pmax)
20 ns=120*50/12
21 ws=ns*2*%pi/60
22 Tmax=Pmax/ws           // //// calculation mistake in the
                           book at this point
23 disp(Tmax)
24
25 delta=90
26 Efmin=Pm/3*Xs/Vt
27 Efmin_line=sqrt(3)*Efmin
28 disp(Efmin_line)
29
```

```
30 Ia=(Vt+%i*Efmin)/%i/Xs
31 disp(norm(Ia))
32 pf=real(Ia)/norm(Ia)
33 disp(pf)
```

---

# Chapter 12

## Induction Motor

Scilab code Exa 12.1 Problem1

```
1 V=400
2 I=80
3 pf=0.75
4 Pin=sqrt(3)*V*I*pf
5 Pshaft=Pin*0.85
6 disp(Pshaft)
7 ns=1000
8 s=0.04
9 n=(1-s)*ns
10 w=2*pi*n/60
11 Tshaft=Pshaft/w
12 disp(Tshaft)
```

---

Scilab code Exa 12.2 Problem2

```
1 f=50
2 f2=120/60
3 s=f2/f
```

```
4 ns=1500
5 n=(1-s)*ns
6 w=2*pi*n/60
7
8 T=100
9 Pshaft=T*w
10 disp(Pshaft)
11 Pm=(T+7)*w
12 Pcur=Pm*s/(1-s)
13 disp(Pcur)
14 Pin=Pm+Pcur+700
15 disp(Pin)
16 effi=Pshaft/Pin
17 disp(effi)
```

---

### Scilab code Exa 12.3 Problem3

```
1
2 ns=120*50/20
3 sf1=1-292.5/ns
4
5 R2=0.12
6 X2=1.12
7 smaxT=R2/X2
8 disp(smaxT)
9
10 Tmax_by_Tf1=0.5/X2/(R2/sf1/((R2/sf1)^2+X2^2))
11 disp(Tmax_by_Tf1)
```

---

### Scilab code Exa 12.5 Problem5

```
1
2 ns=750
```

```

3 R2=0.5
4 X2=5
5 smaxT=R2/X2
6 n=(1-smaxT)*ns
7 disp(n)
8
9 k=R2/X2
10 Tmax_by_Tstart=(1+k*k)/2/k
11 disp(Tmax_by_Tstart)
12
13 p=poly([1,-4,1],"k","coeff")
14 w=roots(p)
15 R2=w*5
16 R2ext=R2-0.5
17
18 R2total=18.66
19 smaxT=R2total/X2
20 R2ext=R2ext(2)
21 disp(R2ext)

```

---

### Scilab code Exa 12.6 Problem6

```

1
2 Tmax=200
3 Tstart=80
4
5 p=poly([1,-2*Tmax/Tstart,1],"smaxT","coeff")
6 smaxT=roots(p)
7 smaxT=smaxT(2)
8 disp(smaxT)
9
10
11 p=poly([1,-4,1],"w","coeff")
12 w=roots(p)
13 sf1=smaxT/w(1)

```

```
14 disp(sfl)
15
16 ratio=sqrt(((smaxT/sfl)^2+1)/(smaxT^2+1))
17 disp(ratio)
18
19 p=poly([1,-((smaxT/sfl)^2+1)*sfl,smaxT^2],"k","coeff"
    ")
20 k=roots(p)
21 k=k(2)
22 disp(k)
```

---

### Scilab code Exa 12.7 Problem7

```
1 V=440
2 ns=1000
3 ws=2*pi*ns/60
4 n=975
5 s=1-n/ns
6 Z=1.06+0.576/s+%i*(1.68+0.75)
7 I2=V/sqrt(3)/Z
8 Im=-%i*V/sqrt(3)/44.2
9 I1=Im+I2
10 pf=real(I1)/norm(I1)
11 Pin=sqrt(3)*V*norm(I1)*pf
12 Pout=norm(3*I2*I2*0.576*(1/s-1))-415
13 effi=Pout/Pin
14 Tnet=Pout/ws/(1-s)
15
16 disp(Tnet)
17 disp(Pin)
18 disp(norm(I1))
19 disp(pf)
20 disp(effi)
```

---

### Scilab code Exa 12.8 Problem8

```
1 V=400
2 P0=1210
3 I0=8.7
4 Ri=(V/sqrt(3))^2/P0*3
5 disp(Ri)
6 pf=P0/sqrt(3)/V/I0
7 theta0=acos(pf)
8 Xm=Ri/tan(theta0)
9 disp(Xm)
10
11 P1=6050
12 V1=200
13 I1=47.8
14 R=P1/3/I1/I1
15 R1=0.42
16 disp(R1)
17 R2=R-R1
18 disp(R2)
19 Z=V1/sqrt(3)/I1
20 X=sqrt(Z*Z-R*R)
21 disp(X)
22
23 ns=750
24 n=710
25 ws=ns*2*%pi/60
26 s=1-n/ns
27 Z=R1+R2/s+%i*X
28 I2=V/sqrt(3)/Z
29 I0=I0*exp(-%i*theta0)
30 I1=I0+I2
31 disp(norm(I1))
32 pf=real(I1)/norm(I1)
```

```

33 disp(pf)
34 T=norm(3*I2*I2*R2/s/ws)
35 disp(T)
36 Pout=T*ws*(1-s)
37 Pin=sqrt(3)*V*norm(I1)*pf
38 effi=Pout/Pin
39 disp(effi)
40
41 s=1
42 Z=R+%i*X
43 I2=V/sqrt(3)/Z
44 I1=I0+I2
45 disp(norm(I1))
46 Tstart=norm(3*I2*I2*R2/s/ws)
47 disp(Tstart)
48
49 smaxT=R2/sqrt(R1^2+X^2)
50 Z=R1+R2/smaxT+%i*X
51 I2=V/sqrt(3)/norm(Z)
52 Tmax=3*I2*I2*R2/smaxT/ws
53 disp(Tmax)
54 disp(smaxT)

```

---

### Scilab code Exa 12.9 Problem9

```

1 Is_by_Ifl=5
2 sfl=0.04
3 Ts_by_Tfl=Is_by_Ifl^2*sfl
4 disp("pu",Ts_by_Tfl)

```

---

### Scilab code Exa 12.10 Problem10

```
2 R2=0.5
3 X2=5
4 Tm_by_Tf1=3.5
5
6 Ts_by_Tf1=R2*Tm_by_Tf1*2*X2/(R2^2+X2^2)
7 disp(Ts_by_Tf1)
8
9 Ts_by_Tf12=Ts_by_Tf1/3
10 disp(Ts_by_Tf12)
11
12 Ts_by_Tf13=0.7*0.7*Ts_by_Tf1           // calculation
     mistake in the book at this point
13 disp(Ts_by_Tf13)
```

---

### Scilab code Exa 12.11 Problem11

```
1
2 s1=1-960/1000
3 s2=1-800/1000
4 R2ext=4/3*s2*0.25/s1-0.25
5 disp(R2ext)
```

---

### Scilab code Exa 12.12 Problem12

```
1
2 smaxT=1-860/1000
3 R2=0.25
4 X2=R2/smaxT
5 Tmax=180
6 k=Tmax*X2
7
8 s=0.045
```

```
9 T=2*100.6/((R2/s)^2+X2^2)*R2/s //some mistake in
   the book at this point. (What is V1/a)
10 T=105
11 disp(T)
12
13 R2ext=X2-R2
14 disp(R2ext)
```

---

### Scilab code Exa 12.13 Problem13

```
1 V=400
2 Poutmech=5000
3 Prl=285
4 Pm=Poutmech+Prl
5 s=1-1445/1500
6 s2=1-900/1500
7
8
9
10 p=poly([0,-(1-s)*V*V/Pm/s,1/s/s+1/s2/s2],"R2","coeff")
11 r=roots(p)
12 R2=r(1)
13 X2=R2/s2
14
15 ws=2*pi*1500/60
16 Tmax=3/ws*V*V/3*0.5/X2
17 disp(Tmax)
```

---

### Scilab code Exa 12.14 Problem14

```
1 Pmout=20000
2 Pwf1=1500
```

```
3 Pm=Pmout+Pwfl  
4 disp(Pm)  
5 ns=1500  
6 n=1440  
7 s=1-n/ns  
8 Pg=Pm/(1-s)  
9 disp(Pg)  
10 Pcu=s*Pg  
11 disp(Pcu)
```

---

### Scilab code Exa 12.15 Problem15

```
1 V1=400  
2 R1=2.28*3/2  
3 R1ac=1.1*3.42  
4  
5 Y0=3.5/sqrt(3)/V1  
6 Gi=(445/3)/V1/V1  
7 Bm=sqrt(Y0^2-Gi^2)  
8 Ri=1/Gi  
9 Xm=1/Bm  
10  
11 V2=200  
12 Z=V2/16.7*sqrt(3)  
13 R=2220/16.7/16.7  
14 X=sqrt(Z*Z-R*R)  
15 R2=R-R1ac  
16  
17 n=935  
18 ns=1000  
19 s=1-n/ns  
20 Z=R1ac+R2/s+%i*X  
21 I2=V1/Z  
22 Ii=V1/Ri-%i*V1/Xm  
23 I1=I2+Ii
```

```

24 Iline=norm(I1)*sqrt(3)
25 pf=real(I1)/norm(I1)
26 ws=2*pi*ns/60
27 T=norm(3*I2*I2*R2/s/ws)
28 disp(T)
29 disp(Iline)
30
31 Pm=norm(3*I2*I2*R2*(1-s)/s)
32 Pin=sqrt(3)*V1*Iline*pf
33 effi=Pm/Pin
34 disp(effi)
35
36 V=400
37 s=1
38 Z=R1ac+R2/s+%i*X
39 I2=V/sqrt(3)/Z      /////////////// calculation mistake in the
                         book at this step
40 Ts=norm(3*I2*I2*R2/ws)
41 disp(Ts)

```

---

### Scilab code Exa 12.16 Problem16

```

1 V=400
2 Pmout=5000
3 Prl=285
4 Pm=Pmout+Prl
5
6 s=1-1445/1500
7 smaxT=1-900/1500
8 R2=(1/s-1)*V*V/Pm/(1/s^2+1/smaxT^2)
9 X2=R2/smaxT
10 ws=2*pi*1500/60
11 Tmax=V*V/ws/2/X2
12 disp(Tmax)

```

---

### Scilab code Exa 12.17 Problem17

```
1 V=440
2 I=25
3 pf=0.85
4 Pin=sqrt(3)*V*I*pf
5 ns=1500
6 Pcore=750
7 Pcus=950
8 Pcur=450
9 Pwf1=250
10
11 Pg=Pin-Pcore-Pcus
12 disp(Pg)
13
14 Pm=Pg-Pcur
15 disp(Pm)
16
17 Pmout=Pm-Pwf1
18 disp(Pmout)
19
20 effi=Pmout/Pin
21 disp(effi)
22
23 s=Pcur/Pg
24 n=(1-s)*ns
25 disp(n)
26
27 w=2*%pi*n/60
28 Tdev=Pm/w
29 disp(Tdev)
30 Tnet=Pmout/w
31 disp(Tnet)
```

---

# Chapter 14

## Measurement Techniques and Electric and Electronic Instrumentation

Scilab code Exa 14.1 Problem1

```
1 Rv1=60/1000*10000
2 Rv2=120/1000*10000
3 Rx=(Rv2-Rv1)*(1/(27.5/30*2-1)-1)
4 I=27.5/1000/600*(Rx+600)/Rx
5 Vact=Rx*I
6 disp(Vact)
```

---

Scilab code Exa 14.2 Problem2

```
1
2 Ifsd=25/1000
3 Ix=4.975
4 Rx=Ifsd*5/Ix
5 disp(Rx)
```

```
6  
7 Rx=20/Ifsd-5  
8 disp(Rx)
```

---

#### Scilab code Exa 14.3 Problem3

```
1  
2 R1=40/0.025-5  
3 R2=60/0.025-5-R1  
4 disp(R1)  
5 disp(R2)
```

---

#### Scilab code Exa 14.4 Problem4

```
1  
2 W1=500  
3 W2=-200  
4 P=W1+W2  
5 phi=atan((W1-W2)/(W1+W2))  
6 pf=cos(phi)  
7 disp(pf)  
8 disp(P)
```

---

#### Scilab code Exa 14.5 Problem5

```
1  
2 E=4  
3 R1=800  
4 R2=80  
5 R3=1605
```

```

6 R4=160
7 Rg=80
8 s=8
9
10 Eth=E*(R2/(R2+R4)-R1/(R1+R3))
11 Rth=R1*R3/(R1+R3)+R2*R4/(R2+R4)
12 Ig=Eth/(Rth+Rg)
13 D=s*Ig*1000000
14 disp(D)

```

---

### Scilab code Exa 14.6 Problem6

```

1 function Zeq=parallel(Z1,Z2)
2     Zeq=Z1*Z2/(Z1+Z2)
3 endfunction
4
5 f=1000
6 w=2*%pi*f
7
8 //AB
9 R=2000
10 C=0.045E-6
11 Xc=1/%i/w/C
12 Z1=parallel(R,Xc)
13
14 ////BC
15 R=1000
16 C=0.45E-6
17 Xc=1/%i/w/C
18 Z2=R+Xc
19
20 ////AD
21 C=0.4E-6
22 Z3=1/%i/w/C
23

```

```
24 Z4=Z2*Z3/Z1  
25 disp(Z4)
```

---

### Scilab code Exa 14.7 Problem7

```
1  
2 ksine=1.11  
3 ksqr=1  
4  
5 err=(ksine-ksqr)/ksqr*100  
6 disp(" percent",err)
```

---

### Scilab code Exa 14.8 Problem8

```
1  
2 f=50E6  
3 w=2*%pi*f  
4 theta=5*%pi/180  
5  
6  
7 C=1E-12  
8 R=1/theta/w/C  
9 disp(R)  
10  
11 C=10E-12  
12 R=1/theta/w/C  
13 disp(R)  
14  
15 C=100E-12  
16 R=1/theta/w/C  
17 disp(R)
```

---

### **Scilab code Exa 14.9 Problem9**

```
1
2 f=8E6
3 w=2*%pi*f
4 C=150E-12
5 R=5
6
7 Q1=1/w/C/R
8
9 Rins=0.1
10 Q2=1/w/C/(R+Rins)
11 err=(Q1-Q2)/Q1*100
12 disp(err)
```

---

### **Scilab code Exa 14.10 Problem10**

```
1 f=100E3
2 w=2*%pi*f
3 C=400E-12
4
5 L=1/C/w/w
6 disp(L)
```

---

### **Scilab code Exa 14.11 Problem11**

```
1
2 Resolution=1/10^4
3 disp(Resolution)
```

```
4
5 disp("14.760")
6
7 R_1V=1*Resolution
8 disp("0.5434") //since any digits upto 4th decimal
      can be shown
9
10 R_10V=10*Resolution
11 disp("00.543") //since only three decimal digits
      can be shown
```

---

### Scilab code Exa 14.12 Problem12

```
1
2 Vp=10
3 Vref=5
4 R=100000
5 C=0.22E-6
6 T=Vp*R*C/Vref
7 disp(T)
```

---

### Scilab code Exa 14.13 Problem13

```
1
2 V=3.217
3 bits=4
4 base=5
5 a=0
6
7 for i=1:bits
8     a=floor(V/base*(2^i))
9     disp(a);
10    V=V-a*base/(2^i)
```

```
11 end
```

---

### Scilab code Exa 14.14 Problem14

```
1
2 reading=5
3 x=0.005/100*reading      //0.005% of reading
4 err=x+1E-6      //final digit
5 disp("seconds",err)
6
7 reading=500
8 x=0.005/100*reading      //0.005% of reading
9 err=x+1      //final digit
10 disp("seconds",err)
```

---

### Scilab code Exa 14.15 Problem15

```
1 V=5.9
2 Rx=0
3 Rm=2000
4 R1=49000
5 Ifsd=100E-6
6 Vam=Rm*Ifsd
7 I=(V-Vam)/R1
8 Ish=I-Ifsd
9 R2=Vam/Ish
10 disp(R2)
11
12 I=0.6*I
13 Req=V/I
14 Rx=Req-R1-Rm*R2/(R2+Rm)
15 disp(Rx)
```

---

### Scilab code Exa 14.17 Problem17

```
1 f=50
2 w=2*%pi*f
3
4 Z2=1000
5 Z3=16800
6
7 C=0.38E-6
8 Xc=1/%i/w/C
9 Z4=833+Xc
10
11 Z1=Z2*Z3/Z4
12 Rx=real(Z1)
13 Lx=imag(Z1)/w
14
15 disp(Rx)
16 disp(Lx)
```

---

### Scilab code Exa 14.18 Problem18

```
1 f=50
2 w=2*%pi*f
3 T=1/f
4
5 Iav=1/(T/2)*integrate('sin(w*t)', 't', 0, T/2)
6 disp(Iav)
```

---

# Chapter 15

## Power Systems

Scilab code Exa 15.1 Problem1

```
1 V1=250
2 V2=480
3 Vol2_by_Vol1=V1/V2
4
5 sav=(1-Vol2_by_Vol1)*100
6 disp(sav)
```

---

Scilab code Exa 15.2 Problem2

```
1 P=5E6
2 pf=0.85
3 V=33000
4 l=50000
5 rho=3E-8
6 Pt=P*pf
7 P1=Pt*0.1
8 I=P/V
9 A1=2*I*I*rho*l/P1
```

```
10 Vol1=2*l*A1
11 disp(Vol1)
12
13 I1=P/sqrt(3)/V
14 A2=3*I1*I1*rho*l/P1
15 Vol2=3*l*A2
16 disp(Vol2)
```

---

### Scilab code Exa 15.3 Problem3

```
1 f=50
2 w=2*%pi*f
3 I=0.8
4 V=220
5 P=75
6 phi=acos(P/V/I)
7
8 phi_new=acos(0.9)
9 Ic=I*cos(phi)*(tan(phi)-tan(phi_new))
10 C=Ic/V/w
11 disp(C)
12
13 phi_new=acos(1)
14 Ic=I*cos(phi)*(tan(phi)-tan(phi_new))
15 C=Ic/V/w
16 disp(C)
```

---

### Scilab code Exa 15.4 Problem4

```
1 Cond_cost=100
2 charge=60
3 phi2=asin(0.1*Cond_cost/charge)
4 pf=cos(phi2)
```

```
5 disp(pf)
```

---

### Scilab code Exa 15.5 Problem5

```
1
2 0c=400000
3 pf1=0.8
4 phi1=acos(pf1)
5 ab=0c/cos(phi1)*sin(phi1)
6 pf2=0.25
7 phi3=acos(pf2)
8 pf2=0.484
9
10 gammaa=(ab-pf2*0c)/(pf2*cos(phi3)+sin(phi3))
11 disp(gammaa)
```

---

### Scilab code Exa 15.6 Problem6

```
1 f=50
2 w=2*pi*f
3 P=2E6
4 V=11000
5 pf=0.8
6 phi=acos(pf)
7 Xl=10
8 IR=P/sqrt(3)/V/pf
9 Vr=V/sqrt(3)
10 Vs=Vr+IR*Xl*sin(phi)
11 Vsll=Vs*sqrt(3)
12 disp(Vsll)
13 VR=Vsll/V-1
14 disp(VR)
15
```

```

16 pf=1
17 disp(pf)
18 Qc=P*tan(phi)
19 C=Qc/V/V/w
20 disp(C)

```

---

### Scilab code Exa 15.7 Problem7

```

1 f=50
2 w=2*%pi*f
3 V=33000
4 Vr=V/sqrt(3)
5 P=24E6/3
6 pf=0.8
7 phi=acos(pf)
8 Ia=P/Vr/pf
9 Rl=4
10 Xl=20
11 Vs=Vr+Ia*(Xl*sin(phi)+Rl*cos(phi))
12 Vsll=sqrt(3)*Vs
13 VR=Vsll/V-1
14 disp(Vsll)
15 Ia=Ia*exp(-%i*phi)
16 disp(norm(Ia))
17
18 phi1=atan(-Rl/Xl)
19 pf=cos(phi1)
20 Ia1=P/Vr/pf
21 Ia1=Ia1*exp(-%i*phi1)      //calculation mistake
in the book at this step
22
23 Ic=Ia1-Ia
24 C=norm(Ic/w/Vr)
25 disp(C)
26

```

```
27 LL1=norm(Ia*Ia*R1)
28 effi1=P/(P+LL1)
29 LL2=norm(Ia1*Ia1*R1)
30 effi2=P/(P+LL2)
31 disp(effi1)
32 disp(effi2)
```

---