

Scilab Textbook Companion for  
Electronic Measurements And Instrumentation  
by P. Sharma<sup>1</sup>

Created by  
Priya Bardhan Kumar  
B.Tech  
Electrical Engineering  
College of engineering Roorkee  
College Teacher  
Rahul Ranjan  
Cross-Checked by  
Madhu N.belur

May 23, 2016

<sup>1</sup>Funded by a grant from the National Mission on Education through ICT, <http://spoken-tutorial.org/NMEICT-Intro>. This Textbook Companion and Scilab codes written in it can be downloaded from the "Textbook Companion Project" section at the website <http://scilab.in>

# Book Description

**Title:** Electronic Measurements And Instrumentation

**Author:** P. Sharma

**Publisher:** Umesh Publications, New Delhi

**Edition:** 3

**Year:** 2008

**ISBN:** 8188114715

Scilab numbering policy used in this document and the relation to the above book.

**Exa** Example (Solved example)

**Eqn** Equation (Particular equation of the above book)

**AP** Appendix to Example(Scilab Code that is an Appednix to a particular Example of the above book)

For example, Exa 3.51 means solved example 3.51 of this book. Sec 2.3 means a scilab code whose theory is explained in Section 2.3 of the book.

# Contents

List of Scilab Codes	4
1 Measurement measurement units and standards and standards	5
2 Errors and their analysis	7
3 Transducers	21
4 Bridge measurement	27
5 Analog meters	37
6 data converters	48
7 Display devices and digital systems	55
8 cathode ray oscilloscope	61

# List of Scilab Codes

Exa 1.3	find system accuracy system precision . . . . .	5
Exa 1.5	Find resolution of the meter . . . . .	6
Exa 2.1	Find maximum and minimum value of resistor . . . . .	7
Exa 2.2	Find limiting error in percentage . . . . .	7
Exa 2.3	Find unknown resistance relative limiting error in percentage and in ohms . . . . .	8
Exa 2.4	Find limiting error . . . . .	9
Exa 2.5	Find magnitude of limiting error fot R1 and R2 . . . . .	9
Exa 2.6	Find error in computed value of power dissipation . . . . .	10
Exa 2.7	find the limiting error for the power calculated . . . . .	11
Exa 2.8	Find limiting error . . . . .	11
Exa 2.9	Find limiting error when measured voltage is a V1 b V2 . . . . .	12
Exa 2.10	Find volume percentage error and absolute error . . . . .	13
Exa 2.11	Find unknown resistance percent error and error in ohm . . . . .	13
Exa 2.12	Find arithmetic mean . . . . .	14
Exa 2.13	Find deviation . . . . .	15
Exa 2.14	Find deviation . . . . .	16
Exa 2.15	find arithmetic mean standard deviation and probable error of onereading . . . . .	17
Exa 2.16	Find a arithmetic mean b deviation of each value c algebraic sum of deviation d average deviation e standard deviation . . . . .	18
Exa 2.17	find a arithmetic mean b deviation from mean c average deviation d standard deviation e variance f probable reading of one error . . . . .	19
Exa 3.2	Find change in resistance . . . . .	21
Exa 3.3	Find output voltage of an ac LVDT for a minus point 3 inch b minus point 25 inch . . . . .	21

Exa 3.4	Find sensitivity of LVDT . . . . .	22
Exa 3.5	Find output voltage . . . . .	23
Exa 3.6	Find a Sensitivity of LVDT b sensitivity of entire setup c resolution of the instrument . . . . .	23
Exa 3.7	Find value of capacitance after application of pressure	24
Exa 3.8	Find thermoelectric sensitivity and emf developed . .	25
Exa 3.9	Find value of protection resistance . . . . .	25
Exa 4.1	Find value of unknown resistance and fractional uncer- tainty in its value . . . . .	27
Exa 4.2	Find output voltage . . . . .	28
Exa 4.3	Find temperature at which thevenin voltage is 50mV .	28
Exa 4.4	Find deflection of the galvenometer . . . . .	29
Exa 4.5	Find limiting value of unknown resistance . . . . .	30
Exa 4.6	Find magnitude and phase angle of Z4 arm . . . . .	31
Exa 4.7	find value of unknown inductance resistance and Q for maxwell bridge . . . . .	31
Exa 4.8	find relative permittivity of specimen . . . . .	32
Exa 4.9	Find equivalent parallel resistance and capacitance . .	33
Exa 4.10	find value of arm CD . . . . .	34
Exa 4.11	find value of arm CD . . . . .	34
Exa 4.12	find value of arm AD . . . . .	35
Exa 4.13	find value of frequency of the bridge arm resistance of arm AD . . . . .	36
Exa 5.1	Find terminal voltage when load impedance is a 10 ohm b 20 ohm c 40 ohm . . . . .	37
Exa 5.2	Find load current when variable load are a 100 ohm b10 ohm . . . . .	38
Exa 5.3	Find equivalent voltage source of the ac current source	38
Exa 5.4	Find equivalent current source . . . . .	39
Exa 5.5	Find value of shunt resistance for ammeter . . . . .	39
Exa 5.6	Find value of shunt resistance for the range a 0 to 1A b 0 to 5A c 0 to 10A . . . . .	40
Exa 5.8	Find the value of multiplier resistance for the range a 0 to 10V b 0 to 50V c 0 to 100V d 0 to 200V . . . . .	41
Exa 5.9	Find the value of multiplier resistance for the range a 0 to 10V b 0 to 50V c 0 to 100V d 0 to 200V using sensitivity method . . . . .	42

Exa 5.10	Find reading of voltmeter and percentage error when a sensitivity of voltmeter is 100 kilo ohm per volt b sensitivity of voltmeter is 500 kilo ohm per volt . . . . .	43
Exa 5.11	Find a value of R1 and R2 b change in value of R2 c half scale deflection . . . . .	44
Exa 5.12	Find R1 and Rsh . . . . .	44
Exa 5.13	Find value of required multiplier resistance . . . . .	45
Exa 5.14	Find value of multiplier resistance . . . . .	46
Exa 5.15	Find value of multiplier resistance . . . . .	46
Exa 6.1	Find output voltage for a binary input a 1111 b 1100 .	48
Exa 6.2	Find output voltage . . . . .	49
Exa 6.3	Find output voltage if input is 101101111 . . . . .	49
Exa 6.4	Find values of a LSB b MSB c full scale output . . . . .	50
Exa 6.5	Find resolution and voltage . . . . .	50
Exa 6.6	Find conversion time required for inverter . . . . .	51
Exa 6.9	Find total number of pulses and display reading . . . . .	52
Exa 6.10	Find input voltage . . . . .	52
Exa 6.11	Find a output voltage after 1 sec b fall time of reference voltage waveform . . . . .	53
Exa 7.1	convert 1101 into decimal . . . . .	55
Exa 7.2	convert 17 octal into decimal . . . . .	55
Exa 7.3	convert 1E hexadecimal into decimal . . . . .	56
Exa 7.20	Find input frequency applied to the system . . . . .	56
Exa 7.21	find frequency of the system . . . . .	57
Exa 7.22	find frequency time period of the system . . . . .	57
Exa 7.23	Find a resolution of the voltmeter b display of point 6368 in voltmeter on the 10V range c display of point 6368 in voltmeter on the 1V range . . . . .	58
Exa 7.24	Find a resolution of the voltmeter b display of 16 point 58 in voltmeter on the 10V range c display of point 7254 in voltmeter on the 1V and 10V range . . . . .	59
Exa 7.25	find out range of measured reading . . . . .	60
Exa 8.1	find deflection sensitivity of CRO . . . . .	61
Exa 8.2	Find peak to peak amplitude of the signal and frequency of the signal . . . . .	61
Exa 8.3	Find amplitude of the waveform . . . . .	62
Exa 8.4	Find rms value of signal under test . . . . .	63
Exa 8.5	Find value of current . . . . .	63

Exa 8.6	Find value of current . . . . .	64
Exa 8.7	Find peak amplitude and frequency of the signal . . . .	64
Exa 8.8	Find frequency of horizontal signal . . . . .	65
Exa 8.9	Find frequency of the waveform . . . . .	66
Exa 8.10	what will be the setting of time base knob . . . . .	66
Exa 8.11	Find ratio of frequencies of vertical and horizontal signals	67
Exa 8.12	find phase angle . . . . .	68
Exa 8.13	Find bandwidth of CRO . . . . .	68



# Chapter 1

## Measurement measurement units and standards and standards

Scilab code Exa 1.3 find system accuracy system precision

```
1 //caption:find (a)system accuracy(b)system precision
2 //Ex1.3
3 clc
4 clear
5 close
6 Tmin=100.3//minimum measured temperature at true
   value(in degree centigrate)
7 Tmax=100.5//maximum measured temperature at true
   value(in degree centigrate)
8 T1=100.4//measured temperature at true value(in
   degree centigrate)
9 T2=100.3//measured temperature at true value(in
   degree centigrate)
10 Tt=100//true value(in degree centigrate)
11 A=((Tmax-Tt)/Tt)*100
12 disp(A, '(a)system accuracy (in %)=')
13 M=(T1+Tmin+Tmax+T2)/4
```

```
14 Md=Tmax-M
15 disp(Md, '(b)system precision (in %)=')
```

---

**Scilab code Exa 1.5** Find resolution of the meter

```
1 //caption:Find resolution of the meter
2 //Ex1.5
3 clc
4 clear
5 close
6 Rmax=100//maximum range of voltmeter(in V)
7 D=200//division on scale
8 Sd=0.5//divisions which can be read
9 V=Rmax/D
10 R=Sd*V
11 disp(R, 'resolution of the meter is (in V)=')
```

---

## Chapter 2

# Errors and their analysis

Scilab code Exa 2.1 Find maximum and minimum value of resistor

```
1 //caption:Find maximum and minimum value of resistor
2 //Ex2.1
3 clc
4 clear
5 close
6 R=100//magnitude of resistor(in ohm)
7 Lmin=-5//minimum limiting error(in %)
8 Lmax=5//maximum limiting error(in %)
9 Le=(R*Lmax)/100
10 Rmax=R+Le
11 disp(Rmax,'maximum value of resistor(in ohm)=')
12 Rmin=R-Le
13 disp(Rmin,'minimum value of resistor(in ohm)=')
```

---

Scilab code Exa 2.2 Find limiting error in percentage

```

1 //caption:Find limiting error in percentage
2 //Ex2.2
3 clc
4 clear
5 close
6 V=150//maximum range of voltmeter(in V)
7 A=0.02//magnitude of accuracy(in V)
8 Vm=83//voltage measured
9 dA=A*V
10 %er=(dA/Vm)*100
11 disp(%er, 'limiting error(in %)=')

```

---

**Scilab code Exa 2.3** Find unknown resistance relative limiting error in percentage and in ohms

```

1 //caption:Find unknown resistance ,relative limiting
  error in percentage and in ohms
2 //Ex2.3
3 clc
4 clear
5 close
6 R1=90//resistance of arm wheatstone bridge(in ohm)
7 R1e1=0.5//limiting error for R1(in %)
8 R2=900//resistance of arm wheatstone bridge(in ohm)
9 R1e2=0.8//limiting error for R2(in %)
10 R3=825//resistance of arm wheatstone bridge(in ohm)
11 R1e3=0.6//limiting error for R3(in %)
12 Rx=(R2*R3)/R1
13 disp(Rx, 'unknown resistance(in ohm)=')
14 dR1=(R1*R1e1)/100
15 dR2=(R2*R1e2)/100

```

```

16 dR3=(R3*R1e3)/100
17 dR=((dR2/R2)+(dR3/R3)+(dR1/R1))*100
18 disp(dR,'relative limiting error(in %)=')
19 Le=(dR*Rx)/100
20 disp(Le,'limiting error(in ohm)=')

```

---

**Scilab code Exa 2.4** Find limiting error

```

1 //caption:Find limiting error
2 //Ex2.4
3 clc
4 clear
5 close
6 V1=500//referance reading of voltmeter(in V)
7 V2=150//Voltage at which limiting error to be
   calculated(in V)
8 Ar=0.015//magnitude of accuracy limit
9 dA=Ar*V1
10 er=(dA/V2)*100
11 disp(er,'limiting error(in %)=')

```

---

**Scilab code Exa 2.5** Find magnitude of limiting error fot R1 and R2

```

1 //caption:Find magnitude of limiting error fot R1
   and R2

```

```

2 //Ex2.5
3 clc
4 clear
5 close
6 R1=36//resistance(in ohm)
7 R2=75//resistance(in ohm)
8 er=0.005//limiting error(in ohm)
9 dR1=R1*er
10 disp(dR1,'magnitude of limiting error for R1(in ohm)
    =')
11 dR2=R2*er
12 disp(dR2,'magnitude of limiting error for R2(in ohm)
    =')

```

---

**Scilab code Exa 2.6** Find error in computed value of power dissipation

```

1 //caption:Find error in computed value of power
    dissipation
2 //Ex2.6
3 clc
4 clear
5 close
6 R=100//resistor(in ohm)
7 Rer=0.2//error in current measurment(in ohm)
8 I=2//current(in A)
9 Ier=0.01//error in current measurment(in ohm)
10 dR=(Rer/R)*100
11 dI=(Ier/I)*100
12 P=(I^2)*R
13 dPo=2*dI+dR
14 dP=(P*dPo)/100

```

```
15 disp(dP, 'error in computed value of power
    dissipation (in W)=')
```

---

**Scilab code Exa 2.7** find the limiting error for the power calculated

```
1 //caption:find the limiting error for the power
  calculated
2 //Ex2.7
3 clc
4 clear
5 close
6 A=0.01//magnitude of accuracy
7 V=150//range of voltmeter(in V)
8 Vr=100//Reading of voltmeter(in V)
9 I=100//range of ammeter(in mA)
10 Ir=55//ammeter reading(in mA)
11 dV=A*V
12 dEv=(dV/Vr)*100
13 dA=A*I
14 dEi=(dA/Ir)*100
15 dE=(dEv+dEi)
16 disp(dE, 'limiting error for the power calculated(in
    %)=')
```

---

**Scilab code Exa 2.8** Find limiting error

```

1 //caption:Find limiting error
2 //Ex2.8
3 clc
4 clear
5 close
6 dP=1.5//limiting error in power(in %)
7 dI=1//limiting error in current(in %)
8 dR=(dP+2*dI)
9 disp(dR,'limiting error(in %)=')

```

---

**Scilab code Exa 2.9** Find limiting error when measured voltage is a V1 b V2

```

1 //caption:Find limiting error when measured voltage
  is (a)V1(b)V2
2 //Ex2.9
3 clc
4 clear
5 close
6 Ar=0.01//magnitude of accuracy(in V)
7 V1=50//measured voltage(in V)
8 V2=25//measured voltage(in V)
9 Vmax=100//maximum range of voltage
10 dA=Ar*Vmax
11 er1=(dA/V1)*100
12 disp(er1,'limiting error when measured voltage is V1
  (in %)=')
13 er2=(dA/V2)*100
14 disp(er2,'limiting error when measured voltage is V2
  (in %)=')

```

---



**Scilab code Exa 2.10** Find volume percentage error and absolute error

```
1 //caption:Find volume,percentage error and absolute
  error
2 //Ex2.10
3 clc
4 clear
5 close
6 a=0.80//side of the cube(in m)
7 er=0.5//possible error in measurement(in %)
8 V=(a*a*a)
9 disp(V, 'volume(in meter ^3)=')
10 %er=3*er
11 disp(%er, 'percentage error(in %)=')
12 Aer=(%er*V)/100
13 disp(Aer, 'absolute error(in meter ^3)=')
```

---

**Scilab code Exa 2.11** Find unknown resistance percent error and error in ohm

```
1 //caption:Find unknown resistance ,percent error and
  error in ohm
2 //Ex2.11
3 clc
```

```

4 clear
5 close
6 P=100//resistance of arm of wheatstone bridge(in ohm
   )
7 ep=0.5//error in P(in %)
8 Q=50//resistance of arm of wheatstone bridge(in ohm)
9 eq=0.5//error in Q(in %)
10 S=75.5//resistance of arm of wheatstone bridge(in
    ohm)
11 es=0.5//error in S(in %)
12 X=(P*S)/Q
13 disp(X,'unknown resistance (in ohm)=')
14 xo1=ep+es-eq
15 disp(xo1,'percent error when Q is taken positive(in
    %)=')
16 ex1=(xo1*X)/100
17 disp(ex1,'error in ohm(in ohm)=')
18 xo2=ep+es+eq
19 disp(xo2,'percent error when Q is taken negative(in
    %)=')
20 ex2=(xo2*X)/100
21 disp(ex2,'error in ohm(in ohm)=')

```

---

**Scilab code Exa 2.12** Find arithmetic mean

```

1 //caption:Find arithmetic mean
2 //Ex2.12
3 clc
4 clear
5 close
6 x1=25.65//first reading(in W)

```

```
7 x2=24.39//second reading(in W)
8 x3=23.75//third reading(in W)
9 x4=26.42//fourth reading(in W)
10 x5=24.92//fifth reading(in W)
11 X=(x1+x2+x3+x4+x5)/5
12 disp(X, 'arithmetic mean(in W)=')
```

---

#### Scilab code Exa 2.13 Find deviation

```
1 //caption:Find deviation
2 //Ex2.13
3 clc
4 clear
5 close
6 x1=25.65//first reading(in W)
7 x2=24.39//second reading(in W)
8 x3=23.75//third reading(in W)
9 x4=26.42//fourth reading(in W)
10 x5=24.92//fifth reading(in W)
11 X=(x1+x2+x3+x4+x5)/5
12 d1=x1-X
13 disp(d1, 'deviation=')
14 d2=x2-X
15 disp(d2, 'deviation=')
16 d3=x3-X
17 disp(d3, 'deviation=')
18 d4=x4-X
19 disp(d4, 'deviation=')
20 d5=x5-X
21 disp(d5, 'deviation=')
```

---

**Scilab code Exa 2.14** Find deviation

```
1 //caption:Find deviation
2 //Ex2.14
3 clc
4 clear
5 close
6 x1=25.65//first reading(in W)
7 x2=24.39//second reading(in W)
8 x3=23.75//third reading(in W)
9 x4=26.42//fourth reading(in W)
10 x5=24.92//fifth reading(in W)
11 n=5//number of readings
12 X=(x1+x2+x3+x4+x5)/5
13 d1=x1-X
14 d2=x2-X
15 d3=x3-X
16 d4=x4-X
17 d5=x5-X
18 D1=d1//mod of d1
19 D2=-(d2)//mod of d2
20 D3=-(d3)//mod of d3
21 D4=d4//mod of d4
22 D5=-(d5)//mod of d5
23 D=(D1+D2+D3+D4+D5)/n
24 disp(D, 'deviation(in W)=')
```

---

**Scilab code Exa 2.15** find arithmetic mean standard deviation and probable error of onereading

```
1 //caption:find arithmetic mean,standard deviation
   and probable error of onereading
2 //Ex2.15
3 clc
4 clear
5 close
6 x1=30.30//level of liquid(in mm)
7 x2=30.25//level of liquid(in mm)
8 x3=30.40//level of liquid(in mm)
9 x4=30.00//level of liquid(in mm)
10 n=4//numberof readings
11 x=(x1+x2+x3+x4)/n
12 disp(x,'arithmatic mean(in mm)=')
13 d1=x1-x
14 d2=x2-x
15 d3=x3-x
16 d4=x4-x
17 S=((d1^2+d2^2+d3^2+d4^2)/(n-1))^0.5
18 disp(S,'standard deviation(in mm)=')
19 P=0.6745*S
20 disp(P,'probable error(in mm)=')
```

---

**Scilab code Exa 2.16** Find a arithmetic mean b deviation of each value c  
algebraic sum of deviation d average deviation e standard deviation

```
1 //caption:Find(a) arithmetic mean(b) deviation of each
    value(c) algebraic sum of deviation(d) average
    deviation(e) standard deviation
2 //Ex2.16
3 clc
4 clear
5 close
6 x1=10//first reading
7 x2=11//second reading
8 x3=9//third reading
9 x4=10.5//fourth reading
10 x5=9.5//fifth reading
11 n=5//number of reading
12 x=(x1+x2+x3+x4+x5)/n
13 disp(x, '(a) arithmetic mean=')
14 d1=x1-x
15 d2=x2-x
16 d3=x3-x
17 d4=x4-x
18 d5=x5-x
19 disp(d5,d4,d3,d2,d1, '(b) value of deviation=')
20 d=d1+d2+d3+d4+d5
21 disp(d, '(c) algebraic sum of deviation=')
22 D=((d1)+(d2)+(-d3)+(d4)+(-d5))/n//taking mod of
    deviation value
23 disp(D, '(d) average deviation=')
24 S=((d1^2+d2^2+d3^2+d4^2+d5^2)/(n-1))^(0.5)
```

25 `disp(S, '(e) standard deviation=')`

---

**Scilab code Exa 2.17** find a arithmetic mean b deviation from mean c average deviation d standard deviation e variance f probable reading of one error

```
1 //caption:find (a) arithmetic mean(b) deviation from
   mean(c) average deviation(d) standard deviation(e)
   variance(f) probable reading of one error
2 //Ex2.17
3 clc
4 clear
5 close
6 x1=12.8//first reading(in V)
7 x2=12.2//second reading(in V)
8 x3=12.5//third reading(in V)
9 x4=13.1//fourth reading(in V)
10 x5=12.9//fifth reading(in V)
11 x6=12.4//sixth value(in V)
12 n=6//number of reading
13 x=(x1+x2+x3+x4+x5+x6)/n
14 disp(x, '(a) arithmetic mean(in V)=')
15 d1=x1-x
16 d2=x2-x
17 d3=x3-x
18 d4=x4-x
19 d5=x5-x
20 d6=x6-x
21 disp(d6,d5,d4,d3,d2,d1, '(b) value of deviation(in V)=
   ' )
22 D=((d1)+(-d2)+(-d3)+(d4)+(d5)+(-d6))/n//taking mod
```

```
    of deviation value
23 disp(D, '(c) average deviation=')
24 S=((d1^2+d2^2+d3^2+d4^2+d5^2)/(n-1))^(0.5)
25 disp(S, '(d) standard deviation (in V)=')
26 V=S^2
27 disp(V, '(e) variance (in V)=')
28 P=0.6745*V
29 disp(P, '(f) probable error of one reading (in V)=')
```

---



# Chapter 3

## Transducers

**Scilab code Exa 3.2** Find change in resistance

```
1 //caption:Find change in resistance
2 //Ex3.2
3 clc
4 clear
5 close
6 G=2//gauge factor
7 S=500//stress applied(in Kg/cm^2)
8 v=2*10^6//modulus of elasticity(in Kg/cm^2)
9 e=(S/v)
10 R=(e*G)*100
11 disp(R,'change in resistance(in %)=')
```

---

**Scilab code Exa 3.3** Find output voltage of an ac LVDT for a minus point 3 inch b minus point 25 inch

```

1 //caption:Find output voltage of an ac LVDT for (a)
  -0.3 inch(b) -0.25 inch
2 //Ex3.3
3 clc
4 clear
5 close
6 R=-0.5//range of core displacement(in inch)
7 V=-5.2//output voltage(in V)
8 D1=-0.3//displacement(in inch)
9 D2=-0.25//displacement(in inch)
10 V1=(D1/R)*V
11 disp(V1, '(a)output voltage at -0.3 inch(in V)=')
12 V2=(D2/R)*V
13 disp(V2, '(b)output voltage at -0.25 inch(in V)=')
```

---

**Scilab code Exa 3.4** Find sensitivity of LVDT

```

1 //caption:Find sensitivity of LVDT
2 //Ex3.4
3 clc
4 clear
5 close
6 R=1.2//rms value of output voltage(in V)
7 d=0.6//displacement(in micro meter)
8 S=(R/d)
9 disp(S, 'sensitivity of LVDT(in volt per micro meter)
  =')
```

---

**Scilab code Exa 3.5** Find output voltage

```
1 //caption:Find output voltage
2 //Ex3.5
3 clc
4 clear
5 close
6 V=5//secondary voltage(in V)
7 d=10//displacement(in mm)
8 D=8//displcement at which output voltage to be
   calculated(in mm)
9 S=(V/d)
10 O=S*D
11 disp(0, 'output voltag(in V)=')
```

---

**Scilab code Exa 3.6** Find a Sensitivity of LVDT b sensitivity of entire setup c resolution of the instrument

```
1 //caption:Find (a)Sensitivity of LVDT(b)sensitivity
   of entire setup(c)resolution of the instrument
2 //Ex3.6
3 clc
4 clear
5 close
```

```

6 V=5//LVDT connection voltage(in V)
7 Vo=2//output voltage of LVDT(in mV)
8 D=0.5//displacement(in mm)
9 A=250//amplification factor
10 Do=100//divisions of scale
11 Ds=0.2//reading capacity of LVDT division
12 S=Vo/D
13 disp(S, '(a) sensitivity of LVDT(in mV/mm)=')
14 So=A*S
15 disp(So, '(b) sensitivity of entire setup(in mV/mm)=')
16 C=V/Do
17 M=Ds*C
18 R=M/S
19 disp(R, '(c) resolution of the instrument(in mm)=')

```

---

**Scilab code Exa 3.7** Find value of capacitance after application of pressure

```

1 //caption:Find value of capacitance after
  application of pressure
2 //Ex3.7
3 clc
4 clear
5 close
6 A=600*10^-6//area of plates(in meter square)
7 D=2.5*10^-3//separation of distance(in meter)
8 C=400*10^-12//capacitance(in F)
9 Do=0.5*10^-3//deflection(in mm)
10 e=(C*D)/A
11 d=D-Do
12 Co=(e*A)/d

```

```
13 disp(Co, 'capacitance(in F)=')
```

---

**Scilab code Exa 3.8** Find thermoelectric sensitivity and emf developed

```
1 //caption:Find thermoelectric sensitivity and emf
  developed
2 //Ex3.8
3 clc
4 clear
5 close
6 T=50//temperature difference(in degree centigrate)
7 Scp=7.4*10^-6//sensitivity of copper against
  platinum(in Voli per degree centigrate)
8 Sccp=-34.8*10^-6//sensitivity of constantan against
  platinum(in Voli per degree centigrate)
9 Sccc=(Scp)-(Sccp)
10 disp(Sccc, 'sensitivity(in Volt per degree centigrate
  )=')
11 E=Sccc*T
12 disp(E, 'emf developed(in V)=')
```

---

**Scilab code Exa 3.9** Find value of protection resistance

```
1 //caption:Find value of protection resistance
2 //Ex3.9
```

```
3 clc
4 clear
5 close
6 I=0.01//current through LDR(in A)
7 R=15//Resistance of LDR(in ohms)
8 V=9//supply voltage(in V)
9 Vo=I*R
10 Vp=V-Vo
11 R=Vp/I
12 disp(R, 'value of protection resistance(in ohm)=')
```

---

# Chapter 4

## Bridge measurement

**Scilab code Exa 4.1** Find value of unknown resistance and fractional uncertainty in its value

```
1 //caption:Find value of unknown resistance and
   fractional uncertainty in its value
2 //Ex4.1
3 clc
4 clear
5 close
6 R1=500//resistance of first arm of wheatstone bridge
   (in ohm)
7 dR1=0.5//uncertainty of first arm (in ohm)
8 R2=1000//resistance of arm of wheatstone bridge(in
   ohm)
9 dR2=0.5//uncertainty of second arm(in ohm)
10 R3=600//resistance of third arm of wheatstone bridge
   (in ohm)
11 dR3=0.5//uncertainty of third arm(in ohm)
12 R4=(R2*R3)/R1
13 disp(R4, 'unknown resistance (in ohm)=')
14 d4=((dR1/R1)^2+(dR2/R2)^2+(dR3/R3)^2)^1/2
```

```
15 dR4=R4*d4
16 disp(dR4, 'fractional uncertainty (in ohm)=')
```

---

**Scilab code Exa 4.2** Find output voltage

```
1 //caption:Find output voltage
2 //Ex4.2
3 clc
4 clear
5 close
6 R1=1000//resistance of first arm(in ohm)
7 R2=1000//resistance of second arm(in ohm)
8 R3=1000////resistance of third arm(in ohm)
9 V=10//applied voltage(in V)
10 T=20//temperature of thermometer(in degree
    centigrade)
11 Ro=1020//resistance of thermometer(in ohm)
12 V1=(R2/(R1+R3))*V
13 V2=(Ro/(R2+Ro))*V
14 Vo=V2-V1
15 disp(Vo, 'output voltage (in V)=')
```

---

**Scilab code Exa 4.3** Find temperature at which thevenin voltage is 50mV

```
1 //caption:Find temperature at which thevenin voltage
    is 50mV
2 //Ex4.3
```



```

3  clc
4  clear
5  close
6  R=1000//resistance of all the arms ofwheatstone
    bridge(in ohm)
7  a=10//temperature coefficient of thermistor(in ohm/
    degree centigrade)
8  Eth=0.05//thevenin voltage(in V)
9  V=20//input voltage(in V)
10 T=50//temperature(in degree centigrade)
11 Ro=1000//resistance of thermometer(in ohm)
12 dR=(Eth*4*R)/V
13 To=T-1
14 disp(To,'temperature at which thevenin voltage is 50
    mV(in degree centigrade)=')

```

---

#### Scilab code Exa 4.4 Find deflection of the galvenometer

```

1  //caption:Find deflection of the galvenometer
2  //Ex4.4
3  clc
4  clear
5  close
6  R1=80//resistance of first arm(in ohm)
7  R2=800//resistance of second arm(in ohm)
8  R3=160//resistance of third arm(in ohm)
9  R4=1605//resistance of fourth arm(in ohm)
10 E=4//battery voltage(in V)
11 S=8//galvenometer sensitivity(in milimeter per micro
    ampere)
12 Ro=80//internal resistance of the galvenometer(in

```

```

    ohm)
13 Eth=E*(R1/(R1+R3)-R2/(R2+R4))
14 Rth=R1*R3/(R1+R3)+R2*R4/(R2+R4)
15 Ig=Eth/(Rth+Ro)
16 D=S*Ig
17 disp(D, 'deflection of the galvenometer(in m)=')

```

---

#### Scilab code Exa 4.5 Find limiting value of unknown resistance

```

1 //caption:Find limiting value of unknown resistance
2 //Ex4.5
3 clc
4 clear
5 close
6 R1=100//value of resistance(in ohm)
7 R2=100//value of resistance(in ohm)
8 R3=230//value of standard arm resistance(in ohm)
9 dR1=0.02//ratio arms accuracy range(in %)
10 dR2=0.02//ratio arms accuracy range(in %)
11 dR3=0.01//standard ratio arm accuracy range(in %)
12 Rx=(R2*R3)/R1
13 dRx=dR1+dR2+dR3
14 Rx1=R3-((R3*dRx)/100)
15 Rx2=R3+((R3*dRx)/100)
16 disp(Rx1, 'lower value of limiting resistance(in ohm)
    =')
17 disp(Rx2, 'upper value of limiting resistance(in ohm)
    =')

```

---

**Scilab code Exa 4.6** Find magnitude and phase angle of Z4 arm

```
1 //caption:Find magnitude and phase angle of Z4 arm
2 //Ex4.6
3 clc
4 clear
5 close
6 Z1=200//impedance of first arm(in ohm)
7 Za=30//phase angle of first arm(in degree)
8 Z2=250//impedance of second arm(in ohm)
9 Zb=-40//phase angle of second arm(in degree)
10 Z3=150//impedane of third arm(in ohm)
11 Zc=0//phase angle of third arm(in degree)
12 Z4=(Z2*Z3)/Z1
13 disp(Z4,'magnitude of Z4 arm(in ohm)=')
14 Zd=Zb+Zc-Za
15 disp(Zd,'phase angle of Z4 arm(in degree)=')
```

---

**Scilab code Exa 4.7** find value of unknown inductance resistance and Q for maxwell bridge

```
1 //caption:find value of unknown inductance ,
   resistance and Q for maxwell bridge
2 //Ex4.7
```

```

3  clc
4  clear
5  close
6  R1=220//resistance of first arm(in ohm)
7  C1=0.22*10^-6//capacitance of first arm(in F)
8  R2=1000//resistance of second arm(in ohm)
9  R3=1000//resistance of third arm(in ohm)
10 f=1000//frequency of arm(in Hz)
11 w=2*%pi*f
12 R=(R2*R3)/R1
13 disp(R, 'resistance (in ohm)=')
14 L=R2*R3*C1
15 disp(L, 'inductance (in H)=')
16 Q=w*R1*C1
17 disp(Q, 'Q value of the bridge=')

```

---

**Scilab code Exa 4.8** find relative permittivity of specimen

```

1 //caption:find relative permittivity of specimen
2 //Ex4.8
3 clc
4 clear
5 close
6 C1=120//capacitance of first arm without specimen(in
   pF)
7 C3=150//capacitance of third arm without specimen(in
   pF)
8 R1=5000//resistance of first arm without specimen(in
   ohm)
9 R2=5000//resistance of second arm without specimen(
   in ohm)

```

```

10 C1o=200 //capacitance of first arm with specimen(in
    pF)
11 C3o=900 //capacitance of third arm with specimen(in
    pF)
12 R1o=5000 //resistance of first arm with specimen(in
    ohm)
13 R2o=5000 //resistance of second arm with specimen(in
    ohm)
14 Cs=(C3*R1)/R2
15 Css=(C3o*R1o)/R2o
16 er=Css/Cs
17 disp(er,'relative permittivity of the specimen=')

```

---

**Scilab code Exa 4.9** Find equivalent parallel resistance and capacitance

```

1 //caption:Find equivalent parallel resistance and
    capacitance.
2 //Ex4.9
3 clc
4 clear
5 close
6 R1=3.1 //resistance(in kilo ohm)
7 R2=25 //resistance(in kilo ohm)
8 C1=5.2*10^-6 //capacitance(in F)
9 R4=100 //resistance(in kilo ohm)
10 f=2500 //frequency (in Hz)
11 w=2*%pi*f
12 R3=(R4/R2)*((R1)+1/(w^2)*R1*(C1^2))
13 disp(R3,'equivalent parallel resistance(in kilo ohm)
    =')
14 C3=1/((w^2)*C1*R1*R3)

```

```
15 disp(C3, 'equivalent parallel capacitance (in F)=')
```

---

**Scilab code Exa 4.10** find value of arm CD

```
1 //caption:find value of arm CD
2 //Ex4.10
3 clc
4 clear
5 close
6 R1=2000//resistance of arm AB(in ohm)
7 C1=0.047*10^-6//capacitance of arm AB(in F)
8 R2=1000//resistance of arm BC(in ohm)
9 C2=0.47*10^-6//capacitance of arm BC(in F)
10 C3=0.5*10^-6//capacitance of arm AD(in F)
11 f=1000//frequency of bridge(in Hz)
12 w=2*%pi*f
13 Y1=(1/R1)+(%i*w*C1)
14 Z2=R2-(%i/(w*C2))
15 Z3=-%i/(w*C3)
16 Z4=Y1*Z2*Z3
17 disp(Z4, 'value of arm CD=')
```

---

**Scilab code Exa 4.11** find value of arm CD

```
1 //caption:find value of arm CD
```

```

2 //Ex4.11
3 clc
4 clear
5 close
6 C1=0.2*10^-6//capacitance of arm AB(in F)
7 R2=500//resistance of arm BC(in ohm)
8 R3=300//resistance of arm BC(in ohm)
9 C3=0.1*10^-6//capacitance of arm AD(in F)
10 f=1000//frequency of bridge(in Hz)
11 w=2*%pi*f
12 Z1=-%i/(w*C1)
13 Z2=R2
14 Z3=1/((1/R3)+%i*w*C3)
15 Z4=(Z2*Z3)/Z1
16 disp(Z4,'value of arm CD=')

```

---

**Scilab code Exa 4.12** find value of arm AD

```

1 //caption:find value of arm AD
2 //Ex4.12
3 clc
4 clear
5 close
6 R1=1000//resistance of arm AB(in ohm)
7 C1=0.5*10^-6//capacitance of arm AB(in F)
8 R3=1000//resistance of arm BC(in ohm)
9 C3=0.5*10^-6//capacitance of arm BC(in F)
10 R4=200//resistance of arm BC(in ohm)
11 L4=30*10^-3//inductance of arm(in henery)
12 f=1000//frequency of bridge(in Hz)
13 w=2*%pi*f

```

```

14 Z1=1/((1/R1)+(%i*w*C1))
15 Z3=R3+(1/(%i*w*C3))
16 Z4=R4+(%i*w*L4)
17 Z2=(Z1*Z4)/Z3
18 disp(Z2,'value of arm CD=')

```

---

**Scilab code Exa 4.13** find value of frequency of the bridge arm resistance of arm AD

```

1 //caption:find value of frequency of the bridge arm
  resistance of arm AD
2 //Ex4.13
3 clc
4 clear
5 close
6 R1=1000//resistance of arm AB(in ohm)
7 C1=0.159*10^-6//capacitance of arm AB(in F)
8 R2=1000//resistance of arm BC(in ohm)
9 C3=0.636*10^-6//capacitance of arm BC(in F)
10 R4=500//resistance of arm BC(in ohm)
11 R3=R1*((R4/R2)-(C1/C3))
12 disp(R3,'resistance of the arm AD(in ohm)=')
13 f=1/(2*pi*sqrt(C1*C3*R1*R3))
14 disp(f,'frequency of the bridge(in Hz)=')

```

---



# Chapter 5

## Analog meters

**Scilab code Exa 5.1** Find terminal voltage when load impedance is a 10 ohm b 20 ohm c 40 ohm

```
1 //caption:Find terminal voltage when load impedance
   is (a)10 ohm(b)20 ohm(c)40 ohm
2 //Ex5.1
3 clc
4 clear
5 close
6 Vs=5//source voltage(in V)
7 Zi=10//internal imedance of load(in ohm)
8 Z1=10//load impedance(in ohm)
9 Z2=20//load impedance(in ohm)
10 Z3=40//load impedance(in ohm)
11 Vt1=(Vs/(Zi+Z1))*Z1
12 disp(Vt1, '(a) internal voltage at load impedance 10
   ohm(in ohm)=')
13 Vt2=(Vs/(Zi+Z2))*Z2
14 disp(Vt2, '(b) internal voltage at load impedance 20
   ohm(in ohm)=')
15 Vt3=(Vs/(Zi+Z3))*Z3
16 disp(Vt3, '(c) internal voltage at load impedance 40
   ohm(in ohm)=')
```

---

**Scilab code Exa 5.2** Find load current when variable load are a 100 ohm  
b) 10 ohm

```
1 //caption:Find load current when variable load are(a)
   100 ohm(b)10 ohm
2 //Ex5.2
3 clc
4 clear
5 close
6 Zs=100//current source impedance(in ohm)
7 Zl1=100//load impedance(in ohm)
8 Zl2=10//load impedance(in ohm)
9 Is=10//current source value(in A)
10 I11=(Is/(1+(Zl1/Zs)))
11 disp(I11, '(a)load current when variable load is 100
   ohm(in ohm)=')
12 I12=(Is/(1+(Zl2/Zs)))
13 disp(I12, '(b)load current when variable load is 10
   ohm(in ohm)=')
```

---

**Scilab code Exa 5.3** Find equivalent voltage source of the ac current source

```

1 //caption:Find equivalent voltage source of the ac
  current source
2 //Ex5.3
3 clc
4 clear
5 close
6 Is=1//current value(in A)
7 Zs=100//source impedance(in ohm)
8 Veq=Is*Zs
9 disp(Veq,'equivalent voltage source of the ac
  current source(in V)=')

```

---

**Scilab code Exa 5.4** Find equivalent current source

```

1 //caption:Find equivalent current source
2 //Ex5.4
3 clc
4 clear
5 close
6 Vs=5//source voltage(in V)
7 Rs=1//source resistance(in ohm)
8 I=Vs/Rs
9 disp(I,'equivalent current source(in A)=')

```

---

**Scilab code Exa 5.5** Find value of shunt resistance for ammeter

```

1 //caption:Find value of shunt resistance for ammeter

```

```

2 //Ex5.5
3 clc
4 clear
5 close
6 Im=2//ammeter current(in mA)
7 I=50//max range of ammeter(in mA)
8 Rm=100//internal ammeter resistance(in ohm)
9 Rs=(Rm/((I/Im)-1))
10 disp(Rs,'shunt resistance(in ohm)=')

```

---

**Scilab code Exa 5.6** Find value of shunt resistance for the range a 0 to 1A  
b 0 to 5A c 0 to 10A

```

1 //caption:Find value of shunt resistance for the
   range(a)0-1A(b)0-5A(c)0-10A
2 //Ex5.6
3 clc
4 clear
5 close
6 Im=0.001//meter current(in A)
7 I1=1//maximum range(in A)
8 I2=5//maximum range(in A)
9 I3=10//maximum range(in A)
10 R=100//internal resistance(in ohm)
11 Rs1=(R/((I1/Im)-1))
12 disp(Rs1,'(a)shunt resistance(in ohm)=')
13 Rs2=(R/((I2/Im)-1))
14 disp(Rs2,'(b)shunt resistance(in ohm)=')
15 Rs3=(R/((I3/Im)-1))
16 disp(Rs3,'(c)shunt resistance(in ohm)=')

```

---

**Scilab code Exa 5.8** Find the value of multiplier resistance for the range  
a 0 to 10V b 0 to 50V c 0 to 100V d 0 to 200V

```
1 //caption:Find the value of multiplier resistance
   for the range(a)0-10V(b)0-50V(c)0-100V(d)0-200V
2 //Ex5.8
3 clc
4 clear
5 close
6 V1=10//maximum voltage range(in V)
7 V2=50//maximum voltage range(in V)
8 V3=100//maximum voltage range(in V)
9 V4=200//maximum voltage range(in V)
10 I=0.002//deflection current(in A)
11 R=100//internal resistance(in ohm)
12 Rt1=V1/I
13 R1=Rt1-R
14 disp(R1, '(a) multiplier resistance(in ohm)=')
15 Rt2=V2/I
16 R2=Rt2-(R1+R)
17 disp(R2, '(b) multiplier resistance(in ohm)=')
18 Rt3=V3/I
19 R3=Rt3-(R2+R1+R)
20 disp(R3, '(c) multiplier resistance(in ohm)=')
21 Rt4=V4/I
22 R4=Rt4-(R1+R2+R3+R)
23 disp(R4, '(d) multiplier resistance(in ohm)=')
```

---

**Scilab code Exa 5.9** Find the value of multiplier resistance for the range  
a 0 to 10V b 0 to 50V c 0 to 100V d 0 to 200V using sensitivity method

```
1 //caption:Find the value of multiplier resistance
   for the range(a)0-10V(b)0-50V(c)0-100V(d)0-200V
   using sensitivity method
2 //Ex5.9
3 clc
4 clear
5 close
6 V1=10//maximum voltage range(in V)
7 V2=50//maximum voltage range(in V)
8 V3=100//maximum voltage range(in V)
9 V4=200//maximum voltage range(in V)
10 I=0.002//deflection current(in A)
11 R=100//internal resistance(in ohm)
12 S=1/I
13 R1=(S*V1)-R
14 disp(R1, '(a) multiplier resistance(in ohm)=')
15 R2=(S*V2)-(R1+R)
16 disp(R2, '(b) multiplier resistance(in ohm)=')
17 R3=(S*V3)-(R2+R1+R)
18 disp(R3, '(c) multiplier resistance(in ohm)=')
19 R4=(S*V4)-(R1+R2+R3+R)
20 disp(R4, '(d) multiplier resistance(in ohm)=')
```

---

**Scilab code Exa 5.10** Find reading of voltmeter and percentage error when a sensitivity of voltmeter is 100 kilo ohm per volt b sensitivity of voltmeter is 500 kilo ohm per volt

```

1 //caption:Find reading of voltmeter and percentage
  error when(a)sensitivity of voltmeter is 100 kilo
  ohm per volt(b)sensitivity of voltmeter is 500
  kilo ohm per volt
2 //Ex5.10
3 clc
4 clear
5 close
6 R1=50000//load resistance(in ohm)
7 S1=10000//sensitivity (in kilo ohm per volt)
8 S2=50000//sensitivity (in kilo ohm per volt)
9 Vi=10//input voltage(in V)
10 R=5//range of voltmeter(in V)
11 V1=(R1/(S1+R1))*Vi
12 Vo=R*S1
13 Rth=((R1*Vo)/(R1+Vo))
14 V1=(Rth/(R1+Rth))*Vi
15 disp(V1, '(a)reading of voltmeter (in V)=')
16 e=((R-V1)/R)*100
17 disp(e, '(a) error (in %)=')
18 Vc=R*S2
19 Rt=((R1*Vc)/(R1+Vc))
20 V2=(Rt/(R1+Rt))*Vi
21 disp(V2, '(b)reading of voltmeter (in V)=')
22 eo=((R-V2)/R)*100
23 disp(eo, '(b) error (in %)=')
```

---

**Scilab code Exa 5.11** Find a value of R1 and R2 b change in value of R2  
c half scale deflection

```
1 //caption:Find (a) value of R1 and R2(b) change in
   value of R2(c) half scale deflection
2 //Ex5.11
3 clc
4 clear
5 close
6 Ifsd=0.001//current(in A)
7 Rm=100//internal resistance(in ohm)
8 E=9//battery voltage(in V)
9 Rh=5000//half scale deflection(in ohm)
10 R1=Rh-((Ifsd*Rm*Rh)/E)
11 disp(R1, '(a) value of R1(in ohm)=')
12 R2=(Ifsd*Rm*Rh)/(E-Ifsd*Rh)
13 disp(R2, '(a) value of R2(in ohm)=')
14 Eo=E-0.9
15 Ro=(Ifsd*Rm*Rh)/(Eo-Ifsd*Rh)
16 disp(Ro, '(b) change in value of R2(in ohm)=')
17 Rh2=R1+((Ro*Rm)/(Ro+Rm))
18 disp(Rh2, '(c) half scale deflection(in ohm)=')
```

---

**Scilab code Exa 5.12** Find R1 and Rsh



```

1 //caption:Find R1 and Rsh
2 //Ex5.12
3 clc
4 clear
5 close
6 Ifsd=0.001//current value(in A)
7 Rm=100//resistance(in ohm)
8 E=3//voltage(in V)
9 Rh=1//deflection resistance(in ohm)
10 Im=Ifsd/2
11 Ish=Im*((Rm-Rh)/Rh)
12 Rsh=(Im*Ish)/(Ish)
13 disp(Rsh,'value of Rsh(in ohm)=')
14 It=2*Im*(Rm/Rh)
15 R1=(E-Im*Rm)/It
16 disp(R1,'value of R1(in ohm)=')
```

---

**Scilab code Exa 5.13** Find value of required multiplier resistance

```

1 //caption:Find value of required multiplier
  resistance
2 //Ex5.13
3 clc
4 clear
5 close
6 Iav=100*10^-6//current value(in A)
7 Rm=100//internal resistance(in ohm)
8 Vrms=100//maximum rms range(in V)
9 Rs=0.45*(Vrms/Iav)-Rm
10 disp(Rs,'value of multiplier resistance(in ohm)=')
```

---

**Scilab code Exa 5.14** Find value of multiplier resistance

```
1 //caption:Find value of multiplier resistance
2 //Ex5.14
3 clc
4 clear
5 close
6 Vrms=10//rms voltage of the voltmeter(in V)
7 Ifsd=2*10^-3//ammeter reading(in A)
8 Rm=100//internal resistance(in ohm)
9 Sdc=1/Ifsd
10 Rs=(Sdc*0.45*Vrms)-Rm
11 disp(Rs,'value of multiplier resistance(in ohm)=')
```

---

**Scilab code Exa 5.15** Find value of multiplier resistance

```
1 //caption:Find value of multiplier resistance
2 //Ex5.15
3 clc
4 clear
5 close
6 Vrms=20//voltmeter range(in V)
7 Ifsd=2*10^-3//ammeter reading(in A)
8 Rm=500//internal resistance(in ohm)
```

```
9 Sdc=1/Ifsd
10 Sac=0.9*Sdc
11 Rs=Sac*Vrms-Rm
12 disp(Rs,'value of multiplier resistance(in ohm)=')
```

---

# Chapter 6

## data converters

Scilab code Exa 6.1 Find output voltage for a binary input a 1111 b 1100

```
1 //caption:Find output voltage for a binary input(a)
   1111(b)1100
2 //Ex6.1
3 clc
4 clear
5 close
6 N=4//bit of D/A convertor
7 Rlsb=16//resistance at LSB position(in kilo ohm)
8 Vref=5//reference voltage(in V)
9 Ro=1//feedback resistance(in kilo ohm)
10 R=Rlsb/(2^(N-1))
11 Va=-(Ro/R)*Vref*(2^0*1+2^-1*1+2^-2*1+2^-3*1)
12 disp(Va, '(a) output voltage (in V)=')
13 Vb=-(Ro/R)*Vref*(2^0*1+2^-1*1+2^-2*0+2^-3*0)
14 disp(Vb, '(b) output voltage (in V)=')
```

---

**Scilab code Exa 6.2** Find output voltage

```
1 //caption:Find output voltage
2 //Ex6.2
3 clc
4 clear
5 close
6 Lo=0//input voltage logic0(in V)
7 L1=20//input voltage logic1(in V)
8 V1msb=L1/2
9 V2msb=L1/4
10 V3msb=L1/8
11 V4msb=L1/16
12 Va=V1msb+V2msb+V3msb+V4msb
13 disp(Va,'output voltage(in V)=')
```

---

**Scilab code Exa 6.3** Find output voltage if input is 101101111

```
1 //caption:Find output voltage if input is 101101111
2 //Ex6.3
3 clc
4 clear
5 close
6 V=10.3*10^-3//input voltage of DAC convertor(in V)
7 Vo=(V)
   *(1*2^8+0*2^7+1*2^6+1*2^5+0*2^4+1*2^3+1*2^2+1*2^1+1*2^0)
```

```
8 disp(Vo, 'output voltage (in V)=')
```

---

**Scilab code Exa 6.4** Find values of a LSB b MSB c full scale output

```
1 //caption:Find values of(a)LSB(b)MSB(c)full scale
  output
2 //Ex6.4
3 clc
4 clear
5 close
6 N=8//bit of the DAC convertor
7 Rmin=0//minimum range(in V)
8 Rmax=10//maximum range(in V)
9 LS=1/(2^N)
10 LSB=Rmax*LS
11 disp(LSB, '(a)LSB(in V)=')
12 MSB=Rmax/2
13 disp(MSB, '(b)MSB(in V)=')
14 F=Rmax-LSB
15 disp(F, '(c)full scale output(in V)=')
```

---

**Scilab code Exa 6.5** Find resolution and voltage

```
1 //caption:Find resolution and voltage
```

```

2 //Ex6.5
3 clc
4 clear
5 close
6 N=3//bit of D/A convertor
7 V=5//full scale voltage(in V)
8 A=0.001//magnitude of accuracy
9 R=1/2^N
10 disp(R, 'resolution(in V)=')
11 Ac=A*V
12 disp(Ac, 'accuracy(in V)=')

```

---

**Scilab code Exa 6.6** Find conversion time required for inverter

```

1 //caption:Find conversion time required for
  cinvertor
2 //Ex6.6
3 clc
4 clear
5 close
6 N=8//bit of A/D convertor
7 Vr=2.56//clock voltage(in V)
8 Vin=1.728//input voltage(in V)
9 F=100*10^3//clock frequency(in Hz)
10 P=173//steps required for conversion
11 Po=1/F
12 T=P*Po
13 disp(T, 'total conversion time(in second)=')

```

---

**Scilab code Exa 6.9** Find total number of pulses and display reading

```
1 //caption:Find total number of pulses and display
  reading
2 //Ex6.9
3 clc
4 clear
5 close
6 V=10//input voltage(in V)
7 S=0.001//ramp slope(in V/second)
8 F=1000000//clock frequency(in Hz)
9 T=1/F
10 t=V*S
11 P=t/T
12 disp(P,'total number of pulses=')
13 disp(P,'display reading=')
```

---

**Scilab code Exa 6.10** Find input voltage

```
1 //caption:Find input voltage
2 //Ex6.10
3 clc
4 clear
5 close
```



```

6 Vref=5//reference voltage(in V)
7 t1=0.2//countts when input voltage is applied(in sec)
8 R=100*10^3//resistance(in ohm)
9 C=10^-6//capacitance(in F)
10 t2=R*C
11 Vin=(t2/t1)*Vref
12 disp(Vin,'input voltage(in V)=')

```

---

**Scilab code Exa 6.11** Find a output voltage after 1 sec b fall time of reference voltage waveform

```

1 //caption:Find(a)output voltage after 1 sec(b)fall
   time of reference voltage waveform
2 //Ex6.11
3 clc
4 clear
5 close
6 R=100000//resistance of DVM(in ohm)
7 C=10^-6//capacitance(in F)
8 Vin=1//input voltage(in V)
9 t1=1//rise time of reference voltage waveform at
   output of integrator(in second)
10 Vref=5//reference voltage(in V)
11 Vo=Vin*(t1/(R*C))
12 disp(Vo,'(a)output voltage after 1sec(in V)=')
13 t2=(Vin/Vref)*t1
14 disp(t2,'(b)fall time reference voltage waveform(in
   second)=')

```

---



# Chapter 7

## Display devices and digital systems

Scilab code Exa 7.1 convert 1101 into decimal

```
1 //caption:convert 1101 into decimal
2 //Ex7.1
3 clc
4 clear
5 close
6 decimal=1*2^3+1*2^2+0*2^1+1*2^0
7 disp(decimal,'decimal conversion=')
```

---

Scilab code Exa 7.2 convert 17 octal into decimal

```
1 //caption:convert 17 octal into decimal
2 //Ex7.2
```

```
3 clc
4 clear
5 close
6 decimal=1*8^1+7*8^0
7 disp(decimal, 'decimal conversion=')
```

---

**Scilab code Exa 7.3** convert 1E hexadecimal into decimal

```
1 //caption:convert 1E hexadecimal into decimal
2 //Ex7.3
3 clc
4 clear
5 close
6 E=14
7 decimal=1*16^1+E*16^0
8 disp(decimal, 'decimal conversion=')
```

---

**Scilab code Exa 7.20** Find input frequency applied to the system

```
1 //caption:Find input frequency applied to the system
2 //Ex7.20
3 clc
4 clear
5 close
6 F=1//frequency of crystal oscillator(in kilo Hz)
```

```
7 p=10//pulses
8 f=F*p
9 disp(f,'input frequency applied to the system(in
    kilo Hz)=')
```

---

**Scilab code Exa 7.21** find frequency of the system

```
1 //caption:find frequency of the system
2 //Ex7.21
3 clc
4 clear
5 close
6 n=45//reading of digital frequency counter
7 T=10*10^-3//gate time period(in second)
8 F=1/T
9 f=n*F
10 disp(f,'frequency of the system(in Hz)=')
```

---

**Scilab code Exa 7.22** find frequency time period of the system

```
1 //caption:find frequency time period of the system
2 //Ex7.22
3 clc
4 clear
5 close
```

```

6 n=30//reading of digital frequency counter
7 F=10^6//gate time period(in second)
8 T=1/F
9 t=n*T
10 disp(t,'frequency time period of the system(in
    second)=')

```

---

**Scilab code Exa 7.23** Find a resolution of the voltmeter b display of point 6368 in voltmeter on the 10V range c display of point 6368 in voltmeter on the 1V range

```

1 //caption:Find (a)resolution of the voltmeter(b)
    display of 0.6368 in voltmeter on the 10V range(c
    )display of 0.6368 in voltmeter on the 1V range
2 //Ex7.23
3 clc
4 clear
5 close
6 n=4//precise digit value of voltmeter
7 Va=10//range(in V)
8 Vb=1//range(in V)
9 R=1/10^n
10 disp(R,'(a)resolution of the voltmeter(in V)=')
11 Vo=Va*R
12 d=0.636
13 disp(d,'(b)display of 0.6368 in voltmeter on the 10V
    range(in V)=')
14 V=Vb*R
15 do=0.6368
16 disp(do,'(c)display of 0.6368 in voltmeter on the 1V
    range(in V)=')

```

---

**Scilab code Exa 7.24** Find a resolution of the voltmeter b display of 16 point 58 in voltmeter on the 10V range c display of point 7254 in voltmeter on the 1V and 10V range

```
1 //caption:Find (a) resolution of the voltmeter(b)
   display of 16.58 in voltmeter on the 10V range(c)
   display of 0.7254 in voltmeter on the 1V and 10V
   range
2 //Ex7.24
3 clc
4 clear
5 close
6 n=4//precise digit value of voltmeter
7 Va=10//range(in V)
8 Vb=1//range(in V)
9 R=1/10^n
10 disp(R, '(a) resolution of the voltmeter(in V)=')
11 Vo=Va*R
12 d=16.58
13 disp(d, '(b) display of 16.58 in voltmeter on the 10V
   range(in V)=')
14 V=Vb*R
15 do=0.7254
16 disp(do, '(c) display of 0.7254 in voltmeter on the 1V
   range(in V)=')
```

---

**Scilab code Exa 7.25** find out range of measured reading

```
1 //caption:find out range of measured reading
2 //Ex7.25
3 clc
4 clear
5 close
6 V=50//reading of voltmeter(in V)
7 A=0.02//accracy magnitude
8 Vo=V*A
9 Rmin=V-Vo
10 Rmax=V+Vo
11 disp(Rmax,Rmin,'range(in V)=')
```

---



# Chapter 8

## cathode ray oscilloscope

Scilab code Exa 8.1 find deflection sensitivity of CRO

```
1 //caption:find deflection sensitivity of CRO
2 //Ex8.1
3 clc
4 clear
5 close
6 l=20*10-3//axial length of deflection plate(in
   meter)
7 L=0.2//distance from the centre of the deflection
   plates to the screen(in meter)
8 s=5*10-3//spacing between two plates(in meter)
9 V=2500//accelerating voltage(in Volt)
10 S=(1*L)/(2*s*V)
11 disp(S,'deflection sensitivity of CRO(in m/V)=')
```

---

**Scilab code Exa 8.2** Find peak to peak amplitude of the signal and frequency of the signal

```
1 //caption:Find peak to peak amplitude of the signal
   and frequency of the signal
2 //ex8.2
3 clc
4 clear
5 close
6 V=0.5//vertical attenuation(in V/division)
7 n=4//number of divisions of vertical axis
8 P=V*n
9 disp(P, 'peak to peak amplitude of the signal(in V)=')
   )
10 T=P*n
11 f=1/T
12 disp(f, 'frequency of the signal(in Hz)=')
```

---

**Scilab code Exa 8.3** Find amplitude of the waveform

```
1 //caption:Find amplitude of the waveform
2 //ex8.3
3 clc
4 clear
5 close
6 V=5//vertical attenuation(in V/division)
7 n=2.5//number of divisions/cycle
8 P=V*n
9 disp(P, 'amplitude of the waveform(in V)=')
```

---

**Scilab code Exa 8.4** Find rms value of signal under test

```
1 //caption:Find rms value of signal under test
2 //ex8.4
3 clc
4 clear
5 close
6 S=100//Y sensitivity (in mV/division)
7 n=5//number of divisions of vertical axis
8 P=S*n
9 Vrms=P/(2*sqrt(2))
10 disp(Vrms, 'rms value of signal under test (in V)=')
```

---

**Scilab code Exa 8.5** Find value of current

```
1 //caption:Find value of current
2 //Ex8,5
3 clc
4 clear
5 close
6 V=10//voltage across resistor (in V)
7 R=1000//resistance (in ohm)
8 i=V/R
9 disp(i, 'value of current (in A)=')
```

---

**Scilab code Exa 8.6** Find value of current

```
1 //caption:Find value of current
2 //ex8.6
3 clc
4 clear
5 close
6 S=100//Y sensitivity(in mV/division)
7 n=5//number of divisions of vertical axis
8 R=4.7*10^3
9 P=S*n
10 Vrms=P/(2*sqrt(2))
11 i=Vrms/R
12 disp(i,'value of current(in A)=')
```

---

**Scilab code Exa 8.7** Find peak amplitude and frequency of the signal

```
1 //caption:Find peak amplitude and frequency of the
  signal
2 //Ex8.7
3 clc
4 clear
5 close
```

```

6 V=0.5//vertical attenuator(in V/division)
7 Vo=10^-6//horizontal attenuator(in second/division)
8 n=6//number of divisions on vertical axis
9 N=5//number of division for complete one cycle
10 V1=V*n
11 Vp=V1/2
12 disp(Vp,'peak amplitude(in V)=')
13 T=Vo*N
14 f=1/T
15 disp(f,'frequency of the signal(in Hz)=')
```

---

**Scilab code Exa 8.8** Find frequency of horizontal signal

```

1 //caption:Find frequency of horizontal signal
2 //Ex8.8
3 clc
4 clear
5 close
6 Y=2//number of Y peaks
7 X=1//number of X peaks
8 fv=2//vertical signal frequency(in kilo Hz)
9 fh=(X/Y)*fv
10 disp(fh,'frequency of horizontal signal(in kilo Hz)=')
    ')
```

---

**Scilab code Exa 8.9** Find frequency of the waveform

```
1 //caption:Find frequency of the waveform
2 //Ex8.9
3 clc
4 clear
5 close
6 t=0.5//time base(in microcond/division)
7 d=2//divisions/cycle
8 T=t*d
9 F=1/T
10 disp(F,'frequency of the waveform(in MHz)=')
```

---

**Scilab code Exa 8.10** what will be the setting of time base knob

```
1 //caption:what will be the setting of time base knob
2 //Ex8.10
3 clc
4 clear
5 close
6 f=1//frequency of sine wave(in kHz)
7 n=10//number of divisions in a cycle
8 T=1/f
9 To=T/n
10 disp(To,'setting of time base knob(in ms)=')
```

---

**Scilab code Exa 8.11** Find ratio of frequencies of vertical and horizontal signals

```
1 //caption:Find ratio of frequencies of vertical and
  horizontal signals
2 //Ex8.11
3 clc
4 clear
5 close
6 P1=1//positive Y peaks in pattern
7 P2=1//positive X peaks in pattern
8 f1=P1/P2
9 disp(f1,'ratio of frequencies of vertical and
  horizontal signals=')
10 P3=1//positive Y peaks in pattern
11 P4=3//positive X peaks in pattern
12 f2=P3/P4
13 disp(f2,'ratio of frequencies of vertical and
  horizontal signals=')
14 P5=4.5//positive Y peaks in pattern
15 P6=1//positive X peaks in pattern
16 f3=P5/P6
17 disp(f3,'ratio of frequencies of vertical and
  horizontal signals=')
```

---

**Scilab code Exa 8.12** find phase angle

```
1 //caption: find phase angle
2 //Ex8.12
3 clc
4 clear
5 close
6 Y1=4//vertical pattern
7 Y2=8//vertical pattern
8 o=Y1/Y2
9 Y=asind(o)
10 disp(Y,'phase angle(in degree)=')
11 Y3=4//vertical pattern
12 Y4=4//vertical pattern
13 oo=Y3/Y4
14 Ya=asind(oo)
15 disp(Ya,'phase angle(in degree)=')
```

---

**Scilab code Exa 8.13** Find bandwidth of CRO

```
1 //caption:Find bandwidth of CRO
2 //Ex8.13
3 clc
4 clear
5 close
6 tr=20*10-9//rise time(in second)
```



```
7 B=0.35/tr
8 disp(B, 'bandwidth of CRO(in Hz)=')
```

---