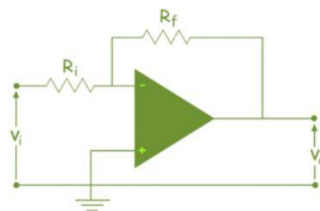


AVERAGE SUMMING AMPLIFIER


An op amp is an amplifier. But an op amp can also perform summing operation. We can design an op amp circuit to combine number of input signals and to produce single output as a weighted sum of input signals.

Summing amplifier is basically as op amp circuit that can combine numbers of input signal to a single output that is the weighted sum of the applied inputs.

The **summing amplifier** is one variation of inverting amplifier. In inverting amplifier there is only one voltage signal applied to the inverting input as shown below



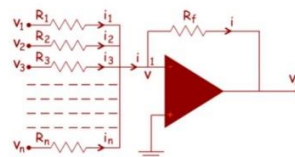This simple inverting amplifier can easily be modified to summing amplifier, if we connect several input terminals in parallel to the existing input terminals as shown below



Here, n numbers of input terminal are connected in parallel. Here in the circuit, the non inverting terminal of the op amp is grounded, hence potential at that terminal is zero. As the op amp is considered as ideal op amp, the potential of the inverting terminal is also zero. So the electric potential at node 1, is also zero. From the circuit, it is also clear that the current I is the sum of currents of input terminals.

Therefore,

$$\begin{aligned}
 i &= i_1 + i_2 + i_3 + \dots + i_n \\
 \Rightarrow i &= \frac{v_1 - 0}{R_1} + \frac{v_2 - 0}{R_2} + \frac{v_3 - 0}{R_3} + \dots + \frac{v_n - 0}{R_n} \\
 \Rightarrow i &= \frac{v_1}{R_1} + \frac{v_2}{R_2} + \frac{v_3}{R_3} + \dots + \frac{v_n}{R_n} \dots \dots \dots (i)
 \end{aligned}$$

Now in the case of ideal op amp the current at the inverting and non inverting terminal are zero. So, as per Kirchoff current law, the entire input current passes through the feedback path of resistance R_f that means,


$$i = \frac{0 - v_0}{R_f} = -\frac{v_0}{R_f} \dots \dots \dots (ii)$$

From equation (i) and (ii), we get,


$$\frac{v_1}{R_1} + \frac{v_2}{R_2} + \frac{v_3}{R_3} + \dots + \frac{v_n}{R_n} = -\frac{v_0}{R_f}$$
$$\Rightarrow v_0 = -\left(\frac{R_f}{R_1}v_1 + \frac{R_f}{R_2}v_2 + \frac{R_f}{R_3}v_3 + \dots + \frac{R_f}{R_n}v_n\right)$$

This indicates that output V_o is weighted sum of numbers of input voltages.


Circuit :

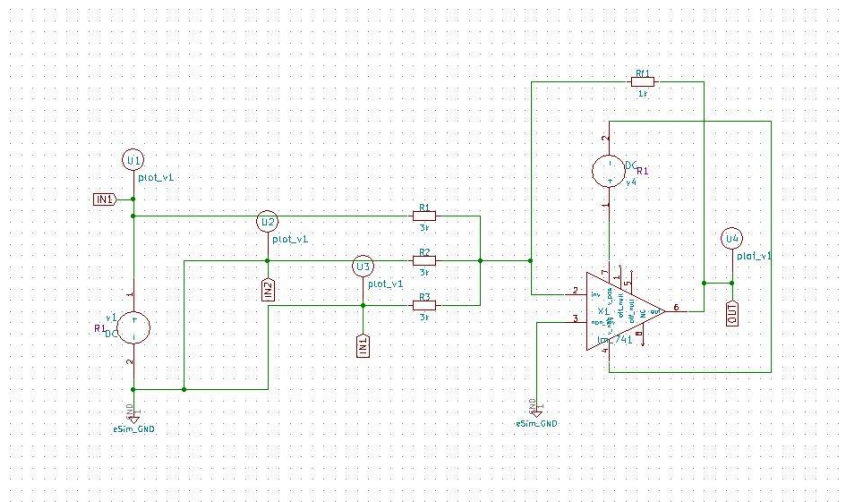

Input :

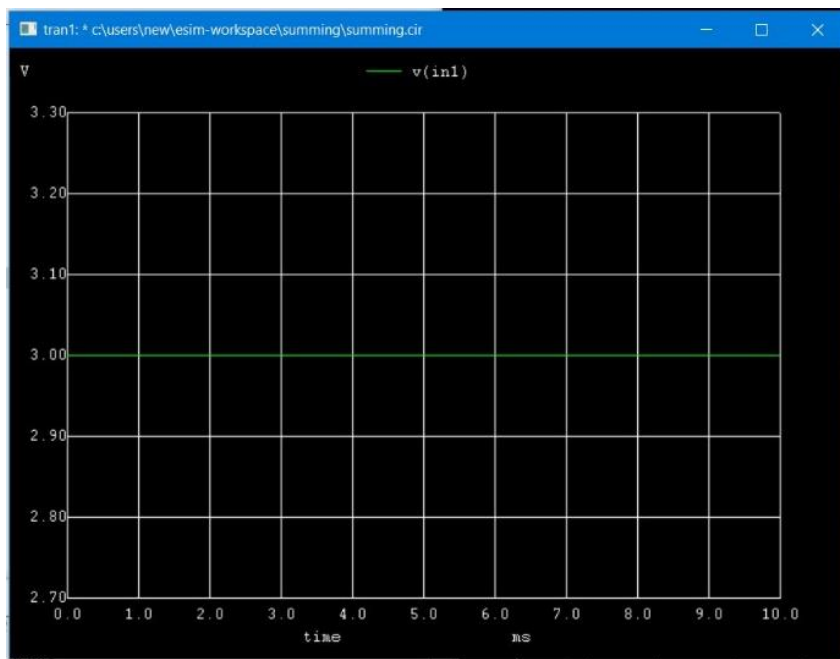

Output :

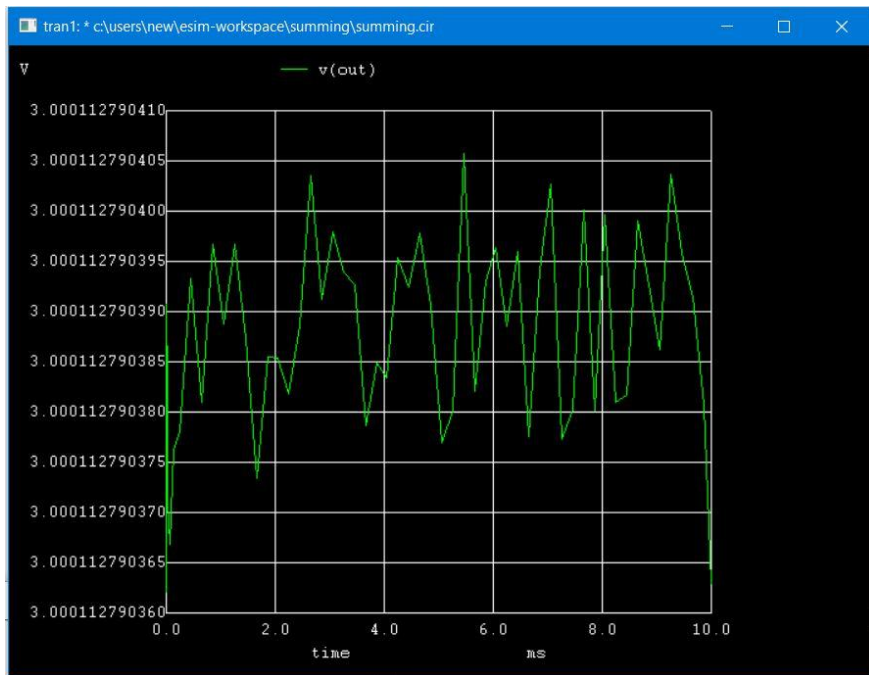

Reference Link: <https://electronicspost.com/application-of-op-amp-as-summing-amplifier-integrator-and-differentiator/amp/>