

Non Inverting Amplifier

Sebin Sunny P

Department of Electrical & Electronics Engineering
Sreepathy Institute of Management And Technology

Vavanoor, Palakkad - 679533

sebinsunny@simat.ac.in

Theory:

This circuit provides a gain to the input signal without any change in polarity. The gain of the non-inverting amplifier is

$$A=1+ (R_f/R_i)$$

where R_f is the feedback resistance and
 R_i is the input resistance.

The R_i of the non-inverting amplifier is extremely large. So it draws a negligible current from signal source.


Design:

Gain of non- inverting amplifier, $A = 1+ (R_f/R_i)$

Let gain $A=11$ so that the ratio

$(R_f/R_i) = 10$. Then $R_i=1K\Omega$, $R_f=10K\Omega$.


Schematic:

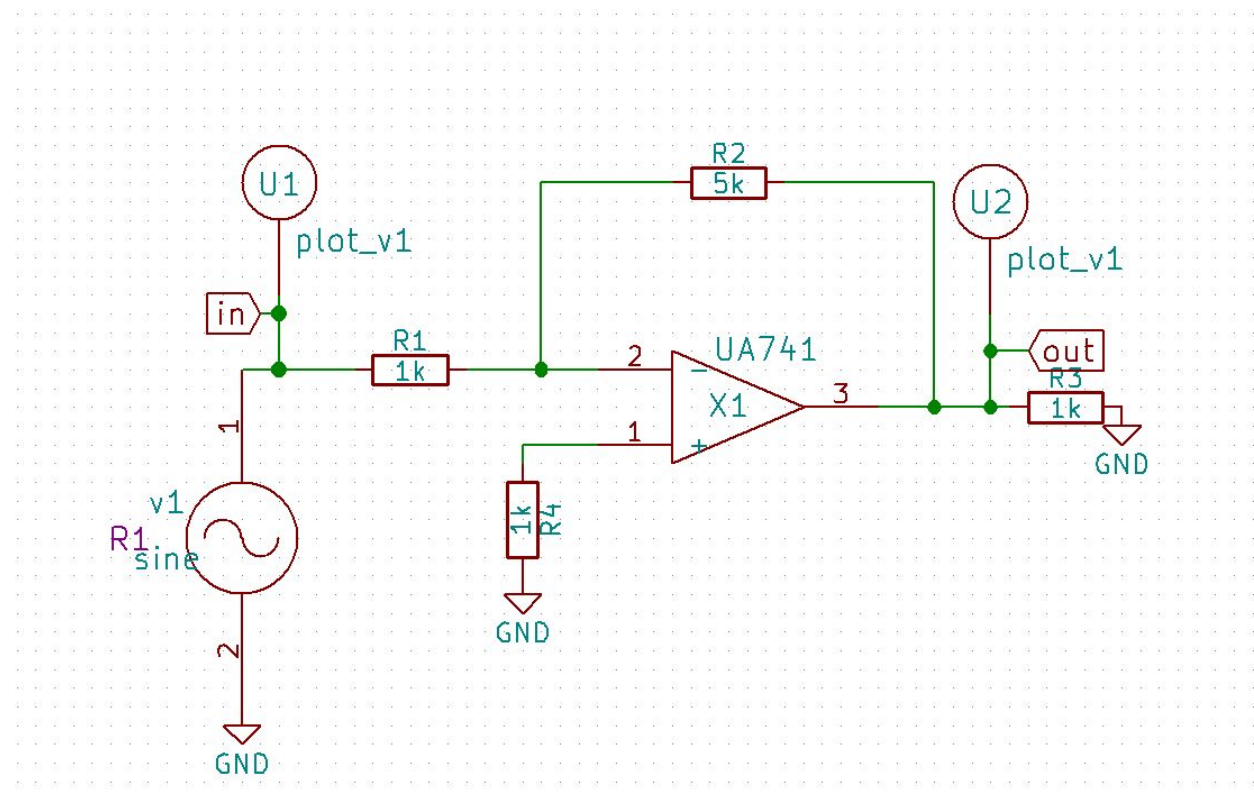


Simulation Output:

Python


Plot

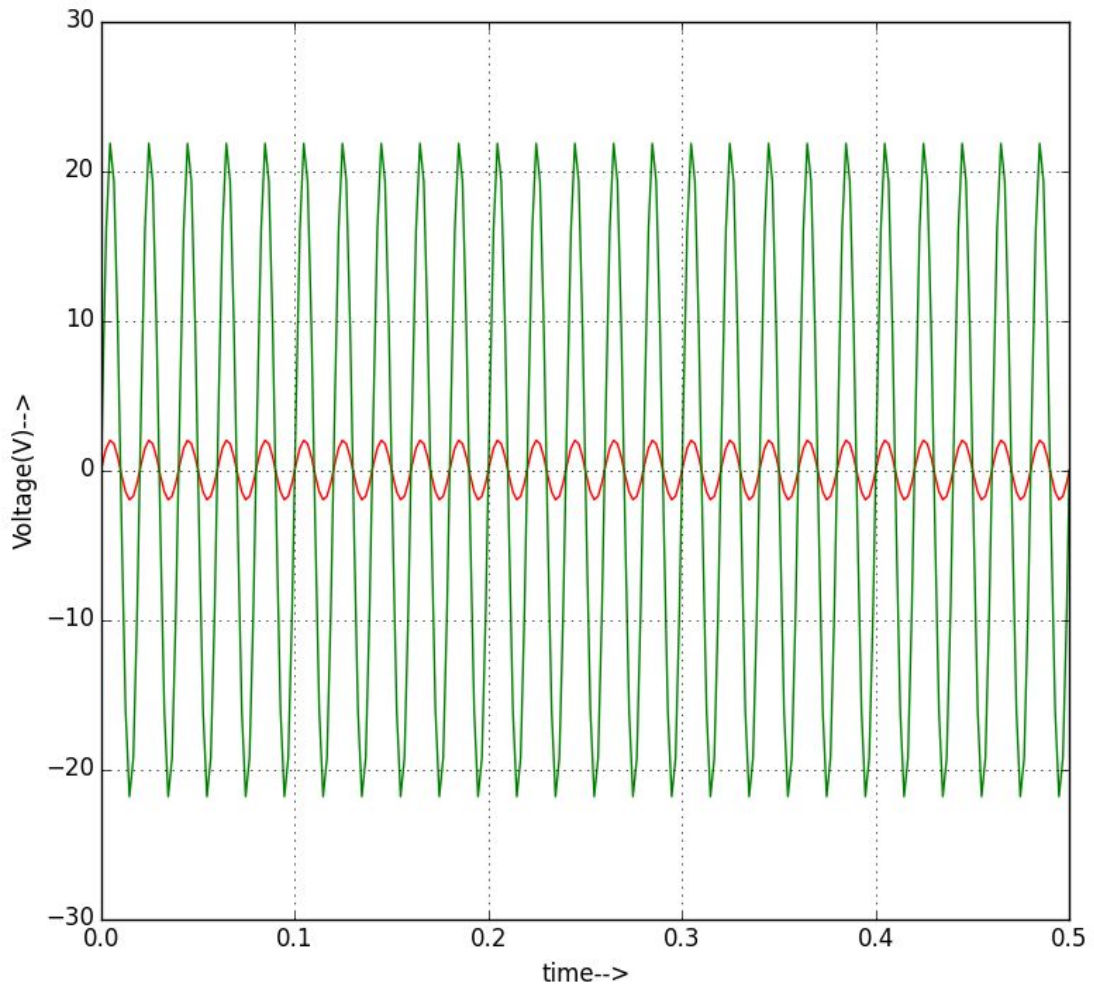

NGSPICE Plot:

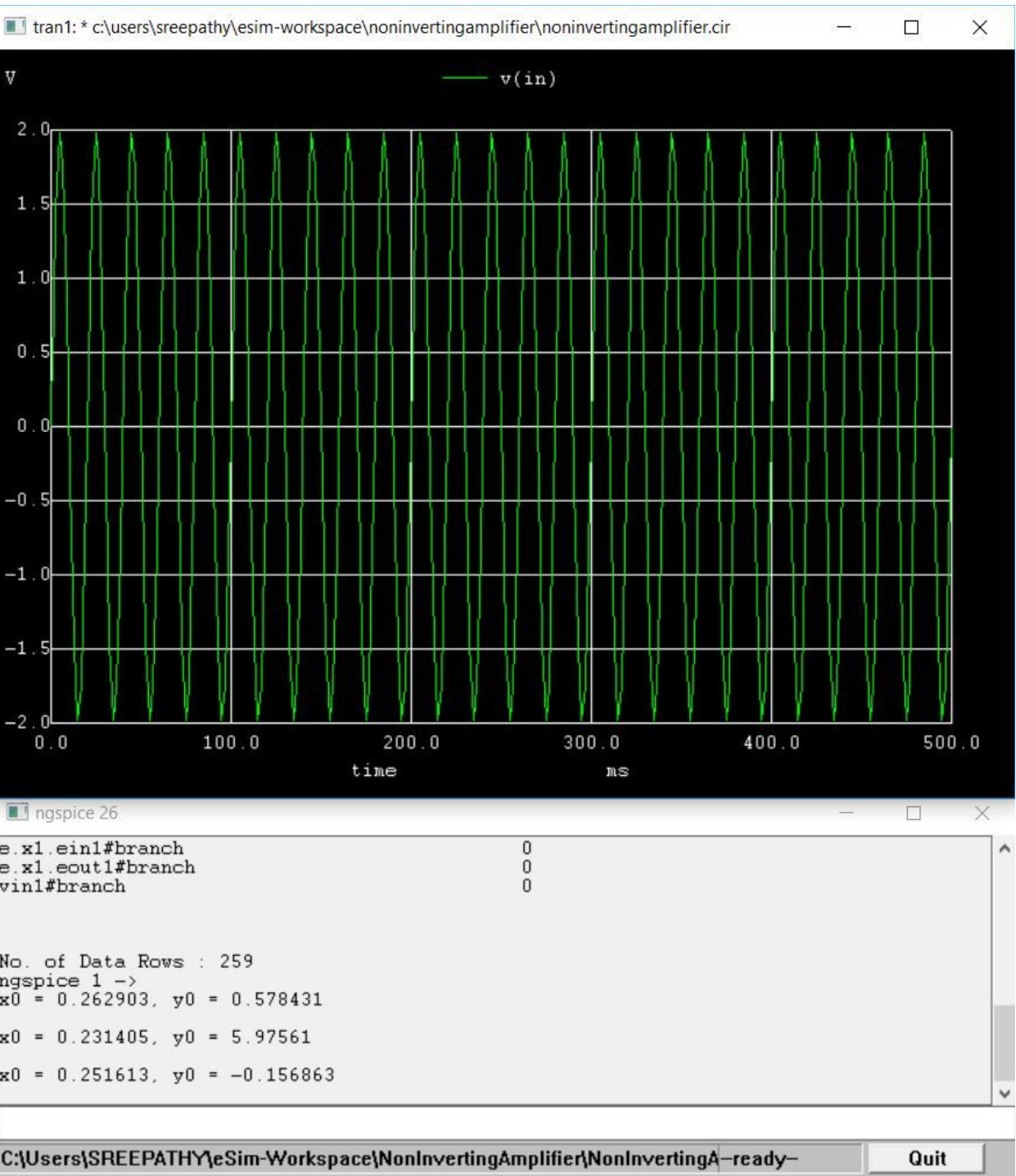

tran1: * c:\users\sreepathy\sim-workspace\noninvertingamplifier\noninvertingamplifier.cir

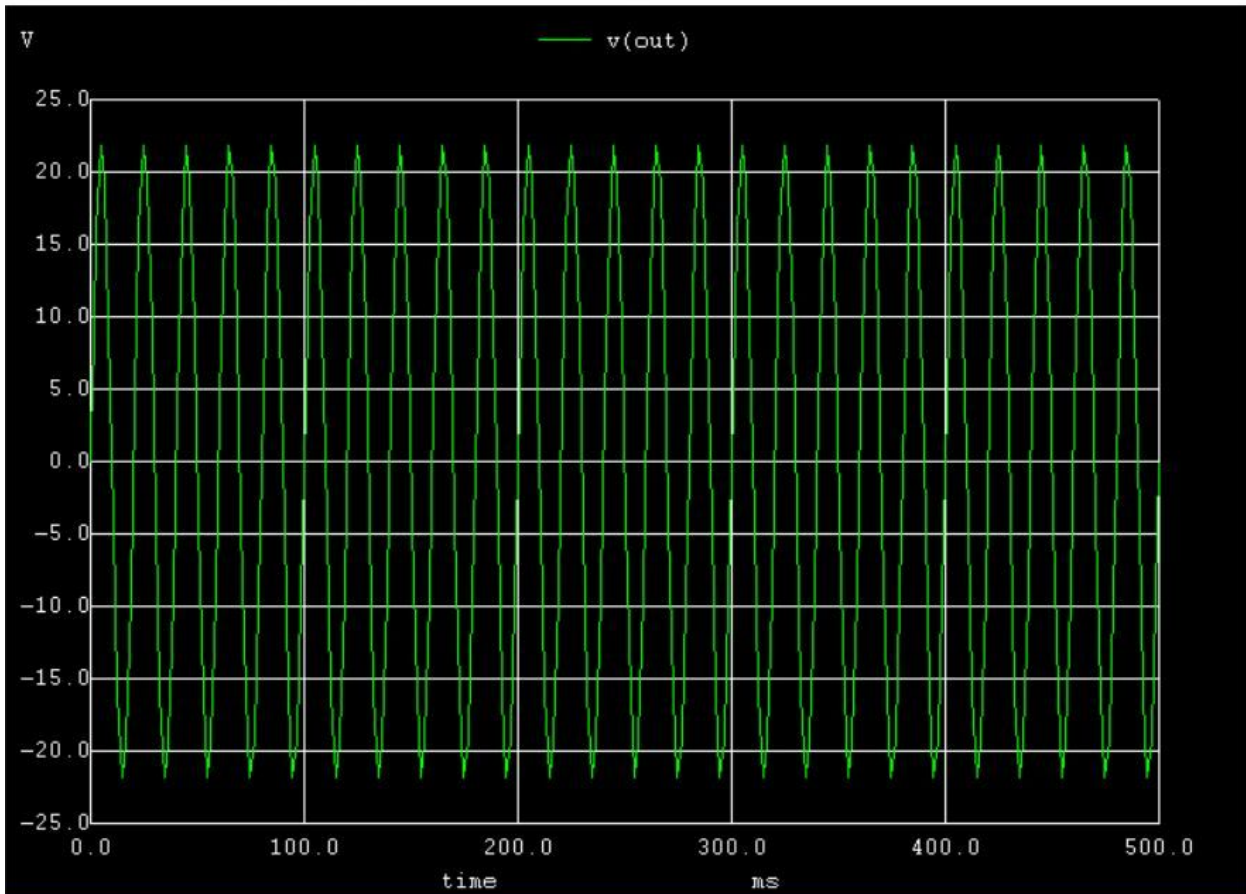

ngspice 26

```
x1.4          0
in            0
e.x1.ein1#branch  0
e.x1.eout1#branch 0
vin1#branch    0

No. of Data Rows : 259
ngspice 1 ->
x0 = 0.262903, y0 = 0.578431
x0 = 0.231405, y0 = 5.97561
```

C:\Users\SREEPATHY\Sim-Workspace\NonInvertingAmplifier\NonInvertingA-ready-

Quit